

Power Electronics 5.0

Standing on the Shoulders of Giants

Johann W. Kolar et al.



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch

Sept. 25, 2023



Power Electronics 5.0

Standing on the Shoulders of Giants

Johann W. Kolar | Jonas E. Huber | Daifei Zhang | David Menzi | Neha Nain



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch

Sept. 25, 2023



„Power Electronics 5.0“— Standing on the Shoulders of Giants

Abstract—Power electronics is a key technology for all forms of generation and utilization of electric power in modern societies, ranging from renewable energy systems and highly diverse power supply applications, including fast-charging of EVs and hyper-scale datacenters, to variable-frequency drives for industrial automation. Over the past 40 years, the progress in the area has been driven by new power semiconductor device concepts and corresponding circuit topologies with a focus on voltage-source converter (VSC) structures and/or the application of switching elements limited to unipolar voltage-blocking capability.

With reference to recently intensifying R&D activities on two-gate monolithic bidirectional switches (M-BDSs) featuring bipolar voltage blocking and bidirectional current control capability, the talk highlights the potential advantages of M-BDSs for the realization of ultra-compact non-isolated and isolated three-phase PFC rectifier systems and next-generation inverter systems with low motor insulation stress. In this context, the performance gains achievable with three-level T-type VSC topologies, new single-stage isolated AC/DC converter structures, and the unique features of current-source converter approaches—today solely employed in thyristor-based high-power medium-voltage motor drives—and AC/AC matrix converter concepts over state-of-the-art VSC systems are emphasized. All this identifies M-BDSs as one of the main drivers of a 4th wave of disruptive performance improvements of power electronic converter systems. The talk will conclude with remarks on the urgency of a transition from a linear economy to a circular economy, which also needs to be considered for future power electronic converter designs. Building on the understanding and knowledge gained by brilliant engineers over the last decades, i.e., standing on the shoulders of giants, power electronics research must now target “beyond tomorrow” improvements and enable a circular-economy-compatible Power Electronics 5.0 in order to ensure that the 2050 net-zero-CO₂ target is reached on a sustainable basis.


Outline



- ▶ *Introduction*
- ▶ *3- Φ AC/DC Grid Interfaces*
- ▶ *3- Φ AC/AC VSD Converter Systems*
- ▶ *GaN/SiC M-BDS R&D Activities*
- ▶ *Outlook*

S-Curve of Power Electronics

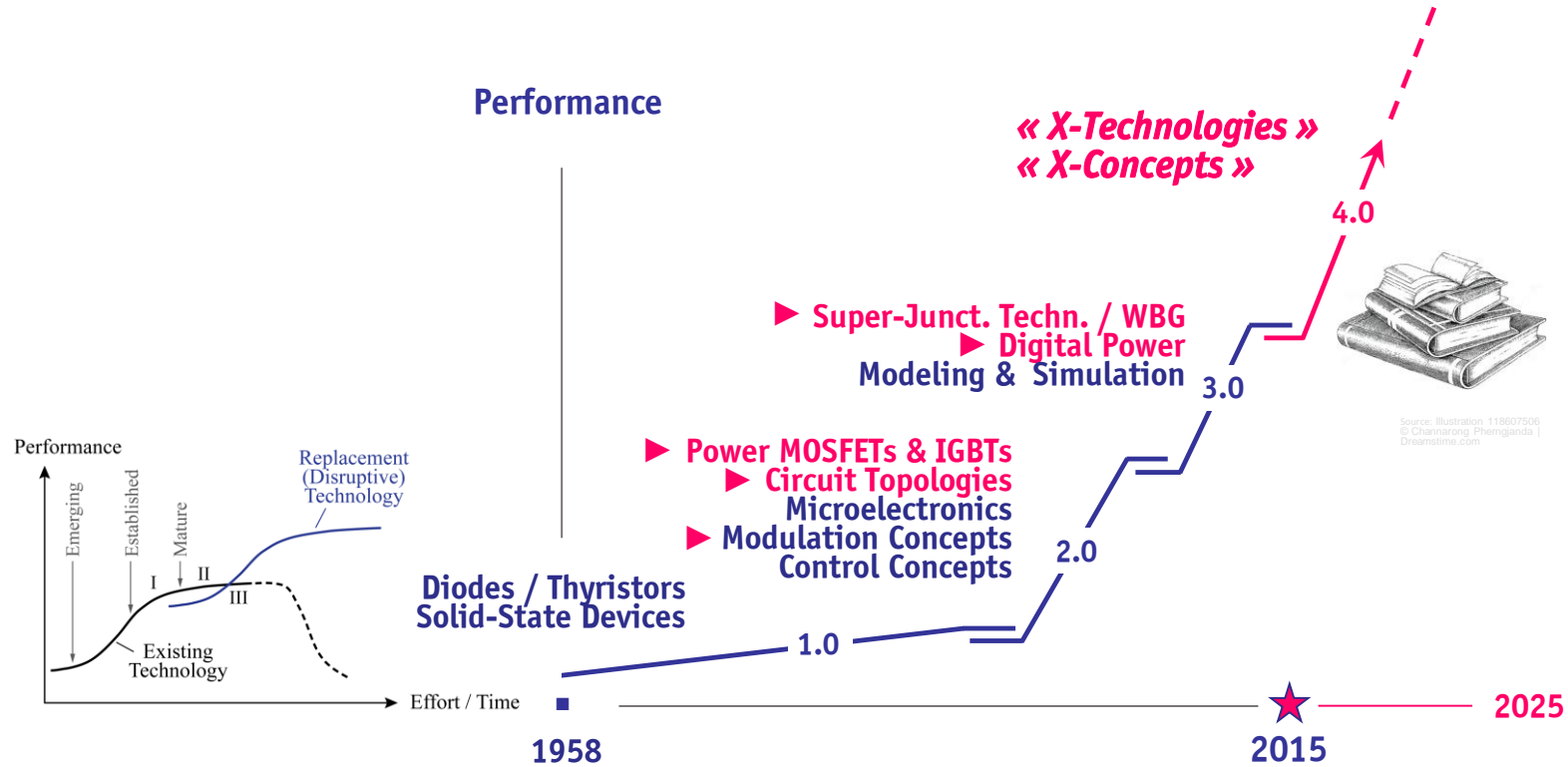- « X-Technologies » / “Moon-Shot” Technologies
- « X-Concepts » → Full Utilization of Basic Scaling Laws & X-Technologies
- Power Electronics 1.0 → Power Electronics 4.0
- 2...5...10x Improvement NOT Only 10% !



Global Megatrends



Renewable Energy
Digitalization →
Sustainable Mobility
Industry Automation
Etc.

Renewable Energy – Photovoltaics

- *3- Φ DC/AC Mains Interface*
- *Lower Costs / Higher Efficiency / Lower Weight*
- *20 Years Lifetime / Life-Cycle Assessment*

Source: REUTERS/Stringer



- *Globally
Installed PV
Capacity
Forecasted to
2.7 Terawatt by
2030 (IEA)*

Digitalization — Datacenters

- **Medium-Voltage** → **Power-Supplies-on-Chip (0.6 ... 0.8V)** **Power Conversion**
- **Trend Towards 380V DC Power Distribution**
- **Short Innovation Cycles**
- **Modularity / Scalability**

Server-Farms
up to **450 MW**
99.9999% / <30s/a
\$1.0 Mio./Outage

Since 2006
Running Costs >
Initial Costs

Source: Facebook




- **Higher Availability**
- **Higher Efficiency**
- **Higher Power Density**
- **Lower Costs**

3- Φ AC/DC Converter Application Areas

- *Datacenter Power Supply*
- *Electric Vehicle Battery Charging*
- *Renewable Energy Applications*

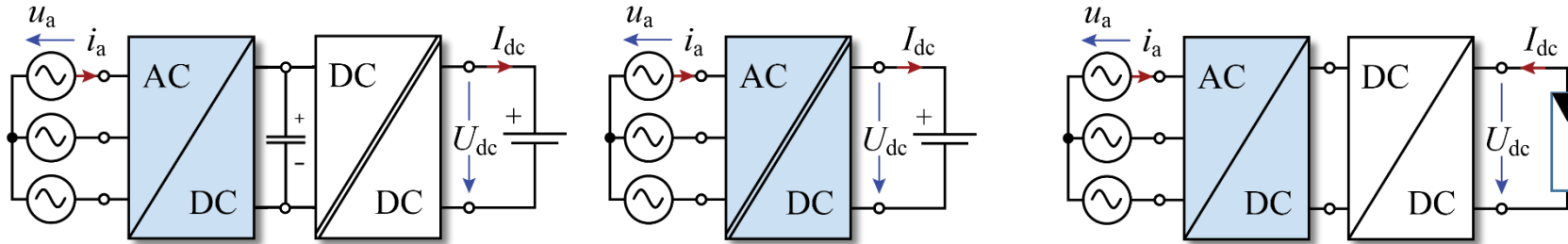Typ. 200...1000V_{DC} EV Battery
Voltage Range





320...530V_{rms}
Line-to-Line

MPP Tracking in 60...90% of
Max. Open Circuit Voltage

- *Non-Isolated* OR *Isolated Output*
- *Wide AC Input* &/OR *DC Output Voltage Range*
- *Unidirectional* OR *Bidirectional Power Transfer*

3- Φ Diode Bridge Rectifier

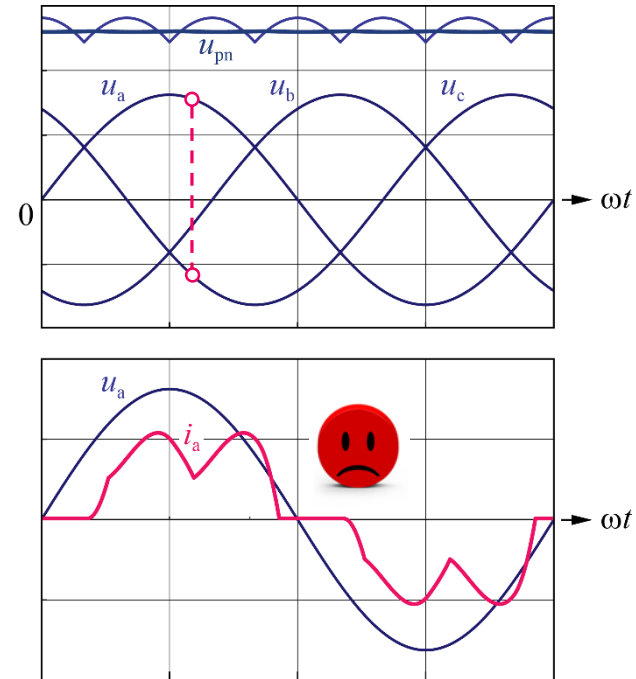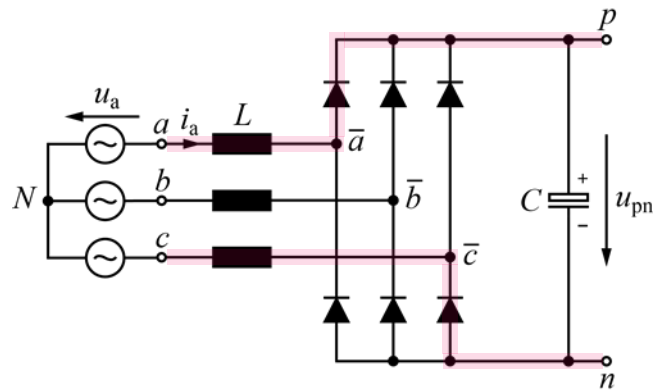
- *Conduction States Defined by Line-to-Line Mains Voltages*
- *Intervals with Zero Phase Current / LF Harmonics*
- *No Output Voltage Control*



→ *Active Mains Current Shaping / Simultaneous Current Flow in All Phases*

Integrated Active Filter (IAF) PFC Rectifier

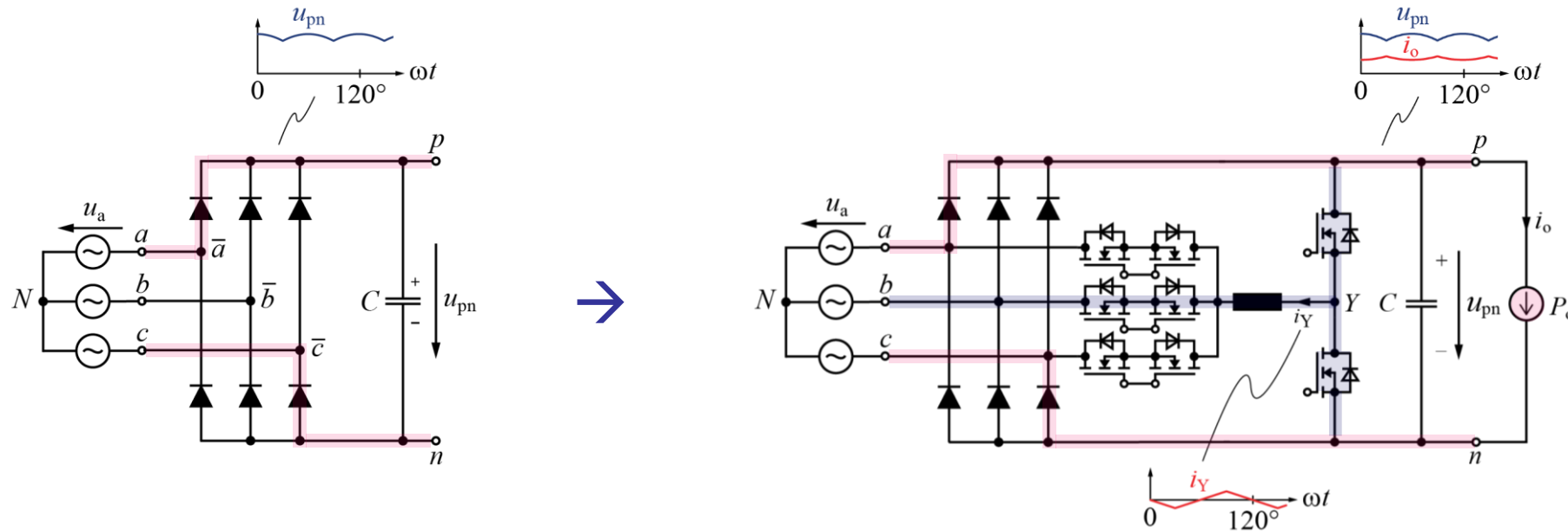- **3rd Harmonic Current Injection** into Phase with Lowest Voltage
- **Phase Selector AC Switches** Operated @ Mains Frequency — “3- Φ Unfolder” Input Stage





- **Non-Sinusoidal Mains Current**

- **DC/DC Output Stage** — $P_o = \text{const.}$
- **Sinusoidal Mains Current**
- **Controlled Output Voltage**

Integrated Active Filter (IAF) PFC Rectifier

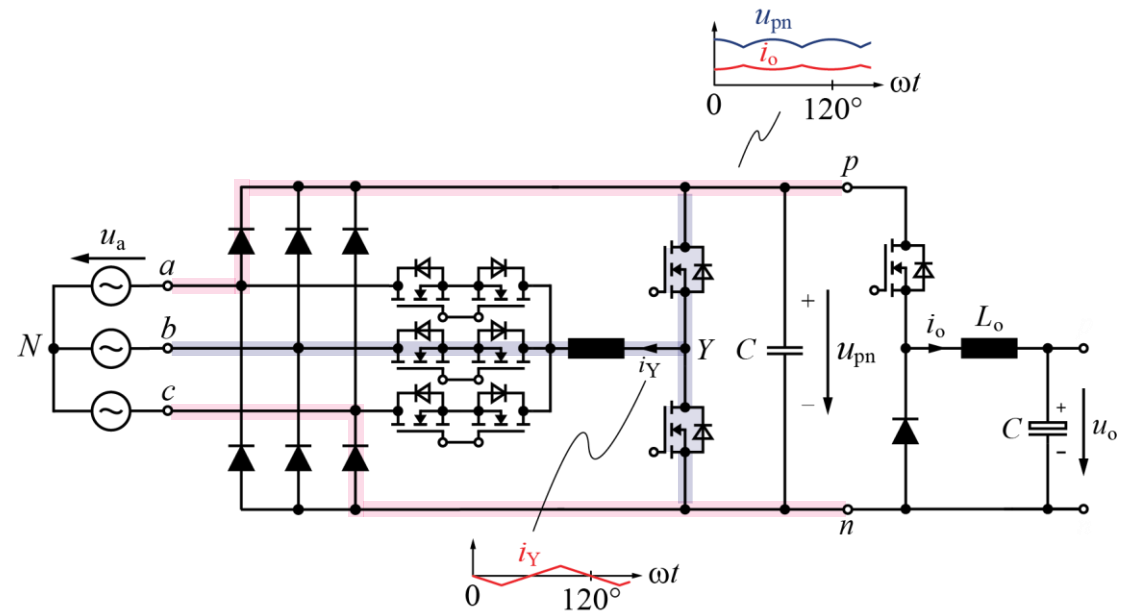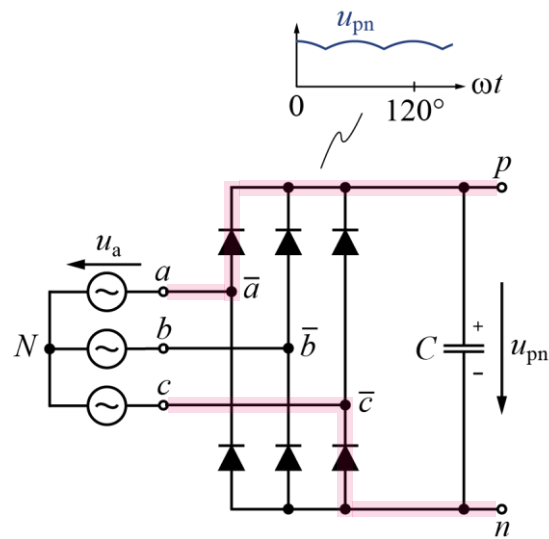- **3rd Harmonic Current Injection** into Phase with Lowest Voltage
- **Phase Selector AC Switches** Operated @ Mains Frequency — “3- Φ Unfolder” Input Stage




- **Non-Sinusoidal Mains Current**

- **DC/DC Output Stage** — $P_o = \text{const.}$
- **Sinusoidal Mains Current**
- **Controlled Output Voltage**



IAF Rectifier & Buck Output Stage

- Efficiency $\eta > 99.1\%$ @ 60% Rated Load
- Mains Current $THD_I \approx 2\%$ @ Rated Load
- Power Density $\rho \approx 4\text{kW}/\text{dm}^3$

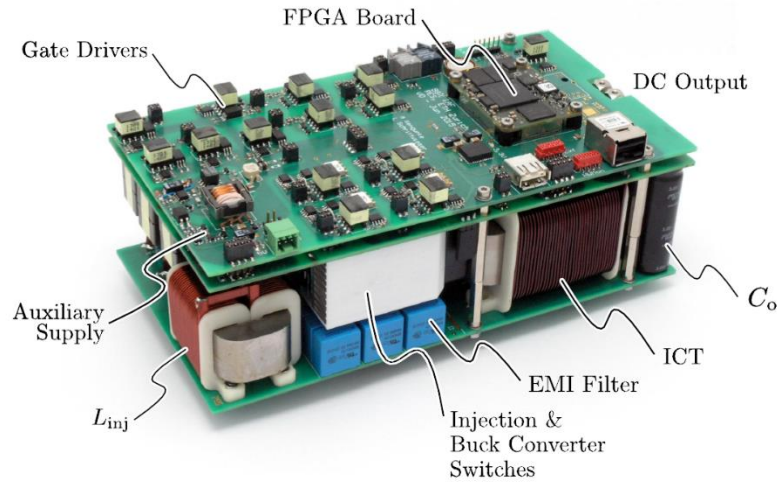$P_o = 8\text{ kW}$
 $U_N = 400\text{V}_{AC} \rightarrow U_o = 400\text{V}_{DC}\text{ const. / Controlled}$
 $f_s = 27\text{kHz}$





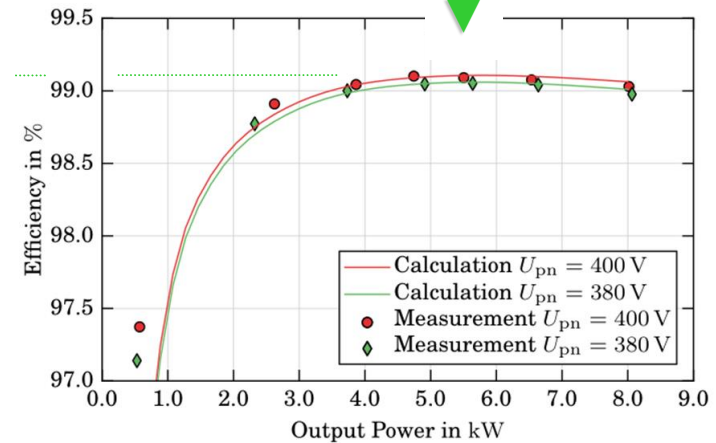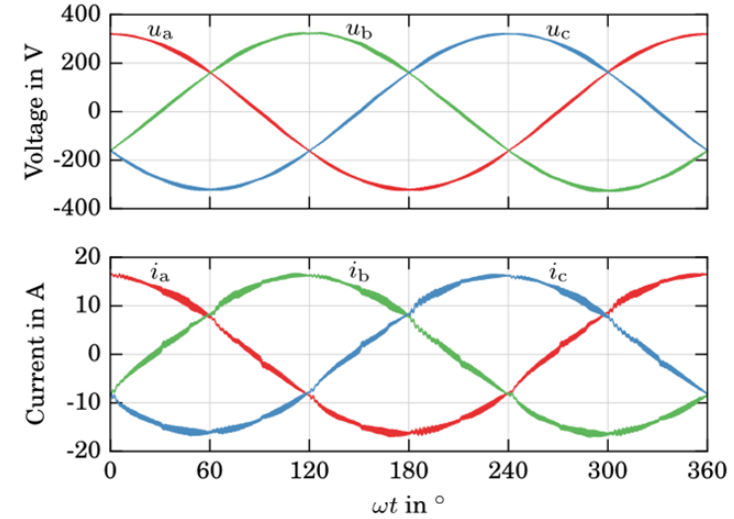- SiC Power MOSFETs & Diodes
- 2 Interleaved Buck DC/DC Output Stages (!)




Remark Application of M-BDSs (1)

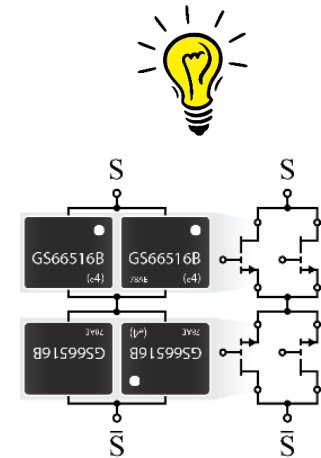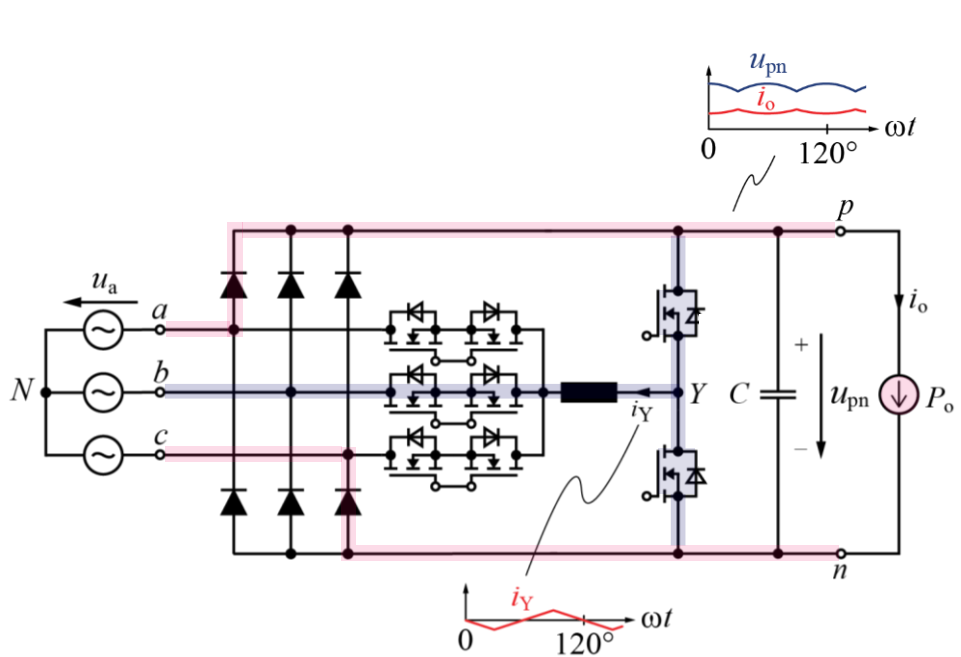- **M-BDS** — *Monolithic Bidirectional / Bipolar Switch*
- Realization of the *Phase Selector Switches* of 3rd Harmonic Inj. PFC Rectifiers
- Bipolar Voltage Blocking / Current Carrying Capability




Source: **Panasonic** ideas for life

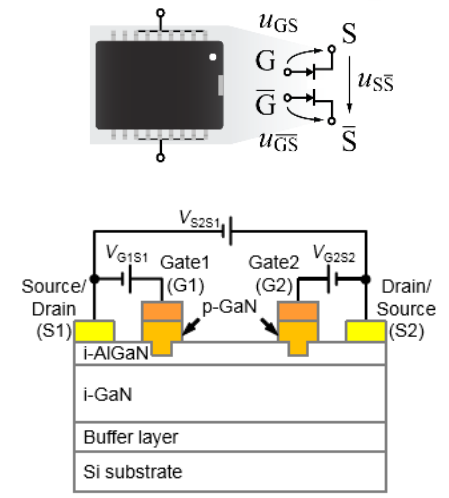

- **M-BDS** → *Factor of 4 Reduction of Chip Area Comp. to Discrete Realization of Same $R_{(on)}$ (!)*

Remark Application of M-BDSs (2)


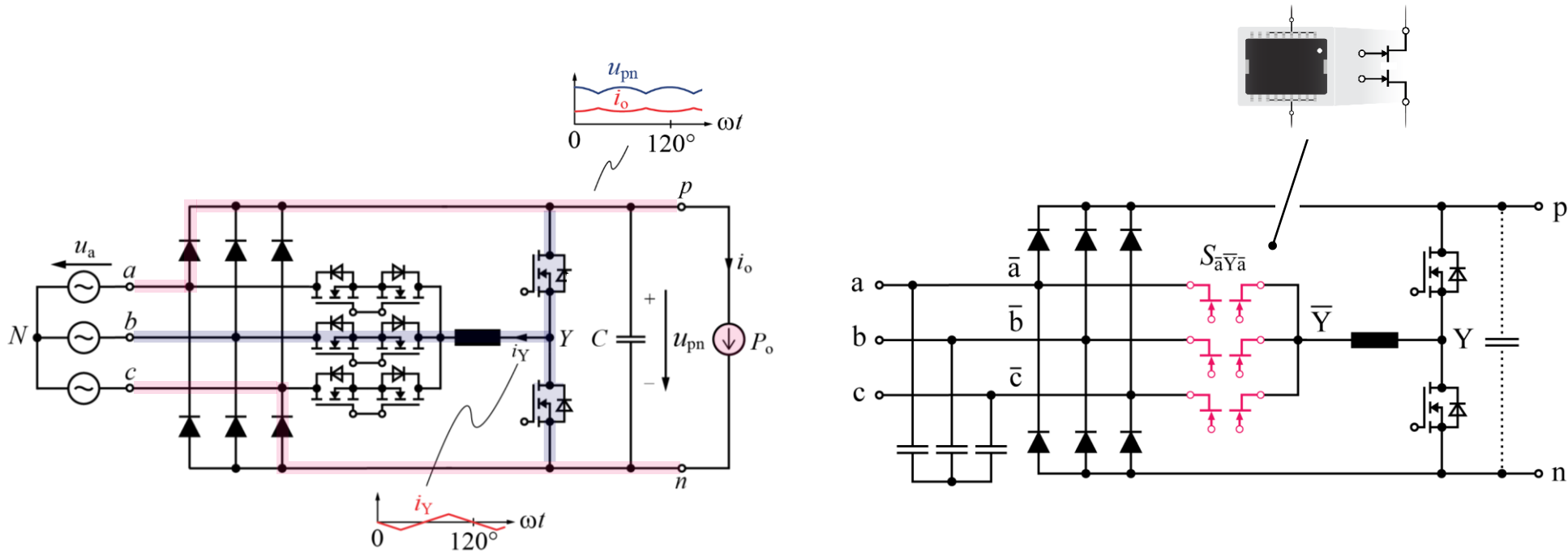
- Realization of the **Phase Selector Switches** of 3rd Harmonic Inj. PFC Rectifiers
- Bipolar Voltage Blocking / Current Carrying Capability
- Low Sw. Freq. / Mains Freq. Operation



- M-BDS \rightarrow Factor of 4 Reduction of Chip Area Comp. to Discrete Realization of Same $R_{(on)}$ (!)

Swiss Rectifier

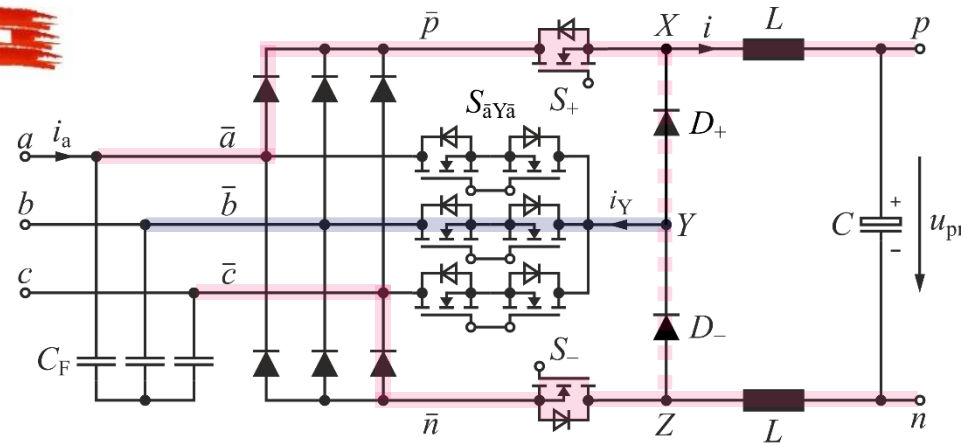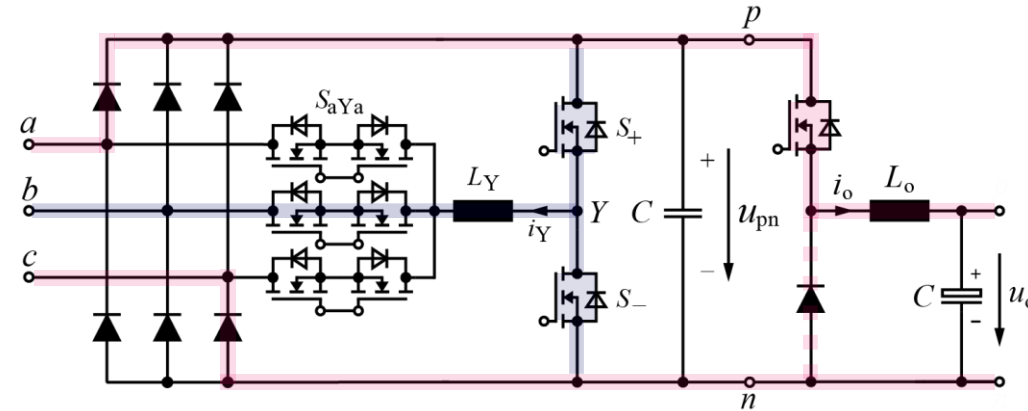- **Integration of 3rd Harmonic Injector Switches & Buck Output Stage**
- **Controlled Output Voltage**
- **Sinusoidal Mains Current**
- **i_y Def. by KCL: E.g. $i_a - i_c$**




- **Low Complexity**



Swiss Rectifier Demonstrator

- Efficiency $\eta = 99.26\%$ @ 60% Rated Load
- Mains Current $THD_I \approx 0.5\%$ @ Rated Load
- Power Density $\rho \approx 4\text{kW}/\text{dm}^3$

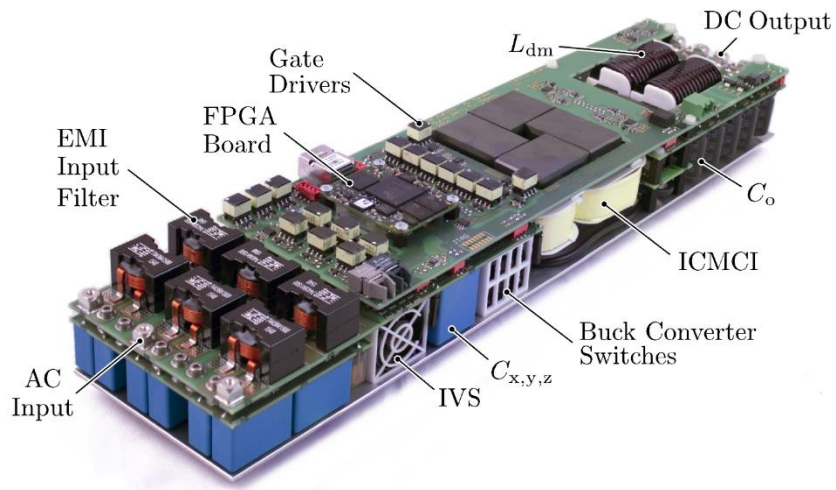$P_o = 8\text{ kW}$
 $U_N = 400\text{V}_{AC} \rightarrow U_o = 400\text{V}_{DC}$
 $f_s = 27\text{kHz}$




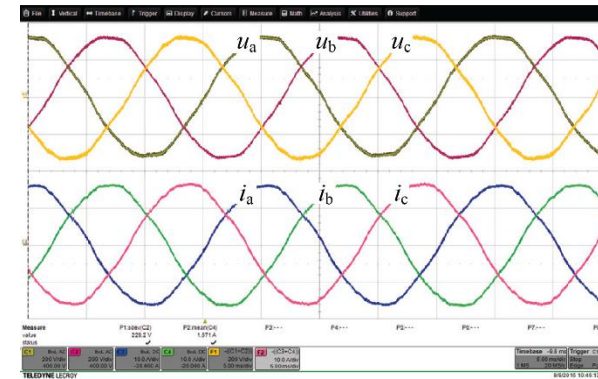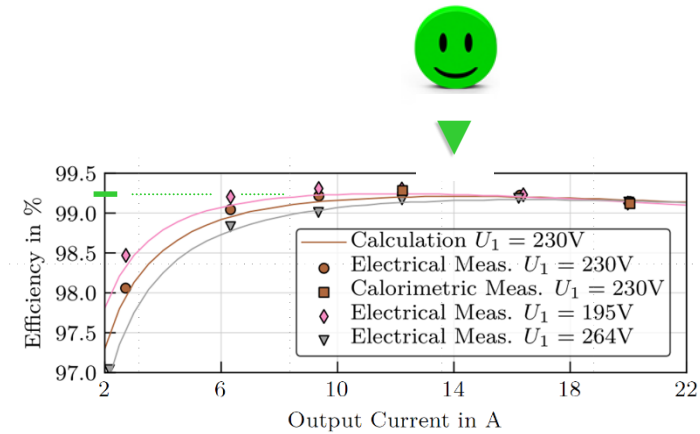- SiC Power MOSFETs & Diodes
- Integr. CM & Output Coupling Inductors (ICMCI)




Remark M-BDS-Based 3rd Harm. Inj. Rectifiers

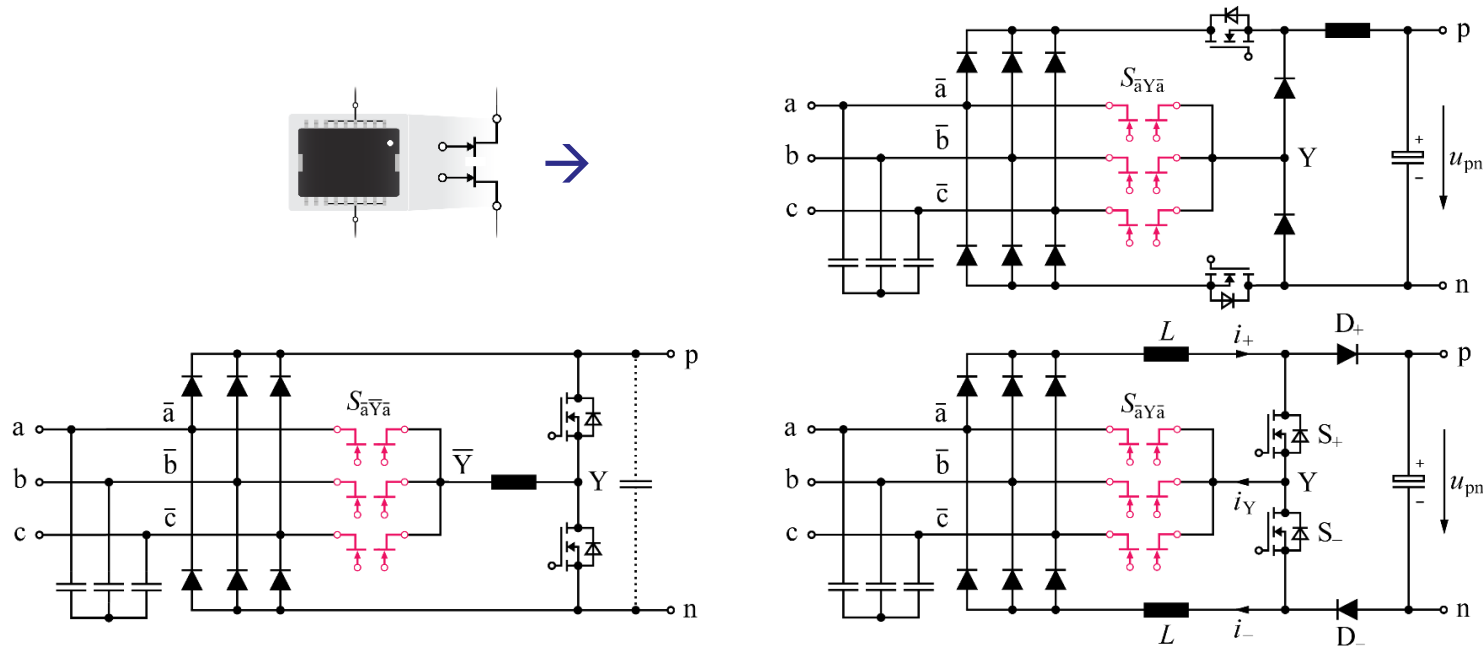- Bipolar Voltage Blocking / Current Carrying Capability
- Factor of 4 Reduction of Chip Area Comp. to Discrete Realization of Same $R_{(on)}$





- Mains Frequ. Operation of the Phase Selector Switches → Conduction Losses Only

3-Level T-Type Boost PFC Rectifier

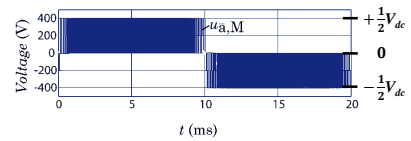

3-Level T-Type PFC (Vienna) Rectifier

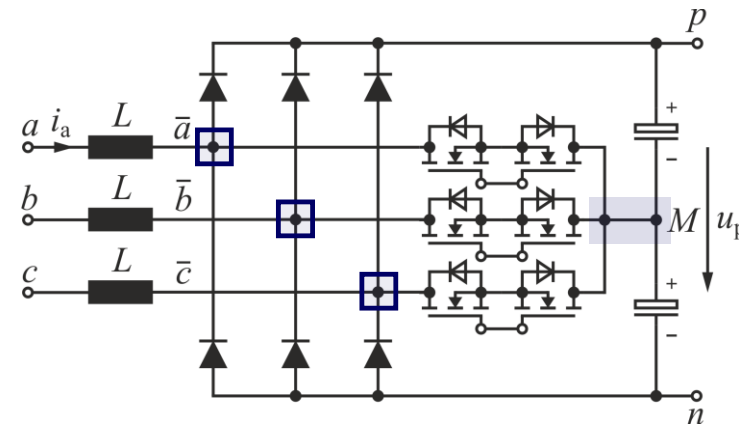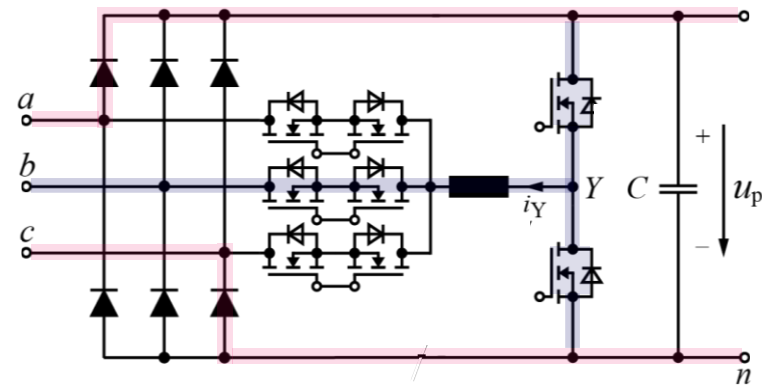- *3rd Harm. Inj. Inductor Shifted to AC-Side & PWM of DC-Midpoint Ref. Inj. Switches*
- *3-Level Diode Bridge Input Voltage*
- *Sinusoidal Input Current*
- *Controlled Output Voltage*




- *Low Sw. Voltage Stress*
- *Low AC-Side Inductance*
- *Low Conduction Losses*
- *Bridge-Leg & Phase Symmetry*

Vienna Rectifier Demonstrator (1)


- *Design for More Electric Aircraft Application*
- *650V CoolMOS & 1200V SiC Diodes*
- *Coldplate Cooling*

$P_o = 10 \text{ kW}$
 $U_N = 400V_{AC} \pm 10\%$
 $f_N = 50\text{Hz or } 360 \dots 800\text{Hz}$
 $U_o = 800V_{DC}$

$\eta = 96.8\%$

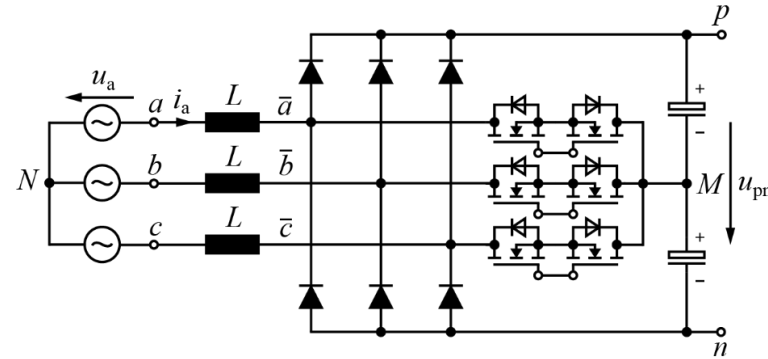

★ $\rho = 10 \text{ kW/dm}^3$

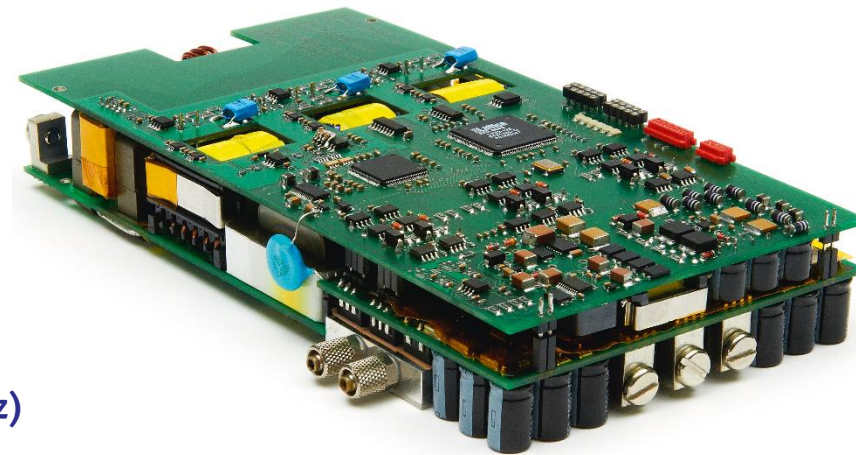

- $THD_i = 1.6\% @ f_N = 800\text{Hz} (f_p = 250\text{kHz})$


Vienna Rectifier Demonstrator (2)

- Design for More Electric Aircraft Application
- 650V CoolMOS & 1200V SiC Diodes
- Coldplate Cooling


$P_o = 10 \text{ kW}$
 $U_N = 400V_{AC} \pm 10\%$
 $f_N = 50\text{Hz or } 360 \dots 800\text{Hz}$
 $U_o = 800V_{DC}$

$\eta = 96.8\%$
 $\rho = 165 \text{ W/in}^3 \text{ (} 10 \text{ kW/dm}^3 \text{)}$
 $f_p = 250\text{kHz}$

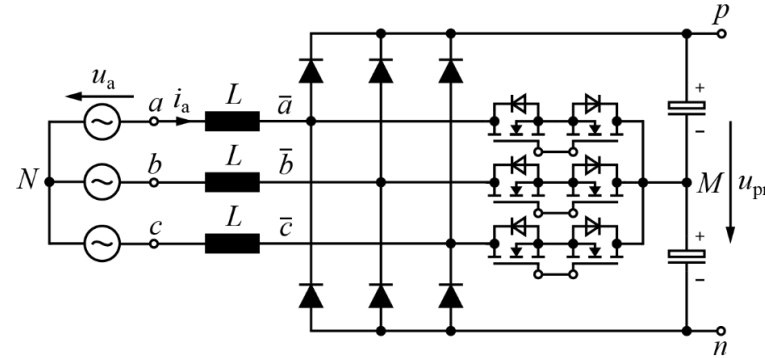- $THD_i = 1.6\% \text{ @ } f_N = 800\text{Hz}$
- System Allows 2- Φ Operation




10A/Div
 200V/Div
 0.5ms/Div

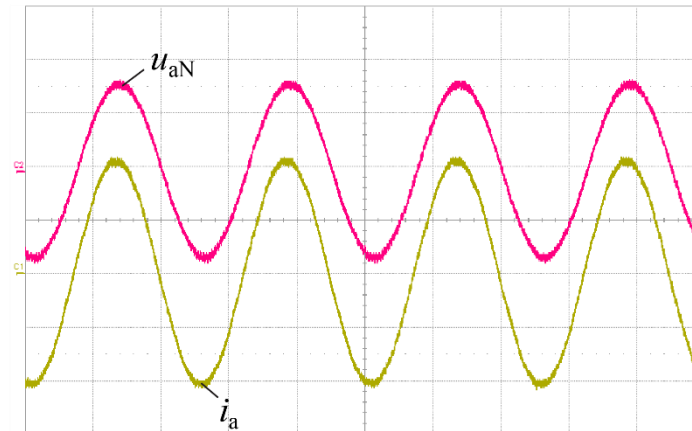

Remark Application of M-BDSs

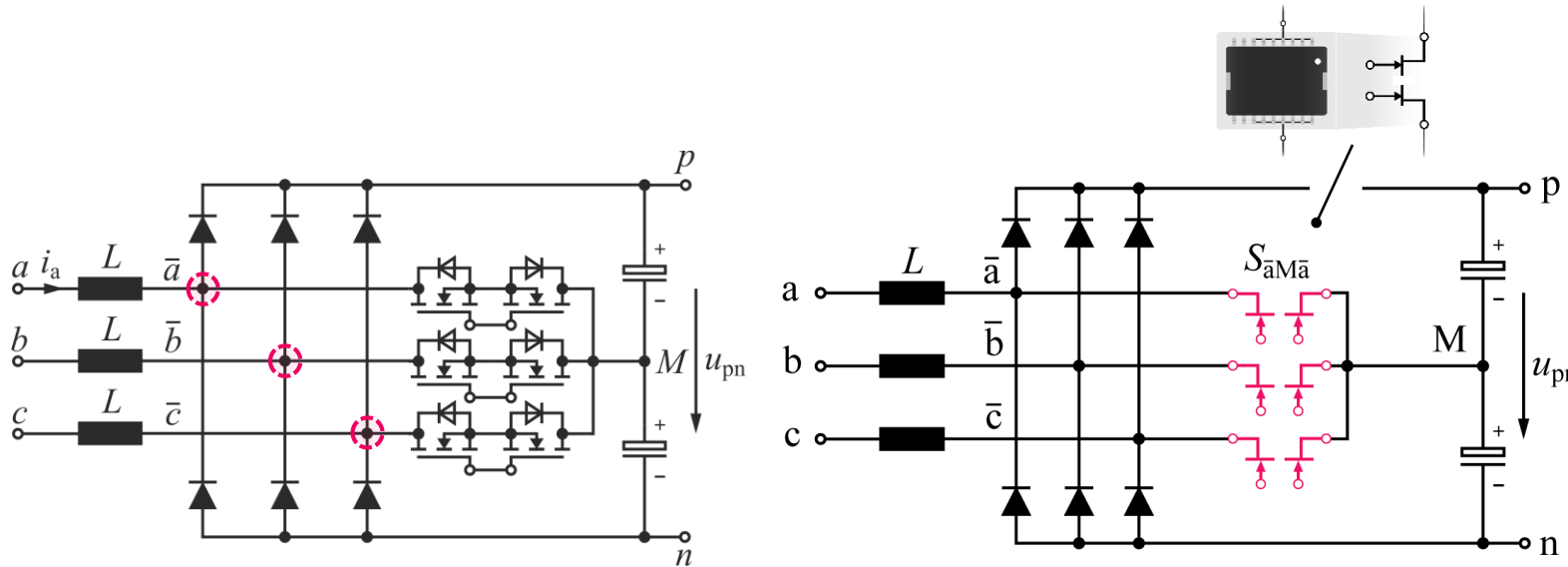- *M-BDS-Realization of the Midpoint-Switches*
- *Significant Reduction of Cond. Losses @ Given Chip Area*



- *600V M-BDSs @ $U_{pn} = 800V_{DC}$ in Combination w/ 1200V SiC Diodes (MOSFETs for Bidir. Power Flow)*

Global Megatrends



Digitalization
Renewable Energy
Sustainable Mobility →
Industry Automation
Etc.

Electric Vehicle Outlook 2019

- **Bloomberg NEF** — **By 2040** — **57%** of All Passenger Vehicle Sales
30% of Global Passenger Vehicle Fleet


Electric Cars Will Win on Price

Falling battery prices undercut gasoline cars by mid-2020s



Global long-term passenger vehicle sales by drivetrain

Million vehicles

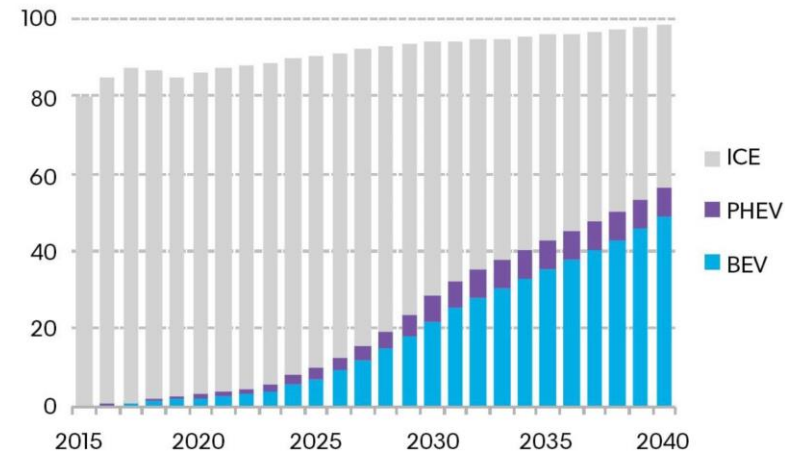

Source: BloombergNEF

- **Falling Battery Costs** → **Price Parity of EVs & ICE-V by Mid-2020s** → **Tipping Point for EV Industry**

Disruptive Innovations

- **Example** — *Rapid Change of Transportation Enabled by New Technology (ICE) & Business Model*
Tony Seba: "All New Vehicles, Globally, will be Electric by 2030"

— NY City, 5th Av., Easter Parade → *Year 1900: One Motor Cycle / Year 1913: One Horse & Carriage (!)*



Source: Tony Seba

- **Further Examples** - *Digital / Analogue Photography, VHS Cassette Tape System / DVD etc.*
- *The Stone Age Didn't End for the Lack of Stone (Disrupted by Bronze Tools)*

Ultra-Fast / High-Power EV Charging

- *Modular Mains Interfaces | Future Non-Isolated Virtually Grounded Systems*
- *Very Wide Output Voltage Range (200...800V)*



- *Local Battery Buffer*
- *320kW → 500km Range in 20min*

ChargePoint stations (projected growth)





Source: ChargePoint




Bidirectional Boost-Buck PFC Rectifier Concepts

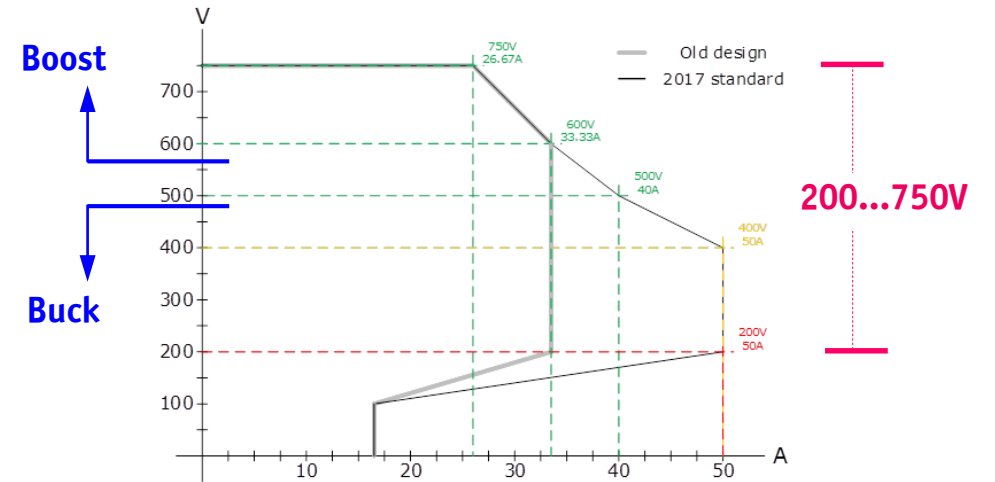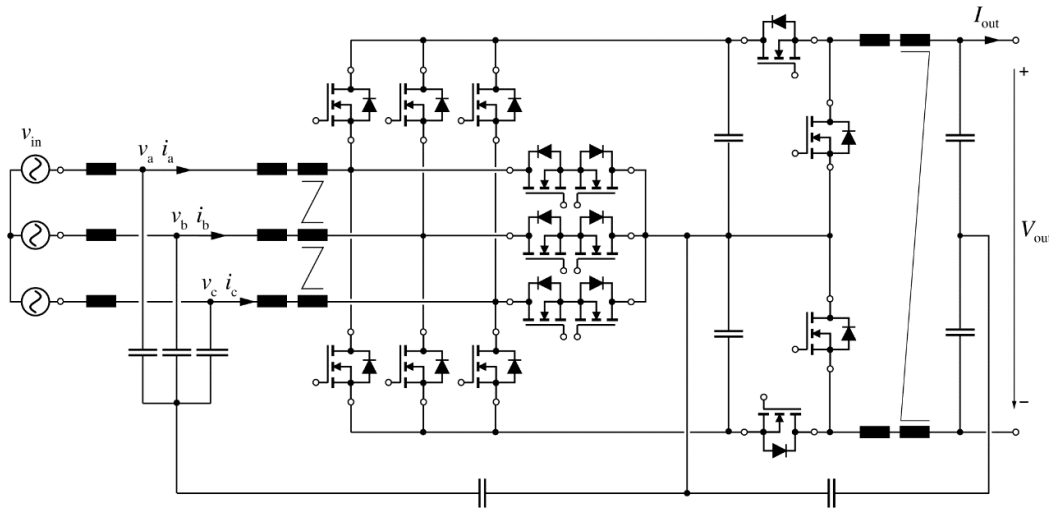- *Vienna Rectifier Type Bidirectional Boost PFC AC/DC Front-End & DC/DC Buck Output Stage*
- *Coordinated "Synergetic Control" of AC/DC and DC/DC Converter Stage for Min. Sw. Losses*



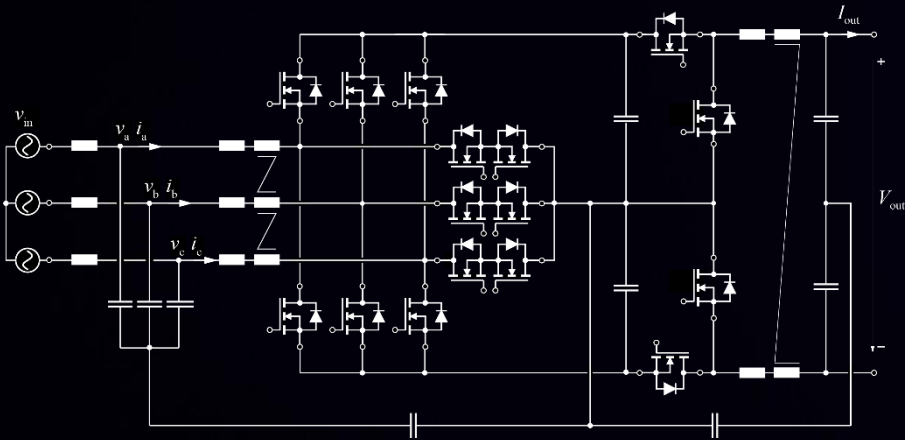- *Future Non-Isolated EV-Charging → Earth Leakage Curr. Limited Using "Virtual Ground Control"*



DUALITY

Boost-
Buck

Buck-
Boost


DUALITY

IEEE TRANSACTIONS ON INDUSTRY APPLICATIONS, VOL. 29, NO. 2, MARCH/APRIL 1993

Quasi-Dual Modulation of Three-Phase PWM Converters

Johann W. Kolar, Member, IEEE, Hans Ertl, Member, IEEE, and Franz Zach, Member, IEEE


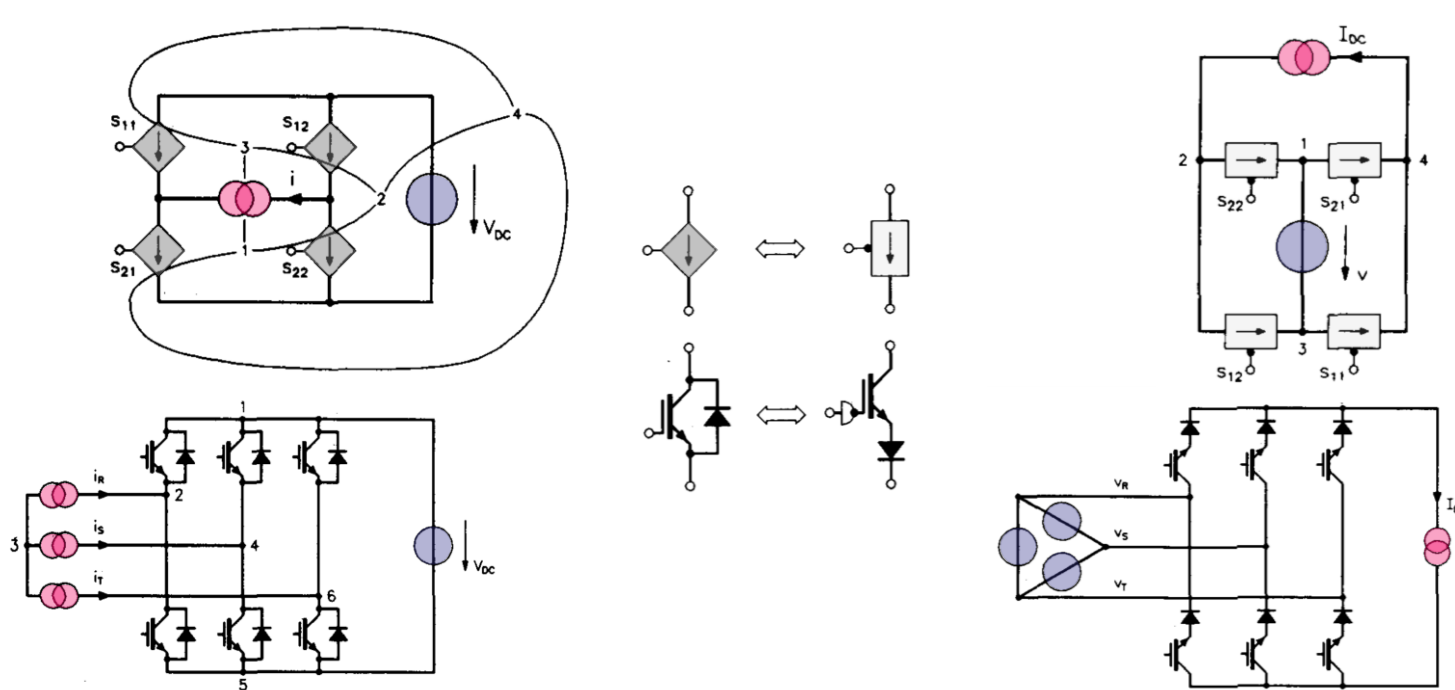
- **Duality of Voltage DC-Link & Current DC-Link Converter Circuits**
- **Unipolar Blocking / Bidir. Current → Bipolar Blocking Unidir. Switches → Appl. of M-BDSs (!)**



- **"Boost-Buck" Translated into "Buck-Boost" Functionality / Lower # of Ind. Components**

Bidirectional *Buck-Boost* PFC Rectifier Concepts

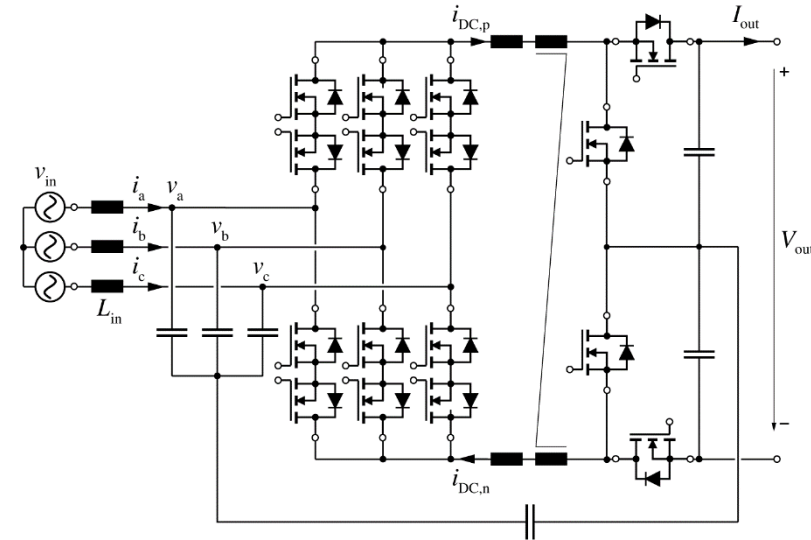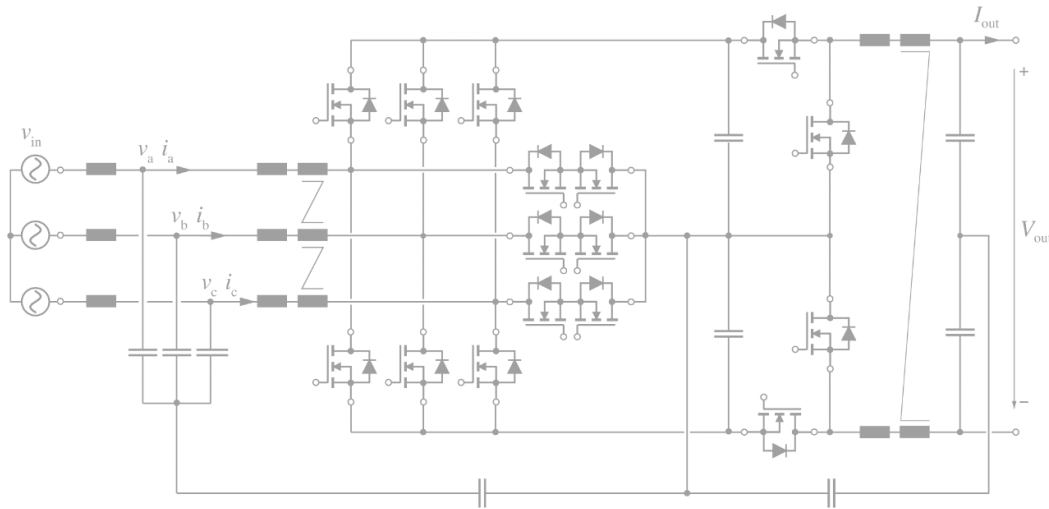- *Boost—Buck OR Buck—Boost Combination*
- *Closed Loop vs. Open Loop Mains Current Control & Active Input Filter Damping*
- *“Synergetic Control” of AC/DC and DC/DC Converter Stage*




- *AC/DC Buck-Stage Output Inductor Utilized as DC/DC Boost Inductor → Min. # of Inductive Components*


Boost-Buck | Buck-Boost Demonstrator Systems

- 10 kW @ 400...800V_{DC} @ 3- Φ 400V_{rms} Mains
- $U_{out} = 200 \dots 800V_{DC}$
- $\eta = 98.8\%$ @ 5.4 kW/dm³
- AC/DC — $f_{sw} = 100$ kHz
- DC/DC — $f_{sw} = 2 \times 100$ kHz/200 kHz *eff.*

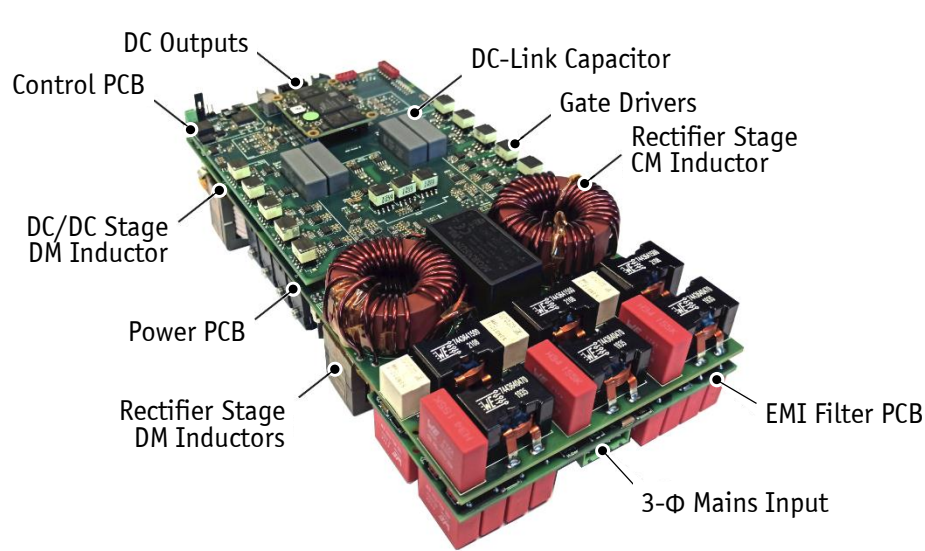- 10 kW @ 400...1000V_{DC} @ 3- Φ 400V_{rms} Mains
- $U_{out} = 200 \dots 1000V_{DC}$
- $\eta = 98.6\%$ @ 6.4 kW/dm³
- AC/DC — $f_{sw} = 100$ kHz
- DC/DC — $f_{sw} = 2 \times 50$ kHz/100 kHz *eff.*





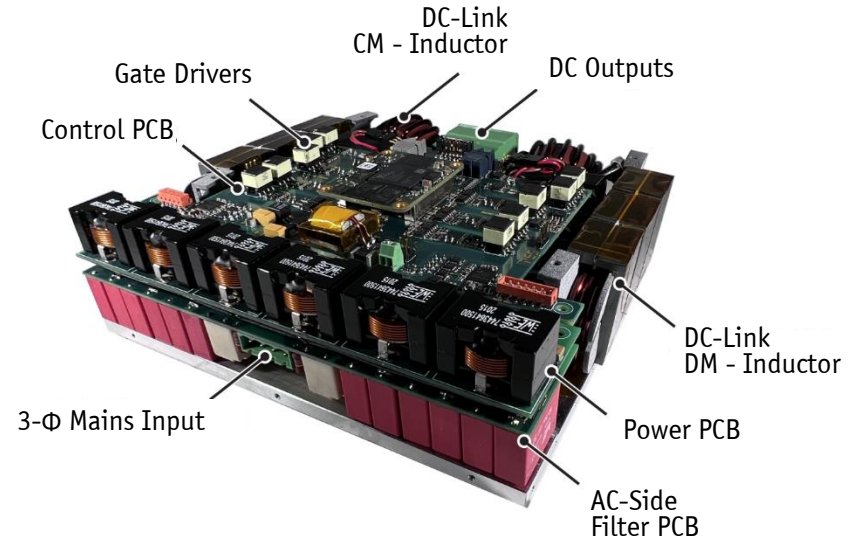
- **Boost-Buck Voltage DC-Link PFC Rectifier**



- **Buck-Boost Current DC-Link PFC Rectifier**

Remark Application of M-BDSs

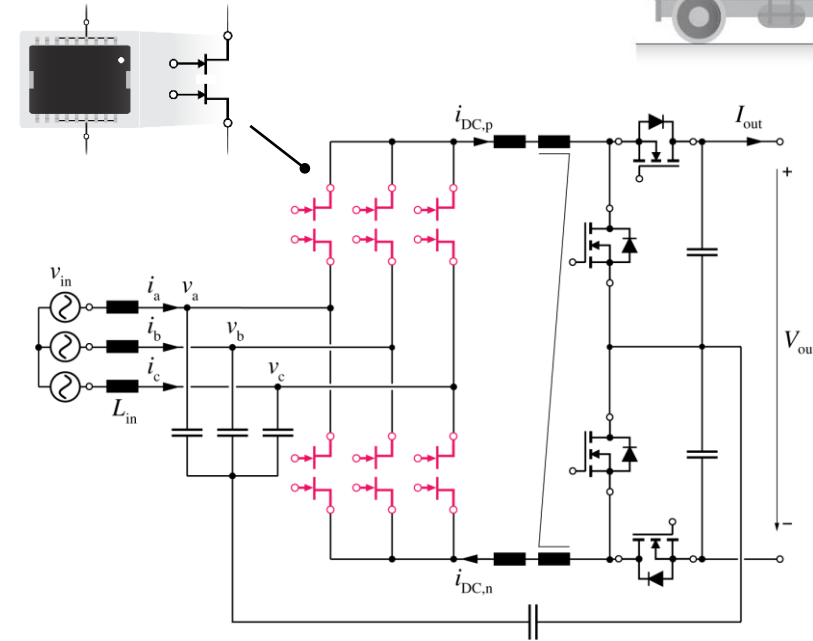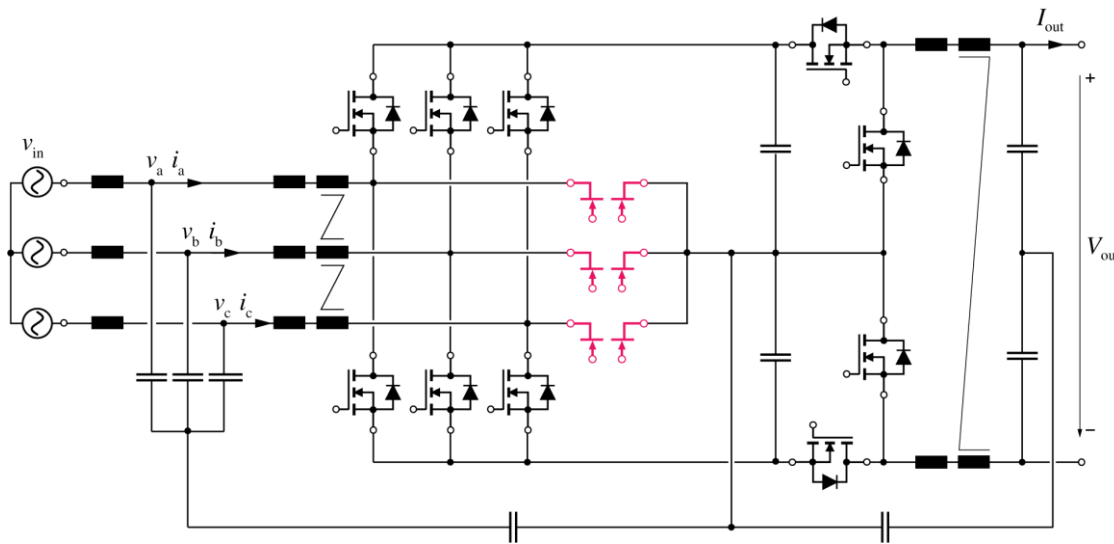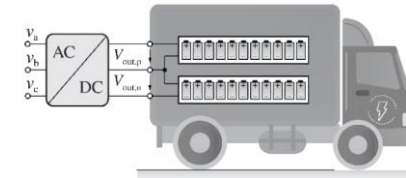- Boost—Buck OR Buck—Boost Combination
- Closed Loop vs. Open Loop Mains Current Control & Active Input Filter Damping
- “Synergetic Control” of AC/DC and DC/DC Converter Stage





- 600V M-BDSs for Boost—Buck & 1200V M-BDSs for Buck—Boost Combination @ 400V_{rms} Mains

*3- Φ Isolated
Matrix-Type Single-Stage
PFC Rectifier*




Isolated Matrix-Type PFC Rectifier (1)

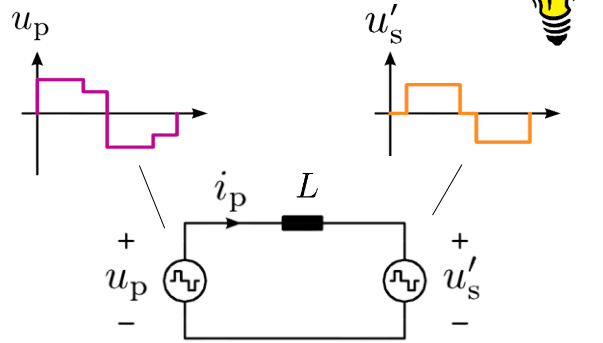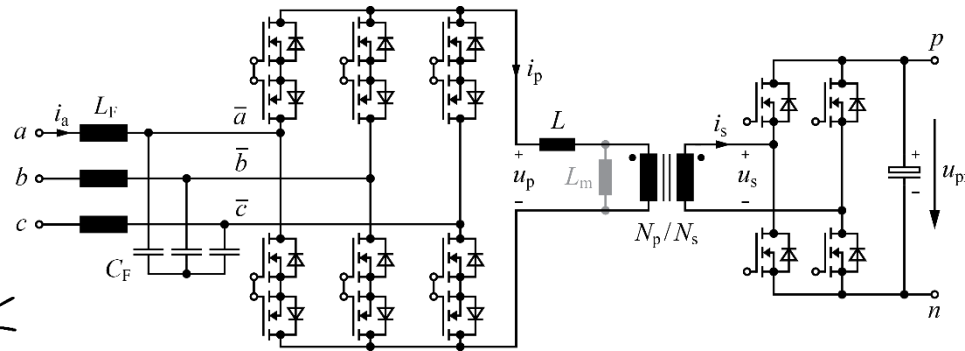- Based on Dual Active Bridge (DAB) Concept
- Opt. Modulation ($t_1 \dots t_4$) for Min. Transformer RMS Curr. & ZVS or ZCS
- Allows Buck-Boost Operation



● Equivalent Circuit

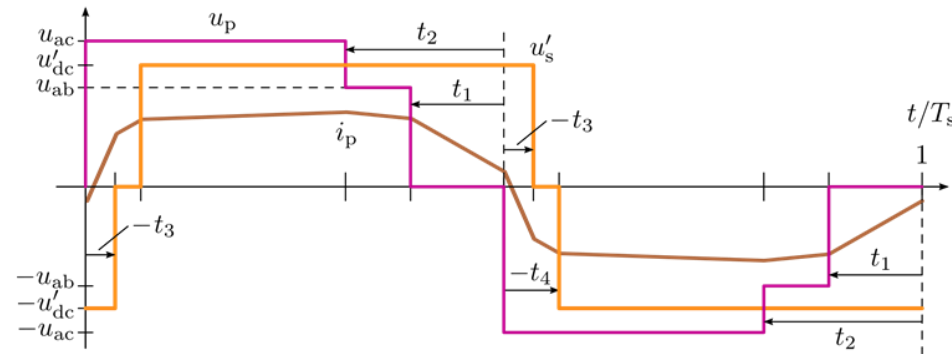


● Transformer Voltages / Currents



Isolated Matrix-Type PFC Rectifier (2)

- Efficiency $\eta = 98.9\%$ @ 60% Rated Load (ZVS)
- Mains Current $THD_I \approx 4\%$ @ Rated Load
- Power Density $\rho \approx 4\text{kW}/\text{dm}^3$

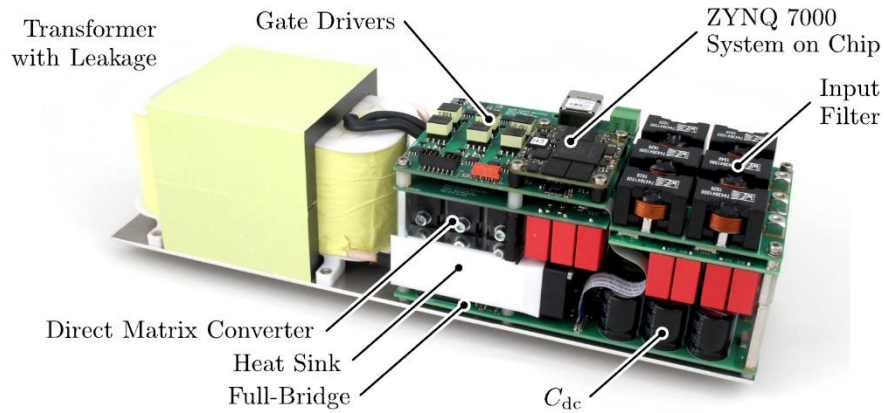$P_o = 8\text{ kW}$
 $U_N = 400\text{V}_{AC} \rightarrow U_o = 400\text{V}_{DC}$
 $f_s = 36\text{kHz}$





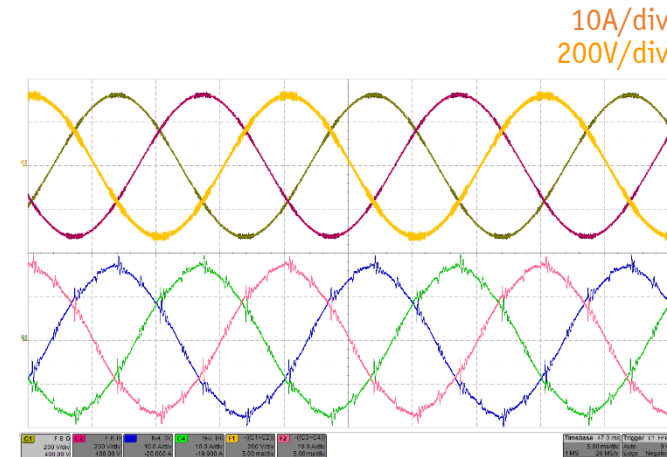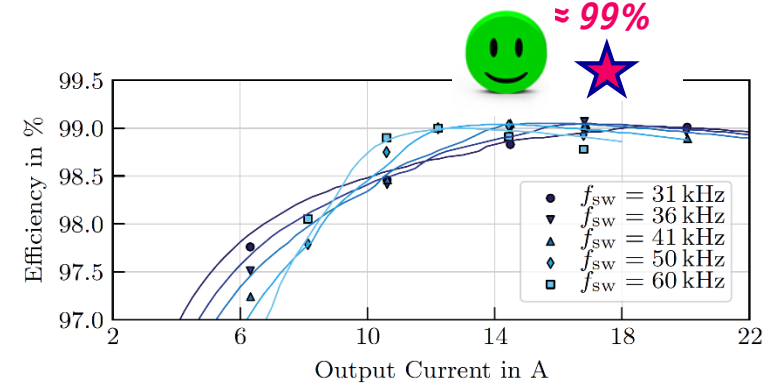- ▶ 900V / 10mΩ SiC Power MOSFETs
- ▶ Opt. Modulation Based on 3D Look-Up Table



Remark Application of M-BDSs

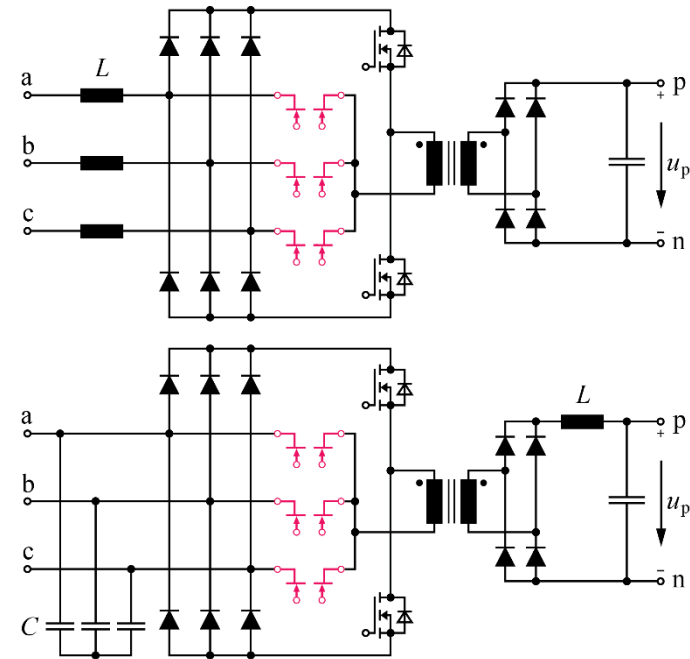
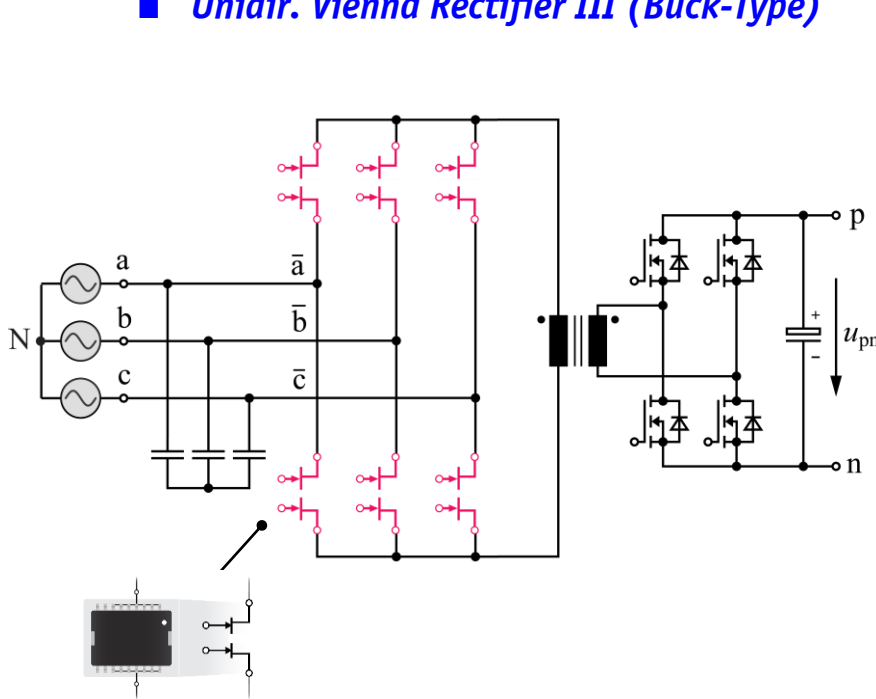
- Matrix-Type Bidirectional DAB-Based Topology
- Unidir. Vienna Rectifier II (Boost-Type)
- Unidir. Vienna Rectifier III (Buck-Type)



- Functional Integration → Lower Complexity BUT Limited Controllability

Remark Phase-Modular Isolated Matrix-Type PFC Rectifier

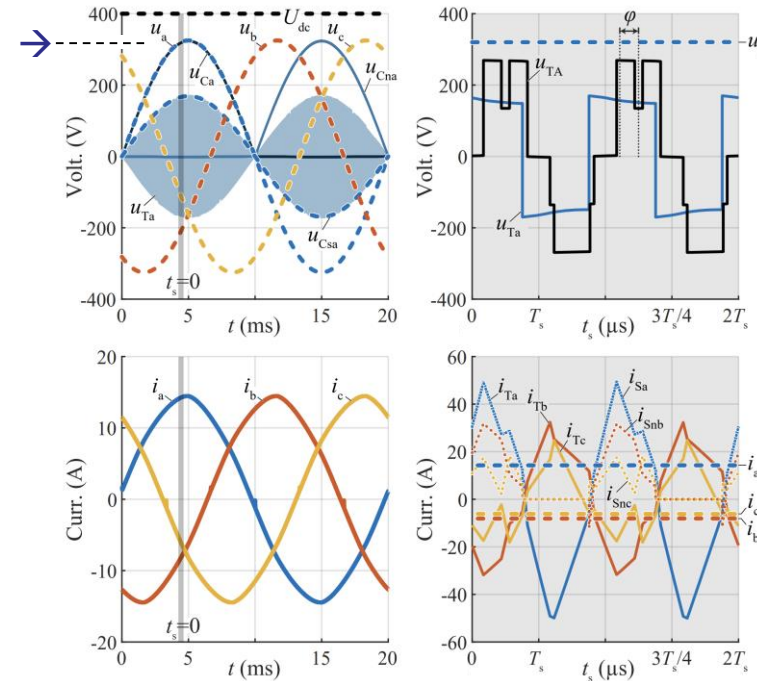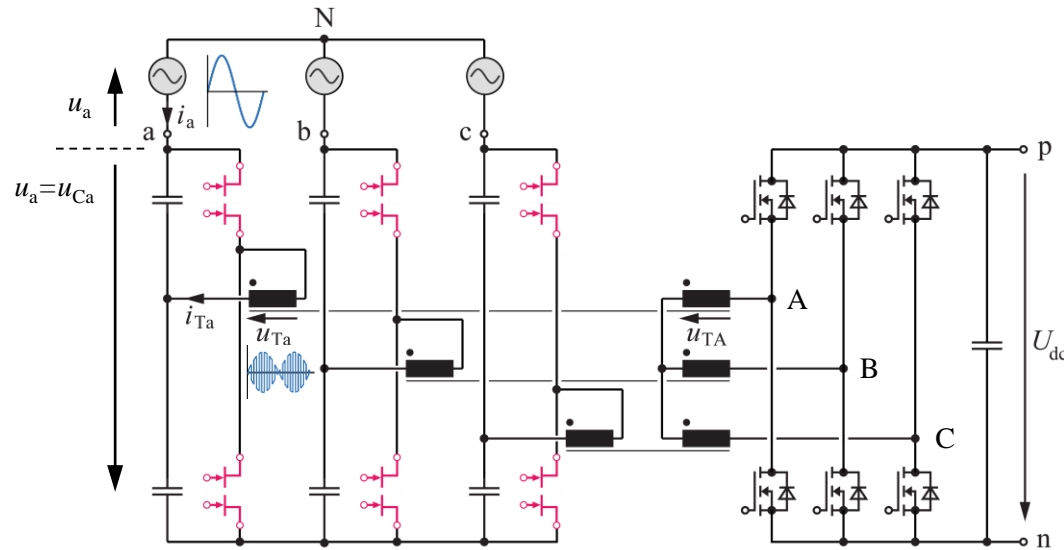- Voltage Stress on AC-Side Power Transistors Determined by PHASE Voltage Amplitude (!)
- 600V GaN MBDS for 400V RMS Line-to-Line Grid ($U_{pk} = 560V$)
- Unity Power Factor / Bidirectional



- Dual Active Bridge-Type Control
- AC-Side Phase Modularity — Full Rated Power Operation @ 1- Φ Input (!)

Global Megatrends




Digitalization
Sustainable Mobility
Renewable Energy
Industry Automation →
Etc.

Variable Speed Motor Drive (VSD) Systems

- *Industry Automation / Robotics*
- *Material Machining / Processing – Drilling, Milling, etc.*
- *Compressors / Pumps / Fans*
- *Transportation*
- *etc., etc.*

.... Everywhere !

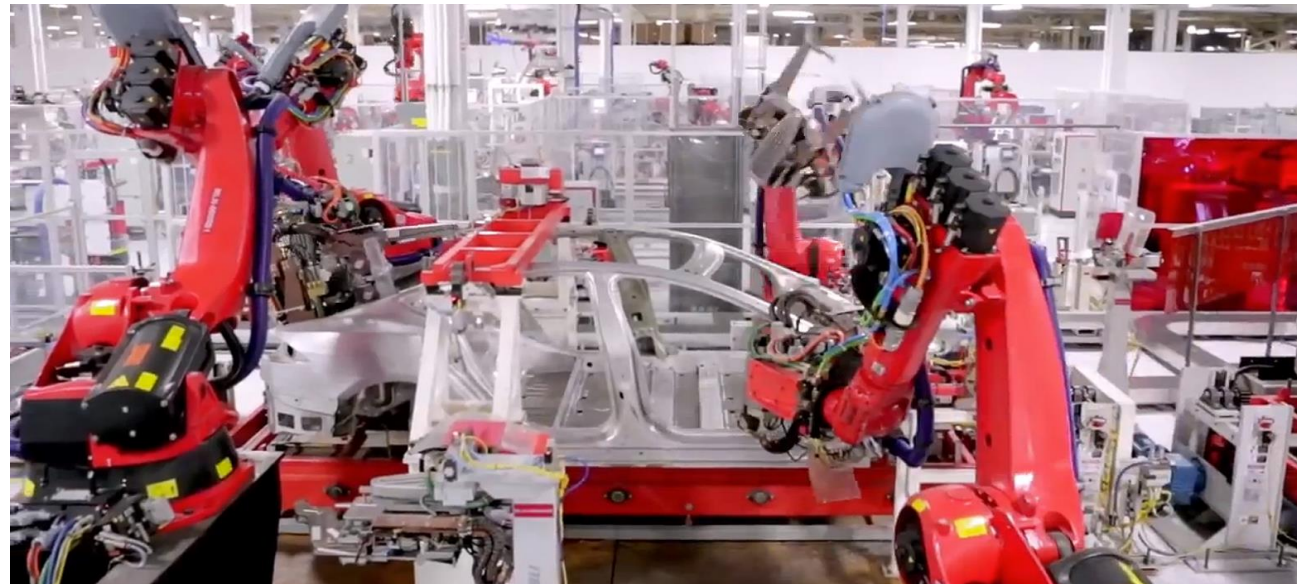


Source:  TESLA MOTORS

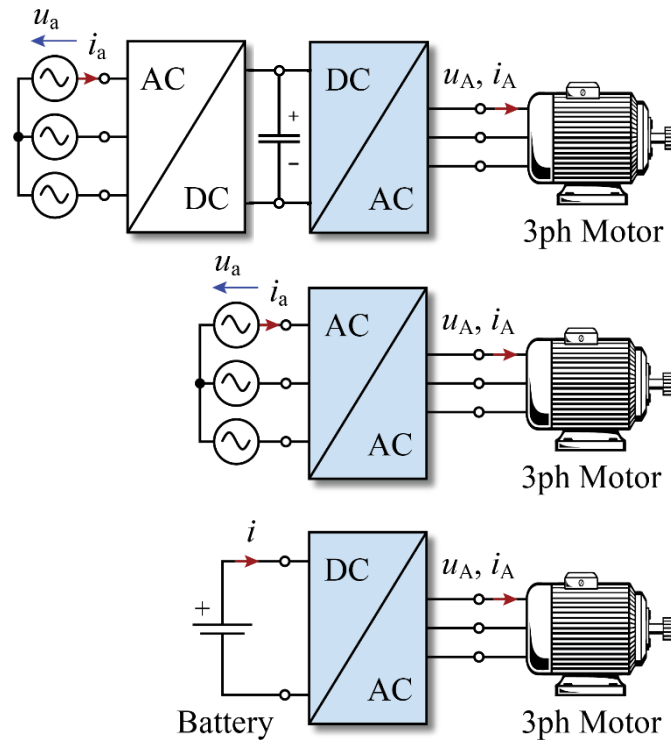- *60...70 % of All Electric Energy Used in Industry Consumed by VSDs*

Variable Speed Drive Concepts

- **DC-Link Based AC/DC/AC OR Matrix-Type AC/AC Converters**
- **Battery OR Fuel-Cell Supply OR Common DC-Bus Concepts**



38%
of electric energy use is for motors
in commercial buildings.

Source: **ABB**




70%
of electricity consumed by industry
is used in electric motor systems.

- **45% of World's Electricity Used for Motors in Buildings & Industrial Applications**

Current DC-Link Buck-Boost Inverter (1)


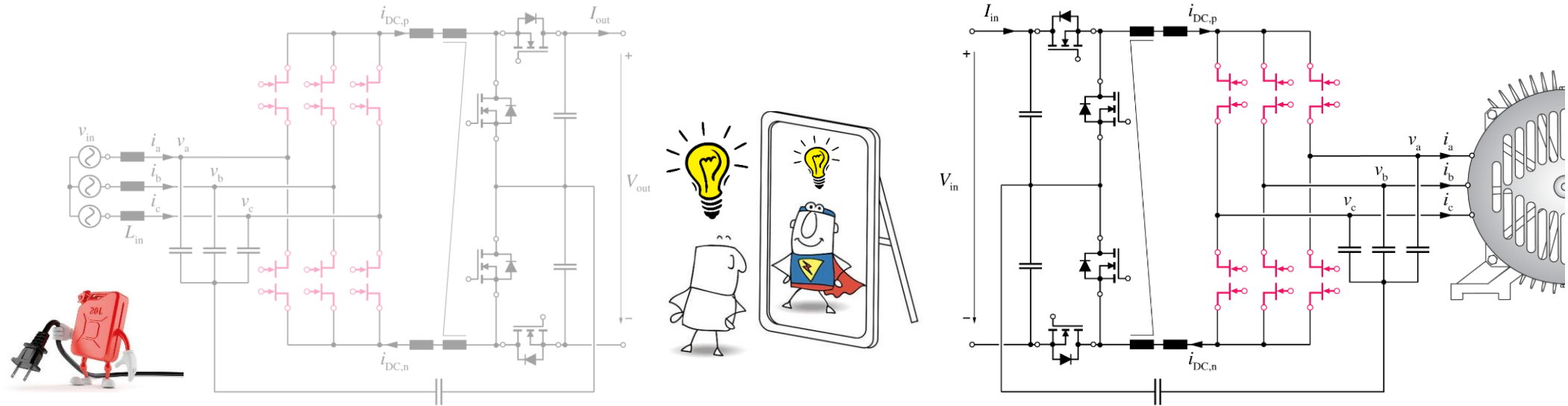
- *Derivation Based on Bidirectional Buck-Boost PFC Rectifier Topology (EV Charger)*
- *Lower # of Ind. Components Compared to Boost-Buck Approach*



- *DC/DC Buck Converter Performs Voltage → Current Translation*
- *Coordinated Control / Modulation of DC/DC & Inverter Stage for Min. Sw. Losses*


Current DC-Link Buck-Boost Inverter (2)

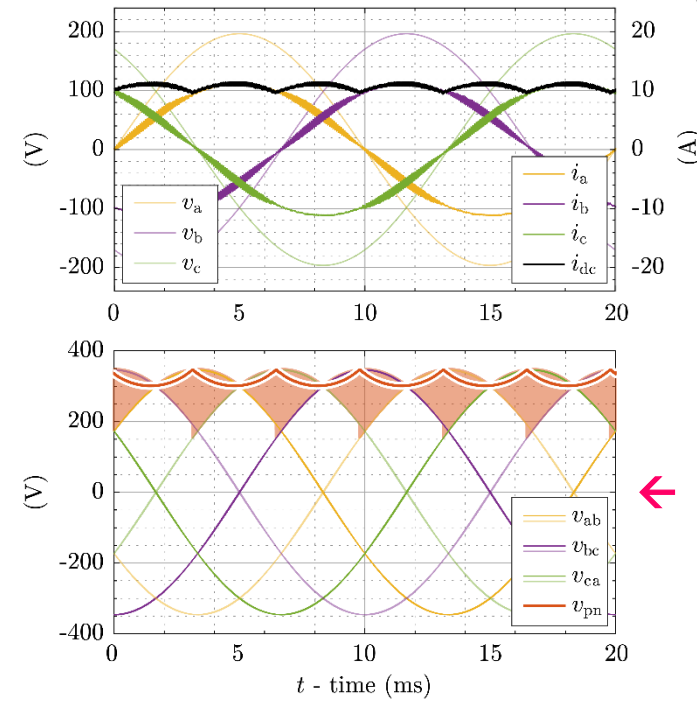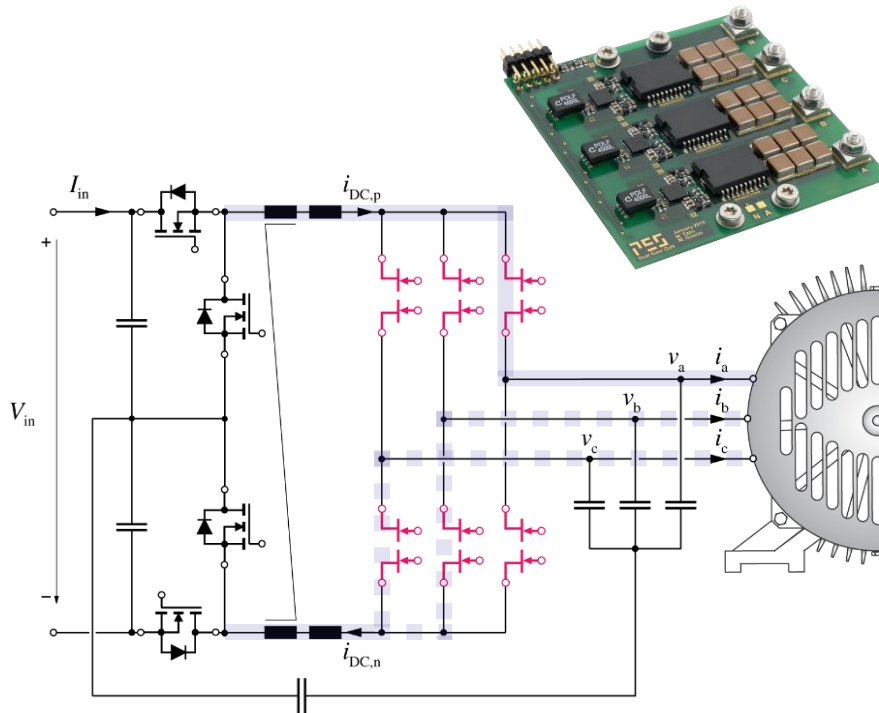- **“Synergetic” Control of DC/DC Buck Converter & Current DC-Link Inverter Stage**
- **6-Pulse-Shaping of DC Current by Buck-Stage → Allows Inverter Phase Clamping**




- **Switching of Only 2 of 3 Phase Legs → Reduction of Sw. Losses by ≈ 86% (!)**

3- Φ AC/AC Conversion

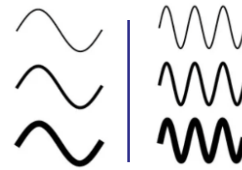

3- Φ Current DC-Link AC/AC Converter (1)

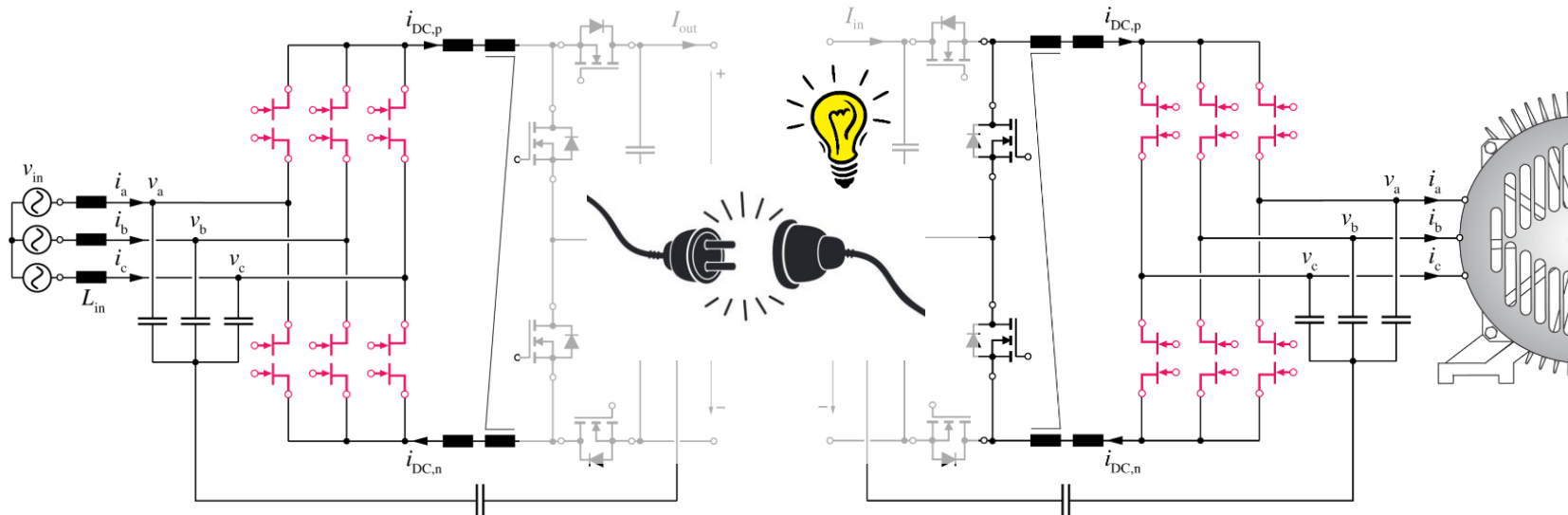- *DC-Side Coupling of Buck-Boost Current DC-Link PFC Rectifier & Inverter — AC/DC/AC*
- *Full Sinewave Filtering @ Input & Output w/ Single Magnetic Component*





- *Bipolar Blocking / Unidir. Switches / Unidir. DC-Link Current Sufficient for Bidir. Power Conversion*
- *Modulation-Based Inversion of DC-Link Voltage Polarity \rightarrow Inv. of Power Flow Direction*

3- Φ Current DC-Link AC/AC Converter (2)

- *Sinusoidal Motor Voltage Achieved w/ Single Ind. Component*
- *Unidir. Valves Sufficient for Bidir. Power Conversion*
- *M-BDSs — Synchronous Rectification*

Source: www.mb-drive-services.com

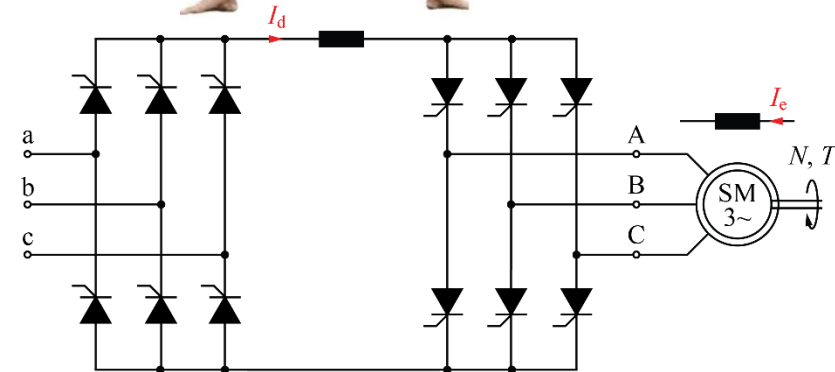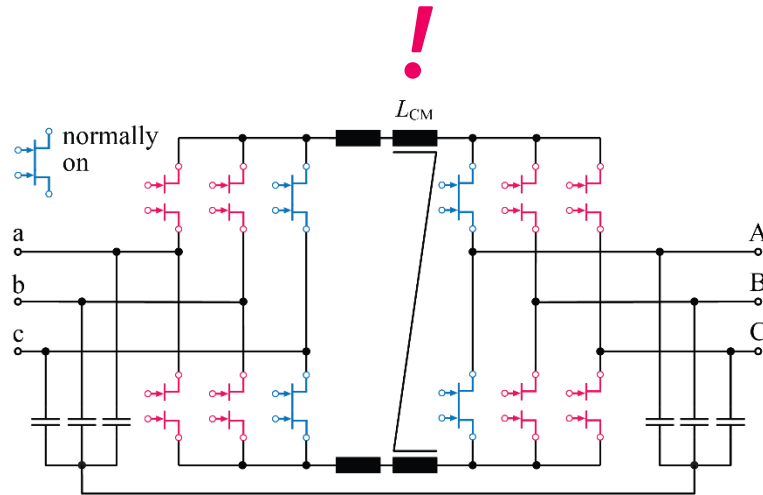



- *Relation to High-Power Thyristor-Based Medium Voltage Synchr. Machine Variable Speed Drives*

Remark Self Reverse-Blocking M-BDS-Concept (1)

■ Bidir. Curr. DC-Link Converters — Unidir. I_{dc} & Bipolar U_{dc} OR Bidir. I_{dc} & Unipolar U_{dc}

- HV Switch + HV Diode
- M-BDS
- "Self-Switching"

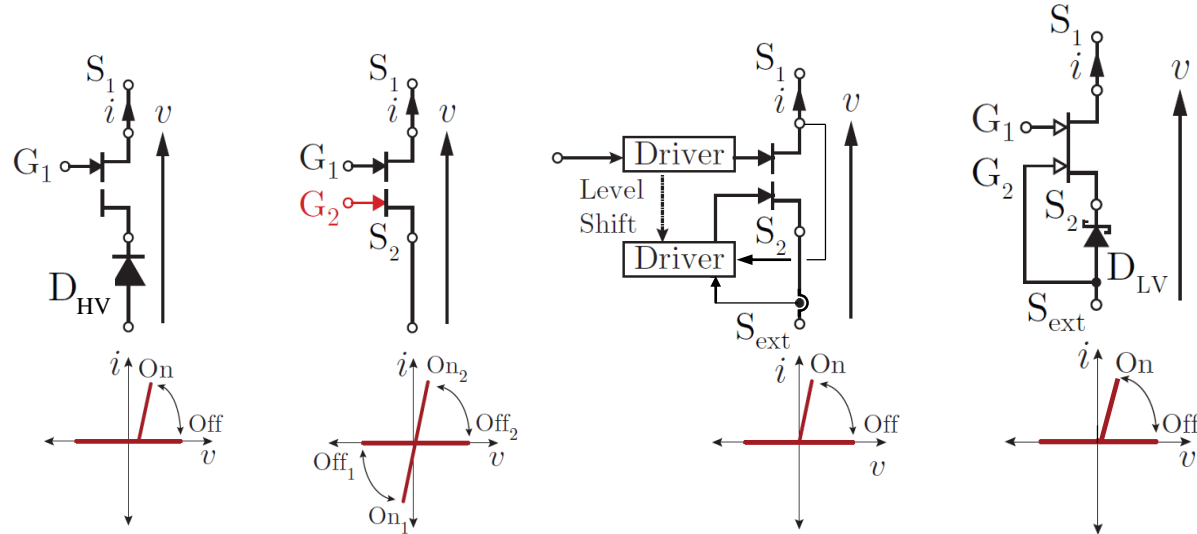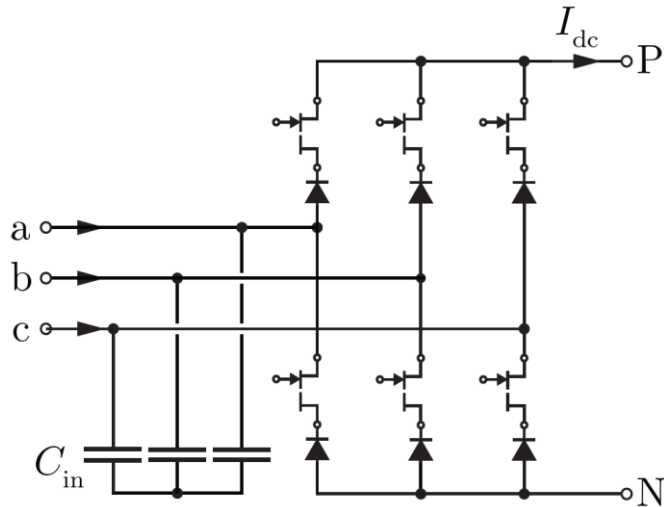HV Diode Characteristic / High Cond. Losses
 Ohmic Cond. Char. BUT 2 External Gate Signals / 2 Gate Drives
 Ohmic Cond. Char. BUT High Local Complexity (Sensing)




• SRB-MBDS Quasi-Ohmic Cond. Char. (Cascode w/ LV Si Schottky Diode) & 1 External Gate


Remark Self Reverse-Blocking M-BDS-Concept (2)

■ Bidir. Curr. DC-Link Converters — Unidir. I_{dc} & Bipolar U_{dc} OR Bidir. I_{dc} & Unipolar U_{dc}

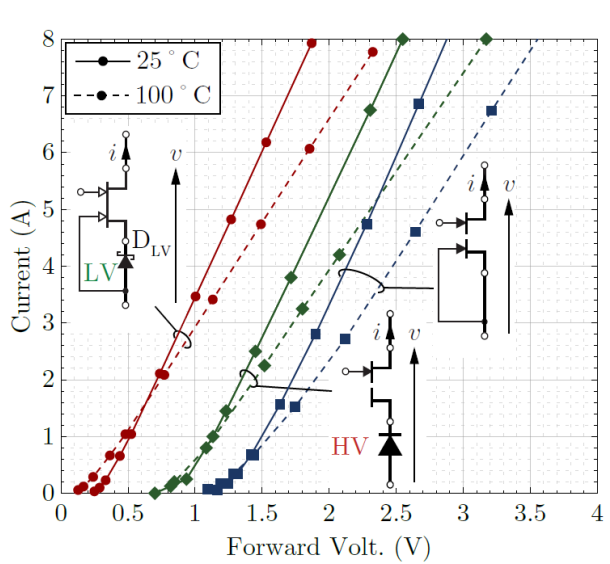- HV Switch + HV Diode HV Diode Characteristic / High Cond. Losses
- M-BDS Ohmic Cond. Char. BUT 2 External Gate Signals / 2 Gate Drives
- "Self-Switching" Ohmic Cond. Char. BUT High Local Complexity (Sensing)



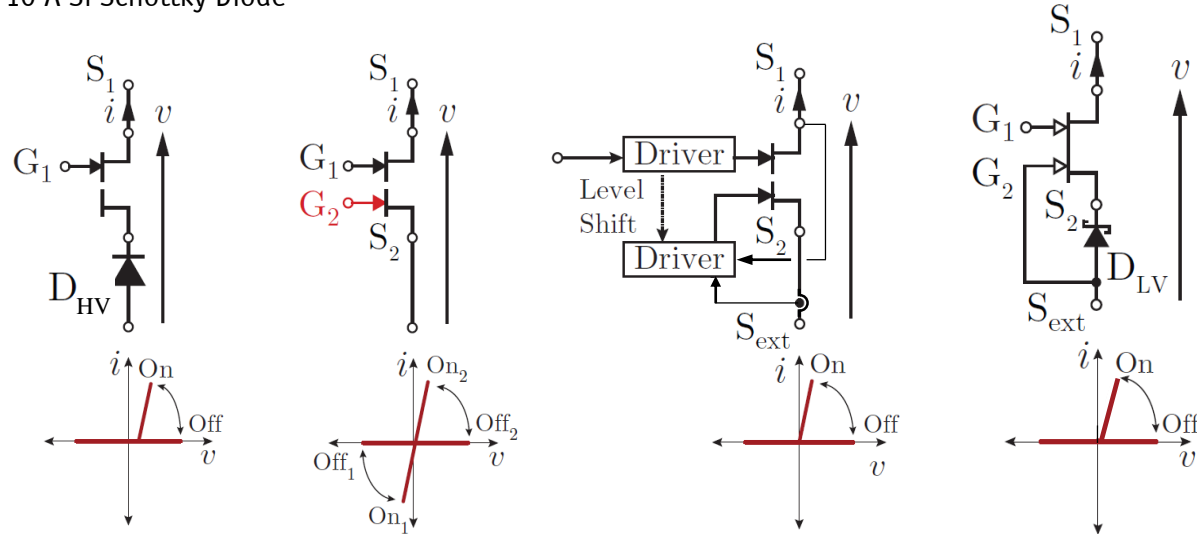600V 190 mΩ GaN M-BDS
40V/10 A Si Schottky Diode




• SRB-MBDS Quasi-Ohmic Cond. Char. (Cascode w/ LV Si Schottky Diode) & 1 External Gate

DUALITY

■ Current DC-Link Topology

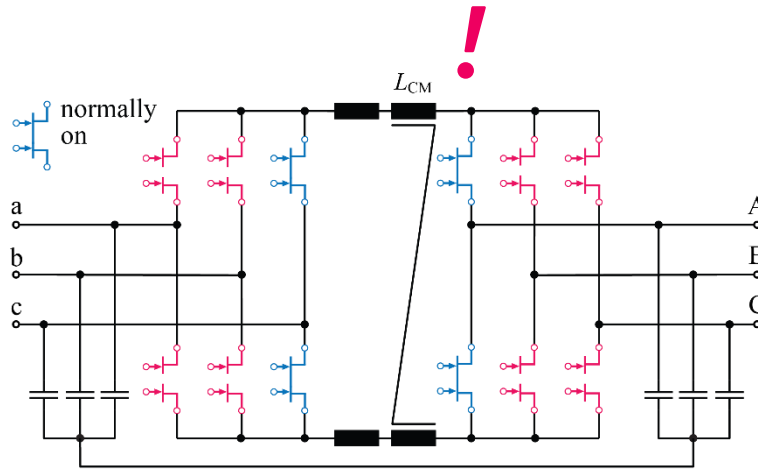
- Application of *M-BDSs*
- Complex 4-Step Commutation
- *Low Filter Volume*



- Challenging *Overvoltage Protection*
- *Limited Control Dynamics*

■ Voltage DC-Link Topology

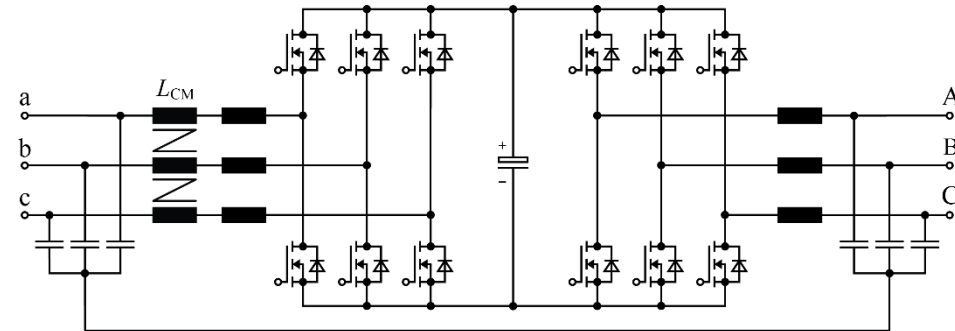- *Standard Bridge-Legs*
- *Low-Complexity Commutation*
- *Defined Semiconductor Voltage Stress*
- *Facilitates DC-Link Energy Storage*




- *High Input / Output Filter Volume*

DUALITY

■ Current DC-Link Topology

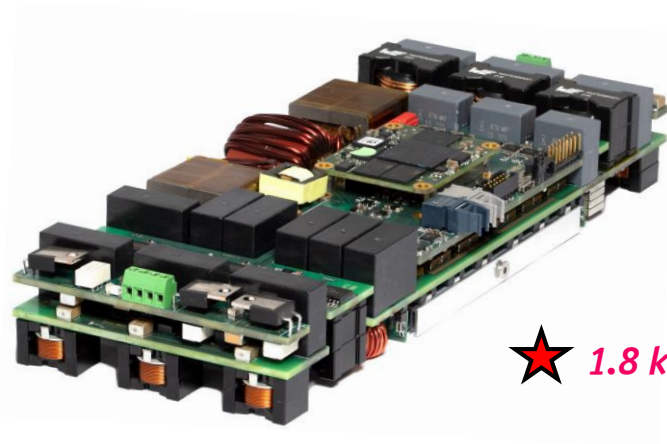
- Application of *M-BDSs*
- Complex 4-Step Commutation
- *Low Filter Volume*



★ 1.8 kW/dm³

■ Voltage DC-Link Topology

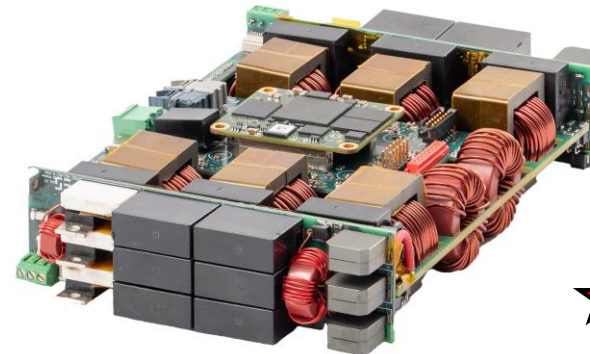- *Standard Bridge-Legs*
- *Low-Complexity Commutation*
- *Defined Semiconductor Voltage Stress*
- *Facilitates DC-Link Energy Storage*



★ 1.7 kW/dm³




- *All-600V-GaN AC-AC VSDs / 1.4 kW, 200 V L-L / Full EMI Filter (Grid & Motor) / 97% Nominal Eff.*

3- Φ AC/AC Matrix Converter

$$\begin{Bmatrix} 1 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 1 & 1 \end{Bmatrix}$$

Indirect & Direct 3- Φ AC/AC Matrix Converter (1)

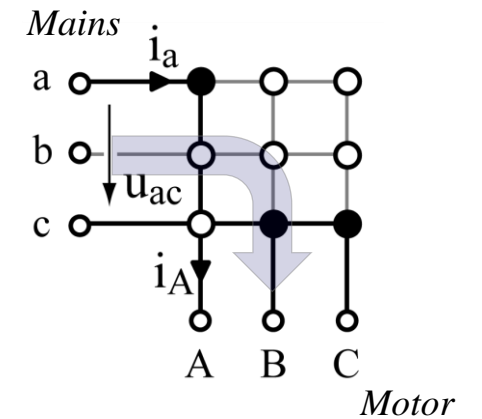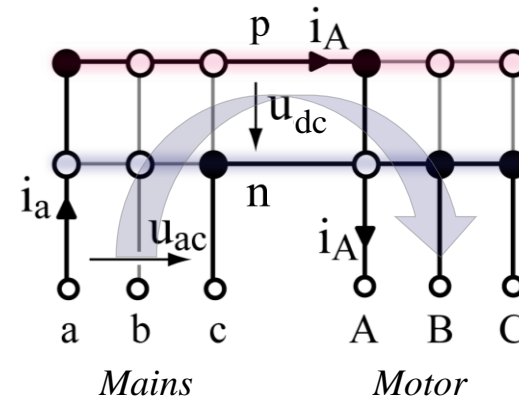
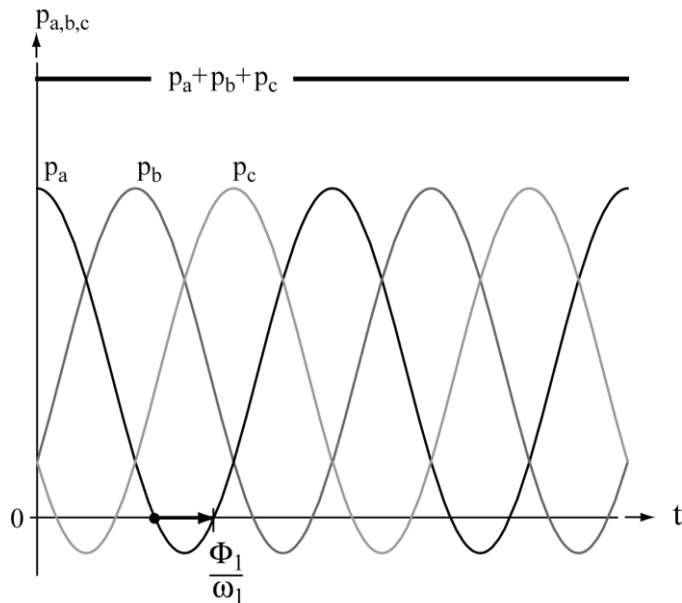
- **Constant 3- Φ Instantaneous Power Flow \rightarrow No Low-Freq. DC-Link Power Pulsation Buffer Requirement (!)**
- **Indirect AC/DC—DC/AC OR Direct AC/AC Power Conversion \rightarrow IMC OR DMC**
- **Switch Matrix w/ Bipolar Voltage Blocking & Current Carrying Devices**



- **Output-Side Motor Inductor \rightarrow Operation Limited to Buck-Type (Step-Down) Voltage Conversion**

Indirect & Direct 3- Φ AC/AC Matrix Converter (2)

- **Input Filter Capacitors | Sw. Stage | Motor Inductance**
- **Buck-Type Power Conversion Topology**

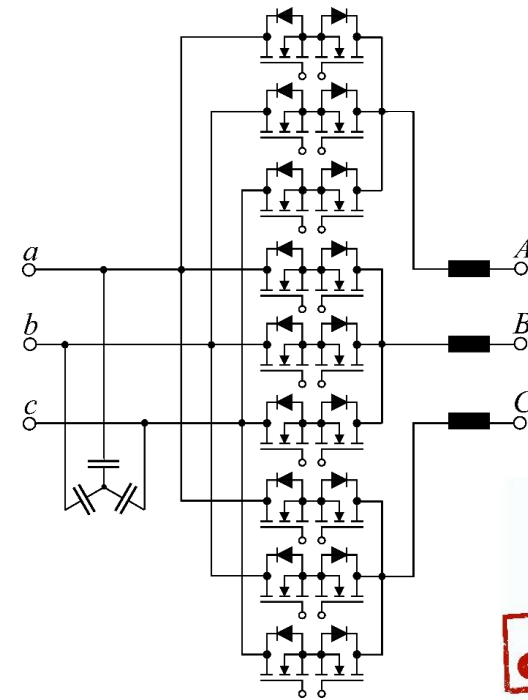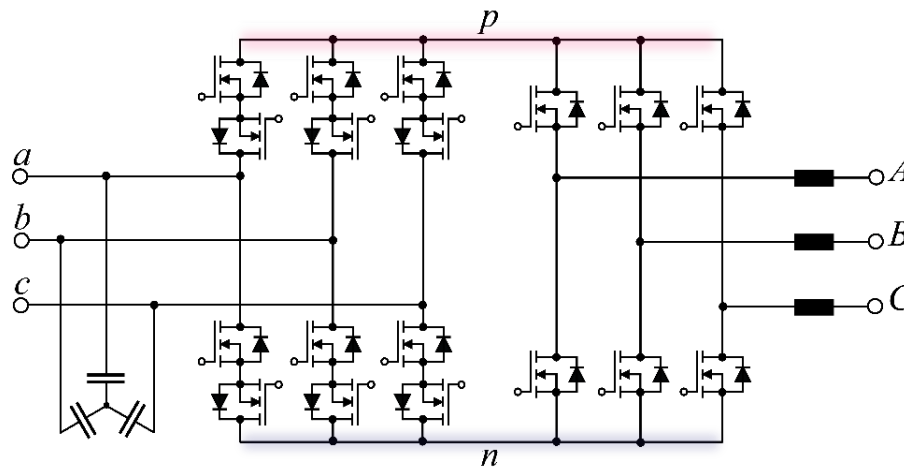


- **IMC Relies on Strictly Pos. DC-Link Voltage / $i=0$ Input Stage Commutation**
- **M-BDS-Based Realization of DMC Features Lower # of Switches / 4-Step Commutation Required**

Remark Application of M-BDSs

■ Indirect Matrix Converter (IMC)

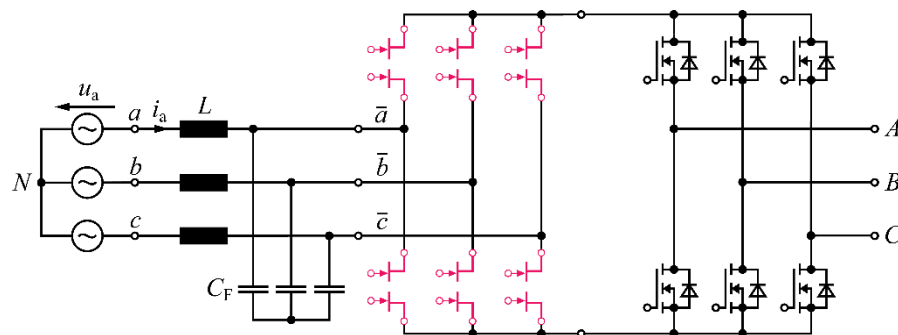
- M-BDS AC/DC Front-End
- ZCS Commutation of AC/DC Stage @ $i_{DC}=0$
- No 4-Step Commutation



- Higher # of Switches Compared to DMC
- Lower Cond. Losses @ Low Output Voltage
- Thermally Critical @ $f_{out} \rightarrow 0$

■ Direct Matrix Converter (DMC)

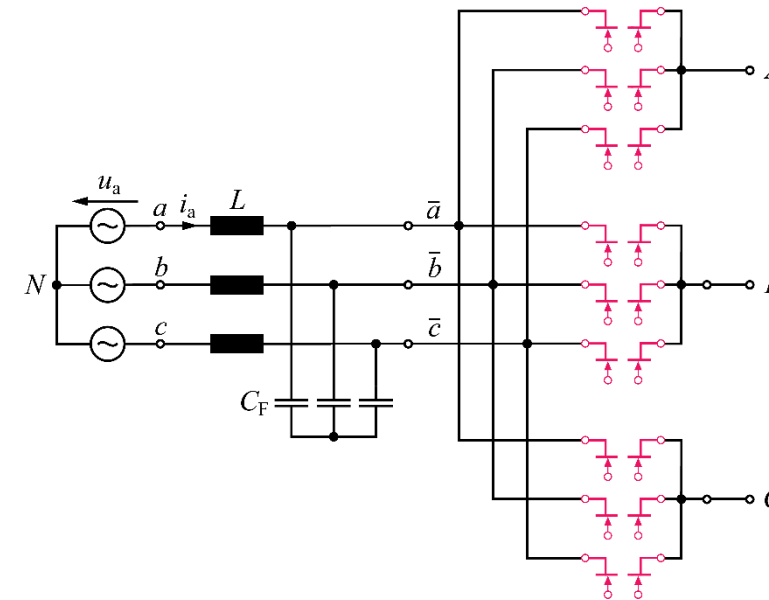- 4-Step Commutation
- Exclusive Use of M-BDSs









- Thermally Critical @ $f_{out} \approx f_{in}$

*Selected
GaN & SiC M-BDS
R&D Activities*



Experimental Analysis of 1st Gen. 600V GaN M-BDS



-  **POWERAMERICA Program** — Based on Infineon's CoolGaN™ HEMT Technology
- **Dual-Gate Device / Controllability of Currents in Both Directions**
- **Bipolar Voltage Blocking Capability | Normally-On or Normally-Off**

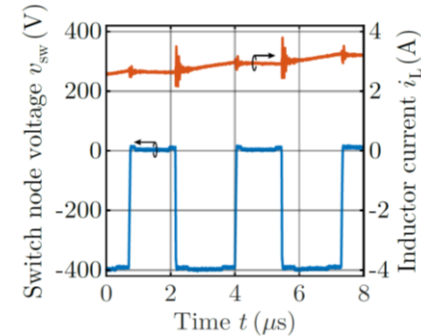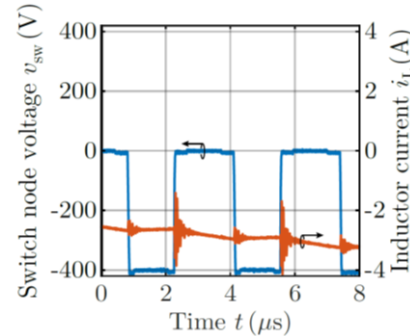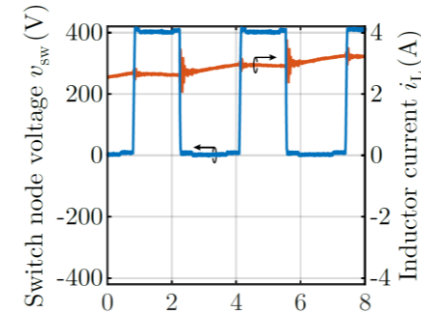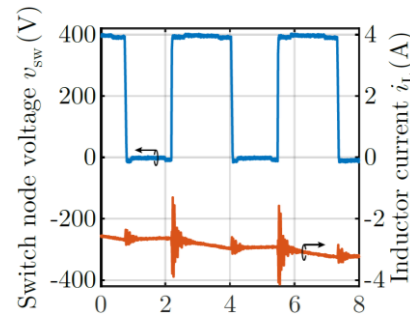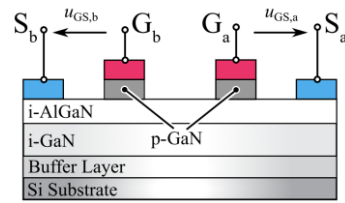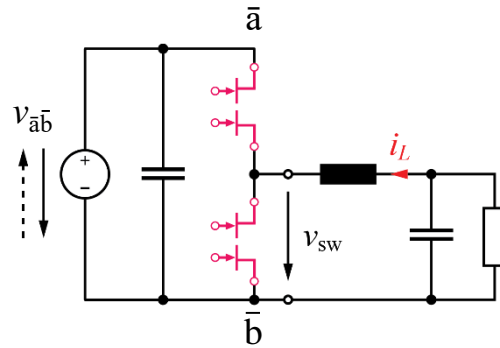

- **Analysis of 4-Quadrant Operation of $R_{DS(on)} = 140m\Omega$ | 600V Sample @ $\pm 400V$**
- **Shared Drift Region \rightarrow "True" Monolithic Bidirectional Switch (TM-BDS)**

Monolithic Bidirectional Diamond Switch

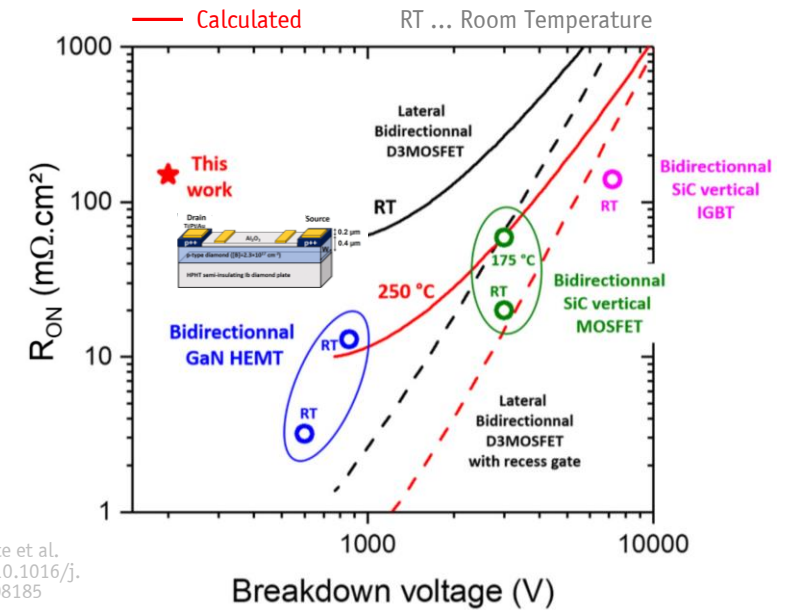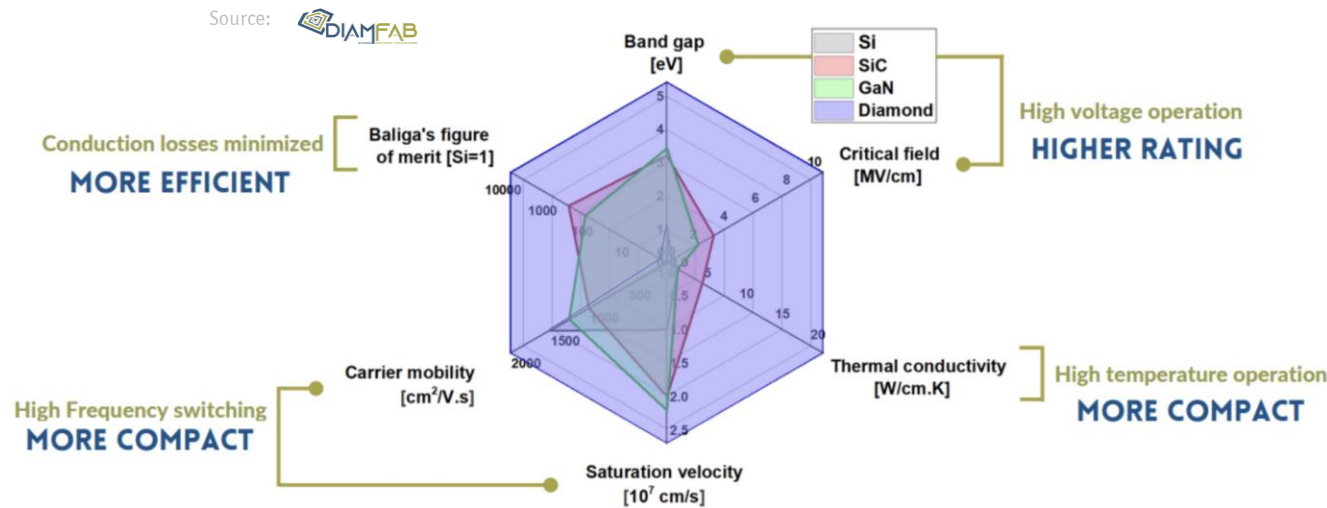- **Diamond** — High Breakdown Field / High Carrier Mobility / High Therm. Conductivity
- **Lateral / Single Drift Layer Double-Gate Reverse Blocking & Reverse Conducting Power MOSFET**




Source: C. Masante et al.
<https://doi.org/10.1016/j.diamond.2020.108185>



- **Very Basic Proof of Concept @ 250°C**
- **Lateral Bidir. Diamond Devices Could Outperform Bidir. Vertical 4H-SiC Devices @ High Temp.**

Monolithically Integrated Bi-Directional SiC IGBT

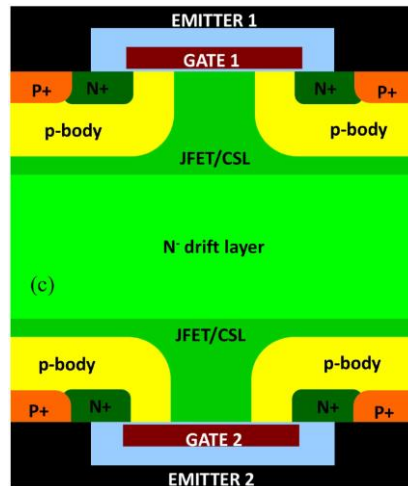- **Planar-Gate Bi-Direct. IGBT Fabricated w/ Double-Sided Lithography Process on Free-Standing n⁻ Wafers**
- **MOS-Cells on Both Sides of Lightly Doped Drift Region / Cond. & Sw. Loss Infl. by Back-Side Gate Volt. Bias**
- **Challenging Packaging & Cooling**




Chow et al., 2016

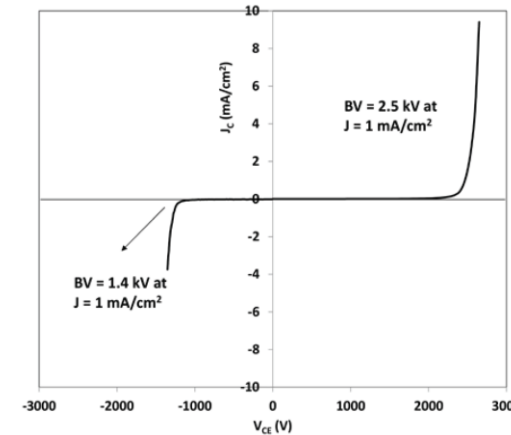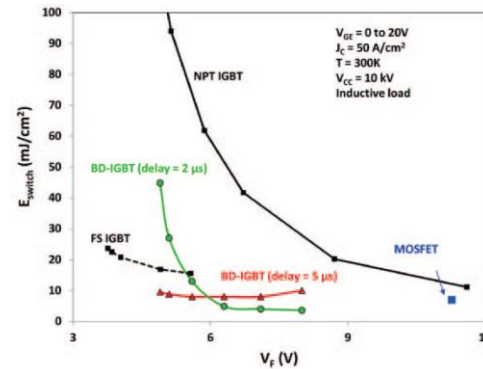

- **Simul. Performance of a 15kV BD-IGBT | Blocking Characteristic (max. 7.2 kV Meas.) – Epi Layer Defects etc.**
- **Shared Drift Region → “True” Monolithic Bidirectional Switch (TM-BDS)**


Remark Solid-State Circuit Breakers (SSCBs)

- Ultra-Fast Fault Interruption | Reduced Fault Stress | Arc-Less | Low Surge Voltage | Long Lifetime
- Software / Remote Configurable Trip Behavior / Remote-Controlled Load Switch

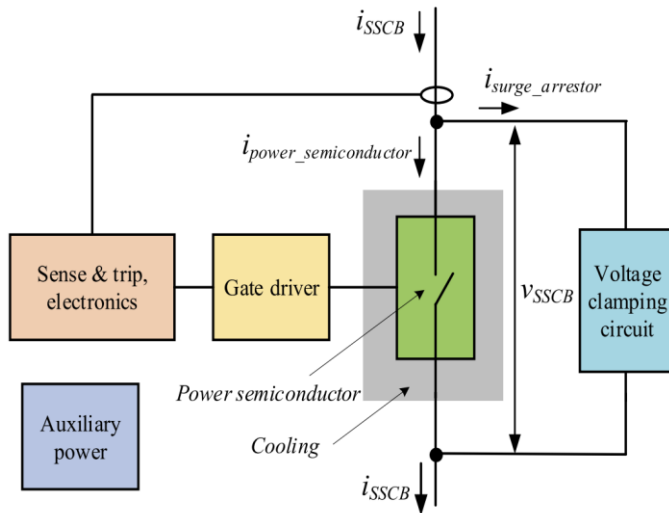


Rodrigues et al., 2021

Traditional Circuit Breaker

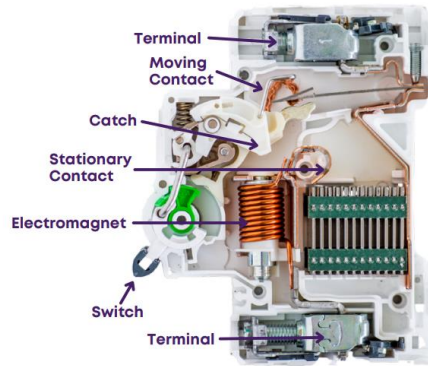

Solid-State Circuit Breaker

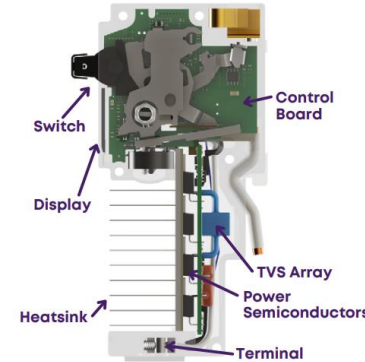


- Recent LV Example w/ Custom SiC Modules / Max. 100A Cont. / UL-Certified
- M-BDSs — Low On-Resistance Mandatory (e.g. 1100V, 22mΩ GaN M-BDS) | Low Leakage Current



Outlook

The in the Room

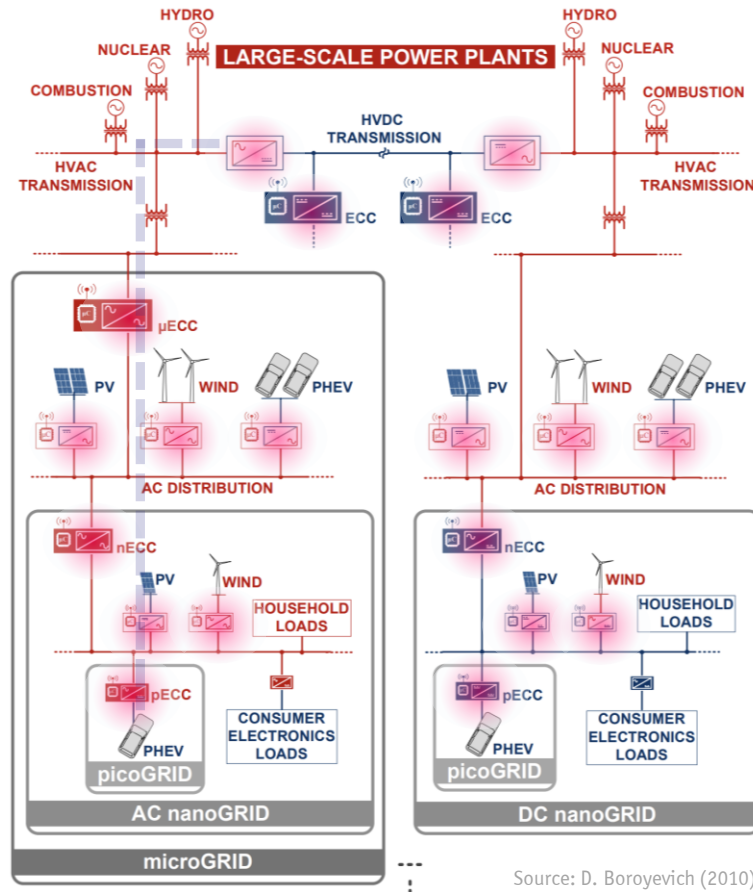

- 25'000 GW Installed Ren. Generation in 2050
- 15'000 GWh Batt. Storage
- 4x Power Electr. Conversion btw Generation & Load
- 100'000 GW of Installed Converter Power
- 20 Years of Useful Life





- 5'000 GW_{eq} = 5'000'000'000 kW_{eq} of E-Waste / Year (!)
- 10'000'000'000 \$ of Potential Value

The Paradigm Shift

- **“Linear” Economy / Take-Make-Dispose** → **“Circular” Economy / Perpetual Flow of Resources**
- **Resources Returned into the Product Cycle at the End of Use**

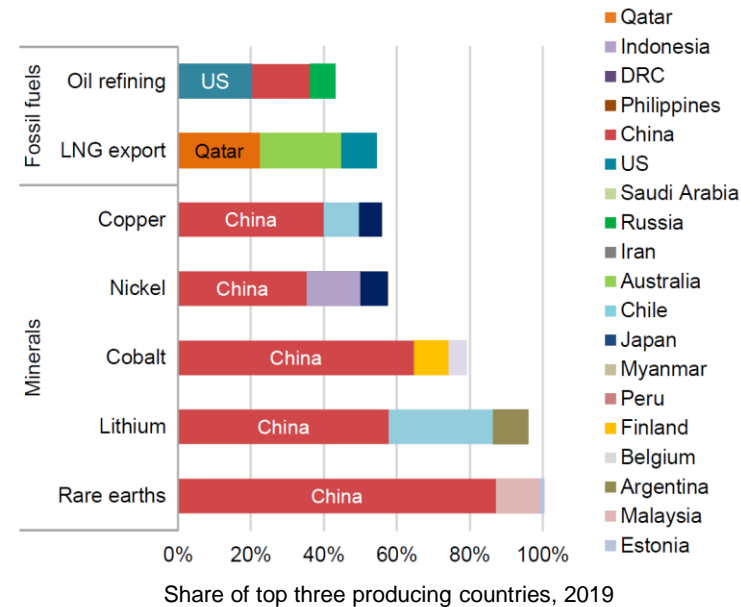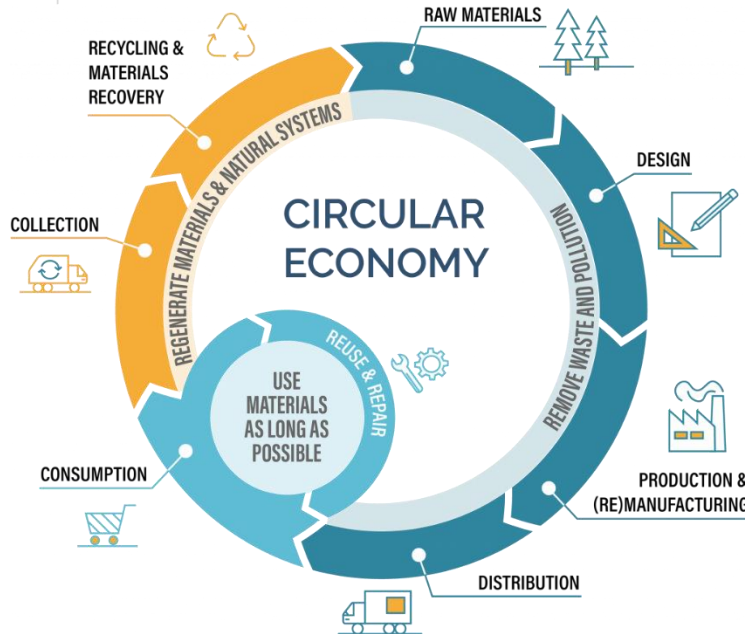
Source: <https://circularphiladelphia.org>



- **Geographically Concentrated Production of Many Energy Transition Critical Minerals**

Power Electronics 5.0

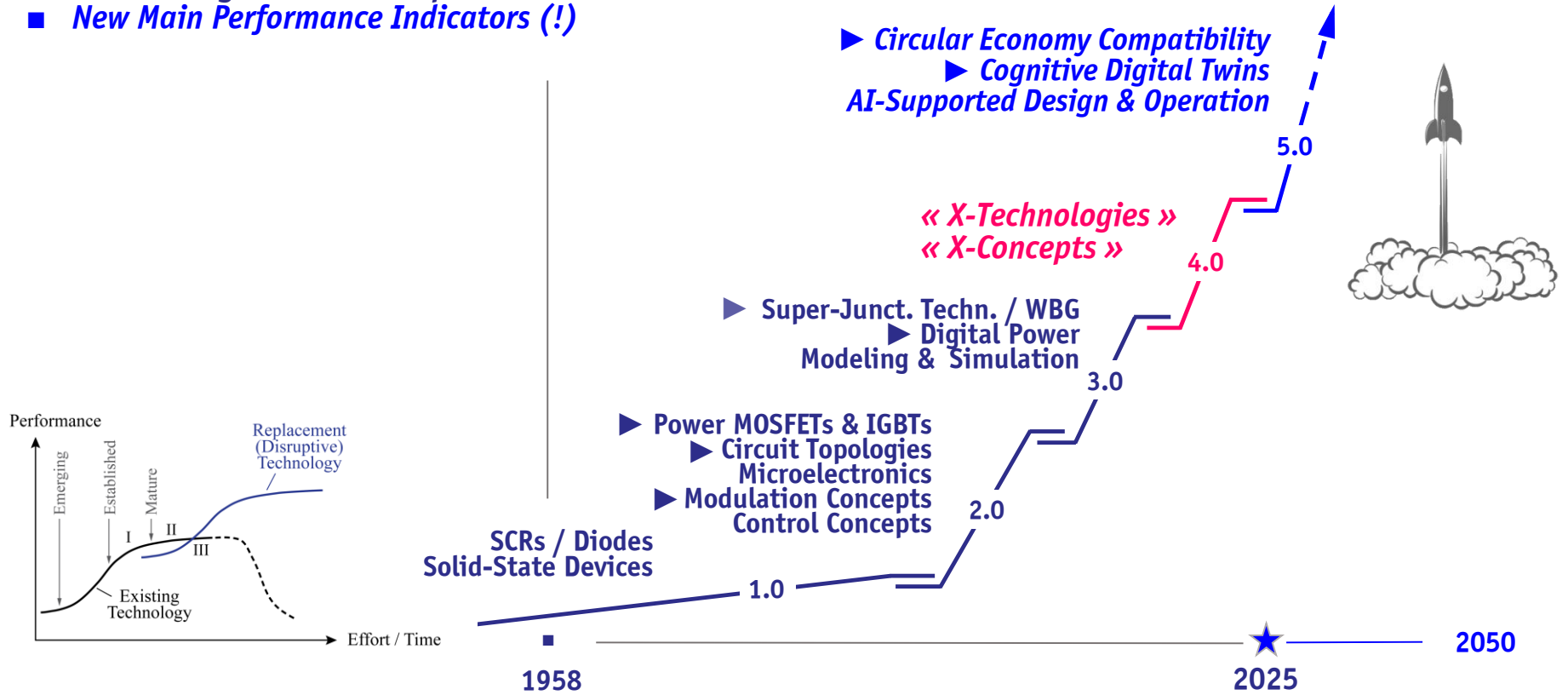- Power Electronics 1.0 → Power Electronics 5.0
- X-Technologies & X-Concepts
- New Main Performance Indicators (!)





Thank you!

