

# Approaches to Overcome the Google/ IEEE Little-Box Challenges

**Johann W. Kolar et al.**

ETH Zurich, Switzerland  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)



# Approaches to Overcome the Google/ IEEE Little-Box Challenges

**All Team Members of ETH Zurich/Fraunhofer/Fraza**

ETH Zurich, Switzerland  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)



# Outline


- ▶ The **Google** Little Box Challenge
- ▶ Selection of Converter Topology / Modulation Scheme
- ▶ *Components / Building Blocks*
- ▶ *3D-CAD Construction*
- ▶ *Experimental Results*
- ▶ Conclusions

# The Google Little Box Challenge

*Requirements*  
*Grand Prize*  
*Team* →
 
# LITTLE BOX CHALLENGE

- Design / Build the 2kW 1-Φ Solar Inverter with the Highest Power Density in the World
- Power Density > 3kW/dm<sup>3</sup> (50W/in<sup>3</sup>)
- Efficiency > 95%
- Case Temp. < 60°C
- EMI FCC Part 15 B



■ Push the Forefront of New Technologies in R&D of High Power Density Inverters



## LITTLE BOX CHALLENGE

Google | IEEE

- Design / Build the 2kW 1- $\Phi$  Solar Inverter with the Highest Power Density in the World
- Power Density > 3kW/dm<sup>3</sup> (50W/in<sup>3</sup>)
- Efficiency > 95%
- Case Temp. < 60°C
- EMI FCC Part 15 B



- Push the Forefront of New Technologies in R&D of High Power Density Inverters

## The Grand Prize

- Highest Power Density ( $> 50\text{W}/\text{in}^3$ )
- Highest Level of Innovation



**\$1,000,000**

- Timeline
  - Challenge Announced in Summer 2014
  - 650 Teams Worldwide
  - 100+ Teams Submitted a Technical Description until July 22, 2015
  - **18 Finalists / Presentation @ NREL on Oct. 21, 2015, Golden, Colorado, USA**
  - Testing @ NREL, Colorado, USA / Winner will be Announced in Early 2016



## Multi-National Team

- Switzerland
- Germany
- Slovenia

**ETH** zürich

 **Fraunhofer**  
IZM

 **Fraza** d.o.o.

■ Acknowledgment





# Converter


Topology  
Modulation  
Control




—— *1- $\Phi$  Power Pulsation Buffer* ——

# Power Pulsation Buffer (1)

- Parallel Buffer @ DC Input

 




- Series Buffer @ DC Input

 

- Parallel Approach for Limiting Voltage Stress on Converter Stage Semiconductors

## Power Pulsation Buffer (2)

- Electrolytic Capacitor

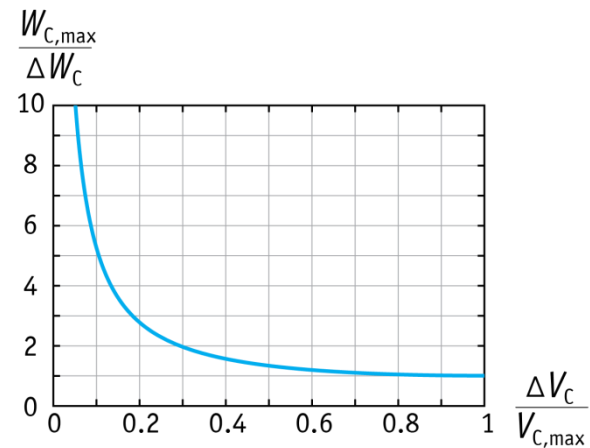  

$S_0 = 2.0 \text{ kVA}$   
 $\cos \Phi_0 = 0.7$   
 $V_{C,max} = 450 \text{ V}$   
 $\Delta V_C / V_{C,max} = 3 \%$





■  $C > 2.2 \text{ mF} / 166 \text{ cm}^3 \rightarrow$  Consumes 1/4 of Allowed Total Volume !


  
# Power Pulsation Buffer (3)

- Series Resonant Circuit / Used in Rectifier Input Stage of Locomotives






- $C_r = 20 \mu\text{F}$
- $L_r = 127 \text{ mH} @ v_{Lr} = 400 \text{ V}$

■ Unacceptably Large Inductor Volume !


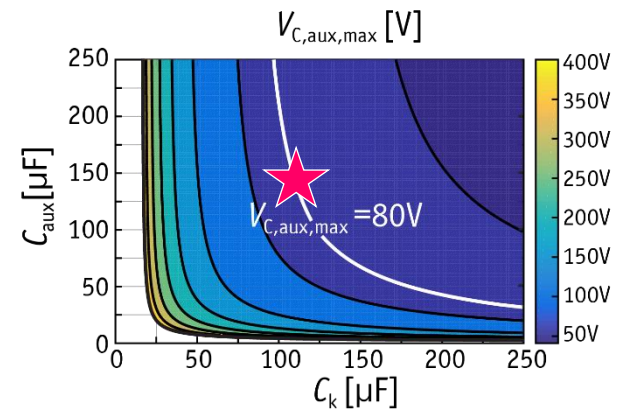  
# Power Pulsation Buffer (4)

- Coupling Capacitor & Electronic Inductor




- Low  $U_{C,aux}$  → Low Converter Losses
- High Values of  $C_k, C_{aux}$  Required for Low  $U_{C,aux}$
- Full-Bridge Aux. Converter Allows Lower  $U_{C,aux}$



▲ Properties of Full-Bridge Aux. Conv.
 
## Power Pulsation Buffer (4-a)

- Large Voltage Fluctuation Capacitor & DC/DC Buck (Boost) Converter Stage
- Foil or Ceramic Capacitor



CeraLink  
TDK




108 x 1.2μF / 400 V  
 $C_r \approx 140\mu\text{F}$   
 $V_{Cr} = 23.7\text{cm}^3$

■ Very Good Compromise →  $C_r$  - Volume / Power Electronics Complexity



 
## Power Pulsation Buffer (4-b)

- Large Voltage Fluctuation Capacitor & DC/DC Buck (Boost) Converter Stage
- Foil or Ceramic Capacitor



**EPCOS**  
5 x 493 $\mu$ F/450 V  
 $C = 2.46$  mF

$V = 48$  cm<sup>3</sup>

 

$V = 166$  cm<sup>3</sup>



- Significantly Lower Volume Compared to Electrolytic Capacitors




*Output Stage  
Topology / Modulation*


## Derivation of Output Stage Topology (1)

- Inversion of Basic 1- $\Phi$  PFC Rectifier Topology

– Boost-Type  
1- $\Phi$  PFC Rectifier

 

 
– DC/DC Buck Converter &  
Mains Frequency “Unfolder”



- Low-Frequency “Folder/ Unfolder” vs. PWM Operation of Output Stage
 
## Derivation of Output Stage Topology (2)

- DC/DC Buck Converter & Output Frequency "Unfolder"




- PWM Operation of Mains Frequency Inverter @  $U < U_{min}$
- CM Component of Generated Output Voltage


 
# Derivation of Output Stage Topology (3)

- Full Bridge Output Stage / Output Frequency Bridge Leg






- PWM Operation of Mains Freq. Bridge Leg @  $|u| < u_{0,min}$
- CM Component  $u_{CM}$  of Generated Output Voltage


   
## Derivation of Output Stage Topology (4)




- Full Bridge Output Stage / Full PWM Operation



- DM Component of  $u_1$  and  $u_2$  Defines Output  $u_o$
- CM Component of  $u_1$  and  $u_2$  Represents Degree of Freedom of the Modulation (!)
   
## Remark: AC Side Power Pulsation Buffer



- Full Bridge Output Stage / Full PWM Operation



- CM Reactive Power of Output Filter Capacitors used for Comp. of Load Power Pulsation
- CM Reactive Power prop.  $2 C$
- DM Reactive Power prop.  $\frac{1}{2} C$
  
# ZVS of Output Stage / TCM Operation


- Full Bridge Output Stage / Full PWM Operation



- Triangular Current Mode (TCM) Operation for Res. Voltage Transition @ Turn-On/Turn-Off
- Required Only Measurement of Current Zero Crossings,  $i = 0$
- Variable Switching Frequency Lowers EMI
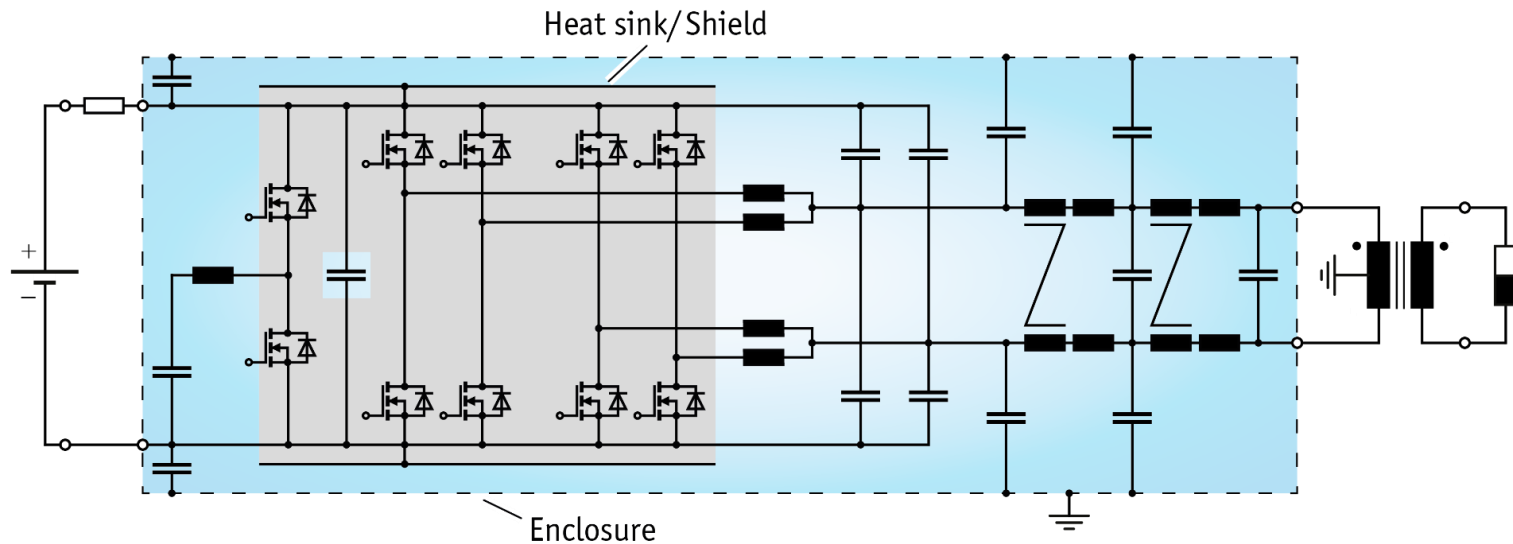
## Selected Converter Topology

- Interleaving of 2 Bridge Legs per Phase - Volume / Filtering / Efficiency Optimum
- Active 1- $\Phi$  Output Power Pulsation Buffer









- ZVS of All Bridge Legs @ Turn-On/Turn-Off in Whole Operating Range – 4D TCM Interleaving
- Heatsinks Connected to DC bus / Shield to Prevent Capacitive Coupling to Grounded Enclosure



*Interleaving  
Switching Frequ. Modulation*
      
# 4D-Interleaving



- Interleaving in Space & Time – Within Output Period
- Alternate Operation of Bridge Legs @ Low Power
- Overlapping Operation @ High Power



- Opt. Trade-Off of Conduction vs. Switching Losses / Opt. Balancing of Thermal Stress

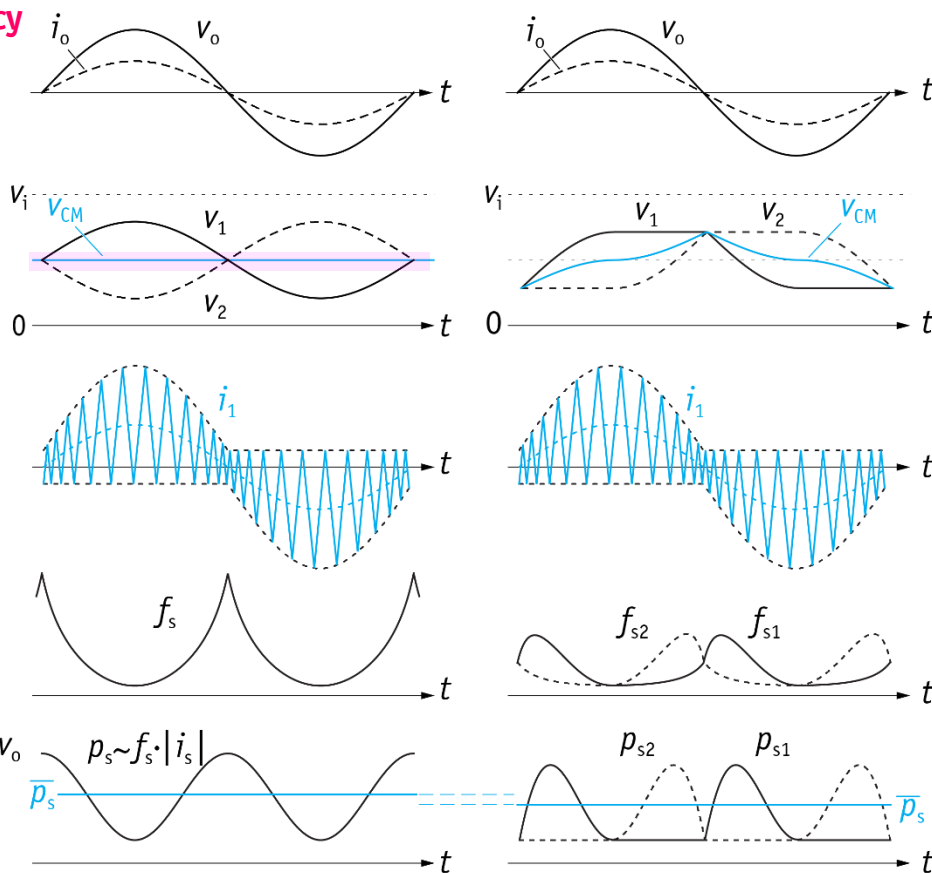 
## Remark: CM-Enhanced TCM Modulation

- CM Comp. of  $u_1, u_2$  Changes Sw. Frequency
- Limits Sw. Frequency Variation
- Lower Sw. Losses


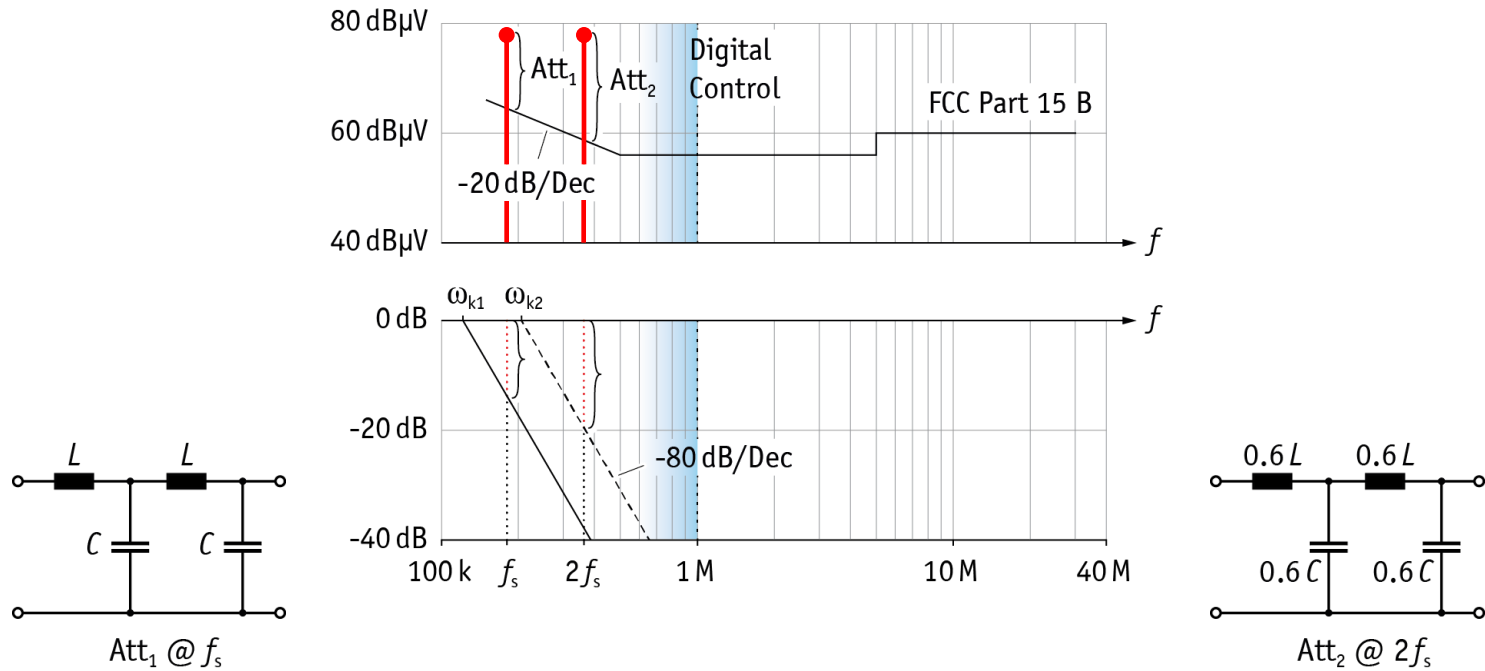
## Selection of Switching Frequency

- Significant Reduction in EMI Filter Volume for Increasing Sw. Frequency





- Doubling Sw. Freq.  $f_s$  Cuts Filter Volume in Half
- Upper Limit due to Digital Signal Processing Delays / Inductor & Sw. Losses – Heatsink Volume


**Realization**  
*Components*  
■ *Building Blocks* →
  
# Power Semiconductors

- 600V IFX Normally-Off GaN GIT - ThinPAK8x8
  - 2 Parallel Transistors / Switch
  - Antiparallel CREE SiC Schottky Diodes
- 1.2V typ. Gate Threshold Voltage
  - 55 mΩ  $R_{DS,on}$  @ 25°C, 120mΩ @ 150°C
  - 5Ω Internal Gate Resistance




$dv/dt = 500kV/\mu s$

 

- CeraLink Capacitors for DC Voltage Buffering
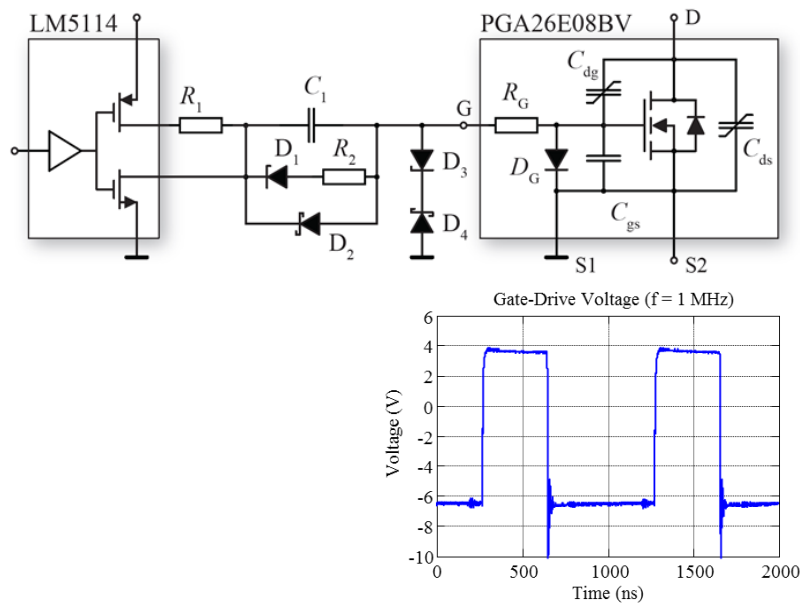
## Advanced Gate Drive

- Fixed Negative Turn-off Gate Voltage Independent of Sw. Frequency and Duty Cycle
- Extreme  $dv/dt$  Immunity ( $500\text{ kV}/\mu\text{s}$ ) Due to CM Choke at Signal Isolator Input




- Total Prop. Delay < 30ns incl. Signal Isolator, Gate Drive, and Switch Turn-On Delay
 
## Advanced Gate Drive

- Fixed Negative Turn-off Gate Voltage Independent of Sw. Frequency and Duty Cycle
- Extreme  $dv/dt$  Immunity ( $500\text{ kV}/\mu\text{s}$ ) Due to CM Choke at Signal Isolator Input

- Gate Voltage  $T+$
- Gate Voltage  $T-$
- TCM Inductor Current
- Transistor Voltage




- Triangular Current Mode (TCM) Operation at No Load → ZVS and No Free Ringing of  $u_{T+}$ ,  $u_{T-}$  or  $i_L$



 
## High Frequency Inductors

- Multi-Airgap Inductor with Patented Multi-Layer Foil Winding Arrangement Minim. Prox. Effect
- Very High Filling Factor / Low High Frequency Losses
- Magnetically Shielded Construction Minimizing EMI
- Intellectual Property of F. Zajc / Fraza

- $L = 10.5 \mu\text{H}$
- 2 x 8 Turns
- 24 x  $80 \mu\text{m}$  Airgaps
- Core Material DMR 51 / Hengdian
- 0.61mm Thick Stacked Plates
- $20 \mu\text{m}$  Copper Foil / 4 in Parallel
- $7 \mu\text{m}$  Kapton Layer Isolation
- $20\text{m}\Omega$  Winding Resistance /  $Q=800$
- Terminals in No-Leakage Flux Area




 
■ Dimensions -  $14.5 \times 14.5 \times 22\text{mm}^3$


  
## Thermal Management

- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters
- Outstanding Cooling Syst. Performance Index


- 200um Fin Thickness
- 500um Fin Spacing
- 3mm Fin Height
- 10mm Fin Length
- CSPI = 37 W/(dm<sup>3</sup>.K)
- 1.5mm Baseplate




 
## Thermal Management

- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters
- Outstanding Cooling Syst. Performance Index





- Two-Side Cooling → Heatsink Temperature = 52°C @ 80W (8W Natural Convection)

## Control Board & $i=0$ Detection

- Fully Digital Control - Overall Control Sampling Frequency of 25kHz
- TI DSC TMS320F28335 / 150MHz / 179-pin BGA / 12mmx12mm
- Lattice FPGA LFXP2-5E / 200MHz / 86-pin BGA / 8mmx8mm
  
### - TCM Current / Induced Voltage / Comparator Output





- $i=0$  Detection of TCM Currents Using R4/N30 Saturable Inductors
- Galv. Isolated / Operates up to 2.5MHz Switching Frequency / <10ns Delay
  
## Power Pulsation Buffer Capacitor

- High Energy Density 2<sup>nd</sup> Gen. 400VDC CeraLink Capacitors Utilized as Energy Storage
- Highly Non-Linear Behavior → Opt. DC Bias Voltage of 280VDC
- Losses of 6W @ 2kVA Output Power


- 108 x 1.2 $\mu$ F / 400 V
- 23.7cm<sup>3</sup> Capacitor Volume



- Effective Large Signal Capacitance of  $C \approx 140\mu$ F

# Control of Power Pulsation Buffer

- Cascaded Control Structure

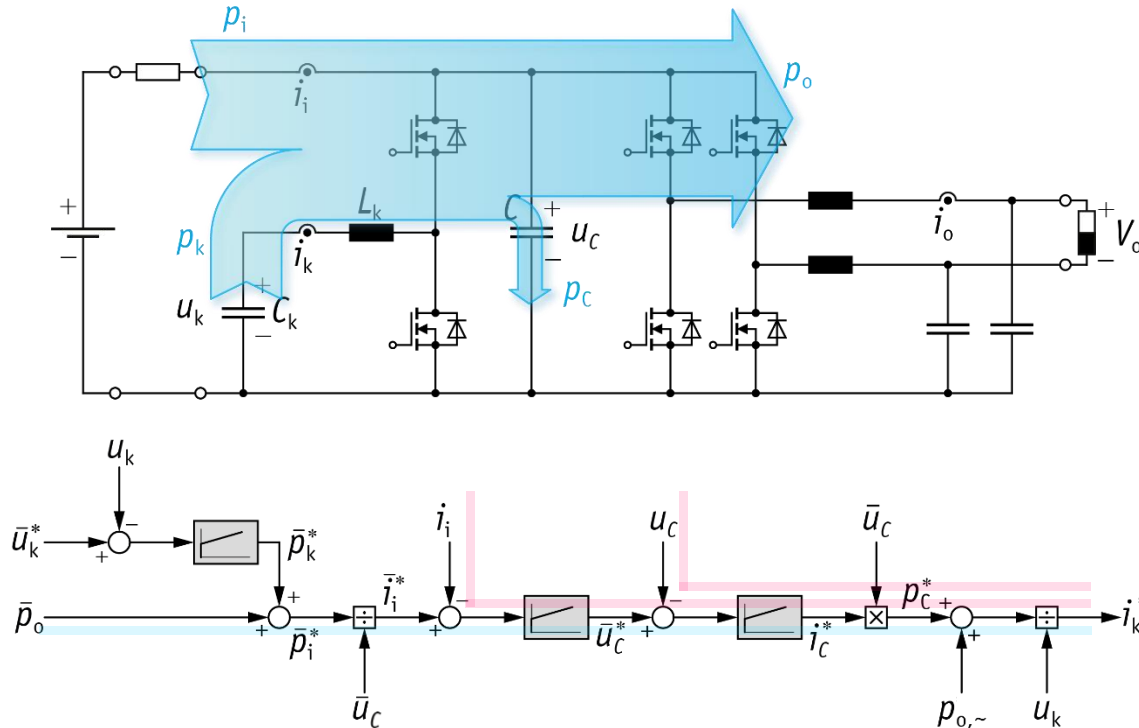


- Feedforward of Output Power Fluctuation
- Underlying Input Current / DC Link Voltage Control

 
## Auxiliary Supply & Measurements

- ZVS Constant 50% Duty Cycle Half Bridge with Synchr. Rectification
- Compact / Efficient / Low EMI

- 10W Max. Output Power
- 380V...450V Input Operating Range
- 16V...16V DC Output in Full Inp. Voltage / Output Power Range
- 90% Efficiency @  $P_{max}$




 - 19mm x 24mm x 4.5mm (2cm<sup>3</sup> Volume )



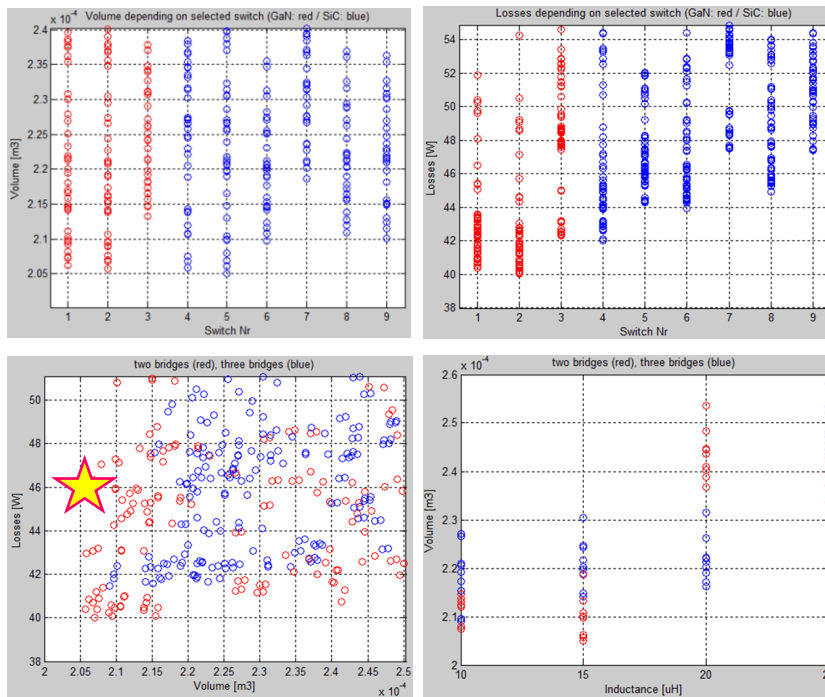
# Multi-Objective Optimization

- Detailed System Models - Power Buffer/Output Stage/EMI
- Detailed Multi-Domain Component Models (incl. GaN & SiC)
- Consideration of Very Large # of Degrees of Freedom



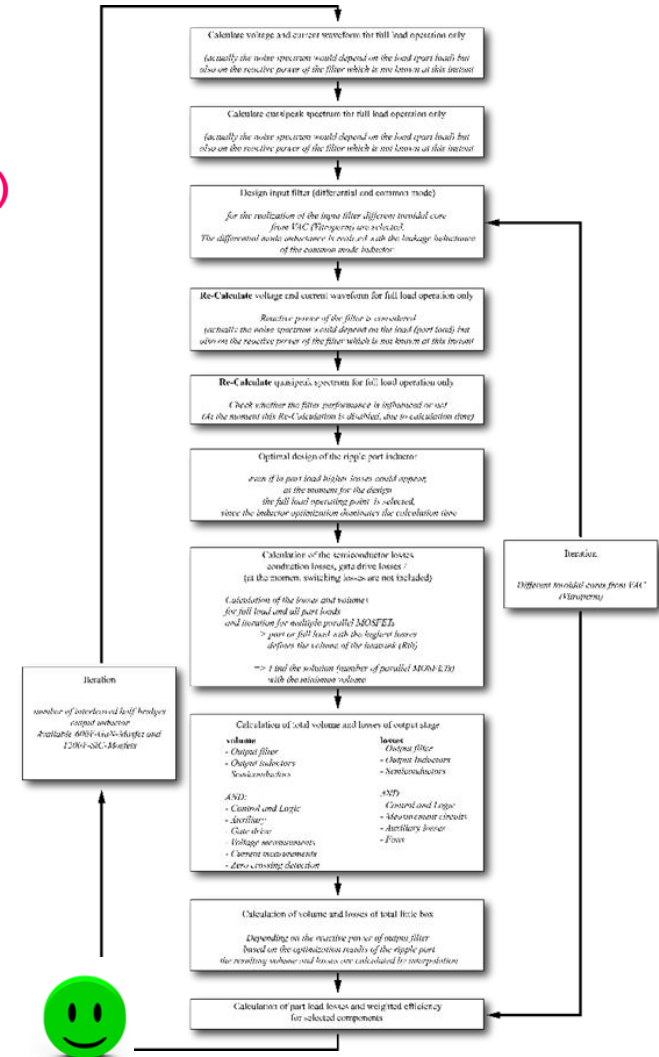■ Pareto Optimiz. → Minim. Vol. of 207cm<sup>3</sup> w/o EMI Filter





*3D-CAD Construction* →

## 3D-CAD Construction (1)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>



- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (2)


- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$



- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (3)


- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$



- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (4)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (5)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (6)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (7)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>


 
## 3D-CAD Construction (8)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (9)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (10)


- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$



- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
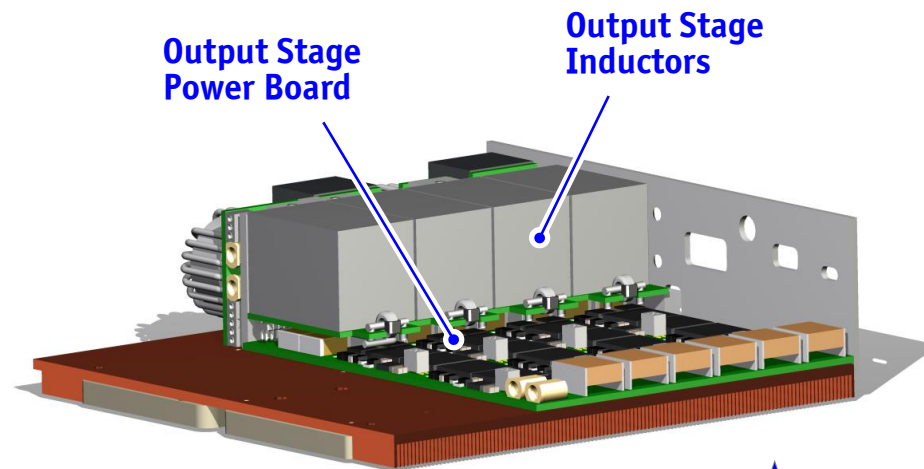
## 3D-CAD Construction (11)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (12)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>
 
## 3D-CAD Construction (13)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$



★ 135 W/in<sup>3</sup>

- 88.7mm x 88.4mm x 31mm = 243cm<sup>3</sup> (14.8in<sup>3</sup>) → 8.2 kW/dm<sup>3</sup>

## *Experimental Results*

*Hardware*  
*Output Voltage/Input Current Quality*  
*Thermal Behavior*  
*Efficiency*  
*EMI* →

## Little-Box Prototype I


- System Employing Electrolytic Capacitors as 1- $\Phi$  Power Pulsation Buffer

273cm<sup>3</sup>  
7.3 kW/dm<sup>3</sup>  
97,5% Efficiency @ 2kW  
 $T_c=58^\circ\text{C}$  @ 2kW

$\Delta u_{DC} = 2.85\%$   
 $\Delta i_{DC} = 15.4\%$   
 $THD+N_U = 2.6\%$   
 $THD+N_I = 1.9\%$

97mm x 90.8 mm x 31mm ( 16.6in<sup>3</sup> )


- Compliant to All Specifications

 


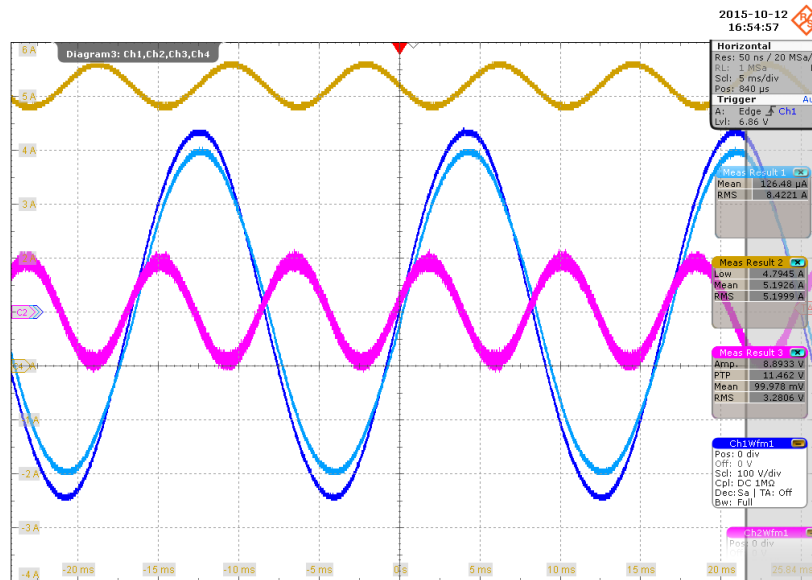
# Measurement Results I-(1)

- System Employing Electrolytic Capacitors as 1- $\Phi$  Power Pulsation Buffer




Ohmic Load / 2kW

DC Input Current  
 DC Voltage Ripple  
 Output Voltage  
 Output Current


- Compliant to All Specifications
 
## Measurement Results I-(2)

- System Employing Electrolytic Capacitors as 1- $\Phi$  Power Pulsation Buffer




 
★  $\eta_w = 96.4\%$  Weighted Efficiency



- Heating of System Lower than Specified Limit ( $T_{c,max} = 60^\circ\text{C}$  @  $T_{amb} = 30^\circ\text{C}$ )
  
# Measurement Results I-(3)

- System Employing Electrolytic Capacitors as 1- $\Phi$  Power Pulsation Buffer



- Compliant to All Specifications

## Little-Box Prototype II-(1)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer


243 cm<sup>3</sup>  
8.2 kW/dm<sup>3</sup>  
96,3% Efficiency @ 2kW  
 $T_c=58^\circ\text{C}$  @ 2kW

$\Delta u_{DC} = 1.1\%$   
 $\Delta i_{DC} = 2.8\%$   
 $THD+N_U = 2.6\%$   
 $THD+N_I = 1.9\%$

88.7mm x 88.4mm x 31mm (14.8in<sup>3</sup>)



★ 135 W/in<sup>3</sup>

 

- Compliant to All Specifications

## Little-Box Prototype II-(1)


- System Employing Active 1- $\Phi$  Power Pulsation Buffer

243 cm<sup>3</sup>  
8.2 kW/dm<sup>3</sup>  
96,3% Efficiency @ 2kW  
 $T_c=58^\circ\text{C}$  @ 2kW

$\Delta u_{\text{DC}} = 1.1\%$   
 $\Delta i_{\text{DC}} = 2.8\%$   
 $\text{THD}+N_U = 2.6\%$   
 $\text{THD}+N_I = 1.9\%$

88.7mm x 88.4mm x 31mm (14.8in<sup>3</sup>)

★ 135 W/in<sup>3</sup>

 


- Compliant to All Specifications

 
# Measurement Results II-(2)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer

Output Current  
 Inductor Current Bridge Leg 1-1  
 Inductor Current Bridge Leg 1-2  
 - Ohmic Load / 2kW



 
DC Link Voltage (AC-Coupl.)  
 Buffer Cap. Voltage  
 Buffer Cap. Current  
 Output Voltage



Compliant to All Specifications
 
## Measurement Results II-(3)


- System Employing Active 1- $\Phi$  Power Pulsation Buffer



- Compliant to All Specifications
 
## Measurement Results II-(5)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer



DC Link Voltage  
 Buffer Cap. Voltage  
 Buffer Cap. Current  
 Inductor Current Bridge Leg 1-1

- Start-up and Shut-Down (No Load Operation)



- *Conclusions* →



## Conclusions

- 2kVA 1- $\Phi$  Inverter @ 240cm<sup>3</sup> (15in<sup>3</sup>) → 8kW/dm<sup>3</sup> (135W/in<sup>3</sup>)
- 400...450VDC Input / 240VAC<sub>rms</sub> Output
- Efficiency > 95%
- Case Temp. < 60°C
- EMI FCC Part 15 B



- 100+ Teams
- 3 Members / Team, 1 Year
- 300 Man-Years
- 3300 USD / Man-Year

## Lessons Learned


- Upper Sw. Frequency Limit of  $\approx$ 1MHz Due to Digital Control /  $i=0$  Detection
- Integrated Gate Driver for Even Higher Power Density
- High Frequency Low Loss Magnetics are Key Issue
- Isol. Distance Requirements Difficult to Fulfill
- Losses of Ceramic Capacitors for Large AC Ripple
- Careful Mounting of Ceramic Caps.
- New U-I-Probes Required for Ultra-Compact Conv. R&D
- Convergence of Sim. & Measur. Tools → Next Gen. Oscilloscope
- New Multi-Obj. Multi-Domain Simulation/Optim. Tools
- Low Frequency (20kHz...120kHz) SiC vs. HF (200kHz...1.2MHz) GaN


 
## Outlook

- Embedded Switching Cell Package for Further Size Reduction
- Integr. Half Bridge Module incl. DC Link Caps and Drivers

- 2 Parallel Chips / Switch
- Embedded in PCB
- 8 mm Smaller than Conv. Design
- Extremely Low DC Link Inductance
- Driver Directly on Top of Switches
- Very Low Gate Inductance



**Thank You!**

# Questions

