


Google /  IEEE
Little-Box Challenge

Johann W. Kolar et al.

ETH Zurich, Switzerland
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Google / IEEE Little-Box Challenge

All Team Members of ETH Zurich/FH-IZM/Fraza

ETH Zurich, Switzerland
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Outline


- ▶ The **Google** Little Box Challenge
- ▶ **ETH / FH-IZM / Fraza Team**
- ▶ *Converter Topology / Control*
- ▶ *New Component Technologies*
- ▶ *Construction*
- ▶ *Experimental Results*
- ▶ *Evaluation / Optimization*
- ▶ **Concepts of Other Finalists**
- ▶ **Conclusions**

The Google Little Box Challenge

Requirements
Grand Prize
Team →

LITTLE BOX CHALLENGE

 - Design / Build the 2kW 1-Φ Solar Inverter with the Highest Power Density in the World
- Power Density > 3kW/dm³ (50W/in³)
- Efficiency > 95%
- Case Temp. < 60°C
- EMI FCC Part 15 B



■ Push the Forefront of New Technologies in R&D of High Power Density Inverters



LITTLE BOX CHALLENGE

Google | IEEE

- Design / Build the 2kW 1- Φ Solar Inverter with the Highest Power Density in the World
- **Power Density > 3kW/dm³ (50W/in³)**
- Efficiency > 95%
- Case Temp. < 60°C
- EMI FCC Part 15 B



- Push the Forefront of New Technologies in R&D of High Power Density Inverters



The Grand Prize

- Highest Power Density ($> 50\text{W}/\text{in}^3$)
- Highest Level of Innovation



\$1,000,000

- Timeline
 - Challenge Announced in Summer 2014
 - **2000+ Teams Registered** Worldwide
 - 100+ Teams Submitted a Technical Description until July 22, 2015
 - **18 Finalists (3 No-Shows)**



The Grand Prize

- Highest Power Density (> 50W/in³)
- Highest Level of Innovation

- * GaN
- * MHz
- * Ceramic Caps
- * HF Inductors
- * etc.

- ▶ Explore New Technologies
- ▶ Secure Intellectual Property
- ▶ Publish Key Results



* Technology Packages Available
incl. Patent Licenses

- Timeline
 - Challenge Announced in Summer 2014
 - **2000+ Teams Registered** Worldwide
 - 100+ Teams Submitted a Technical Description until July 22, 2015
 - **18 Finalists (3 No-Shows)**



LITTLE BOX CHALLENGE



NREL
National Renewable
Energy Laboratory

Innovation for Our Energy Future



- 18 Finalists Invited to NREL / USA
- Presentations on Oct. 21, 2015
- **Winner → Feb. 29, 2016**



City of
Golden

Inverter

● Multi-National Team

- Germany
- Switzerland
- Slovenia



... Packaging, Embedding,
EMI, etc.



... Topologies, Circuits, Control,
Software, System Testing, etc.



... HF Inductor
Technology

● Acknowledgment

- Components
- Academic Award (10)
- Donation (6)




Converter

Topology
Modulation
Control




*Derivation of
Converter Topology*

 



Derivation of Output Stage Topology (1)

- DC/|AC| Buck Converter & Output Frequency “Unfolder”



 


- Temporary PWM Operation of Unfolder @ $U < U_{min}$
- CM Component of Output Voltage v_o



Derivation of Output Stage Topology (2)


 
 
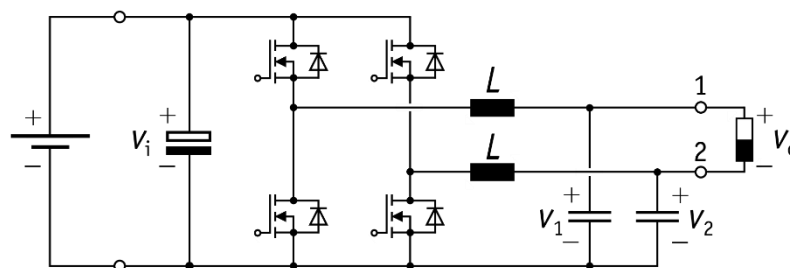
- Full-Bridge Output Stage
- Modulation of Both Bridge Legs



- DM Component of u_1 and u_2 Defines Output u_o
- CM Component of u_1 and u_2 Represents Degree of Freedom of the Modulation (!)

DC-Side Power Pulsation Buffering

 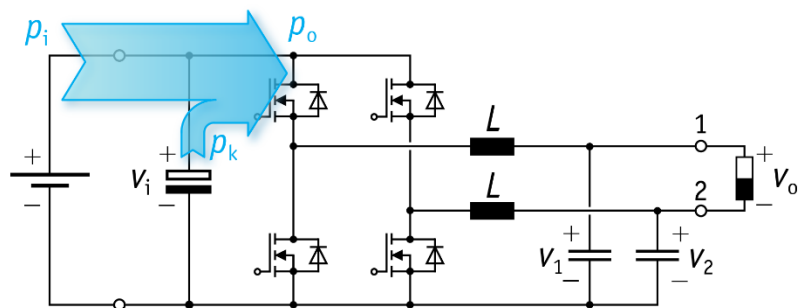
 
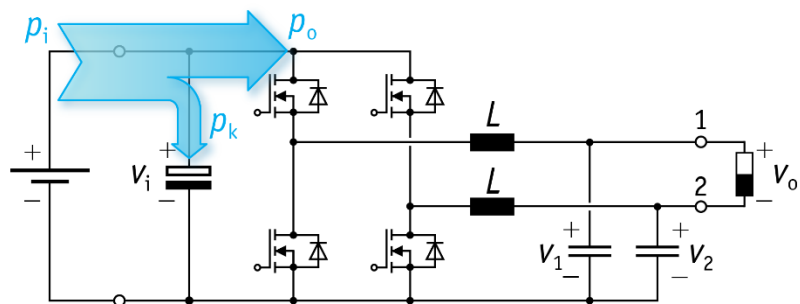
- Compensation of 120Hz Output Power AC Component → **Constant DC Supply Current**



- Parallel or Series / Passive or Active Buffer Concepts
- Parallel Approach for Limiting Voltage Stress on Full-Bridge Semiconductors

DC-Side Passive Power Pulsation Buffer

- Electrolytic Capacitor

   

$S_0 = 2.0 \text{ kVA}$
 $\cos \Phi_0 = 0.7$
 $V_{C,max} = 450 \text{ V}$
 $\Delta V_C / V_{C,max} = 3 \%$




■ $C > 2.2 \text{ mF} / 166 \text{ cm}^3 \rightarrow$ Consumes 1/4 of Allowed Total Allowed Volume !



DC-Side Active Power Pulsation Buffer

 - Large Voltage Fluctuation **Foil or Ceramic Capacitor**
- Buck-Type (Lower Voltage Levels) or Boost-Type DC/DC Interface Converter



CeraLink
TDK




108 x 1.2 μ F / 400 V
 $C_k \approx 140 \mu$ F
 $V_{ck} = 23.7 \text{ cm}^3$

- Significantly Lower Overall Volume Compared to Electrolytic Capacitor



DC-Side Active Power Pulsation Buffer

- Cascaded Control Structure



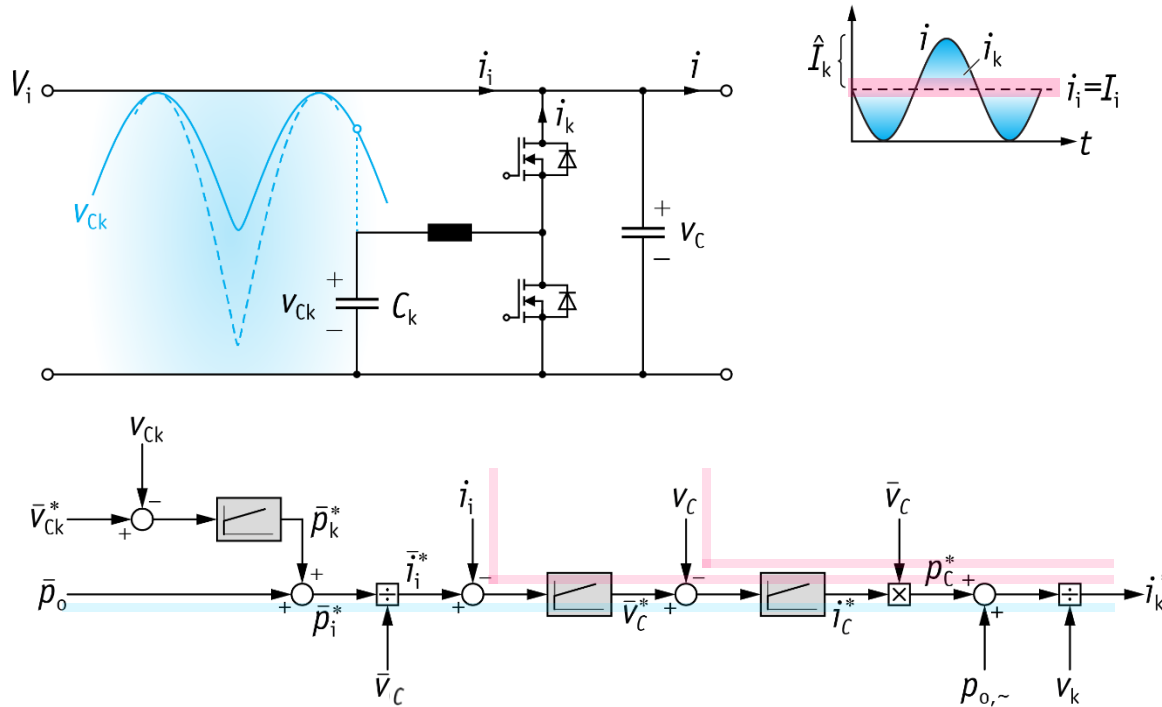


- P-Type Resonant Controller
- Feedforward of Output Power Fluctuation
- Underlying Input Current (i_i) / DC Link Voltage (u_c) Control



AC-Side Power Pulsation Buffering

   - Compensation of 120Hz Output Power AC Component → Constant DC Supply Current





- CM Reactive Power of Output Filter Capacitors used for Comp. of Load Power Pulsation
- CM Reactive Power prop. $2 C$
- DM Reactive Power prop. $\frac{1}{2} C$



— *Modulation* —

ZVS of Output Stage / TCM Operation




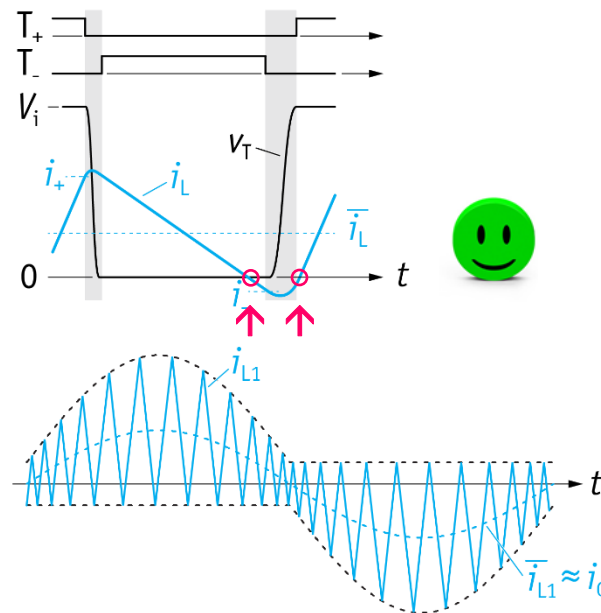
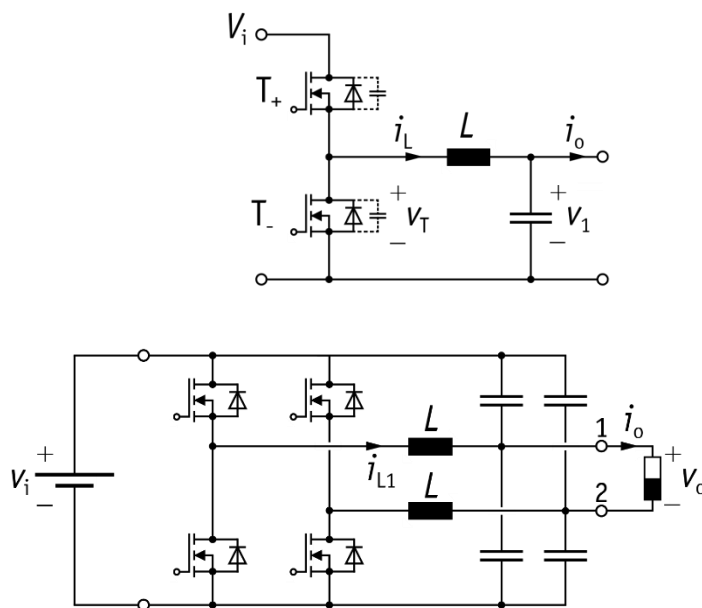
- TCM Operation for Resonant Voltage Transition @ Turn-On/Turn-Off



- Requires Only Measurement of Current Zero Crossings, $i = 0$
- Variable Switching Frequency Lowers EMI

4D-Interleaving

    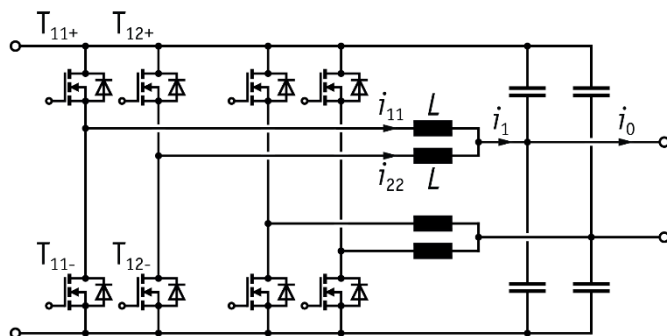- Interleaving of 2 Bridge Legs per Phase - Volume / Filtering / Efficiency Optimum
- Interleaving in Space & Time - Within Output Period
- Alternate Operation of Bridge Legs @ Low Power
- Overlapping Operation @ High Power




- Opt. Trade-Off of Conduction & Switching Losses / Opt. Distribution of Losses



————— *Implemented
Converter Topology /
Output Control* —————

Final Converter Topology

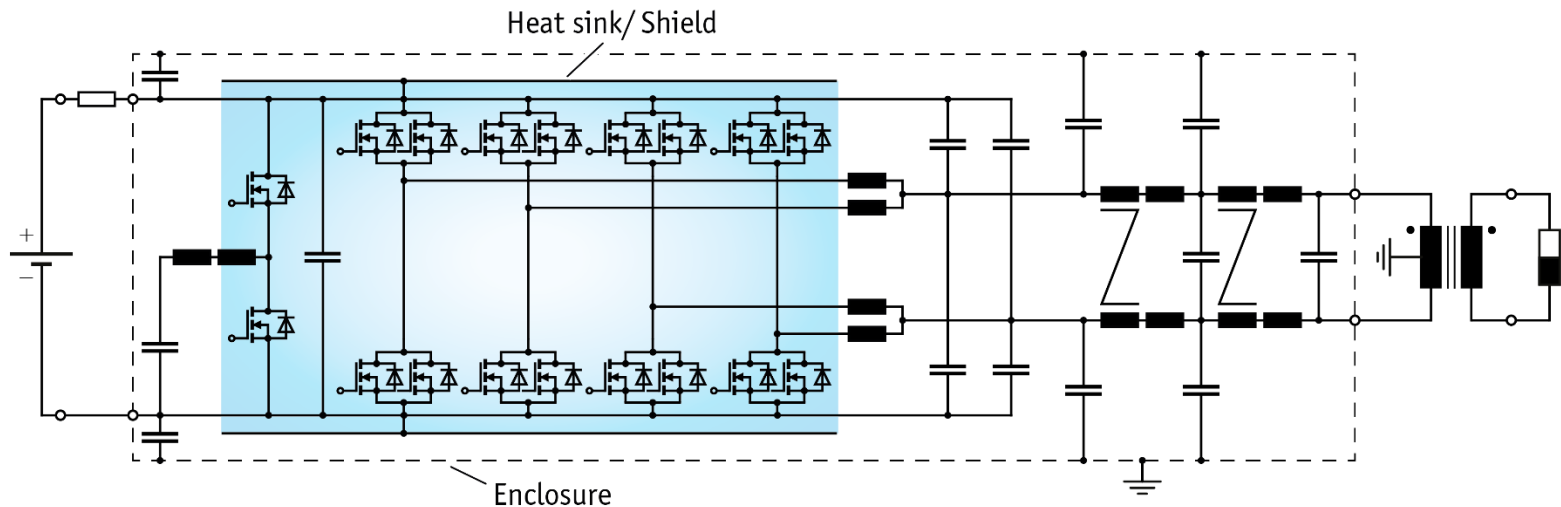- Interleaving of 2 Bridge Legs per Phase
- Active DC-Side Buck-Type Power Pulsation Buffer
- 2-Stage EMI AC Output Filter



- ZVS of All Bridge Legs @ Turn-On/Turn-Off in Whole Operating Range (4D TCM Interleaving)
- Heatsinks Connected to DC Bus / Shield to Prevent Cap. Coupling to Grounded Enclosure


Technologies

Power Semiconductors
Passives
Cooling
■ *DSP/FPGA*



Selection of Switching Frequency

 - Significant Reduction in EMI Filter Volume for Increasing Sw. Frequency





- Doubling Sw. Freq. f_s Cuts Filter Volume in Half
- Upper Limit due to Digital Signal Processing Delays / Inductor & Sw. Losses – Heatsink Volume




Power Semiconductors

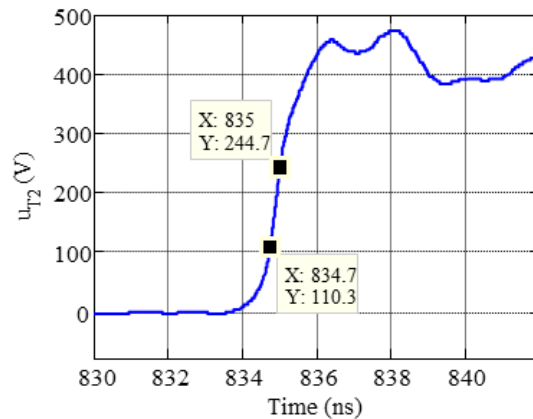 - 600V IFX Normally-Off GaN GIT - ThinPAK8x8
 - 2 Parallel Transistors / Switch
 - Antiparallel CREE SiC Schottky Diodes
- 1.2V typ. Gate Threshold Voltage
 - 55 mΩ $R_{DS,on}$ @ 25°C, 120mΩ @ 150°C
 - 5Ω Internal Gate Resistance




$dv/dt = 500kV/\mu s$

 

- CeraLink Capacitors for DC Voltage Buffering

Advanced Gate Drive (1)

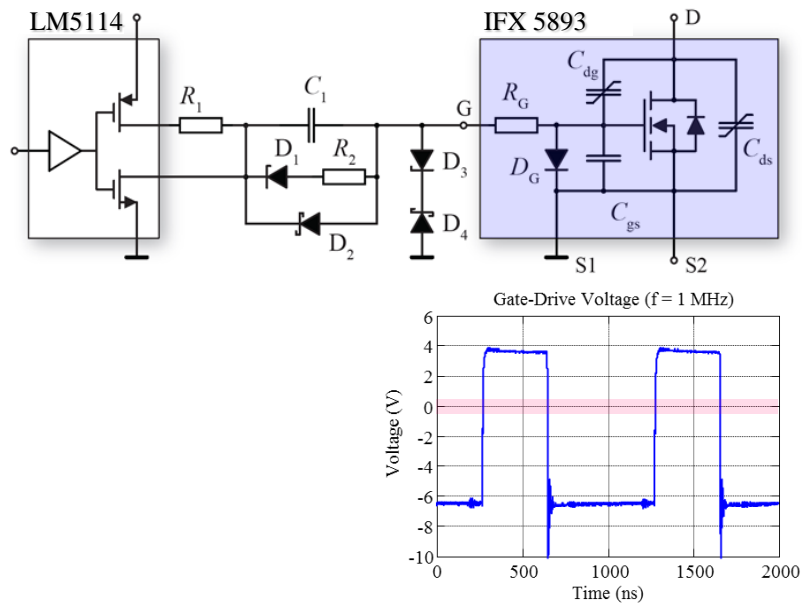- Fixed Negative Turn-off Gate Voltage Independent of Sw. Frequency and Duty Cycle
- Extreme dv/dt Immunity (500 kV/ μ s) Due to CM Choke at Signal Isolator Input




- Total Prop. Delay < 30ns incl. Signal Isolator, Gate Drive, and Switch Turn-On Delay



Advanced Gate Drive (2)

- Fixed Negative Turn-off Gate Voltage Independent of Sw. Frequency and Duty Cycle
- Extreme dv/dt Immunity (500 kV/ μ s) Due to CM Choke at Signal Isolator Input

 - Gate Voltage T+
- Gate Voltage T-
- TCM Inductor Current
- Transistor Voltage





- Triangular Current Mode (TCM) Operation at No Load \rightarrow ZVS and No Free Ringing of u_{T+} , u_{T-} or i_L

High Frequency Inductors (1)

- Multi-Airgap Inductor with Patented Multi-Layer Foil Winding Minimizing Prox. Effect
- Very High Filling Factor / Low High Frequency Losses
- Magnetically Shielded Construction Minimizing EMI
- **Intellectual Property of F. Zajc / Fraza (2012)**



  - $L = 10.5 \mu\text{H}$
- 2 x 8 Turns
- **24 x 80 μm Airgaps**
- Core Material DMR 51 / Hengdian
- 0.61mm Thick Stacked Plates
- 20 μm Copper Foil / 4 in Parallel
- 7 μm Kapton Layer Isolation
- 20m Ω Winding Resistance / $Q=800$
- Terminals in No-Leakage Flux Area



■ Dimensions - 14.5 x 14.5 x 22mm³




High Frequency Inductors (2)

IEEE TRANSACTIONS ON MAGNETICS, VOL. MAG-11, NO. 1, JANUARY 1975 ←

The Origin of the Increase in Magnetic Loss Induced by Machining Ferrites

JOHN E. KNOWLES


 
- Cutting of Ferrite Introduces Mechanical Stress in the Surface (5µm Layer)
- Significant Increase of the Loss Factor
- Reduction by Polishing / Etching



■ Comparison of Temp. Increase of a Bulk and a Sliced Sample @ 70mT / 800kHz

Thermal Management (1)

  
- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters
- 200um Fin Thickness
- 500um Fin Spacing
- 3mm Fin Height
- 10mm Fin Length
- CSPI = 37 W/(dm³.K)
- 1.5mm Baseplate



- $CSPI_{eff} = 25 \text{ W}/(\text{dm}^3.\text{K})$ Considering Heat Distribution Elements
- Two-Side Cooling → Heatsink Temperature = 52°C @ 80W (8W by Natural Convection)

Thermal Management (2)

 - **CSPI = 37 W/(dm³.K)**
- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters
- **CSPI_{eff} = 25 W/(dm³.K) incl. Heat Cond. Layers**





- Two-Side Cooling → Heatsink Temperature = **52°C @ 80W** (8W by Natural Convection)

Control Board & $i=0$ Detection

- Fully Digital Control - Overall Control Sampling Frequency of 25kHz
- TI DSC TMS320F28335 / 150MHz / 179-pin BGA / 12mmx12mm
- Lattice FPGA LFXP2-5E / 200MHz / 86-pin BGA / 8mmx8mm

  - TCM Current / Induced Voltage / Comparator Output





- $i=0$ Detection of TCM Currents Using R4/N30 Saturable Inductors
- Galv. Isolated / Operates up to 2.5MHz Switching Frequency / <10ns Delay

Power Pulsation Buffer Capacitor

- High Energy Density 2nd Gen. 400V_{DC} CeraLink Capacitors Utilized as Energy Storage
- Highly Non-Linear Behavior → Opt. DC Bias Voltage of 280VDC
- Cap. Losses of 16W @ 2kVA Output Power

  - 108 x 1.2μF / 400 V
- 23.7cm³ Capacitor Volume





- Effective Large Signal Capacitance of C ≈ 140μF


Auxiliary Supply & Measurements

- ZVS Constant 50% Duty Cycle Half Bridge with Synchr. Rectification
- Compact / Efficient / Low EMI

  - 10W Max. Output Power
- 380V...450V Input Operating Range
- 13.6V...16.8V DC Output in Full Inp. Voltage / Output Power Range
- 90% Efficiency @ P_{max}



- 19mm x 24mm x 4.5mm (2cm³ Volume)

 

Experimental Results

Hardware
Output Voltage/Input Current Quality
Thermal Behavior
Efficiency
EMI →

Little-Box Prototype I


- Electrolytic Capacitors as DC-Side Power Pulsation Buffer

- 7.3 kW/dm³
- 9.7cm x 9.1cm x 3.1cm
- **97,5% Efficiency @ 2kW**
- **$T_c=58^\circ\text{C}$ @ 2kW**

- $\Delta u_{\text{DC}} = 2.85\%$
- $\Delta i_{\text{DC}} = 15.4\%$
- $\text{THD}+N_U = 2.6\%$
- $\text{THD}+N_I = 1.9\%$


- **Compliant to All Original Specifications (!)**

 - No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



Measurement Results I-(1)

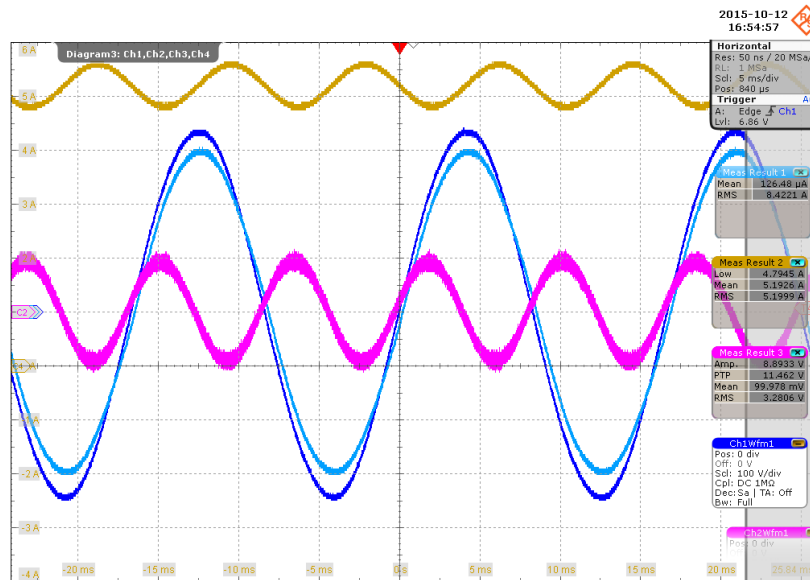- Electrolytic Capacitors as DC-Side Power Pulsation Buffer




Ohmic Load / 2kW

DC Input Current
DC Voltage Ripple
Output Voltage
Output Current


- Compliant to All *Original Specifications* (!)

Measurement Results I-(2)

 - Electrolytic Capacitors as DC-Side Power Pulsation Buffer





★ $\eta_w = 96.4\%$ Weighted Efficiency

 

- Heating of System Lower than Specified Limit ($T_{c,max} = 60^\circ\text{C} @ T_{amb} = 30^\circ\text{C}$)

Measurement Results I-(3)

  - Electrolytic Capacitors as DC-Side Power Pulsation Buffer



- Compliant to All *Original Specifications* (!)

Little-Box Prototype II-(1)

- Active DC-Side Power Pulsation Buffer

- 8.2 kW/dm³
- 8.9cm x 8.8cm x 3.1cm
- 96,3% Efficiency @ 2kW
- $T_c=58^{\circ}\text{C}$ @ 2kW


- $\Delta u_{\text{DC}} = 1.1\%$
- $\Delta i_{\text{DC}} = 2.8\%$
- $\text{THD}+N_U = 2.6\%$
- $\text{THD}+N_I = 1.9\%$

- Compliant to All *Original Specifications* (!)

- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



★ 135 W/in³

 

Little-Box Prototype II-(2)

- Active DC-Side Power Pulsation Buffer

- 8.2 kW/dm³
- 8.9cm x 8.8cm x 3.1cm
- 96,3% Efficiency @ 2kW
- $T_c=58^{\circ}\text{C}$ @ 2kW


- $\Delta u_{\text{DC}} = 1.1\%$
- $\Delta i_{\text{DC}} = 2.8\%$
- $\text{THD}+N_U = 2.6\%$
- $\text{THD}+N_I = 1.9\%$

- Compliant to All *Original Specifications* (!)

- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents




★ 135 W/in³

 


Measurement Results II-(1)

- Active DC-Side Power Pulsation Buffer

 Output Current
Inductor Current Bridge Leg 1-1
Inductor Current Bridge Leg 1-2
- Ohmic Load / 2kW



 DC Link Voltage (AC-Coupl., 2V/Div.)
Buffer Cap. Voltage
Buffer Cap. Current
Output Voltage




- Compliant to All *Original Specifications* (!)

Measurement Results II-(2)

- Active DC-Side Power Pulsation Buffer

 DC Link Voltage
Buffer Cap. Voltage
Buffer Cap. Current
Inductor Current Bridge Leg 1-1




- Start-Up and Shut-Down (No Load Operation)


Evaluation
Volume Distribution
Loss Distribution →

Evaluation / Optimization Potential

Volume Distribution (240cm³)

 

Loss Distribution (75W)

 

- Large Heatsink (incl. Heat Conduction Layers)
- Large Losses in Power Fluctuation Buffer Capacitor (!)
- TCM Causes Relatively High Conduction & Switching Losses @ Low Power
- Relatively Low Switching Frequency @ High Power – Determines EMI Filter Volume


Optimization

Full-Bridge TCM Interleaved
Full-Bridge TCM Not Interleaved
Full-Bridge PWM
Buck-Stage & Unfolder



Multi-Objective Optimization Results

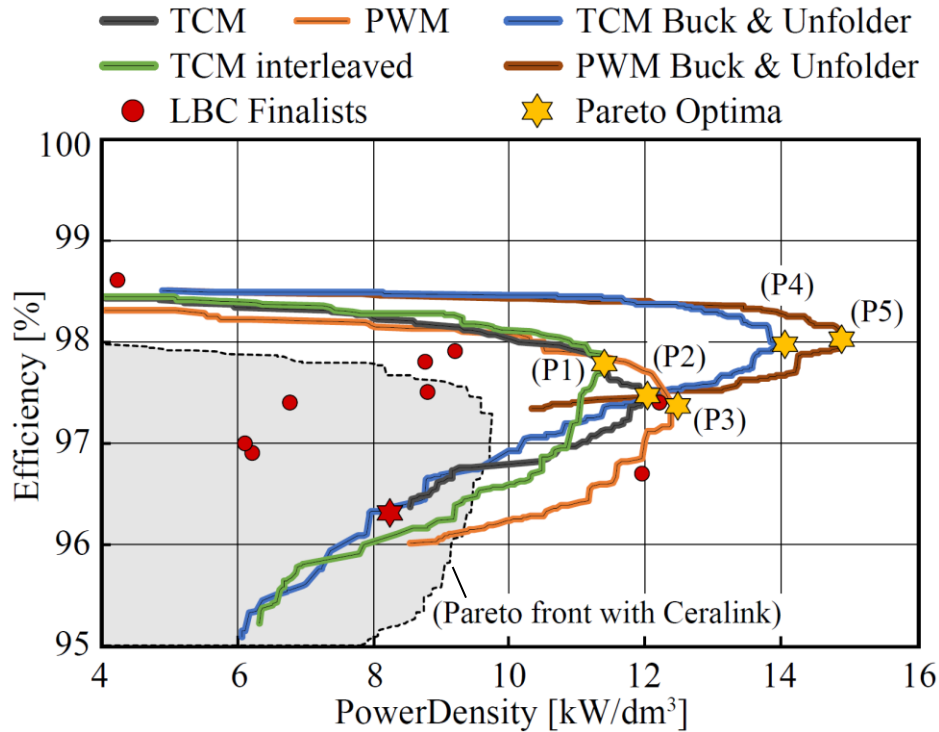- 135 W/in³ → 230 W/in³ (!) @ CSPI = 25 W/(dm³.K)



- No Interleaving
- PWM / Constant Switching Frequency
- X6S Capacitor Technology Employed in Power Pulsation Buffer



- ***Other Finalists***

Topologies
Switching Frequencies
Power Density / Efficiency Comparison →

For Detailed
Descriptions:
www.LittleBoxChallenge.com

Finalists - Performance Overview

  
- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities



- 70...300 W/in^3
- 35 kHz...500kHz...1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps of Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)

Finalists - Performance Overview

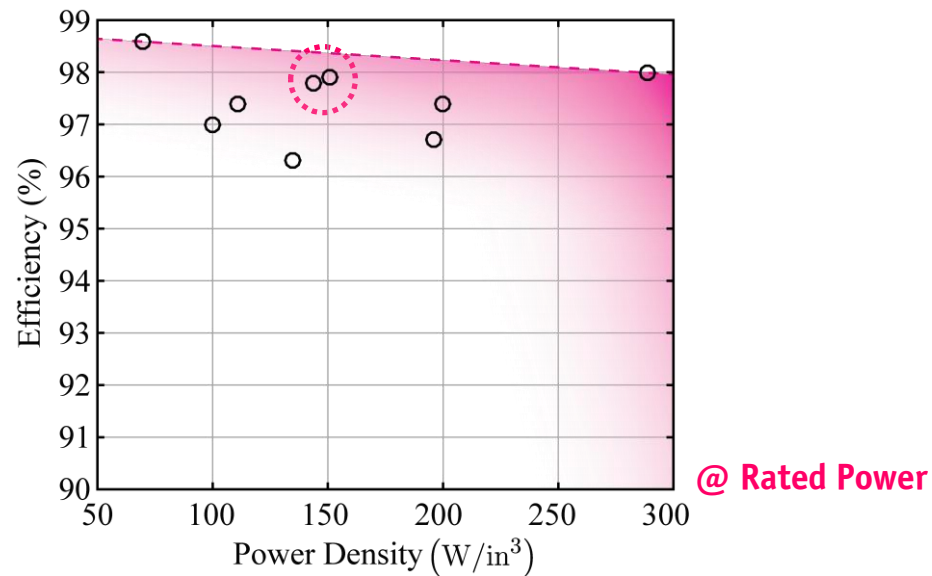- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities




- 70...300 W/in³
- 35 kHz... 500kHz... 1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps of Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)



Category I: 300 – 400 W/in³ (1 Team)

 
- “Over the Edge”
- Hand-Wound Overstressed & Too Small Electrolytic Capacitors (210uF/400V)
- No Voltage Margin of Power Semiconductors (450V GaN, Hard Switching)
- 50V Voltage Source for Semicond. Voltage Stress Reduction
- Low-Frequ. CM AC Output Component



- Alternate Switching of Full-Bridge Legs
- Input Cap. of Full-Bridge Used for Power Pulsation Buffering
- 256 W/in³ (400 W/in³ Claimed) / 1MHz
- Multi-Airgap Toroidal Inductors (3F46, $C_p \approx 1.5\text{pF}$)
- Bare Dies Directly Attached to Pin-Fin Heatsink
- High Speed Fan (Mini Drone Motor & Propeller)

Category I: 300 – 400 W/in³ (1 Team)

 - “Over the Edge”
- Hand-Wound Overstressed Electrolytic Capacitors (210uF (?)/400V)
- No Voltage Margin of Power Semiconductors (450V GaN, Hard Switching)
- 50V Voltage Source for Semicond. Voltage Stress Reduction





- Alternate Switching of Full-Bridge Legs
- Input Cap. of Full-Bridge Used for Power Pulsation Buffering
- 256 W/in³ (400 W/in³ Claimed) / 1MHz
- Multi-Airgap Toroidal Inductors (3F46, $C_p \approx 1.5\text{pF}$)
- Bare Dies Directly Attached to Pin-Fin Heatsink
- High Speed Fan (Mini Drone Motor & Propeller)




Category II: 200 – 300 W/in³ (4 Teams) – Example #1

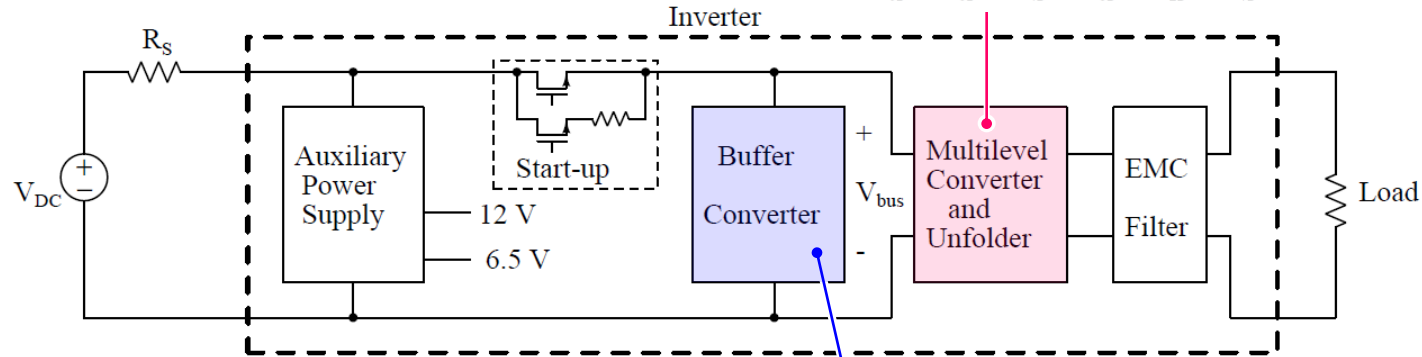 - "At the Edge"
- High Complexity
- 7-Level Flying Capacitor Converter
- Series-Stacked Active Power Buffer




- 216 W/in³
- 100V GaN
- Integrated Switching Cell
- 720kHz Eff. Sw. Frequ. (7 x 120kHz)

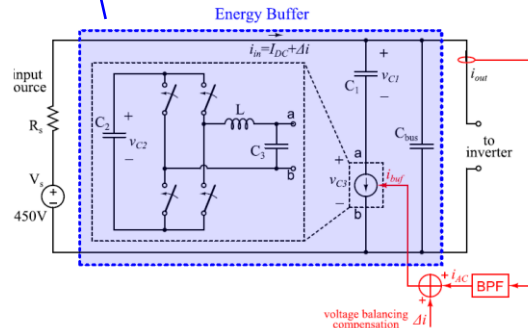



Category II: 200 – 300 W/in³ (4 Teams) – Example #2

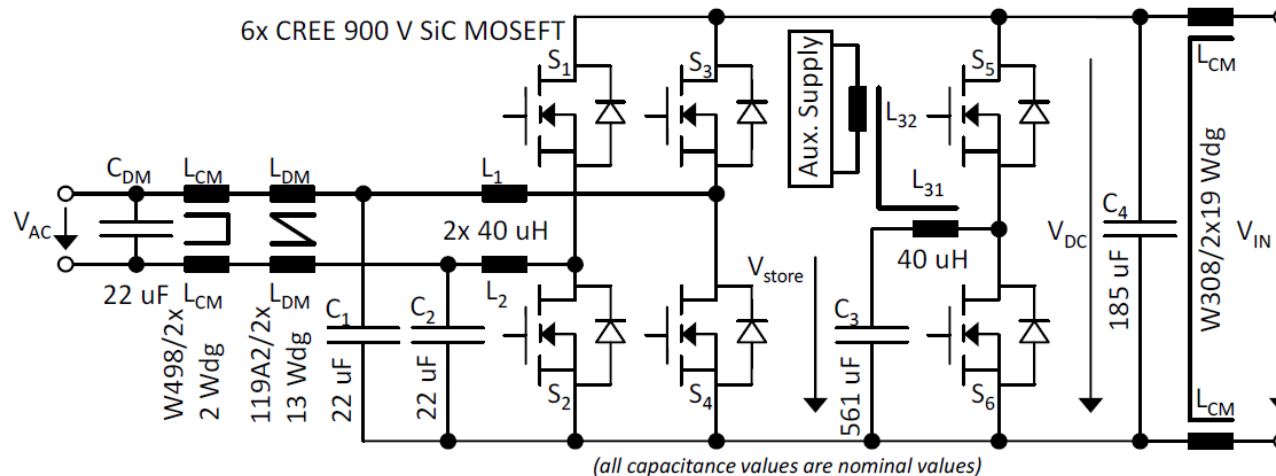- “At the Edge”
- Very Well Engineered Assembly (e.g. 3D-Printed Heatsink w. Integr. Fans, 1 PCB Board, etc.)
- No Low-Frequ. Common-Mode AC Output Component




- 201W / in³
- Multi-Airgap (8 Gaps) Inductors
- 900V SiC @ 140kHz (PWM, Soft & Hard Switching)
- Buck-Type Active DC-Side Power Pulsation Filter / Ceramic Capacitors (X6S)



Category III: 100 – 200 W/in³ (8 Teams) – Example

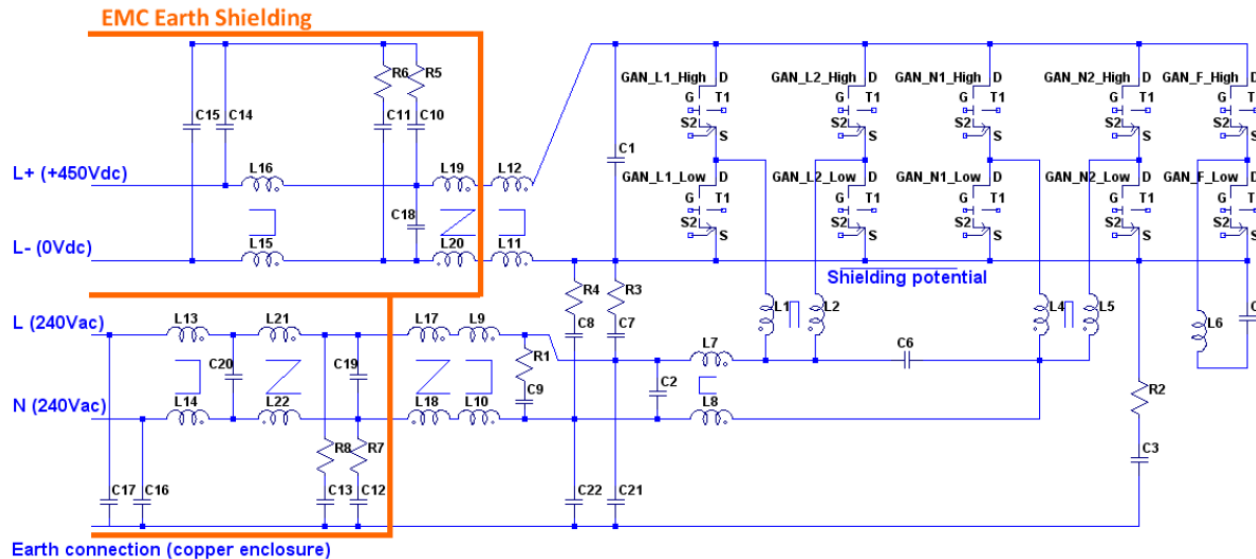- “Advanced Industrial”
- Sophisticated 3D Sandwich Assembly incl. Cu Honeycomb Heatsink
- Shielded Multi-Stage EMI Filter @ DC Input and AC Output
- No Low-Frequ. Common-Mode AC Output Component




- 143 W/in³
- GaN @ ZVS (35kHz...240kHz)
- 2 x Interleaving for Full-Bridge Legs
- Buck-Type DC-Side Active Power Pulsation Filter (<150μF)





Category III: 100 – 200 W/in³ (8 Teams) – Example

 - “Advanced Industrial”
- **Sophisticated 3D Sandwich Assembly** incl. Cu Honeycomb Heatsink
- Shielded Multi-Stage EMI Filter @ DC Input and AC Output
- No Low-Frequ. Common-Mode AC Output Component




- 143 W/in³
- GaN @ ZVS (35kHz...240kHz)
- 2 x Interleaving for Full-Bridge Legs
- Buck-Type DC-Side Active Power Pulsation Filter (<150µF)



Category IV: 50 – 100 W/in³ (1 Team)




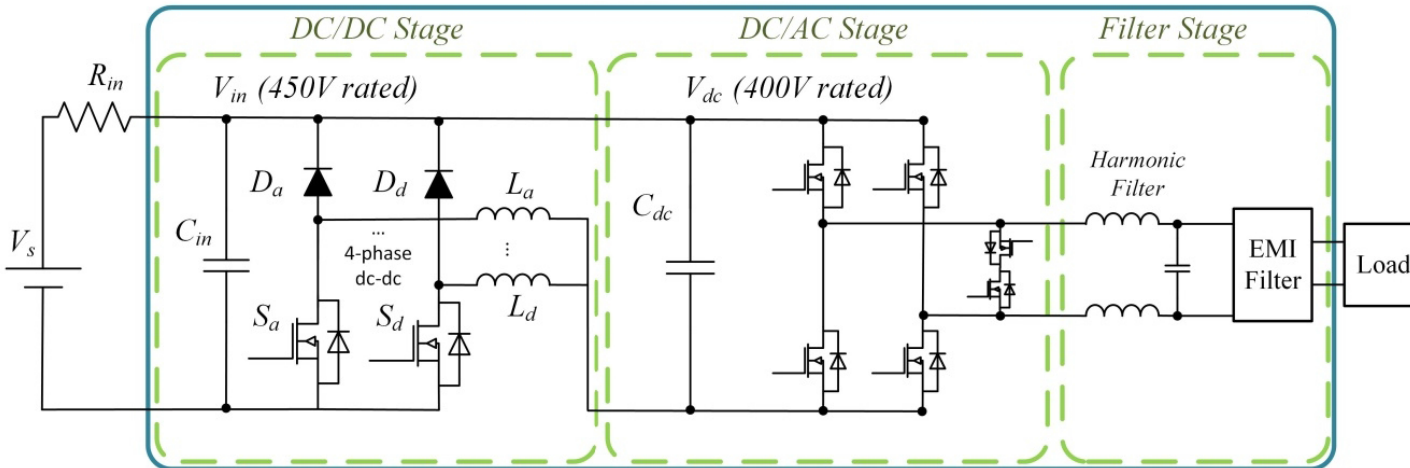- **“Industrial”**
- 400V_{max} Full-Bridge Input Voltage
- **DC-Link Cap. Used as Power Pulsation Buffer** (470uF)
- **GaN Transistors / SiC Diodes** (400kHz DC/DC, 60kHz DC/AC)
- Multi-Stage EMI Filter @ AC Output and L_{CM} + Feed-Trough C_{CM} @ DC Inp. (Not Shown)




- $\approx 70 \text{ W/in}^3$
- **98% CEC Efficiency**
- **4.4% DC Input Current Ripple**
- **54°C Surface Temp. / Cooling with 10 Mirco-Fans**

- *Conclusions* →

 

Conclusions

■ There's **NO** Silver Bullet

 

.... **BUT** a Set of Core
 Concepts & Technologies

- **>200W/in³ (12kW/dm³) Achievable**
- **f_s < 150kHz (Constant) Sufficient**
- **SiC Can Also Do It**
- **ZVS (Partial) Helps**
- **Full-Bridge Output Stage**
- **Active Power Pulsation Buffer (Buck-Type, X6S Cap.)**
- **Conv. EMI Filter Structure**
- **Multi-Airgap Litz Wire Inductors**
- **DSP Can Do It (No FPGA)**
- **Careful Heat Management (Adv. Heat Sink, Heat Distrib., 2-Side Integr. Cooling, etc.)**
- **Careful Mechanical Design (3D-CAD, Single PCB, Avoid Connectors, etc.)**

■ Overall Summary

- **No (Fundamentally) New Approach**
- **Passives & 3D-Packaging are Finally Defining the Power Density → **CIPS (!)****
- **Competition Timeframe Too Short for Advanced Integration**
- **Building a Full System Not Possible for Many Universities – High Drop Out Rate**

Thank You!

Questions

