

Google Little-Box Reloaded



Johann W. Kolar et al.



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Google Little-Box Reloaded

J. W. Kolar, D. Neumayr, D. Bortis, M. Guacci, J. Azurza



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Outline

- ▶ **Google Little Box Challenge**
 - ▶ *Requirements*
 - ▶ *Little Box 1.0*
- ▶ **Further Analysis & New Approach**
 - ▶ *Adv. Measurement Techniques*
 - ▶ *New Circuit Topology*
 - ▶ *Little Box 2.0*
- ▶ **Conclusions**



The 'fraza' logo, consisting of the word 'fraza' in a lowercase, sans-serif font with a horizontal line underneath.

Acknowledgement

M. Kasper
O. Knecht
F. Krismer




Google Little Box Challenge

Requirements
Little Box 1.0
Other Finalists

LITTLE BOX CHALLENGE

 - Design / Build the 2kW 1-Φ Solar Inverter with the Highest Power Density in the World
- Power Density > 3kW/dm³ (50W/in³)
- Efficiency > 95%
- Case Temp. < 60°C
- EMI FCC Part 15 B



■ Push the Forefront of New Technologies in R&D of High Power Density Inverters

The Grand Prize

- Highest Power Density ($> 50\text{W}/\text{in}^3$)
- Highest Level of Innovation






\$1,000,000

- Timeline
 - Challenge Announced in Summer 2014
 - **2000+ Teams Registered** Worldwide
 - 100+ Teams Submitted a Technical Description until July 22, 2015
 - **18 Finalists (3 No-Shows)**




Selected Converter Topology

   - Full-Bridge Output Stage
- Modulation of Both Bridge Legs






 - DM Component of u_1 and u_2 Defines Output Voltage u_o
- No Low-Frequency CM Component of u_1 and u_2 (Different to e.g. 1- Φ PFC Rectifier Systems !)



Triangular Current Mode (TCM) ZVS Operation

 
 
 
- TCM Operation for Resonant Voltage Transition @ Turn-On/Turn-Off



- Requires Only Measurement of **Current Zero Crossings, $i = 0$**
- High f_s Around $i = 0$ Challenging for Digital Control
- Variable Sw. Freq. f_s Lowers EMI

$i=0$ Detection

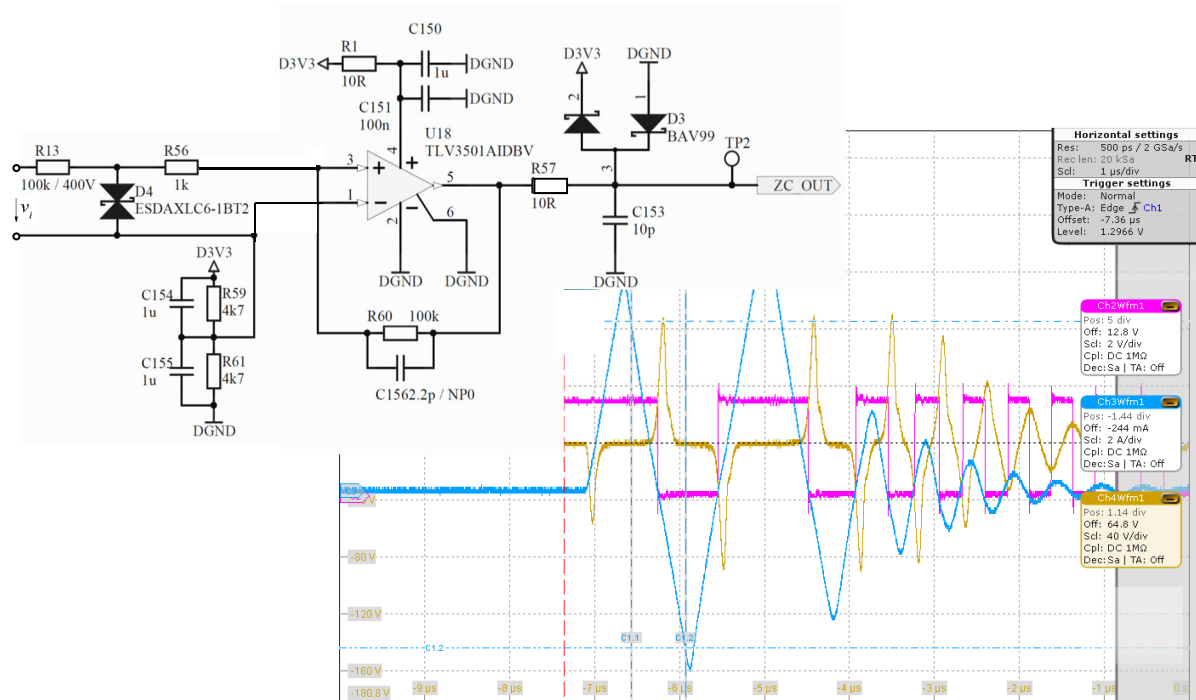  - Saturable Inductor - Toroidal Core R4 x 2.4 x 1.6, EPCOS (4mm Diameter)
- Core Material N30, EPCOS








■ Operation Tested up to 2.5MHz Switching Frequency



4D-Interleaving



   
 
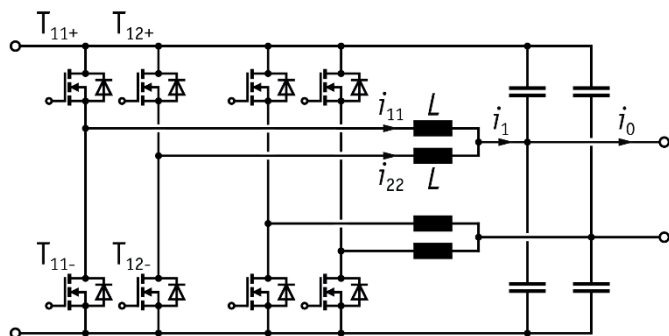
- Interleaving of 2 Bridge Legs per Phase - Volume / Filtering / Efficiency Optimum
- Interleaving in Space & Time – Within Output Period
- Alternate Operation of Bridge Legs @ Low Power
- Overlapping Operation @ High Power



- Opt. Trade-Off of Conduction & Switching Losses / Opt. Distribution of Losses

DC-Side Passive Power Pulsation Buffer

- Electrolytic Capacitor

   

$S_0 = 2.0 \text{ kVA}$
 $\cos \Phi_0 = 0.7$
 $V_{C,max} = 450 \text{ V}$
 $\Delta V_C / V_{C,max} = 3 \%$




■ $C > 2.2 \text{ mF} / 166 \text{ cm}^3 \rightarrow$ Consumes 1/4 of Allowed Total Allowed Volume !



DC-Side Active Power Pulsation Buffer

 - Large Voltage Fluctuation **Foil or Ceramic Capacitor**
- Buck-Type (Lower Voltage Levels) or Boost-Type DC/DC Interface Converter



CeraLink™
TDK




108 x 1.2μF / 400 V
 $C_k \approx 140\mu\text{F}$
 $V_{Ck} = 23.7\text{cm}^3$

- Significantly Lower Overall Volume Compared to Electrolytic Capacitor



DC-Side Active Power Pulsation Buffer

- Cascaded Control Structure

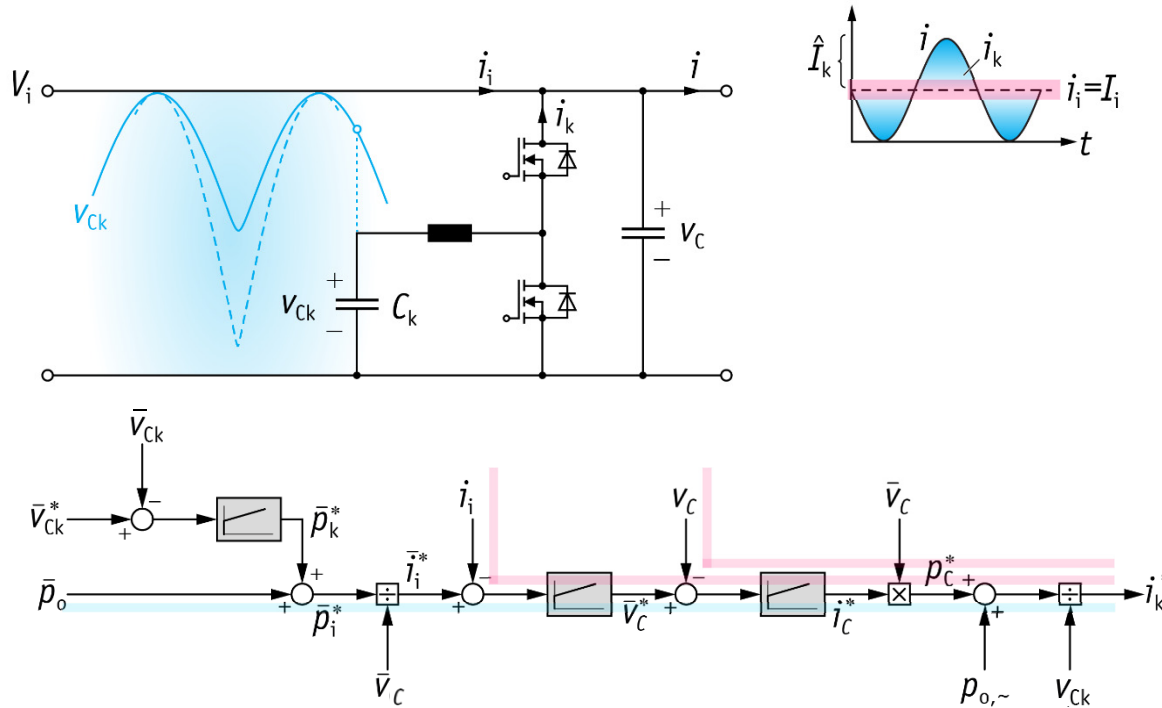


- P-Type Resonant Controller
- Feedforward of Output Power Fluctuation
- Outer Input Current (i_i) / Underlying DC Link Voltage (v_C) Control


Selected Power Semiconductors



 - 600V IFX Normally-Off GaN GIT - ThinPAK8x8
- State-of-the-Art Gate Drive




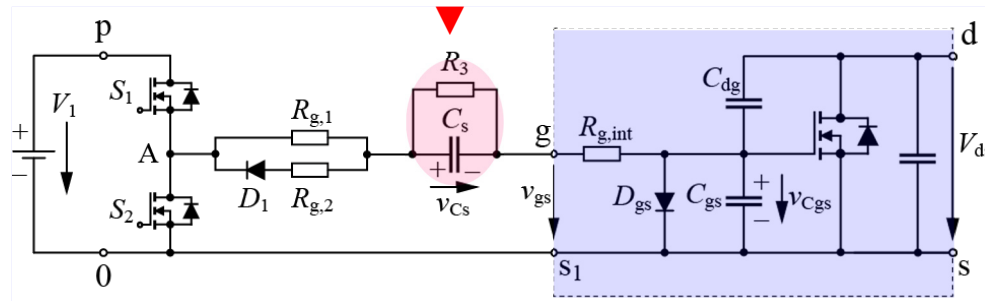$V_{gs,th} = 1.2V$
 $R_{ds,on} = 55\ m\Omega @ 25^\circ C$
 $R_{g,int} = 5\Omega$



- C_s Enables High Gate Current for Fast Turn-On

- R_3 Discharges C_s During Off-State

 


- Duty Cycle & Frequency Dependent Gate Voltage




High dv/dt -Immunity Gate Drive

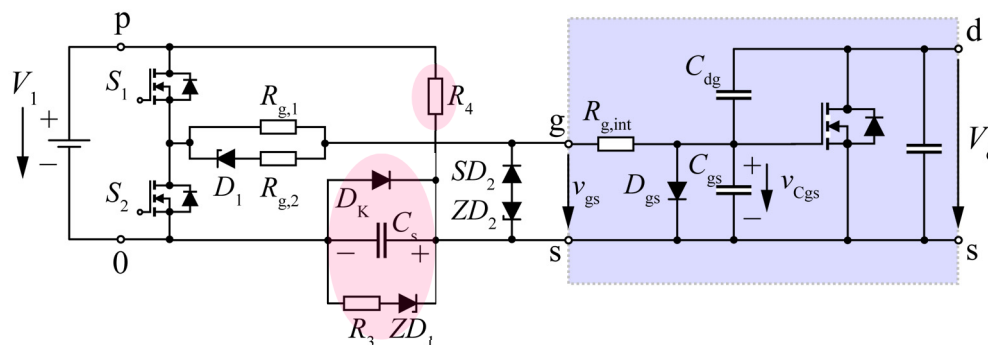- Fixed Negative Turn-Off Gate Voltage - Independent of Sw. Frequency and Duty Cycle
- Extreme dv/dt -Immunity (500kV/ μ s) - Due to CM Choke at Signal Isolator Input
- < 30ns Overall Prop. Delay



- Diode ZD_2 Quickly Discharges C_s to V_{ZD2} @ Turn-Off

 - Diode ZD_1 Prevents Complete Discharge of C_s During Off-State




- R_4 Ensures Precharge of $C_s \rightarrow$ Neg. Gate Voltage @ Start-Up



EMI Filter Topology (1)

- Conventional Filter Structure

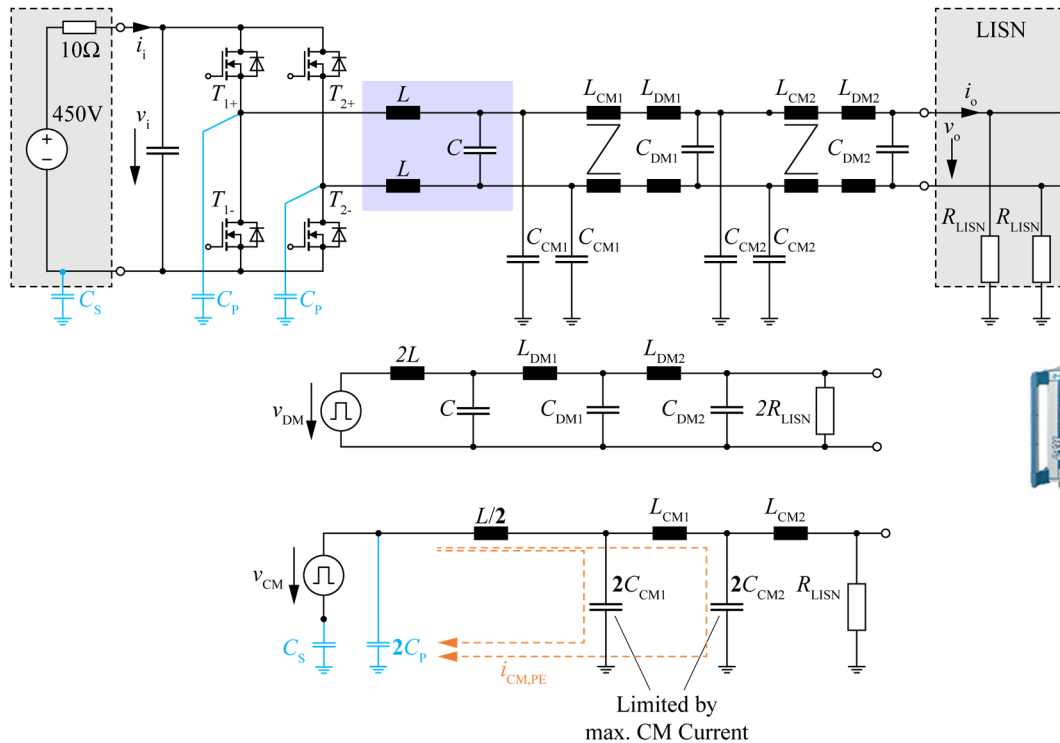
- DM Filtering Between the Phases
- CM Filtering Between Phases and PE



- CM Cap. Limited by Earth Current Limit – Typ. 3.5mA for PFC Rectifiers (GLBC: 5mA, later 50mA !)
- Large CM Inductor Needed – Filter Volume Mainly Defined by CM Inductors

EMI Filter Topology (2)

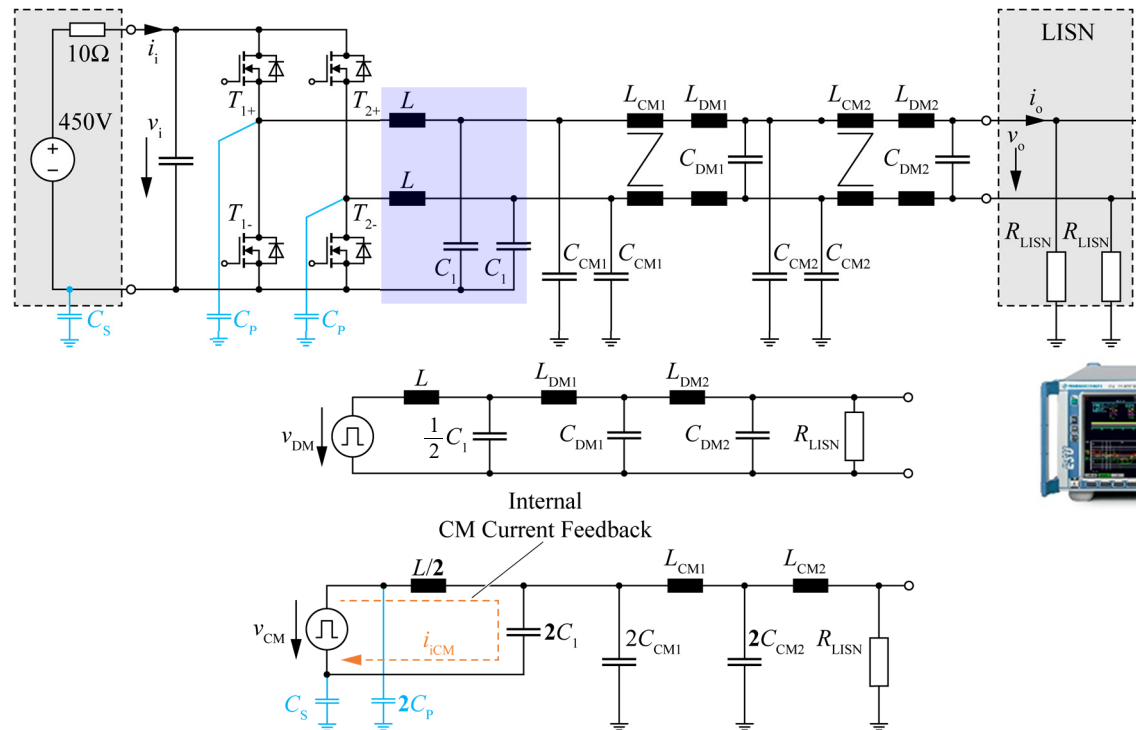- Filter Structure with Internal CM Capacitor Feedback
- Filtering to DC- (and Optional to DC+)




- No Limitation of CM Capacitor C_1 Due to Earth Current Limit → μF Instead of nF Can be Employed
- Allows Downsizing of CM Inductor and/or Total Filter Volume

Final Converter Topology

- Interleaving of 2 Bridge Legs per Phase
- Active DC-Side Buck-Type Power Pulsation Buffer
- First Stage AC Filter Caps Connected to DC-
- 2-Stage EMI AC Output Filter

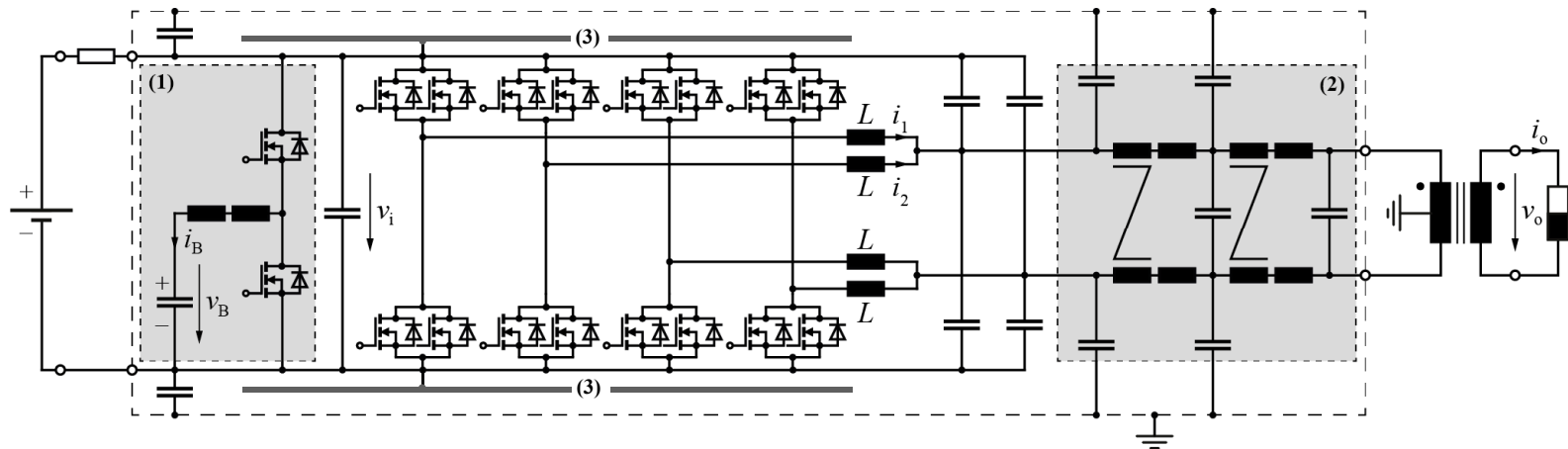- (1) Power Pulsation Buffer
- (2) EMI Output Filter
- (3) Heatsink




- ZVS of All Bridge Legs @ Turn-On/Turn-Off in Whole Operating Range (4D-TCM-Interleaving)
- Heatsinks Connected to DC Bus / Shield to Prevent Cap. Coupling to Grounded Enclosure

High Frequency Inductors (1)




- Multi-Airgap Inductor with Multi-Layer Foil Winding Arrangement Minim. Prox. Effect
- Very High Filling Factor / Low High Frequency Losses
- Magnetically Shielded Construction Minimizing EMI
- Intellectual Property of F. Zajc / Fraza

 - $L = 10.5 \mu\text{H}$
- 2 x 8 Turns
- 24 x $80 \mu\text{m}$ Airgaps
- Core Material DMR 51 / Hengdian
- 0.61mm Thick Stacked Plates
- $20 \mu\text{m}$ Copper Foil / 4 in Parallel
- $7 \mu\text{m}$ Kapton Layer Isolation
- $20\text{m}\Omega$ Winding Resistance / $Q \approx 600$
- Terminals in No-Leakage Flux Area






 
■ Dimensions - $14.5 \times 14.5 \times 22\text{mm}^3$



High Frequency Inductors (2)



   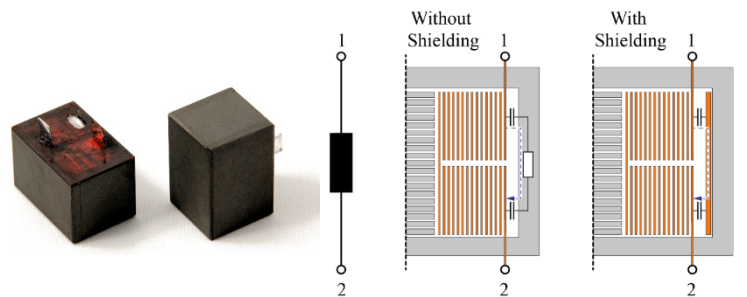- **High Resonance Frequency** → Inductive Behavior up to High Frequencies
- **Extremely Low AC-Resistance** → Low Conduction Losses up to High Frequencies
- **High Quality Factor**



- **Shielding Eliminates HF Current through the Ferrite** → Avoids High Core Losses
- **Shielding Increases the Parasitic Capacitance**


High Frequency Inductors (3)

Comparison of Temp. Increase of a Bulk and a Sliced Ferrite Sample @ 70mT / 800kHz





* Knowles (1975!)

 - Cutting of Ferrite Introduces Mech. Stress
- Significant Increase of the Loss Factor
- Further Treatment Still to be Clarified



Thermal Management (1)

  - 30°C max. Ambient Temperature
- 60°C max. Allowed Surface and Air Outlet Temperature
- Evaluation of Optimum Heatsink Temp. for Thermal Isolation of Converter




- Minimum Volume Achieved w/o Thermal Isolation with Heatsink @ max. Allowed Surface Temp.


Thermal Management (2)

- Overall Cooling Performance Defined by Selected Fan Type and Heatsink


- Radial Blower

 




- Axial Fan

 

 - Square Cross Section of Heatsink for Using a Fan



- Flat and Wide Heatsink for Blower

  
 


- Optimal Fan and Heat Sink Configuration Defined by Total Cooling System Length
- Cooling Concept with Blower Selected → Higher CSPI for Larger Mounting Surface

Thermal Management (3)

- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters

  - 200um Fin Thickness
- 500um Fin Spacing
- 3mm Fin Height
- 10mm Fin Length
- $CSPI = 37 \text{ W}/(\text{dm}^3 \cdot \text{K})$
- 1.5mm Baseplate



- $CSPI_{eff} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$ Considering Heat Distribution Elements
- Two-Side Cooling \rightarrow Heatsink Temperature = 52°C @ 80W (8W by Natural Convection)

Little Box 1.0

★ 135 W/in³


- System Employing Active CeraLink™ 1- Φ Power Pulsation Buffer

- 8.2 kW/dm³
- 8.9cm x 8.8cm x 3.1cm
- $f_s = 250\text{kHz} \dots 1\text{MHz}$
- 96,3% Efficiency @ 2kW
- $T_c = 58^\circ\text{C}$ @ 2kW

- $\Delta u_{\text{DC}} = 1.1\%$
- $\Delta i_{\text{DC}} = 2.8\%$
- $\text{THD} + N_U = 2.6\%$
- $\text{THD} + N_I = 1.9\%$

- Compliant to All "Original" Specifications (!)

 - $i_{\text{gnd}} < 5\text{mA}$ (!)
- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



Little Box 1.0

★ 135 W/in³


- System Employing Active CeraLink™ 1- Φ Power Pulsation Buffer

- 8.2 kW/dm³
- 8.9cm x 8.8cm x 3.1cm
- $f_s = 250\text{kHz} \dots 1\text{MHz}$
- 96,3% Efficiency @ 2kW
- $T_c = 58^\circ\text{C}$ @ 2kW

- $\Delta u_{\text{DC}} = 1.1\%$
- $\Delta i_{\text{DC}} = 2.8\%$
- $\text{THD} + N_U = 2.6\%$
- $\text{THD} + N_I = 1.9\%$

- Compliant to All "Original" Specifications (!)

 - $i_{\text{gnd}} < 5\text{mA}$ (!)
- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents




Measurement Results (1)


- System Employing Active CeraLink™ 1-Φ Power Pulsation Buffer

- Ohmic Load / 2kW

 Output Current (10A/div)
 Inductor Current Bridge Leg 1-1 (10A/div)
 Inductor Current Bridge Leg 1-2 (10A/div)



 
DC Link Voltage (AC-Coupl., 2V/div)
 Buffer Cap. Voltage (20V/div)
 Buffer Cap. Current (10A/div)
 Output Voltage (200V/div)



Compliant to All Specifications

Measurement Results (2)

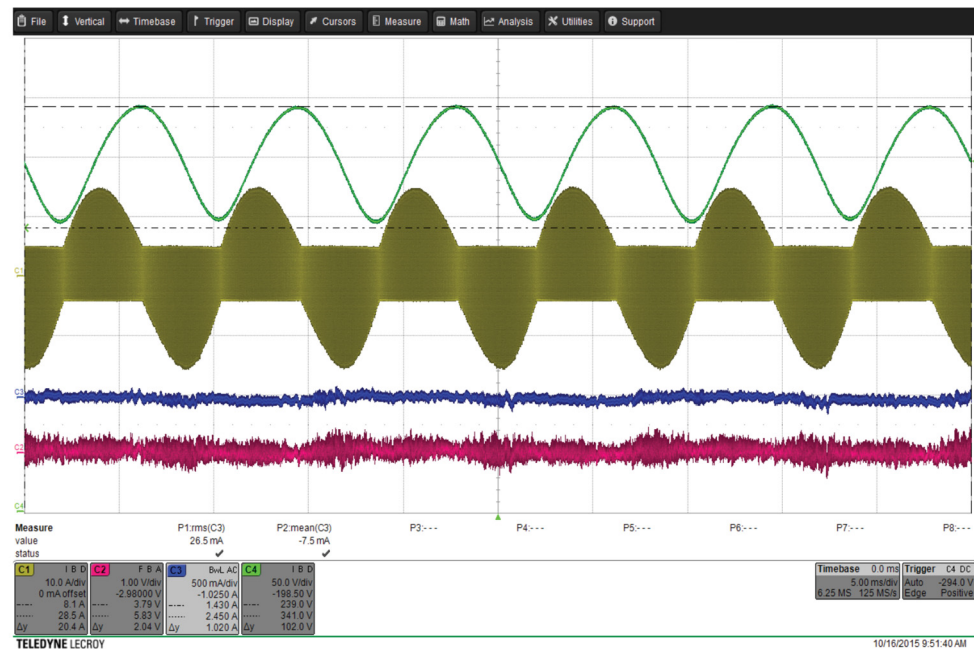- System Employing Active CeraLink™ 1- Φ Power Pulsation Buffer




Buffer Cap. Voltage (50V/div)
 Buffer Cap. Current (10A/div)
 DC Inp. Curr. (AC Coupl. 500mA/div)
 DC Link Voltage (AC Coupl. 1V/div)

- Stationary Operation @ 2kW Output Power

Measurement Results (3)

 
- System Employing Active CeraLink™ 1- Φ Power Pulsation Buffer




- Rel. Low Part Load Efficiency → Rel. High Output Power Independent Loss Components

Volume & Loss Distribution

Volume Distribution (240cm³)

 

Loss Distribution (75W)

 


- Large Heatsink (incl. Heat Conduction Layers)
- Large Losses in Power Fluctuation Buffer Capacitor (!)
- TCM Causes Relatively High Conduction & Switching Losses @ Low Power
- Relatively Low Switching Frequency @ High Power – Determines EMI Filter Volume

Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

Note: Numbering of Teams is Arbitrary

 

- (1) Virginia Tech
- (2) Schneider Electric
- (3) EPRI (Univ. of Tennessee)
- (4) Venderbosch
- (5) Energy Layer
- (6) ETH Zurich
- (7) Rompower
- (8) Tommasi-Bailly
- (9) Red Electric Devils
- (10) AHED
- (11) FH IISB
- (12) Univ. of Illinois
- (13) AMR

- 70... 300 W/in³
- 35 kHz ... 500kHz ... 1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC|Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps of Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)

Google
Little Box Challenge
Grand Prize Winner



Dr. Paul Bleus
Directeur R&D





Red Electric Devils

Olivier Bomboir, Paul Bleus, Fabrice
Frebel, Thierry Joannes, Francois Milstein,
Pierre Stassin, Christophe Geuzaine, Carl
Emmerechts, Philippe Laurent

Red Electric Devils

★ 145 W/in³

 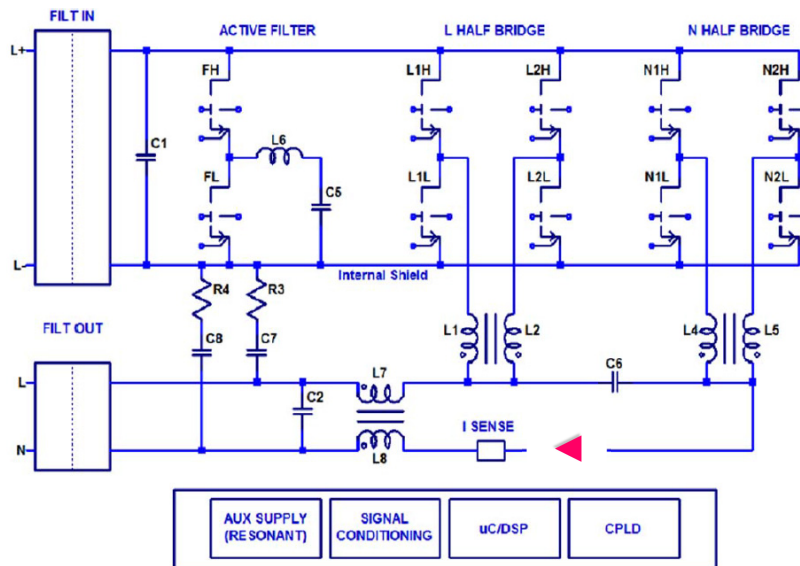- No Low-Freq. Common-Mode Output Voltage Comp. → $i_{gnd} < 5\text{mA}$ (!)
- Buck-Type DC-Side Active Power Pulsation Filter (MLCC Cap. $< 150\mu\text{F}$, 200V_{pp})




- 2 x Interleaved Bridge Legs for Each Half-Bridge
- DM Inductors (L_1/L_2 and L_4/L_5) and Series Connected CM Inductor (L_7/L_8)
- Single Open-Loop Hall Sensor Outp. Curr. Measurement + Observer-Based Curr. Reconstruction



Red Electric Devils

★ 145 W/in³

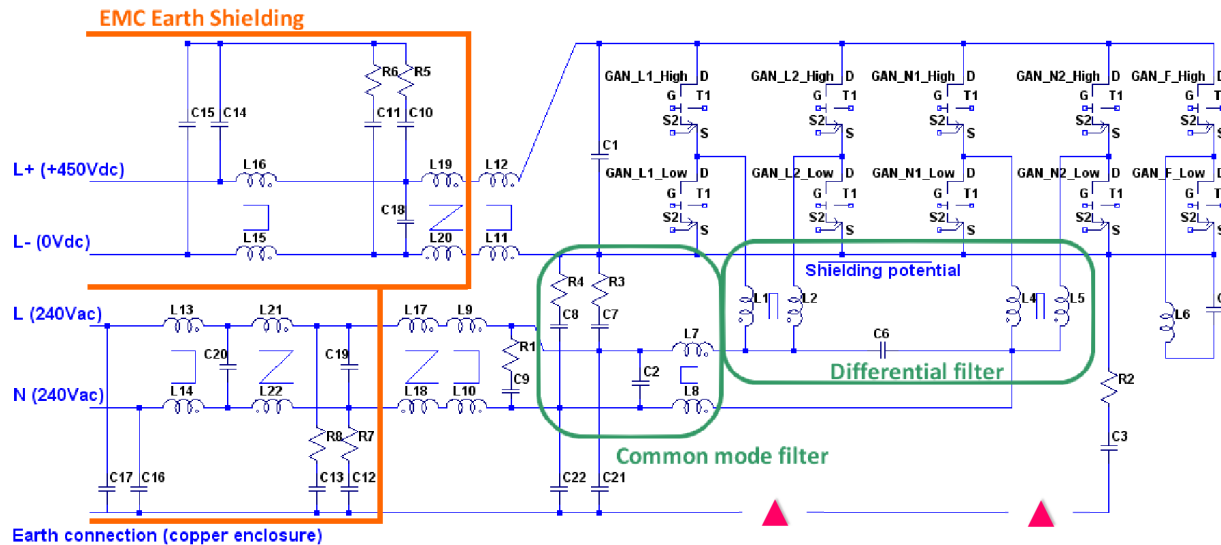- No Low-Freq. Common-Mode Output Voltage Comp. → $i_{\text{gnd}} < 5\text{mA}$ (!)
- Buck-Type DC-Side Active Power Pulsation Filter (MLCC Cap. $< 150\mu\text{F}$, 200V_{pp})





- DSP & CPLD Control
- GaN Systems @ ZVS (35kHz ... 240kHz)
- Shielded Multi-Stage EMI Filter @ DC Input & AC Output



Red Electric Devils

★ 145 W/in³

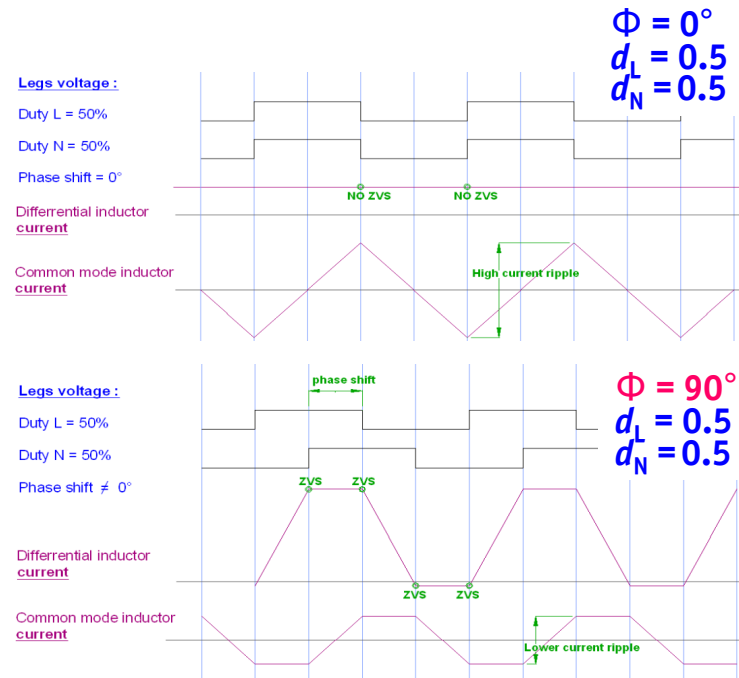 - Variable Phase-Shift of the Half-Bridges (0° or 90°) Dep. on Duty Cycle





- Selection of Opt. Phase Shift & Sw. Frequency for ZVS & Min. Size of Filter Ind. L_{CM} & L_{DM}



Red Electric Devils

★ 145 W/in³

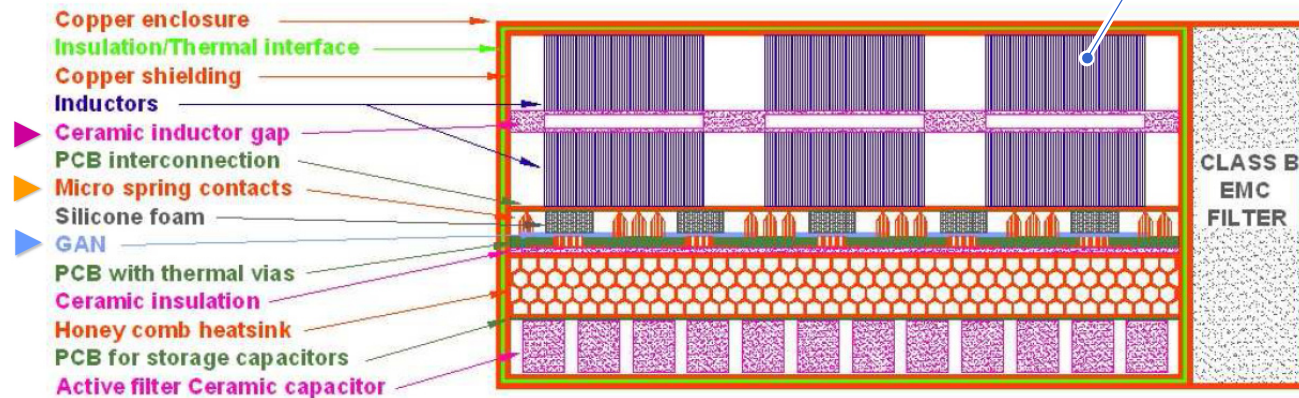 - 3D Sandwich Assembly
- Single Ultra-Thin PCB – Power / Control / Aux.
- Honeycomb Cu-Heatsink & Al Oxide Inductor Cooling
- MMLC Storage Caps Rows Utilized as Heatsink “Fins” (1mm Gaps)





- 145 W/in³
- 95.4 % CEC Efficiency
- $i_{\text{gnd}} < 5\text{mA}$ (!)
- CSPI = 22.6 W/(dm³.K) - Heatsink & Axial Fan



Red Electric Devils

★ 145 W/in³

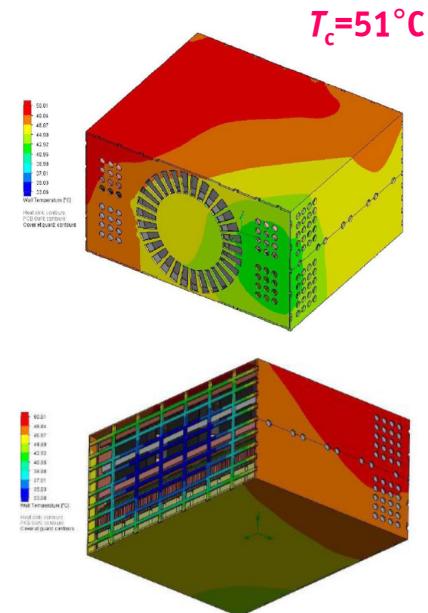 - 3D Sandwich Assembly
- Single Ultra-Thin PCB – Power / Control / Aux.
- Honeycomb Cu-Heatsink & Al Oxide Inductor Cooling
- MMLC Storage Caps Rows Utilized as Heatsink “Fins” (1mm Gaps)



- 145 W/in³
- 95.4 % CEC Efficiency
- $i_{\text{gnd}} < 5\text{mA}$ (!)
- CSPI = 22.6 W/(dm³.K) - Heatsink & Axial Fan

Google
Little Box Challenge
Top 3 Finalist



Schneider
 **Electric Team**

Miao-xin Wang, Rajesh Ghosh, Srikanth
Mudiyula, Radoslava Mitova, David Reilly,
Milind Dighrasker, Sajeesh Sulaiman, Alain
Dentella, Damir Klikic, Michael Hartmann



★ 100 W/in³

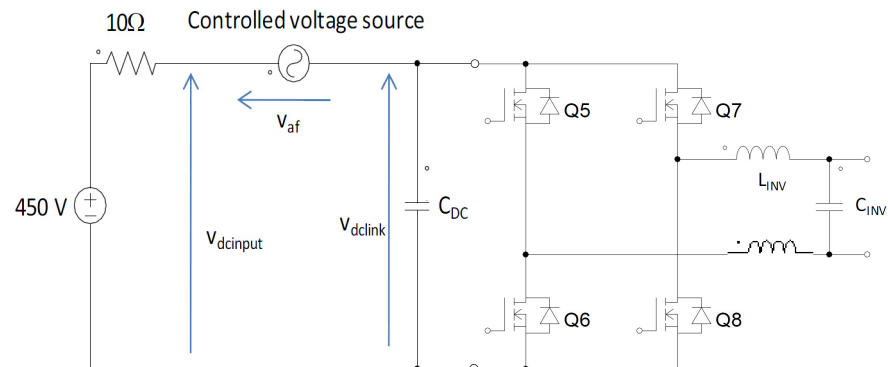 - High Efficiency & Robustness Preferred → Larger Size
- PWM of Both Legs of Output Full-Bridge → No Low. Freq. CM Output Voltage Comp.
- DC-Side Series (!) Active Power Puls. Filter → Compensates 120Hz DC Link Volt. Variation



- $C_{DC} = 400\mu\text{F} / 450\text{V}$
- 1/5 Volume Comp. to only Bulk Capacitors
- $V_{dcininput}$ Ripple <10% (<30V_{pp}) @ Full Load



- Nanocrystalline CM Choke
- DC-Side & AC-Side EMI/RF Filter
- Q_{5...8} - T0247 SiC MOSFETs, 45kHz of Both Legs



Schneider Global Team
Electric

★ 100 W/in³

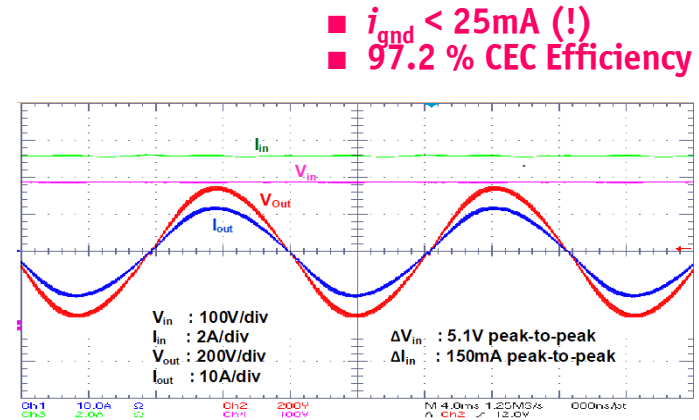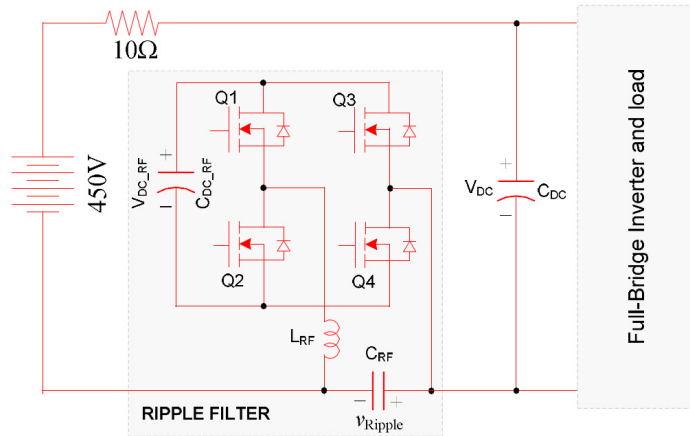- High Efficiency & Robustness Preferred → Larger Size
- PWM of Both Legs of Output Full-Bridge → No Low. Freq. CM Output Voltage Comp.
- DC-Side Series (!) Active Power Puls. Filter → Compensates 120Hz DC Link Volt. Variation



- $C_{\text{DC_RF}} = 2 \times 1500\mu\text{F}/25\text{V}$, $U_{\text{DC_RF}} = 15\text{V}$
- Only 52VA Processed Ripple Filter Power @ Rated Output (!)
- Q_1/Q_2 & Q_3/Q_4 - $R_{\text{ds,on}} = 2.2\text{m}\Omega$ MOSFETs (40V, 100A), w/o Heatsink, $f_s = 130\text{kHz}$ of Both Legs
- TI Piccolo DSP Control of Entire System / Open Loop Control of 120Hz Comp. Filter




Optimization of Little-Box 1.0

Adv. Modulation / Circuit Concepts
Measurement of Buffer Cap. Performance
Measurement of GaN ZVS & On-State Losses
Measurement of Multi-Airgap Core Losses
 η -Pareto Optimization

Eff. Optimal f_s -Modulation



   - TCM → ZVS but Large Current Ripple & Wide Frequency Variation
- PWM → Const. Sw. Frequency but Hard Sw. @ Current Maximum
- Opt. Combination of TCM & PWM → Optim. Variation of Local Sw. Frequ. Over Output Period
- Exp. Determination of Loss-Opt. Local Sw. Frequency f_{OFM} Considering DC/DC Conv. Stage






- Loss-Optimal Local Sw. Frequ. f_{OFM} for Given V_{DC} & Local i_o & v_{CO}
- DC/AC Properties Calculated Assuming Local DC/DC Operation

Eff. Optimal f_s -Modulation



   
- TCM → ZVS but Large Current Ripple & Wide Frequency Variation
- PWM → Const. Sw. Frequency but Hard Sw. @ Current Maximum
- Opt. Combination of TCM & PWM → Optim. Freq. Variation Over Output Period
- Exp. Determination of Loss-Opt. Sw. Frequency f_{OFM} Considering DC/DC Conv. Stage



- DC/AC Properties Calculated Assuming Local DC/DC Operation
- Loss-Optimal Local Sw. Freq. f_{OFM} for Given V_{DC} & Local i_o & v_{CO}

Eff. Optimal f_s -Modulation

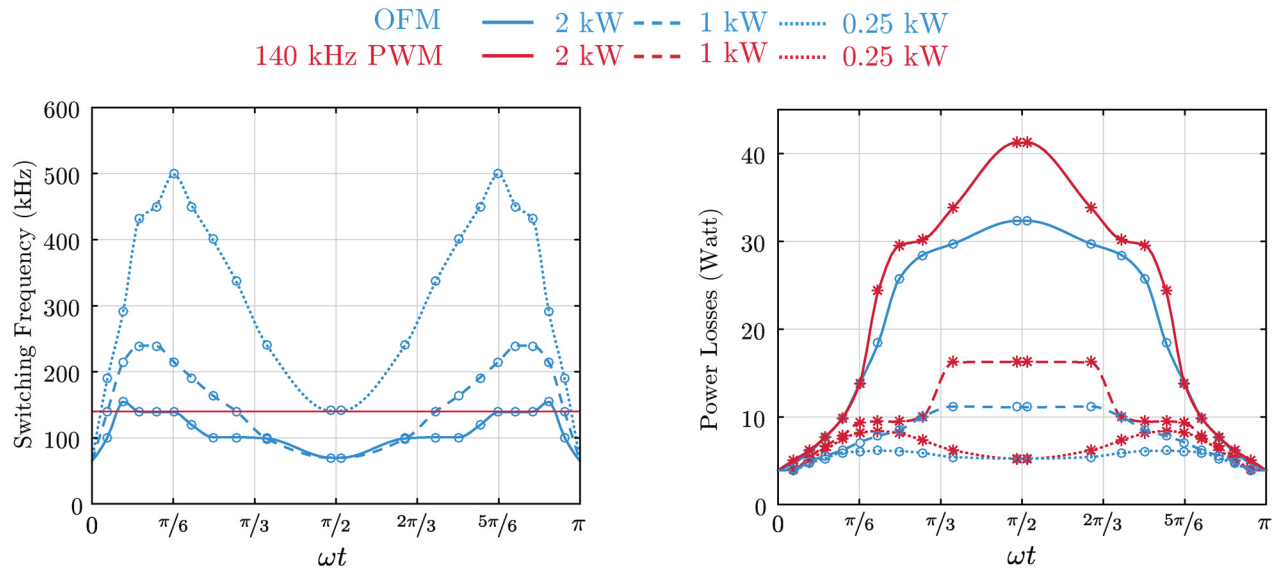
- Resulting Time-Dependency of Optimal Sw. Frequ. & Power Loss
- Comparison with 140 kHz Const. Sw. Frequency PWM



- Higher Average Switching Frequency f_s @ Light Loads
- Reduction of f_s @ Mains Voltage Peak (for Ohmic Load) for Sustaining ZVS

Eff. Optimal f_s -Modulation

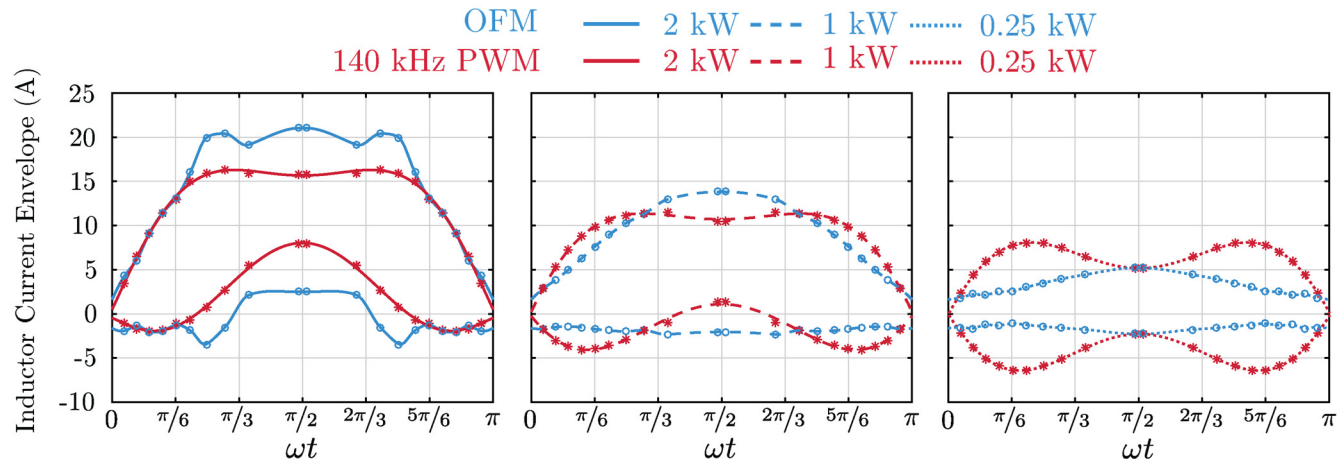- Optimal Inductor Current Envelope for Diff. Output Power Levels




- Higher Average Switching Frequency f_s @ Light Loads
- Reduction of f_s @ Mains Voltage Peak (for Ohmic Load) for Sustaining ZVS

iTCM Inverter Topology

- TCM → Challenging Inductor Design → HF & LF Currents
- iTCM → Add. LC-Circuit / Separation of LF & HF Currents → $L \gg L_B$ (P. Jain, 2015)


- TCM

 

- iTCM :

- Low Output Curr. Ripple / Noise
- Variable f_s PWM Applicable, No $i=0$ Detect.
- Dedicated LF and HF Inductor Designs Possible

- iTCM

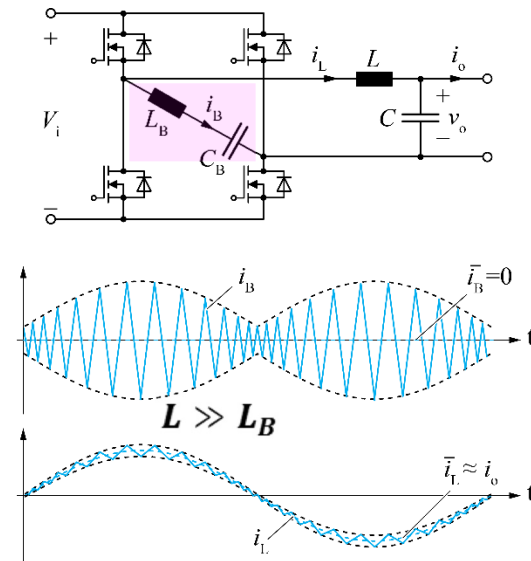



- Reduced Filtering Effort
- Simple Control Strategy (DSP)
- Improved Conv. Efficiency

Measurements

Buffer Capacitor Losses / Cap.
Power Semicond. ZVS & On-State Losses
Ferrite Multi-Airgap Core Losses

CeraLink™ vs. X6S (1)

 
 
- Electrolytic Capacitors → Limited by Lifetime Current Limit
- X6S MLCC, 2.2μF, 450 V Class II → Highest Energy Density but Low Cap. @ High DC Bias
- CeraLink™, 1μF / 2μF, 650 V → PLZT Ceramic, High Cap. @ High DC Bias
- CeraLink™ Allows Op. @ 125°C → Very Low ESR @ High Frequencies



■ PPB Design Optimiz. Requires Large-Signal Capacitance and Power Loss Data in All Operating Points

CeraLink™ vs. X6S (2)


 
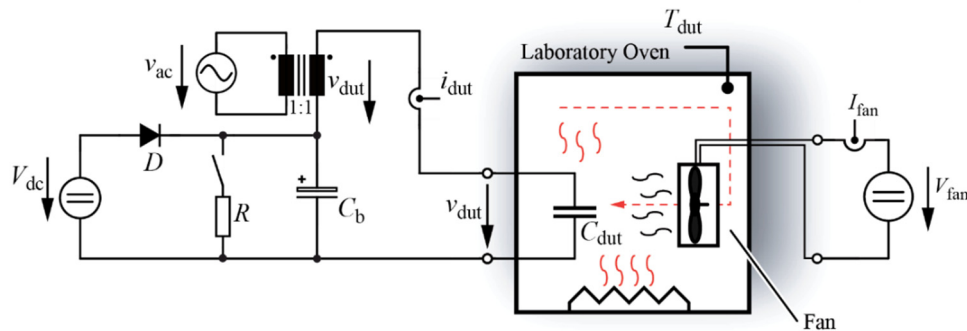
- Electrolytic Capacitors → Limited by Lifetime Current Limit
- X6S MLCC, 2.2 μ F, 450 V Class II → Highest Energy Density but Low Cap. @ High DC Bias
- CeraLink™, 1 μ F / 2 μ F, 650 V → PLZT Ceramic, High Cap. @ High DC Bias
- CeraLink™ Allows Op. @ 125°C → Very Low ESR @ High Frequencies



■ Experimental Setup for Generation of DC Bias & Superimposed AC Voltage

CeraLink™ vs. X6S (3)

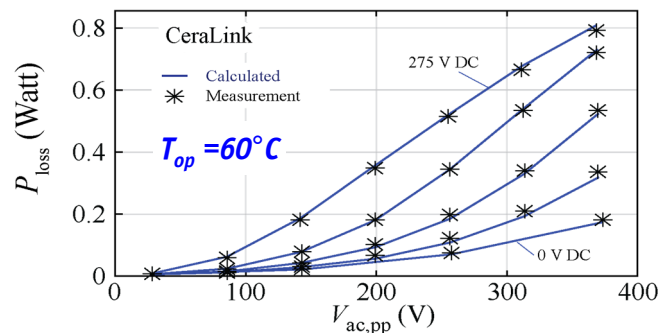  - CeraLink™**
 - Large-Signal 120Hz Excitation Reveals Large Hysteresis
 - Significantly Higher Losses @ 120Hz Comp. to X6S MLCC
 - ESR Drops Significantly @ Higher Temp.
 - 36μF (27μF) Blocks of Prepackaged Single Chips
 - Reliable Mech. Construction
- X6S MMLC**
 - Only Available as Single Chips
 - Complicated Packaging





CeraLink™ vs. X6S (4)



- Variation of DC Bias and Superimposed AC Voltage @ 60°C Operating Temp.

✗ Designed Op. Point

EPCOS/TKD
CeraLink™ 2μF, 600V

  


TDK Class II
X6S MLCC 2.2μF, 450V

 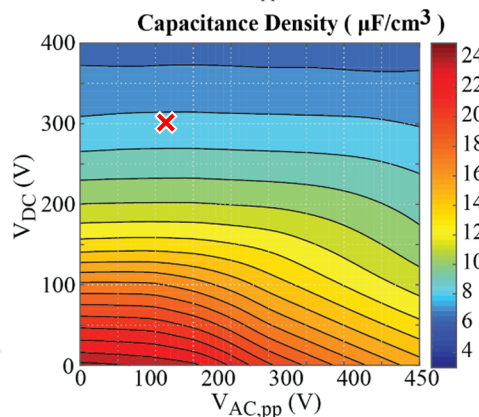



- PPB Design Optimiz. Requires Large-Signal Capacitance and Power Loss Data in All Operating Points

 **Measurement of
GaN ZVS & On-State Losses** →



Analysis of GaN Power Transistor ZVS Losses

 
 
- Little-Box 1.0 Experiments Indicated *Residual ZVS Losses of GaN Power Transistors*
- Losses Cannot be Explained by Remaining i_D, u_{DS} Overlap / Non-Ideal Gate Drive etc.



- Potentially Large Measurement Error for Electric Double-Pulse Sw. Loss Measurement
- Accuracy only Guaranteed by **Direct Loss Measurement** → **Calorimetric Approach**

Analysis of GaN Power Transistor ZVS Losses


 
 
- Little-Box 1.0 Experiments Indicated *Residual ZVS Losses* of GaN Power Transistors
- Losses Cannot be Explained by Remaining i_D, u_{DS} Overlap / Non-Ideal Gate Drive



- Potentially Large Measurement Error for Electrical Double-Pulse Sw. Loss Measurement
- Accuracy only Guaranteed by *Direct Loss Measurement* → *Calorimetric Approach*

Calorimetric Measurement of ZVS Losses

 
 
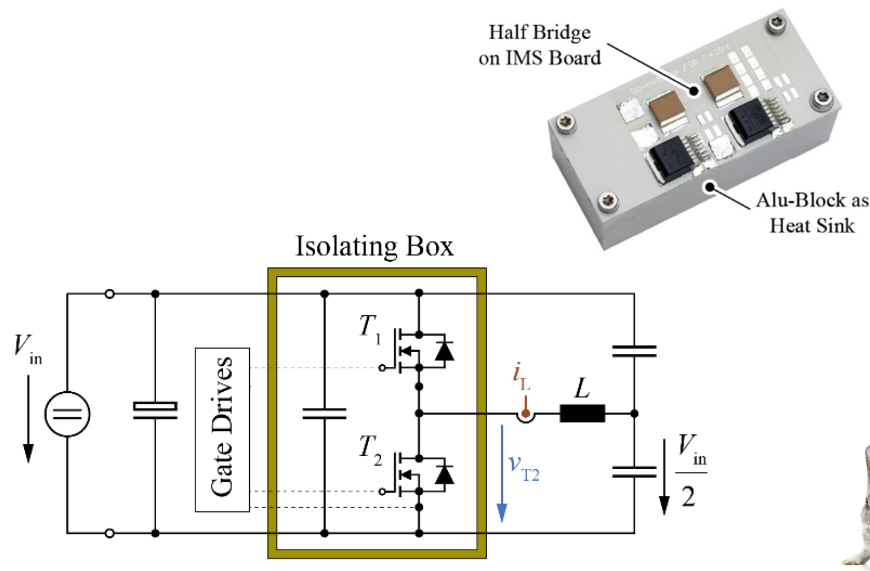
- "Inductor in the Box" → Accurate DC Inp. & Outp. Power Measurement, Subtr. of Ind. Losses
- "Bridge Leg in the Box" → Direct Measurement of the Sum of Cond. & Sw. Losses



- "Bridge Leg in the Box" & Fast Measurement by $C_{th} \cdot \Delta T / \Delta t$ Evaluation
- DC/DC Operation @ High Sw. Frequency for Large Ratio of Sw. and Conduction Losses
- Subtraction of the Cond. Losses from Datasheet or Dir. Measurement

Calorimetric Measurement of ZVS Losses

 
 
 
- “Bridge Leg in the Box” & Fast Measurement by $C_{th} \cdot \Delta T / \Delta t$ Evaluation
- Subtraction of the Cond. Losses from Datasheet or Direct Measurement
- DC/DC Operation @ High Sw. Frequency for Large Ratio of Sw. and Conduction Losses



- Isolated Temp. Measurement with Optical Fiber (GaAs Crystal) Instead of Thermocouple
- Calibration by On-State of T_1 and T_2 & DC Current Operation / DC Power Loss Measurement

Calibration of "Bridge Leg in the Box" Setup

  
 
- Calibration by On-State of T_1 and T_2 & DC Current Operation / DC Power Loss Measurement
- Identification of Thermal Cap. C_{th} and Thermal Resistance R_{th}



- DC Power Loss Measurement Ensures High Accuracy
- Thermal Behavior for Short Measurement Times Mainly Determined by C_{th}

Accurate On-State Voltage Measurement

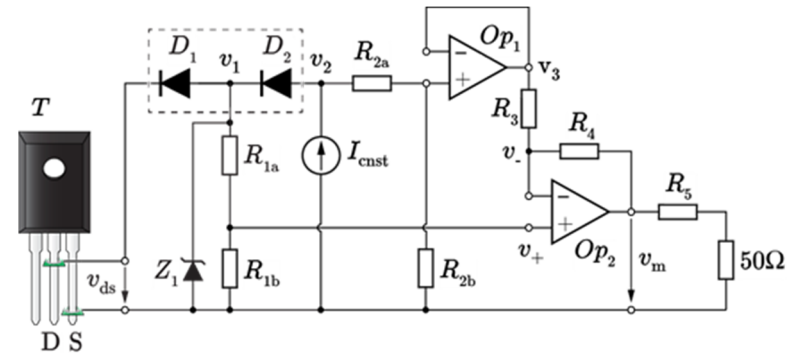
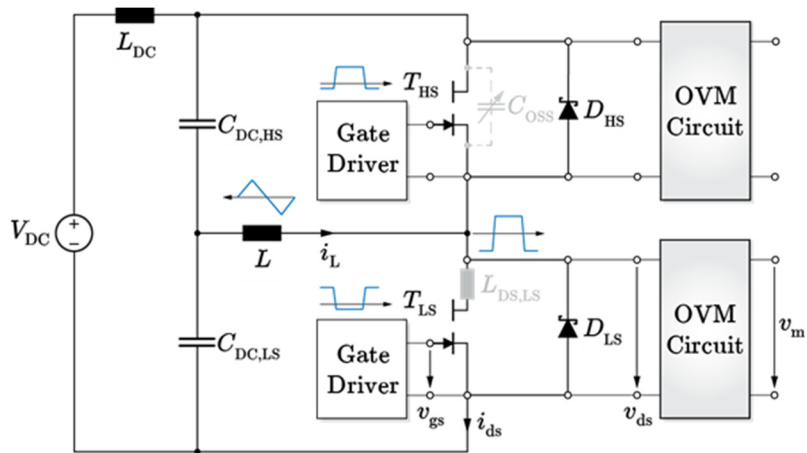
- Clamping Diode for Limiting the On-State Voltage Measurement (OVM) Range to a Few Volts
- Subtraction of the SiC Diode Forward Voltage Drop for High Accuracy (2mV)



- Only 50ns Blanking Time – OVM Circuit Can also be Used for Dynamic $R_{DS,on}$ Measurement

Accurate On-State Voltage Measurement


 
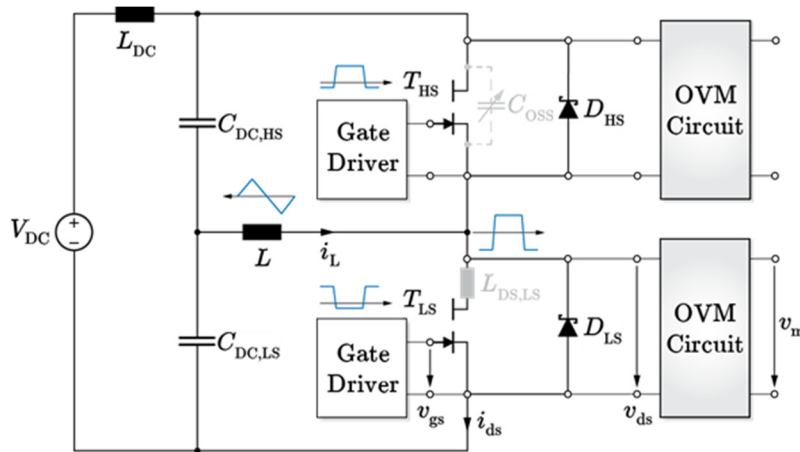
- Clamping Diode for Limiting the On-State Voltage Measurement (OVM) to 2V
- Subtraction of the SiC Diode Forward Voltage Drop for High Accuracy (2mV)



- Only 50ns Blanking Time – OVM Circuit Can also be Used for Dynamic $R_{DS,on}$ Measurement

ZVS Loss Measurement Results (1)

  
 
- Measurement of Energy Loss per Switch and Switching Period
- GaN Enhancement Mode Power Transistor (600V, 70mΩ@25°C)
- Antiparallel CREE SiC Schottky Freewheeling Diode (600V, 3.3A)



- Switching w/ and w/o 100pF Parallel Low-Loss SMD Multilayer Ceramic Chip Capacitor (450V)
- dv/dt Measured in 10%...90% of Turn-off Voltage, Behavior @ at Low dv/dt Still to be Clarified

ZVS Loss Measurement Results (2)

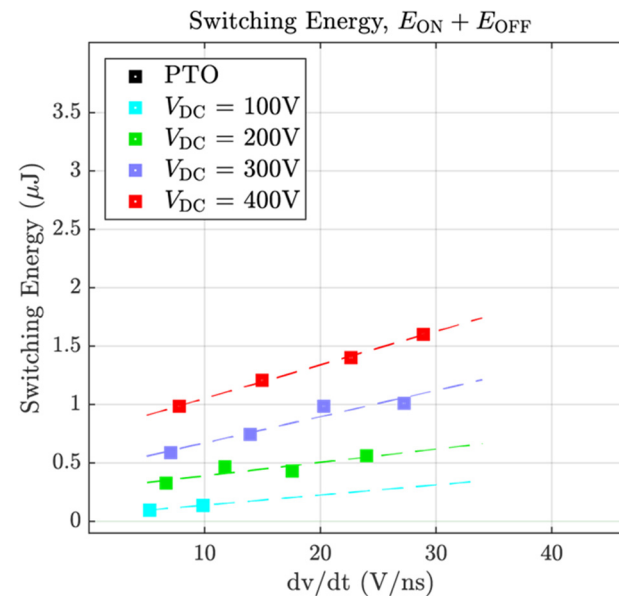
 
- Analysis of a *Permanently-Off Half-Bridge Excited with Switch Node Voltage*
- Measurement of Energy Loss per Switch and Switching Period



- Heating Indicates Losses in the Permanently-Off Devices
- Losses Comparable to the Losses of the Switching Half Bridge for Same dv/dt


ZVS Loss Measurement Results (2)

  - Analysis of a *Permanently-Off Half-Bridge Excited with Switch Node Voltage*
- Measurement of Energy Loss per Switch and Switching Period






- Heating Indicates Losses in the Permanently-Off Devices
- Losses Comparable to the Losses of the Switching Half Bridge for Same dv/dt

 Measurement of Ferrite Multi-Airgap Core "Mystery" Losses



Multi-Airgap Inductor

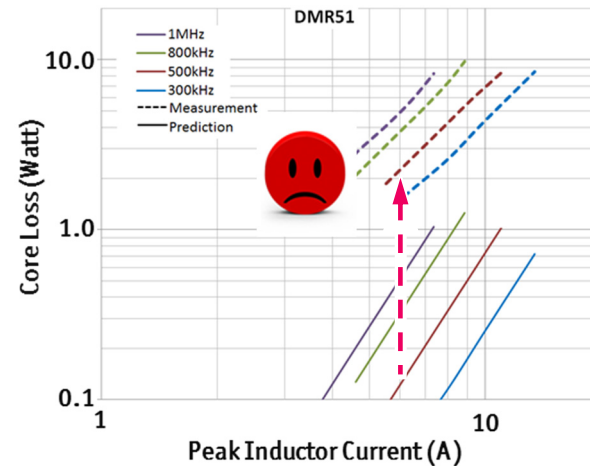  - Ferrite E-Core with *50 x 0.3mm Thick Stacked Plates* as Center Post
- Power Loss of TCM Inductors Sign. Higher than Expected




- Analysis by Fraunhofer IZM Shows Up to Factor 10 High Core Losses (!) → “Mystery” Losses




- Machining Increases Core Losses

 
- 1964 - E. Stern & D. Temme → Machining / Compressive Stress Changes BH-Loop of NiZn Ferrite



 - 1974 - J. Knowles, E. Snelling → Compressive Stress Incr. Loss Fact., Reduces μ_r



 
- 1984 - E. Kloholm & H. Wolfe → 40 μm Magn. Dead Surface Layer of MnZn Ferrite



- 1987 - S. Chandrasekar et al. → Lapping Causes Greater Residual Stress than Grinding



Ferrite Machining Process

 - Cutting of Thin Plates from Ferrite Rod with Diamond Saw
- Abrasive Machining Introduces Mech. Stress into Surface




SEM Image of Machined MnZn Ferrite (3F4)

laboratory for
lmm
nanometallurgy

  

 - Ferrite Properties in Surface Altered → Increase of Loss Factor





Subsurface Condition of Machined Ferrite



Materials Science and Technology

  
- Focused Ion Beam (FIB) Cut into Ferrite (3F4) Sample & Scanning Electron Microscopy (SEM)
- Polishing of Surface with Grain Sizes 2400 SiC → 4000 SiC → Colloidal Silica SiO₂



- Polishing Removes 500µm of Surface → Bulk Material Exposed
- Bulk Ferrite also Exhibits Cavities → Result of (Imperfect) Sintering Process

Thermometric Surface Loss Measurement



 
- Impression of Homogeneous Sin. Flux Density of Desired Ampl. / Frequ.
- Cap. Series Comp. for Lowering Impedance @ High Frequencies
- Measurement of *Transient Temp. Change* → *Calcul. of Losses*



■ Temperature Rise of $\Delta T = 1.5^{\circ} \dots 5^{\circ}\text{C}$ Sufficient (Accuracy $\pm 0.2^{\circ}\text{C}$), Fast Measurement (!)

Test Fixture / Magnetic Circuit

 
 
 
- **E-Type Fixture** for Swift Installation of Diff. Samples (7mm x 6.4mm x 21.6mm)
- **FEM Optimiz. of Dimensions** – Large Core Cross Section / Tapered Outer Limbs



- **Therm. Insul. & Airgap Lattice Ensure Low Heat Flux to Ambient**
- **Measurement of Temp. Increase Over Time Allows to Verify Homog. Flux Density in Sample**

Identification of Therm. Parameters R_{th} , C_{th}

  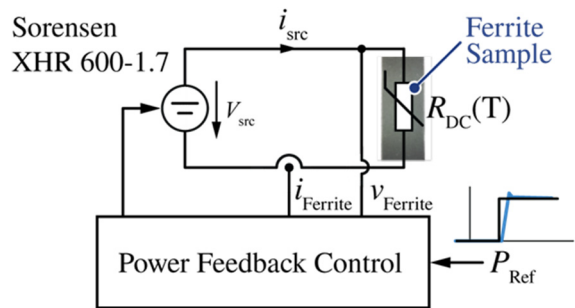- DC Current Impressed in Ferrite, Voltage Control for Const. Power Dissipation as $R_{DC}=R_{DC}(Temp.)$
- Temperature Response of Sample Recorded (FLIR A655sc W with Close-Up Lens)
- Emissivity of Ferrite Determined Using Ferrite on Heating Plate ($\epsilon=0.86$)





- $R_{th} = 37.8 \text{ K/W}$ Can be Neglected
- Obtained Parameter $C_{th}=3.83\text{J/K}$ Close to C_{th} Calc. Based on Vendor Data ($C_{th} = 3.6\text{J/K}$)

Surface Loss Measurement Principle



  
- Hypothesis: Core Loss Density in Surface Layer Higher than in Bulk
- Thinner Plates → Higher Average Losses / Faster Temp. Rise
- Stacking of Plates Does NOT Affect Temperature Rise (!)




- Surface Loss Density Can be Directly Calc. from Mat. Parameters / Geometry & Δt_A and Δt_B

Temperature Rise Recording

 
- Comparison of Solid 3F4 Sample (1 x 21.6mm) and Stacked Plates Sample (7 x 3mm)
- Sinusoidal Excitation *100mT / 400kHz*



3F4 Solid Sample / 21.6mm

 


7 Plates 3F4 / 3mm

 

- Thermal Image shown *25 Seconds After Turn-On* of Magnetic Excitation

Measurement Results – Bulk Losses

 - Comparison of Measurement Results and Datasheet Values, 3F4 @ 25°C
- Measurement Error Approx. $\pm 10\%$ (Worst Case)



- Good Agreement with Datasheet Values / Vendor Steinmetz Parameters





Measurement Results – Surface Losses

- Measurement Error Approx. $\pm 25\%$ (Worst Case)
- Error Determined by Meas. Time & Temp. Reading Accuracy



  
$$p_{Surf} = 0.0615 \times \left(\frac{f}{1\text{Hz}}\right)^{1.13} \times \left(\frac{\hat{B}}{1\text{T}}\right)^{3.47} \left(\frac{\text{mW}}{\text{cm}^2}\right)$$





- Comp. of Steinmetz Parameters of Surface Losses & Bulk Losses $\beta_s > \beta, \alpha_s < \alpha$

“Critical Thickness” of Ferrite Plates

 - “Critical Thickness” Reached for **Equal Losses in Bulk & Surface**
- Critical Plate Thickness is **INDEPENDENT** of Cross Section (!)



  3F4 Critical Thickness for 125mT / 400kHz




- Dependence on Flux Density Ampl. & Frequency !
- Dependence on Material / Machining Process / Power Processing Treatment

Optimization of Little-Box 1.0

η -Pareto Front
TCM vs. Large Ripple PMW
The Ideal Switch is Not Enough (!)
Design Space Diversity

Multi-Objective Optimization

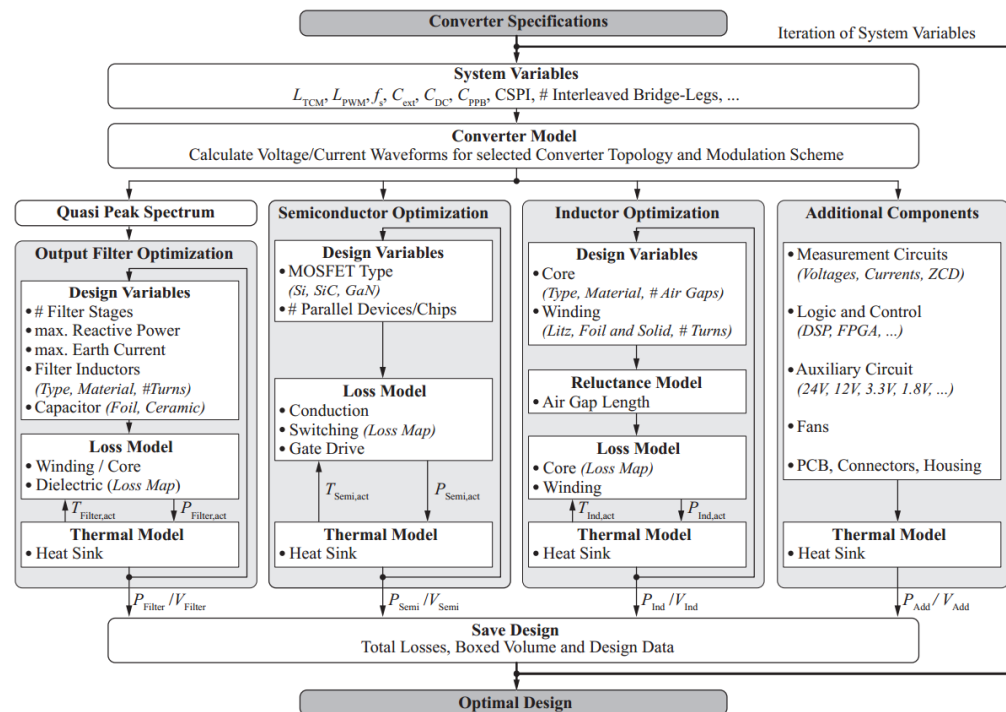
- Detailed System Models → Power Buffer/Output Stage/EMI Filter
- Multi-Domain Component Models → Passives & GaN & SiC Semicond.
- Consideration of Very Large # of Degrees of Freedom



■ Pareto Optimization Shows Trade-Off Between Power Density and Efficiency

Little Box 1.0 η -Performance Limits

 - Multi-Objective Optimization of Little-Box 1.0 (incl. CeraLink™ → X6S)
- Absolute Performance Limits (I) - DSP/FPGA Power Consumption
(II) - Heatsink Volume @ (1- η)




(a) ★ Realized Prototype

(b) CeraLink™ Power Pulsation Buffer
(c) X6S Power Pulsation Buffer

- Further Performance Improvement for Triangular Current Mode (TCM) → PWM

Little Box 1.0 -- Electrolytic Cap. / Active PPB

 
- Analysis for Google Little Box Challenge Specification $\Delta V/V < 3\%$
- Efficiency Benefit of PPB only for $\rho > 9\text{kW/dm}^3$




- Electrol. Cap. Favorable for High Efficiency @ Moderate Power Density ($\Delta\eta = +0.5\%$)
- Electrol. Cap. Show Lower Vol. & Lower Losses if Large $\Delta V/V$ is Acceptable (e.g. for PFC Rectifiers)

Little Box 1.0 -- TCM → PWM

 - Very High Sw. Frequency f_s of TCM Around Current Zero Crossings
- Efficiency Reduction due to Residual TCM Sw. Losses & Gate Drive Losses Reduction
- Wide f_s -Variation Represents Adv. & Disadvantage for EMI Filter Design



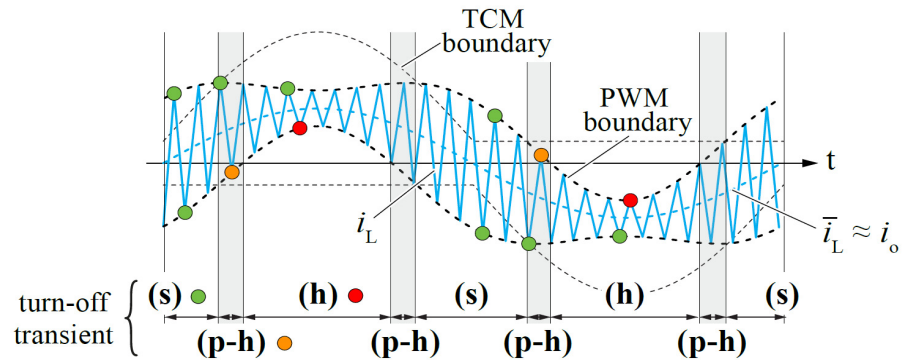(s) Soft-Switching (ZVS)
 (p-h) Partial Hard Switching
 (h) Hard-Switching






- PWM -- Const. Sw. Frequency & Lower Conduction Losses
- PWM @ Large Current Rippel -- ZVS in Wide Intervals




Little Box 1.0 -- TCM → PWM

   - Optimization for GaN GIT & No Interleaving
- Resulting Opt. Inductance of Output Inductor $L=10\mu\text{H}$ (TCM), $L=30\mu\text{H}$ (PWM@140 kHz)



 $\rho = 11.9\text{kW}/\text{dm}^3$
 $\eta = 97.4\%$



$\rho = 12.5\text{kW}/\text{dm}^3$
 $\eta = 97.4\%$



- PWM vs. TCM → Slightly Higher Max. Power Density @ Same Efficiency

The Ideal Switch is
Not Enough (!) →



Little Box 1.0 @ Ideal Switches -- TCM

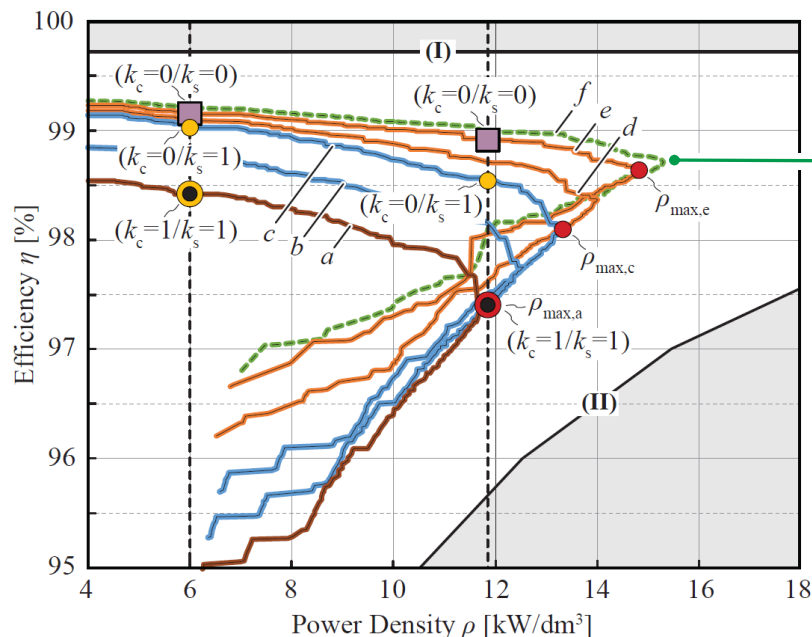 - Multi-Objective Optimization of Little-Box 1.0 (X6S Power Pulsation Buffer)
- Step-by-Step Idealization of the Power Transistors
- Ideal Switches: $k_c = 0$ (Zero Cond. Losses); $k_s = 0$ (Zero Sw. Losses)





Zero Output Cap. and Zero Gate Drive Losses

- Analysis of Improvement of Efficiency @ Given Power Density & Maximum Power Density



Little Box 1.0 @ Ideal Switches -- PWM

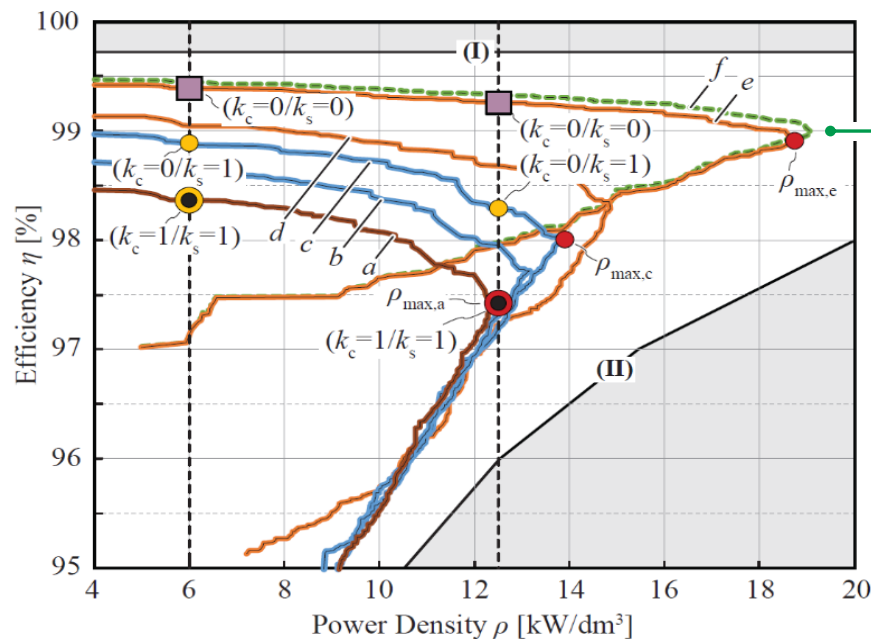 - Multi-Objective Optimization of Little-Box 1.0 (X6S Power Pulsation Buffer)
- Step-by-Step Idealization of the Power Transistors
- Ideal Switches: $k_c=0$ (Zero Cond. Losses); $k_s=0$ (Zero Sw. Losses)







Zero Output Cap. and Zero Gate Drive Losses

- Analysis of Improvement of Efficiency @ Given Power Density & Maximum Power Density



Little Box 1.0 @ Ideal Switches -- PWM

    


$\rho = 6 \text{ kW/dm}^3$
 $\eta \approx 99.35\%$

$L = 50 \mu\text{H}$
 $f_s = 500 \text{ kHz or } 900 \text{ kHz}$

- L & f_s are Independent Variables (Dependent for TCM)
- Large Design Space Diversity (Mutual Compensation of HF and LF Loss Contributions)

Little Box 2.0

 


250 W/in³


DC/ | AC | Converter + Unfolder
PWM vs. TCM incl. Interleaving
 η -Pareto Limits for Non-Ideal Switches
3D-CAD Construction
Exp. Results

Little Box 2.0 -- New Converter Topology (1)

- **Alternative Converter Topology** → Only Single High Freq. Bridge Leg + 60Hz-Unfolder
- **HF Half-Bridge & Half-Bridge Unfolder DC/ | AC |** OR **Buck Converter + Full-Bridge Unfolder**

 


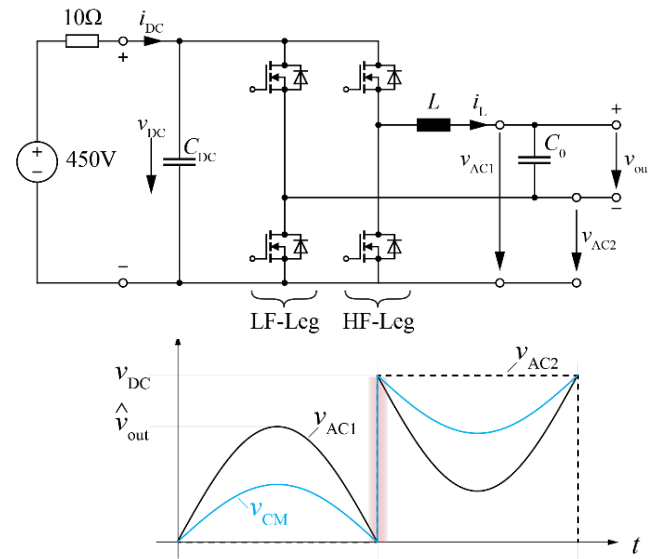
- v_{AC1}, v_{AC2} More Diff. to Gen. but Add. DOF
- Higher Sw. Losses & Gate Drive Losses
- Zero Low-Freq. CM-Noise (DC Comp. Only)
- C_{CM} Not Limited by Allowed Gnd Current





- v_{AC1} More Difficult to Generate/Control
- Lower Sw. Losses & Gate Drive Losses
- Higher CM-Noise (DC and $n \times 120\text{Hz}$ -Comp.)
- $C_{CM}=150\text{nF}$ Allowed for 50mA Gnd Current

Little Box 2.0 -- New Converter Topology (2)

- **Alternative Converter Topology** → Only Single High Freq. Bridge Leg + 60Hz-Unfolder
- **HF Half-Bridge & Half-Bridge Unfolder DC/ | AC |** OR **Buck Converter + Full-Bridge Unfolder**

 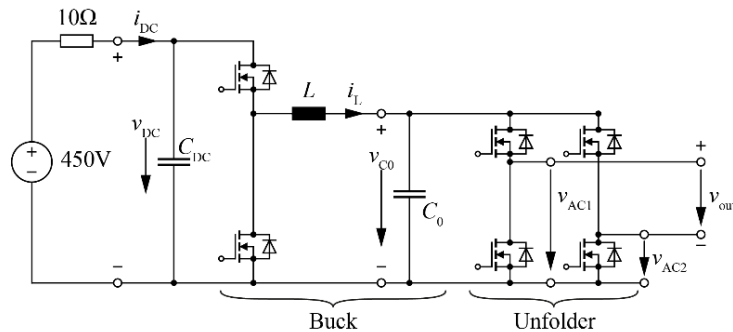

  
- v_{C0} Easy to Generate/Control
- Higher Cond. Losses Due to FB-Unfolder
- Lower CM-Noise (DC & $n \times 120\text{Hz-Comp.}$)
- $C_{CM}=700\text{nF}$ Allowed for 50mA Gnd Current



- v_{AC1} More Difficult to Generate/Control
- Lower Sw. Losses & Gate Drive Losses
- Higher CM-Noise (DC and $n \times 120\text{Hz-Comp.}$)
- $C_{CM}=150\text{nF}$ Allowed for 50mA Gnd Current

Little Box 2.0 -- New Converter Topology (3)

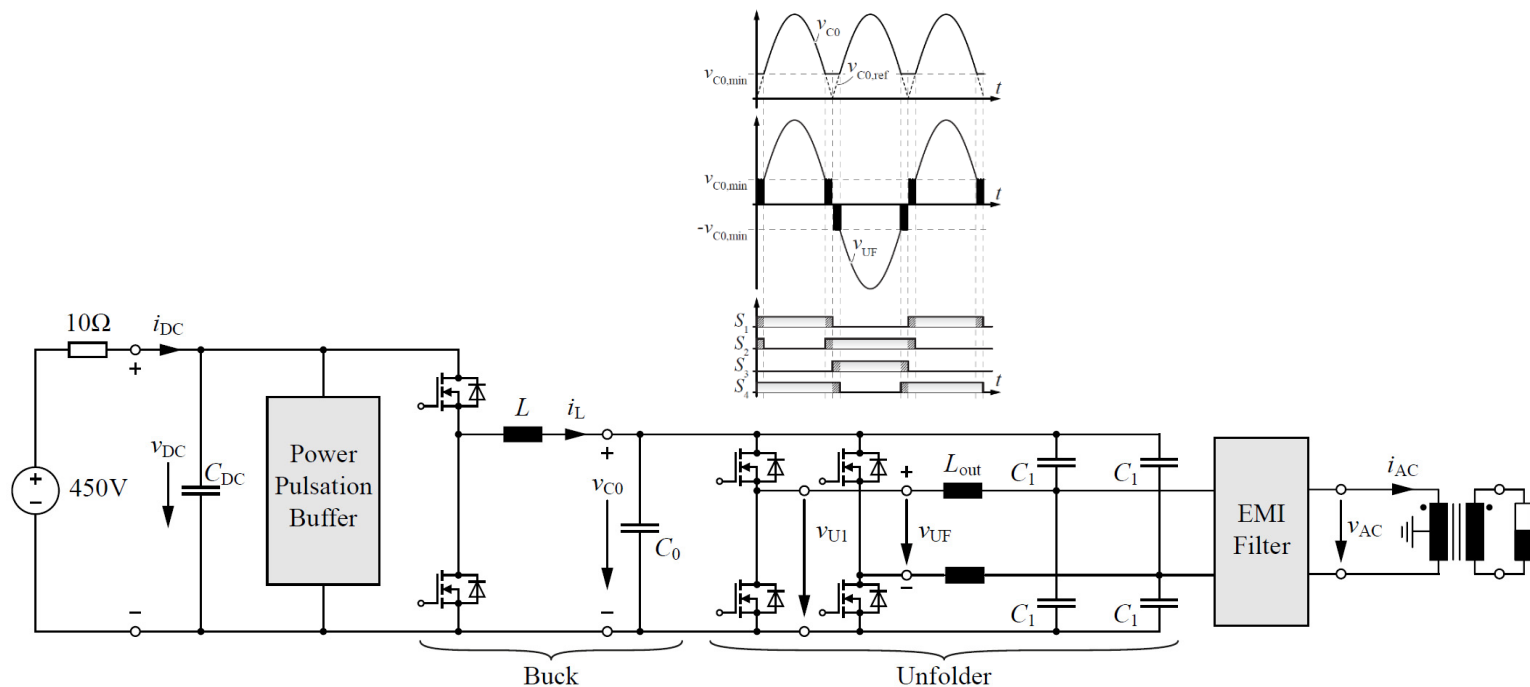
- **Alternative Converter Topology - DC/AC - Buck Converter + Unfolder**
- **60Hz-Unfolder (Temporary PWM for Ensuring Cont. Current Control)**
- **TCM or PWM of DC/AC - Buck-Converter**



- **Full Optimization** of All Converter Options for **Real Switches** / X6S Power Pulsation Buffer

Little Box 2.0 -- Multi-Objective Optimization

 - DC/AC - Buck Converter (Single PWM Bridge Leg) + Unfolder Shows Best Performance
- Full-Bridge Would Employ 2 Switching Bridge Legs - Larger Volume & Losses
- Interleaving Not Advantageous - Lower Heatsink Vol. / Larger Vol. of Switches and Inductors



■ $\rho = 250\text{W/in}^3$ (15kW/dm^3) @ $\eta = 98\%$ Efficiency Achievable for Full Optimization


*3D-CAD Construction
of the Final System*



250 W/in³



 
Little Box 2.0 -- Mechanical Construction (1)



- 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)



 
Little Box 2.0 -- Mechanical Construction (2)



- $60 \text{ mm} \times 50 \text{ mm} \times 45 \text{ mm} = 135 \text{ cm}^3 \text{ (8.2in}^3 \text{)} \rightarrow 14.8 \text{ kW/dm}^3 \text{ (243 W/in}^3 \text{)}$




 Little Box 2.0 -- Mechanical Construction (3)




■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)

 Little Box 2.0 -- Mechanical Construction (4)



■ $60 \text{ mm} \times 50 \text{ mm} \times 45 \text{ mm} = 135 \text{ cm}^3 (8.2 \text{ in}^3) \rightarrow 14.8 \text{ kW/dm}^3 (243 \text{ W/in}^3)$

 Little Box 2.0 -- Mechanical Construction (5)



■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)






Little Box 2.0 -- Demonstrator

★ 240 W/in³

Output Filter

Inductors
(Buck-Stage &
Unfolder)

Power Board
Control Board

 

PPB Capacitor

Heat Sink + Fans

■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)




Little Box 2.0 -- Demonstrator

★ 240 W/in³

PPB Capacitor

Heat Sink + Fans

 

PPB Capacitor

Inductors
(Buck-Stage &
Unfolder)

Power Board


Control Board

■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)

Experimental Results

Control Block Diagram
Output Voltage / Input Current Quality
Efficiency

Little Box 2.0 – Control Structure


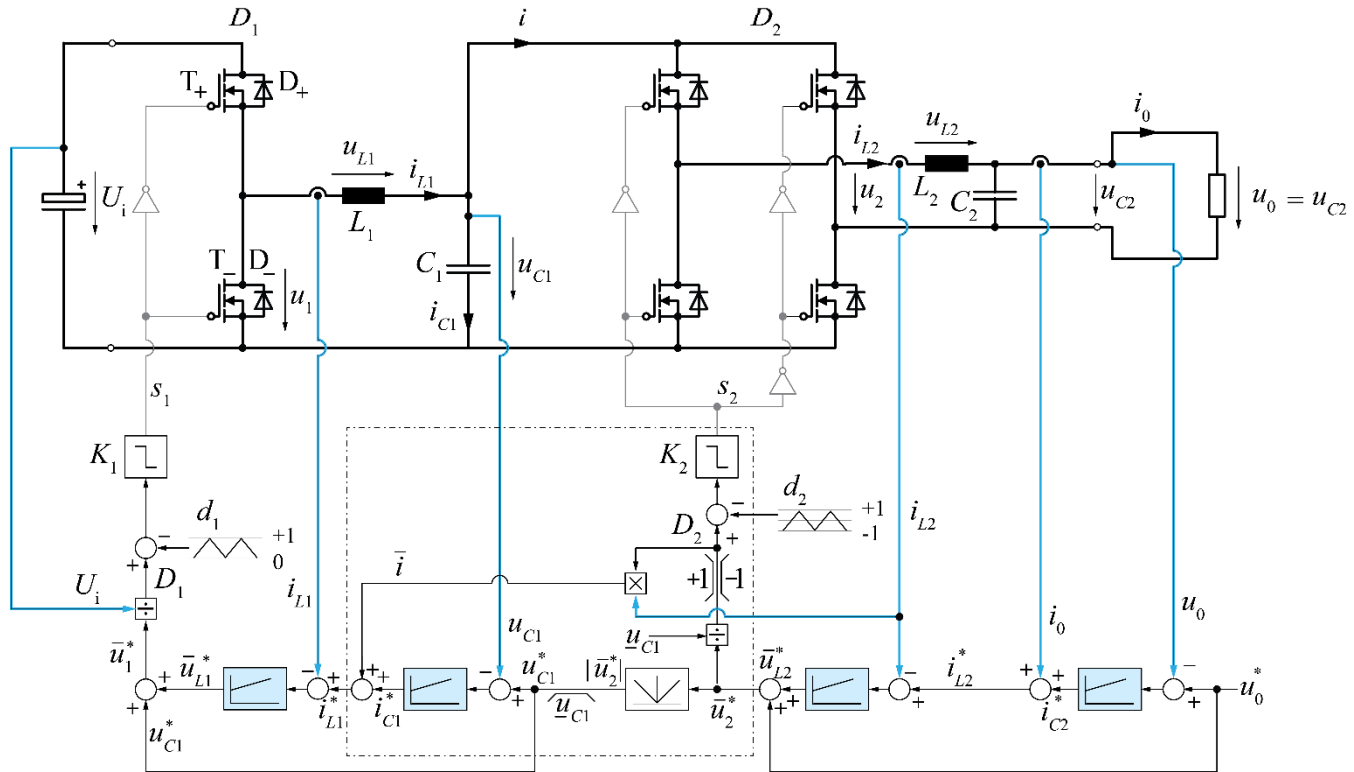


- Each Stage (Buck & Unfolder) Controlled with Cascaded Current and Voltage Loop
- Without Switching of Unfolder Control Like for Conventional Boost PFC Rectifier



Little Box 2.0 – Experimental Results (1)

  - **Voltage Zero Crossing Behavior - With (Right) & Without (Left) Switching of Unfolder**




Output Voltage (200V/div)
Output Current (10A/div)
Buck Inductor Current (10A/div)
Unfolder Output Voltage (200V/div)


- **Output Voltage & Current Fully Controlled Around Voltage Zero Crossings**
- **Slope of Buck Conv. Outp. Curr. can be Decreased – Adv. for React. Loads (No Step-Change of DC Curr.)**

Little Box 2.0 – Experimental Results (2)


- DC/|AC| Buck-Stage Output Voltage & Inductor Current

 

■ Resistive Load

 


■ Inductive Load

 

■ Capacitive Load

Little Box 2.0 – Experimental Results (3)

- Performance of First DC/ | AC | - Buck Converter + Unfolder Prototype
- PWM Operation
- Without Power Pulsation Buffer

 


- 98% for Res. Load Achievable if Cond. Losses of PCB (Copper Cross Sect.) & Unfolder ($R_{ds,on}$) are Red.



Litte Box 2.0 – Performance Comparison


- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

Note: Numbering of Teams is Arbitrary

 

- (1) Virginia Tech
- (2) Schneider Electric
- (3) EPRI (Univ. of Tennessee)
- (4) Venderbosch
- (5) Energy Layer
- (6) ETH Zurich
- (7) Rompower
- (8) Tommasi-Bailly
- (9) Red Electric Devils
- (10) AHED
- (11) FH IISB
- (12) Univ. of Illinois
- (13) AMR

- 70...300 W/in³
- 35 kHz...500kHz...1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC|Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps or Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)

 

Source: whiskeybehavior.info

**Overall
Summary**



Performance Limits / Future Requirements

- 220...250W/in³ for Two-Level Bridge Leg + Unfolder
- 250...300W/in³ for Highly Integrated Multi-Level Approach
- Isol. Distance Requirements Difficult to Fulfill
- Fulfilling Industrial Inp. Overvoltage Requirem. would Signific. Reduce Power Density

- Low Frequency (20kHz...120kHz) SiC vs. HF (200kHz...1.2MHz) GaN
- Multi-Cell Concepts for LV Si (or GaN) vs. Two-Level SiC (or GaN)

- New Integr. Control Circuits and $i=0$ Detection for Sw. Frequency >1MHz
- Integrated Gate Drivers & Switching Cells
- High Frequency Low Loss Magnetic Materials
- High Bandwidth Low-Volume Current Sensors
- Low Loss Ceramic Capacitors Tolerating Large AC Ripple
- Passives w. Integr. Heat Management and Sensors
- 3D Packaging

- New U-I-Probes Required for Ultra-Compact Conv. R&D
- Specific Systems for Testing → Devices Equipped with Integr. Measurement Functions
- Convergence of Sim. & Measur. Tools → Next Gen. Oscilloscope
- New Multi-Obj. Multi-Domain Simulation/Optim. Tools

Thank You!

Questions






Future Development 1/2

- Commoditization / Standardization
- Extreme Cost Pressure (!)

“There is Plenty of Room at the Top”

 → Medium Voltage/Frequency Solid-State Transformers




Power-Supplies on Chip ← “There is Plenty of Room at the Bottom”

► Key Importance of Technology Partnerships of Academia & Industry


Future Development 2/2

■ Extrapolation of Technology S-Curve

 


Technology Progress – *Technology Push*

 - **WBG Semiconductor Technology** → Higher Efficiency, Lower Complexity
- **Microelectronics** → More Computing Power



→ + Advanced Packaging (!)



 


→ Moore's Law

System / Smart Grid Drivers


Metcalfe's Law

   - Moving from Hub-Based Concept to Community Concept Increases Potential Network Value Exponentially ($\sim n(n-1)$ or $\sim n \log(n)$)







Technology Sensitivity Analysis Based on η - ρ -Pareto Front

 - ▶ Sensitivity to Technology Advancements
- ▶ Trade-off Analysis





Converter Performance Evaluation Based on η - ρ - σ -Pareto Surface

► σ : kW/\$

    

Converter Performance Evaluation Based on η - ρ - σ -Pareto Surface

► 'Technology Node'

  

Technology Node: $(\sigma^*, \eta^*, \rho^*, f_P^*)$

Future Development

“Devices”

- Minimize / Avoid Packages → (PCB) Embedding
- Integrate Driver Stage
- Integrate Sensors / Monitoring
- Multiple Use of Isolated Gate Drive Communication Channel
- Offer Test Devices with Integrated Measurement Function
- Facilitate (Double Sided) Heat Extraction

Converters

- Standardized Very Low Cost Building Blocks
- “Application Specific” = Wide Operating Range Standardized Blocks
- Self-Parametrization
- Bidirectional Converters

Systems

- AC and DC Distribution
- Single Converter vs. Combination of Modules / Cells
- Initial Costs / Life Cycle Cost Trade-off
- Grid 4.0

Design

- Minimize Design Time / Fully Computerized
- Maximize Design Flexibility for Appl. Specific Solution (PCB)
- Maximize Design Insight for Trade-off Analysis
- Design for Manufacturing (Planar / PCB Based)

Literature

- More & More “White Noise”