




# Advanced **SiC/GaN** 3- $\Phi$ PWM Inverter Systems for VSD Applications

**J.W. Kolar et al.**

Swiss Federal Institute of Technology (ETH) Zurich  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)

**April 15, 2019**

Source: SIEMENS

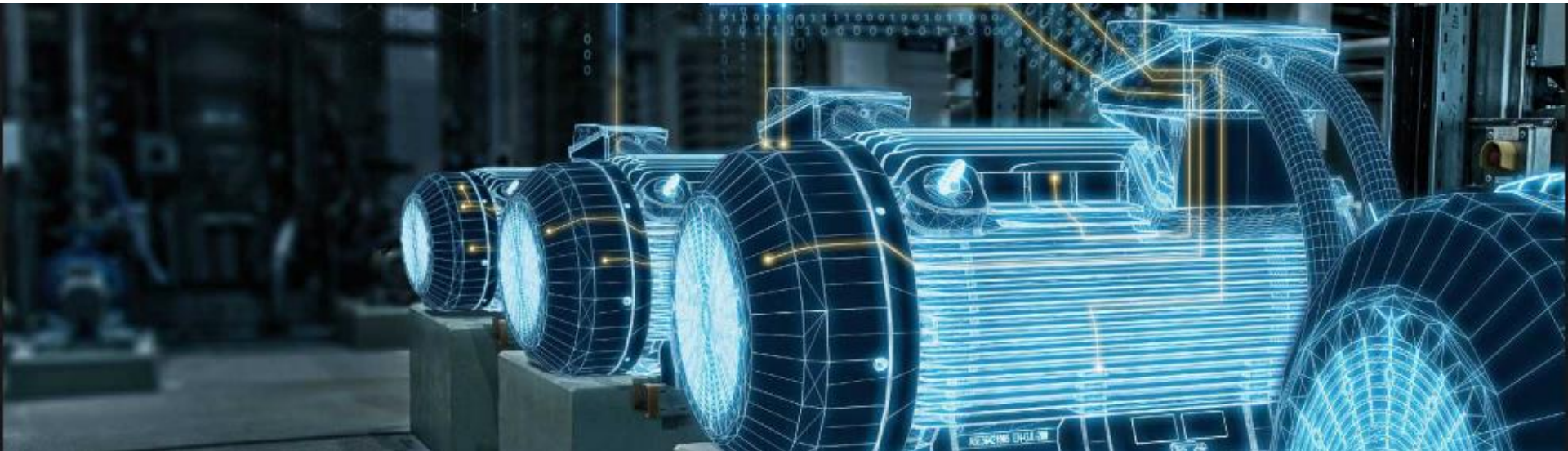




# Advanced **SiC/GaN** 3- $\Phi$ PWM Inverter Systems for VSD Applications

**J.W. Kolar, M. Guacci, M. Antivachis, D. Bortis**

Swiss Federal Institute of Technology (ETH) Zurich  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)

April 15, 2019

Source: SIEMENS

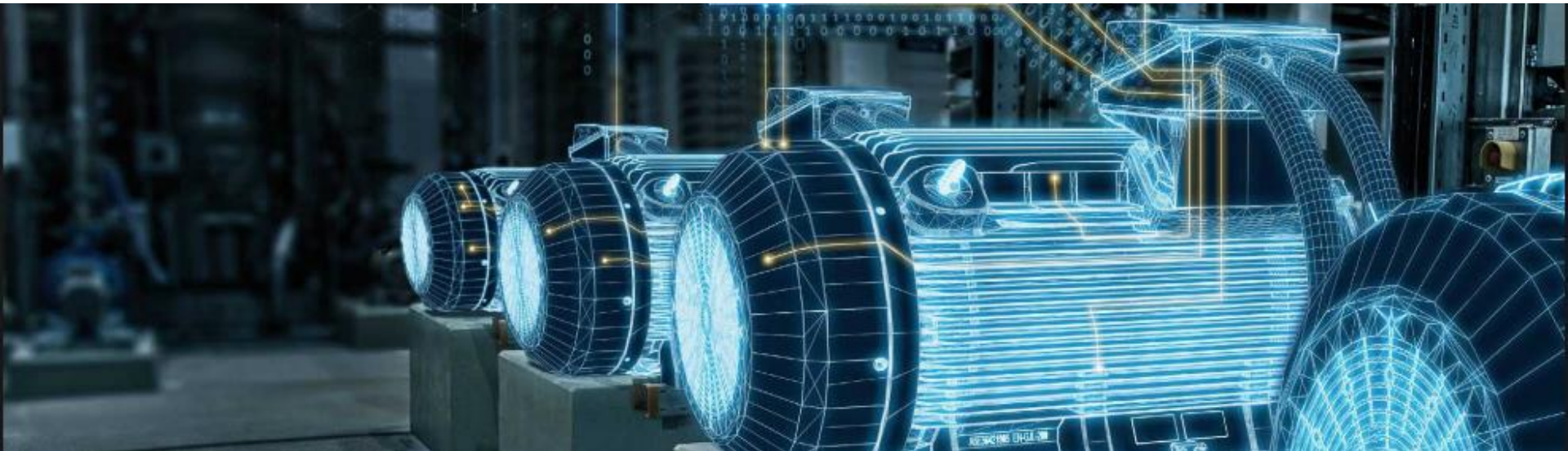

# ETH Zurich

21 Nobel Prizes  
509 Professors  
5800 T&R Staff

2 Campuses  
136 Labs  
35% Int. Students  
90 Nationalities  
36 Languages

150<sup>th</sup> Anniv. in 2005




## Departments

ARCH	Architecture
BAUG	Civil, Environmental and Geomatics Eng.
BIOL	Biology
BSSE	Biosystems
CHAB	Chemistry and Applied Biosciences
ERDW	Earth Sciences
GESS	Humanities, Social and Political Sciences
HEST	Health Sciences, Technology
INFK	Computer Science
<b>ITET</b>	<b>Information Technology and Electrical Eng.</b>
MATH	Mathematics
MATL	Materials Science
MAVT	Mechanical and Process Engineering
MTEC	Management, Technology and Economy
PHYS	Physics
USYS	Environmental Systems Sciences

## Students ETH in total


14'500 B.Sc.+M.Sc.-Students  
4'500 Doctoral Students

# ITET – Research in E-Energy

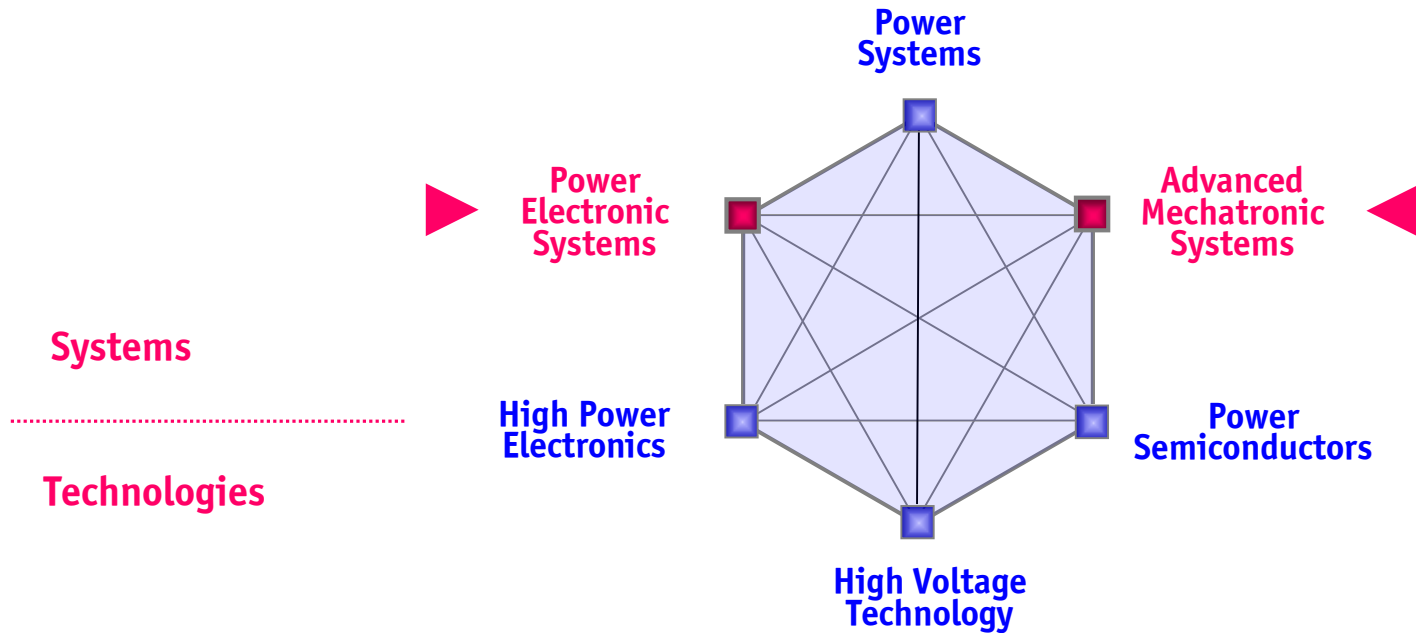

- ▶ Balance of Fundamental and Application Oriented Research

# Power Electronic Systems Laboratory

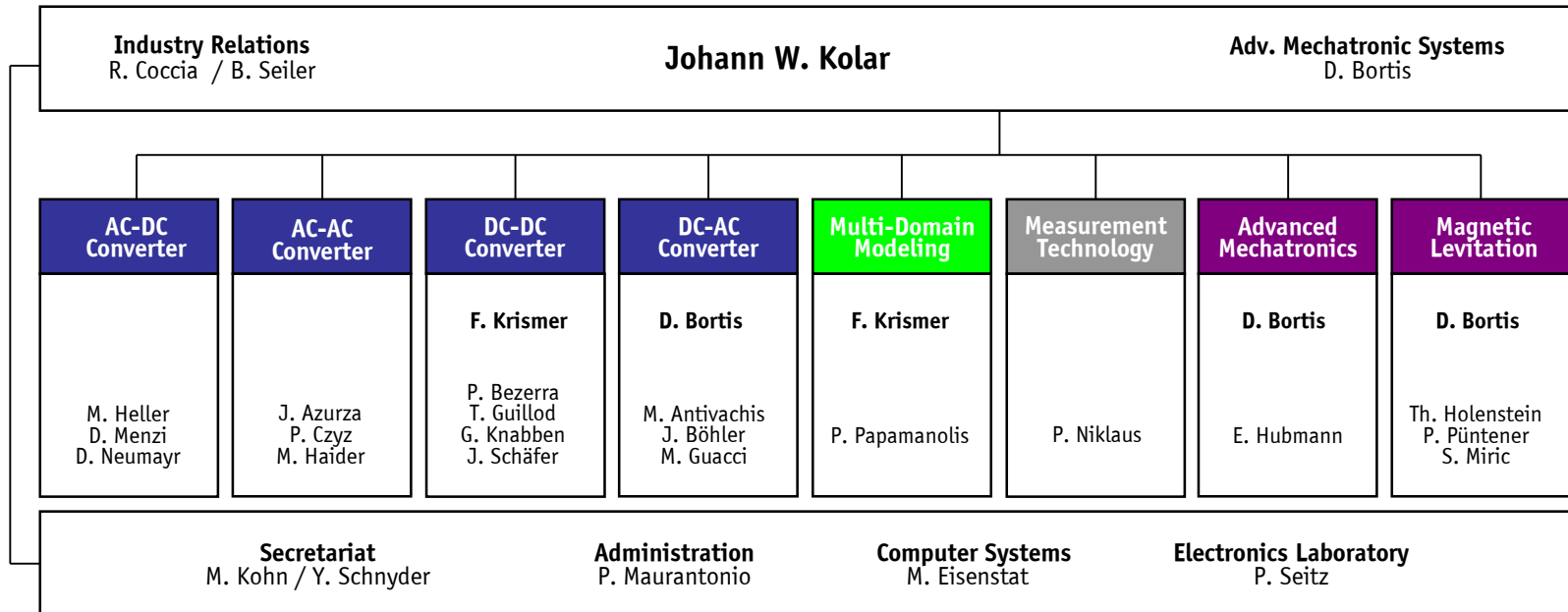

**19 Ph.D. Students**  
**2 Sen. Researchers**



**Leading Univ.  
in Europe**

# Outline

- ▶ *Introduction*
- ▶ *SiC/GaN Application Challenge*
- ▶ *Inverters with Output Filter*
- ▶ *Adv. Inverter Topologies*
- ▶ *Conclusions*

**40 MINUTES**



J. Azurza  
T. Guillod  
F. Krismer  
D. Menzi  
J. Miniböck  
P. Niklaus

Acknowledgement:

## *Introduction*

*State-of-the-Art  
Future Requirements*




## ► Applications of Drive Systems

- Industry Automation / Robotics
- Material Machining / Processing – Drilling, Milling, etc.
- Pumps / Fans / Compressors
- Transportation
- etc., etc.

.... Everywhere !

Source:  TESLA MOTORS

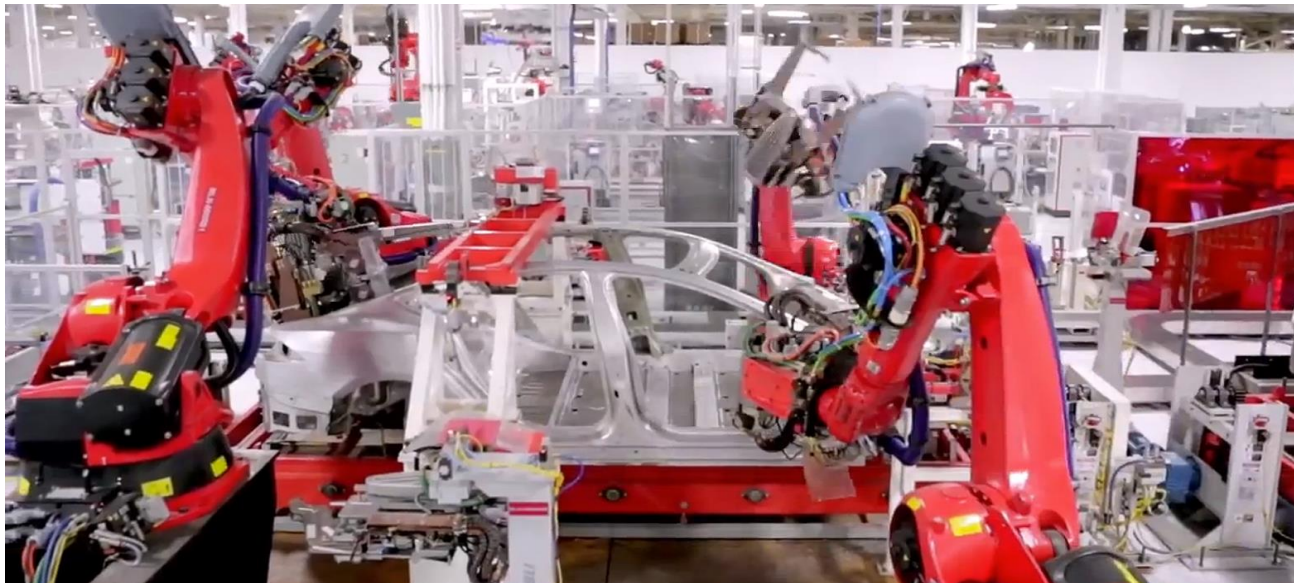


- 60% of El. Energy Used in Industry Consumed by VSDs



## ► State-of-the-Art

- **Mains Interface / 3- $\Phi$  PWM Inverter / Motor — Separated**
  - **Large Installation Space** / \$\$\$
  - **Complicated / Expert Installation** / \$\$\$
- **Conducted EMI / Radiated EMI / Bearing Currents / Reflections on Long Motor Cables**
  - **Shielded Motor Cables** / \$\$\$
  - **Inverter Output Filters (Add. Vol.)** / \$\$\$


Source: FLUKE

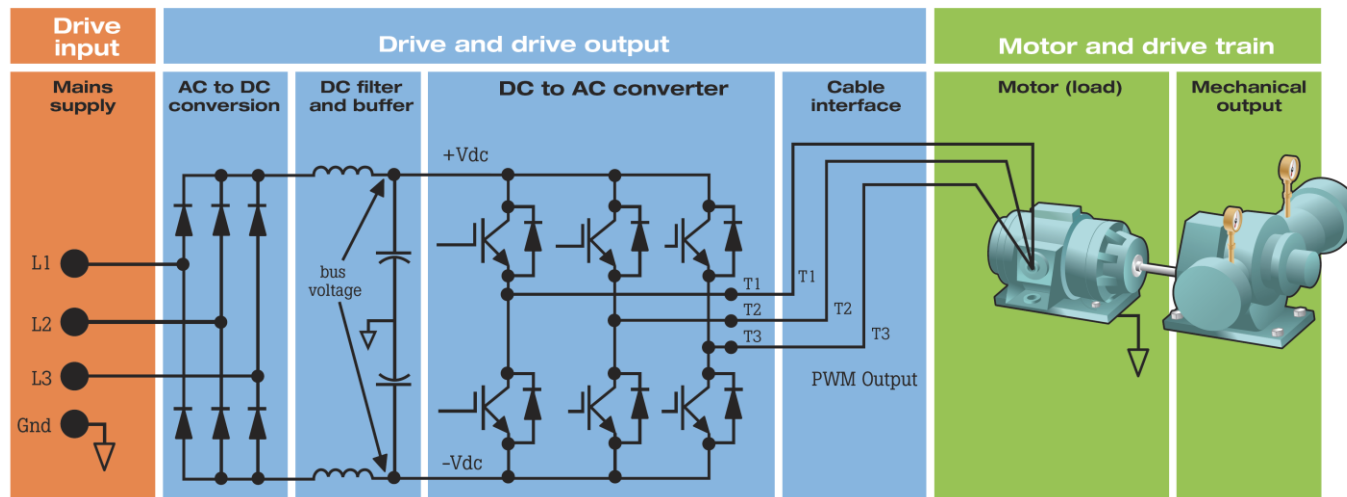



- **High Performance @ High Level of Complexity / High Costs (!)**
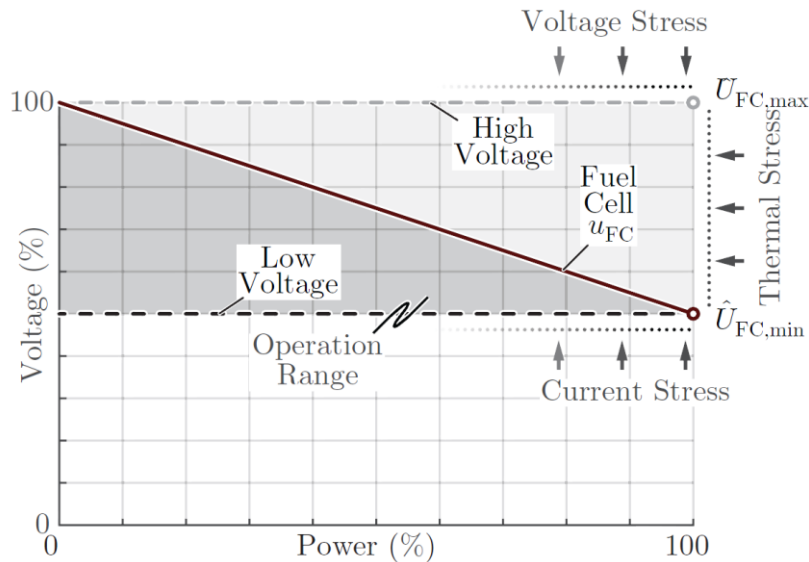
## ► Future Requirements (1)

- **“Non-Expert” Install. / Low-Cost Motors** → **“Sinus-Inverter”**
- **Wide Applicability / Wide Voltage & Speed Range** → **Matching of Supply & Motor Voltage**
- **High Availability**




Source: magazine.fev.com

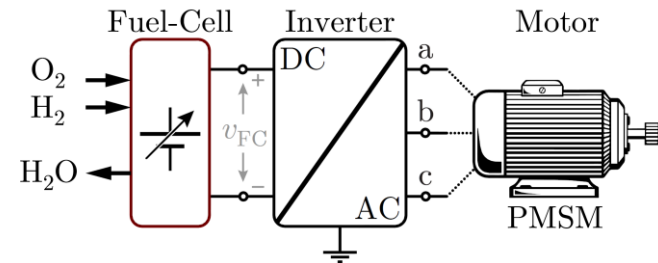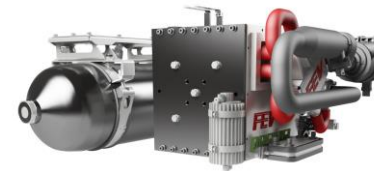

- **Single-Stage Energy Conversion** → **No Add. Converter for Voltage Adaption**
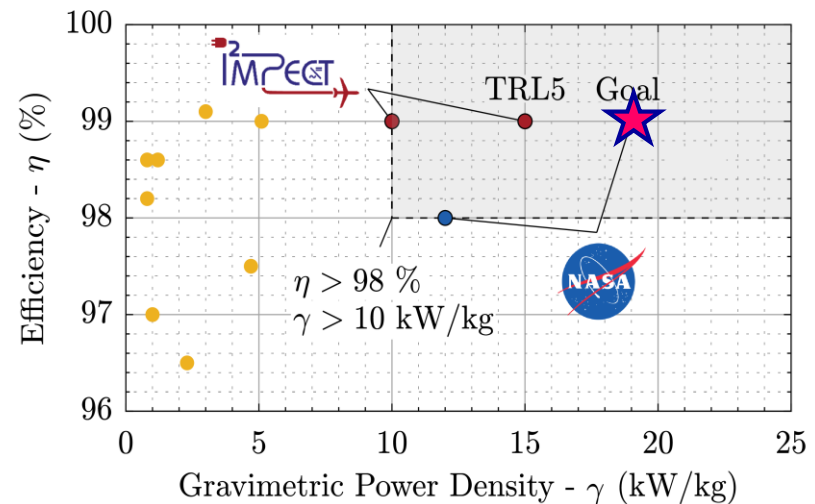
## ► Future Requirements (2)

- Red. Inverter Volume / Weight → Matching of Low High-Speed Motor Volume
- Lower Cooling Requirement → Low Inverter Losses & HF Motor Losses
- High Speed Machines → High Output Frequency Range



→ Main “Enablers” — SiC/GaN Power Semiconductors & Adv. Inverter Topologies


## *Enabling Technologies & Challenges*

*WBG Semiconductors  
Advanced Inverter Topologies*

## ► SiC/GaN

- **Very Low On-State Resistance** → **Low (Partial Load) Conduction Losses**
- **Very Low Switching Losses** → **High Switching Frequencies**
- **Small Chip Area** → **Compact Realization**

$$FOM = \frac{1}{R_{ds,on} Q_{oss}}$$


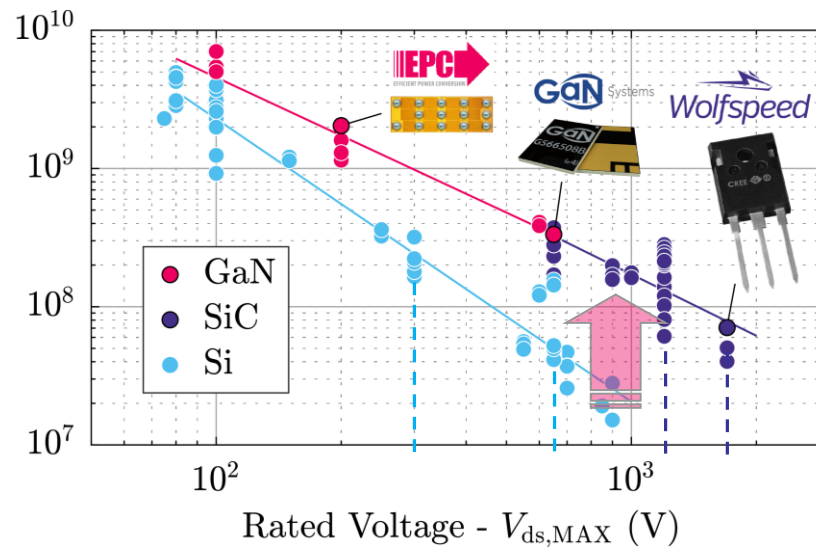


- **Challenges in Packaging / Thermal Management / Gate Drive / PCB Layout**
- **Extremely High Sw. Speed (dv/dt)** → **Motor Isol. Stress / Reflections / Bearing Curr. / EMI**

## ► Si vs. SiC

- **Si-IGBT** →  $dv/dt = 2...6 \text{ kV/us}$  (Inverter for Var. Speed Drives / IEC 61800-3)
- **SiC** →  $dv/dt = 20...60 \text{ kV/us}$

Source: M. Bakran / ECPE 2019

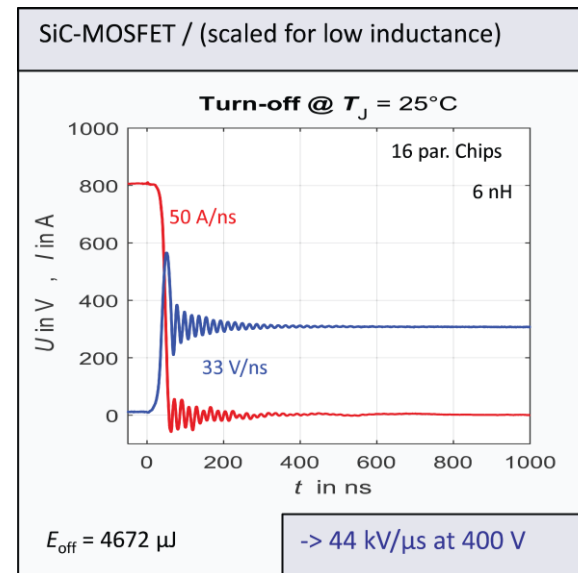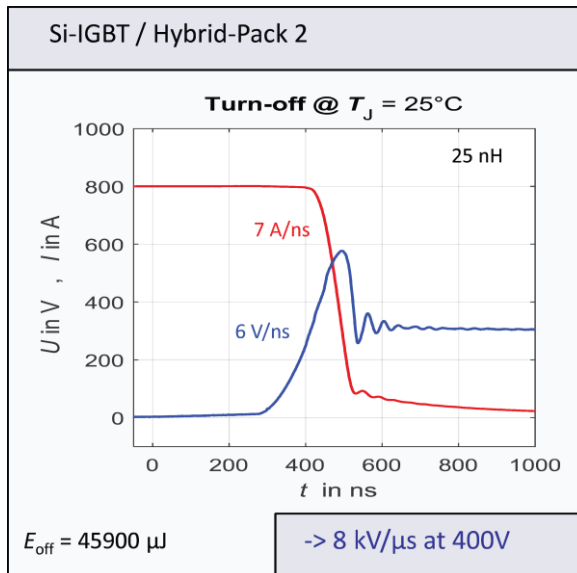


→ Extremely High  $dv/dt$  → Motor Isol. Stress / Reflections / Bearing Curr. / EMI

— *dv/dt - Challenges* —


## ► Motor Insulation Destruction

- **Partial Discharge Due to Insul. Imperfections** (Ionisation & Transient Space Charge Distrib.)
- **Partial Discharge Inception Voltage (PDIV) Dependent on  $dv/dt$**

Basic design of a wire insulation

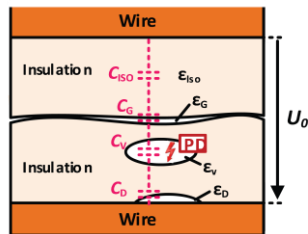

Source: Bakran / ECPE 2019

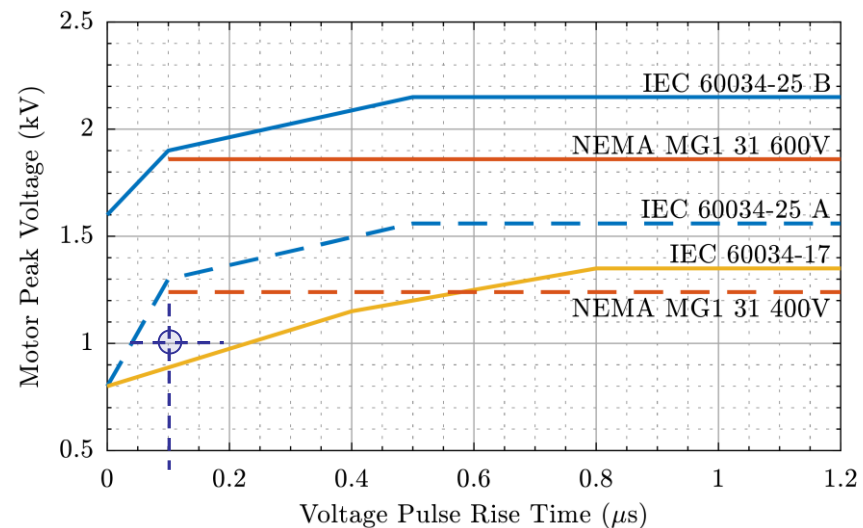



- **$dv/dt$ -Limits Specified by Standards**
- **$dv/dt$ -Filtering or Full Sinewave Filtering**



## ► Surge Voltage Reflections

- Short Rise Time of Inv. Output Voltage
- Impedance Mismatch of Cable & Motor → Reflect. @ Motor Terminals / High Insul. Stress
- Long Motor Cable  $l_c \geq \frac{1}{2} t_r v$


Source: Bakran / ECPE 2019

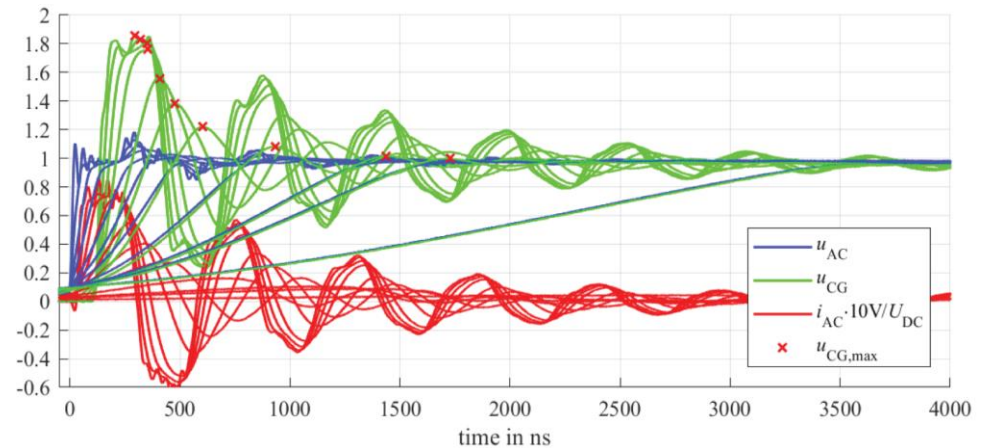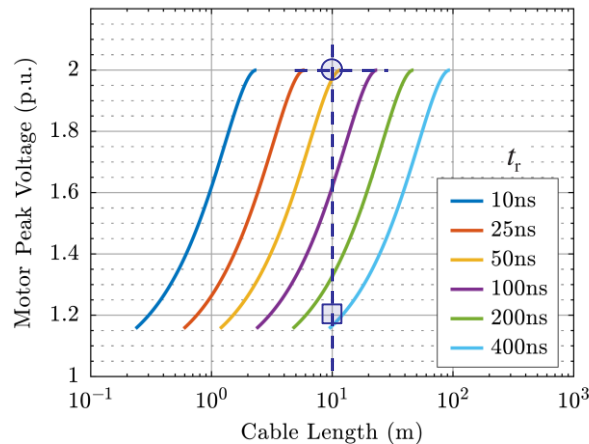

→ *dv/dt-Filtering* or *Full Sinewave Filtering / Termination & Matching Networks etc.*
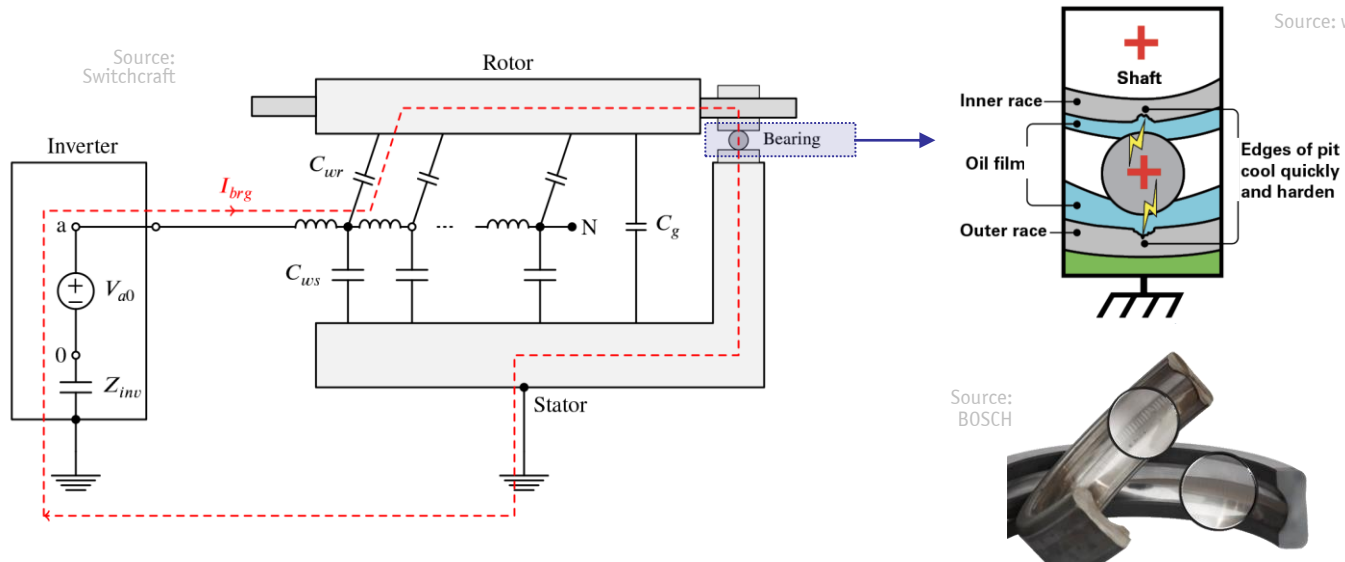
## ► Motor Bearing Currents

- Switching Frequency CM Inverter Output Voltage → Motor Shaft Voltage
- Electrical Discharge in Bearing ("EDM")



→ Cond. Grease / Ceram. Bearings / Shaft Grndg Brushes /  $dv/dt$ - OR Sine Wave Filters




## ► SiC vs. Si Inverter EMI Spectrum

- SiC Enables Higher  $dv/dt$  → Factor 10
- SiC Enables Higher Switching Frequencies → Factor 10
- EMI Envelope Shifted to Higher Frequencies

Source/Idea: M. Schutten / GE

$f_s = 10\text{kHz}$  &  $5\text{ kV}/\mu\text{s}$  for (Si IGBT)  
 $f_s = 100\text{kHz}$  &  $50\text{ kV}/\mu\text{s}$  for (SiC MOSFET)

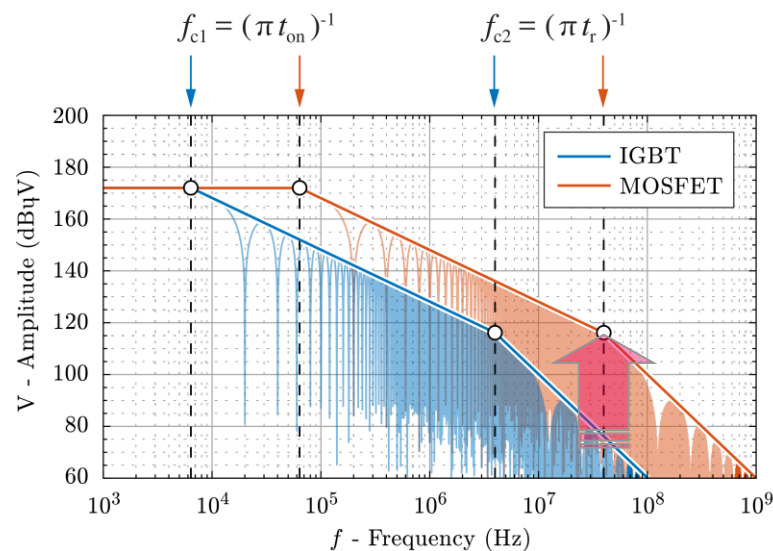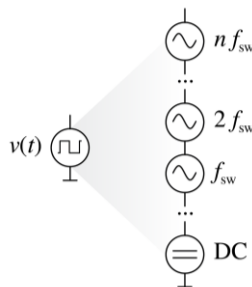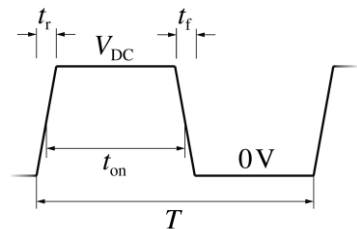
$V_{DC} = 800\text{V}$   
 DC/DC @  $D = 50\%$




- Higher Influence of Filter Component Parasitics and Couplings
- $dv/dt$ -Filtering or Full Sinewave Filtering, Shielded Motor Cables

## DM & CM Conducted / Radiated EMI

### DM Conducted EMI Pathway

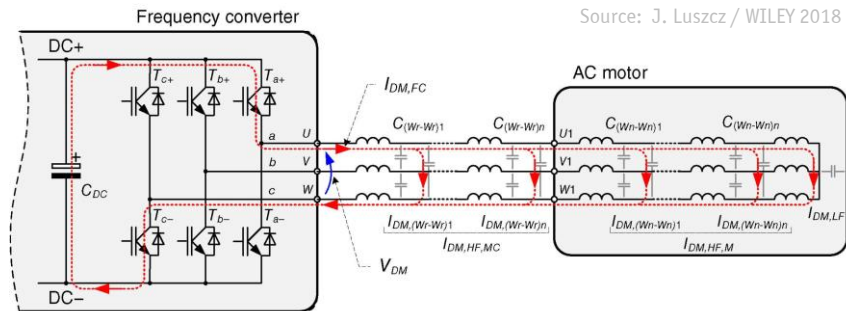




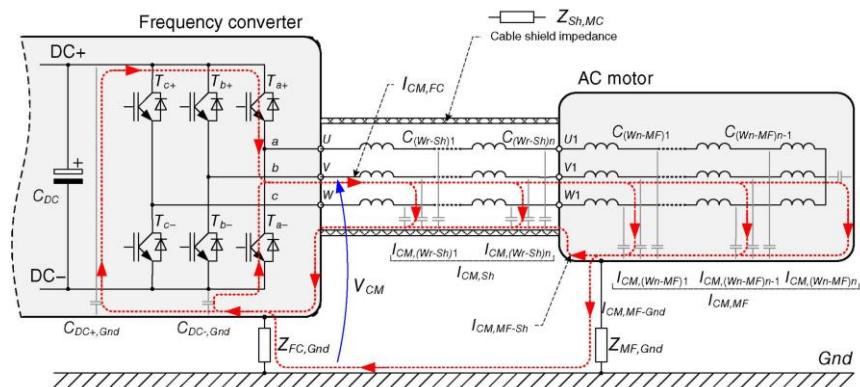
### CM Conducted EMI Pathway (Motor Side)



- EMI Standards (Cond. & Rad.) → **Shielded Motor Cables OR Full Sinewave Filtering**
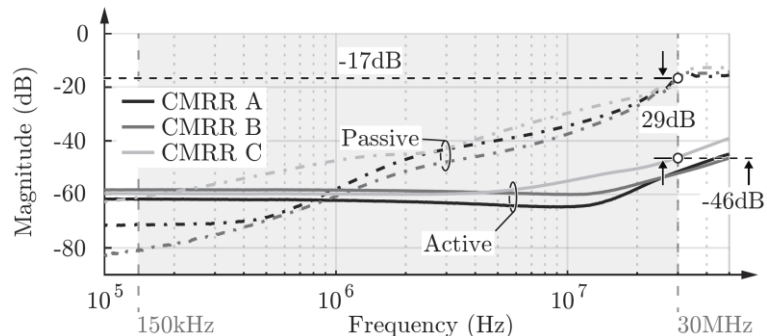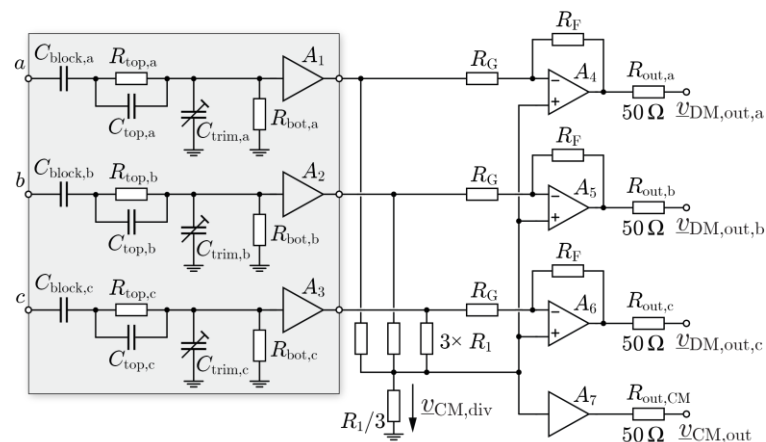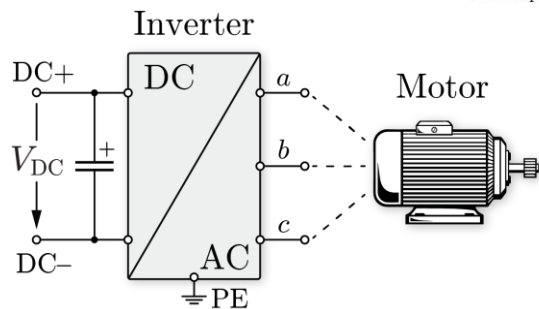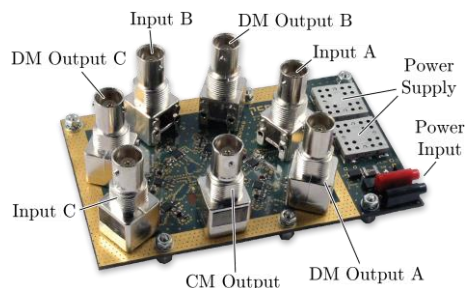
## ▶ 3-Φ DM/CM EMI Measurement & Separation

- EMI Measurement @ Inverter Output
- DM/CM Splitting for Specific Filter Design




- Cap. Coupled Interface Circuit as Replacement for LISN (Var. Output Freq.)

## *Inverter Output Filters*


*dv/dt-Filters*  
*Motor Cable Termination*  
*Staggered Switching*  
*Active CM Filtering*
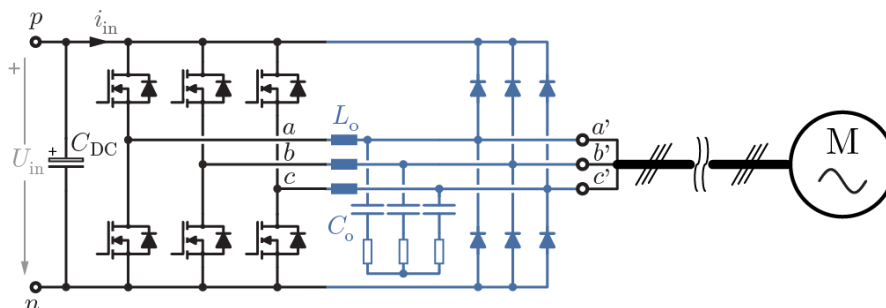
## ► Passive $dv/dt$ -Filter & Cable Termination

- $f_c > f_s \rightarrow$  Reduction of High  $dv/dt$  of Inverter Output Voltage to  $3...5kV/us$



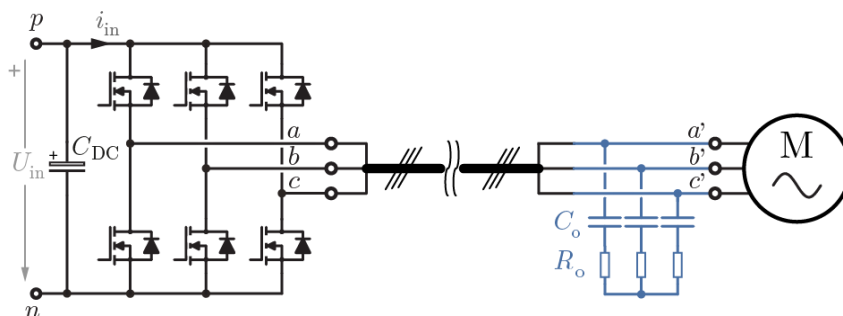- Termination of Cable with Characteristic Impedance & Damping (No  $dv/dt$ -Limit)





- Limited Applicability @ High Output / Sw. Frequencies (Losses)  $\rightarrow$  Full Sinewave Filter
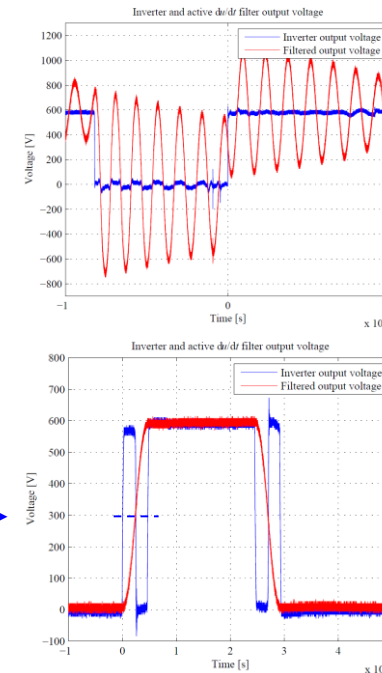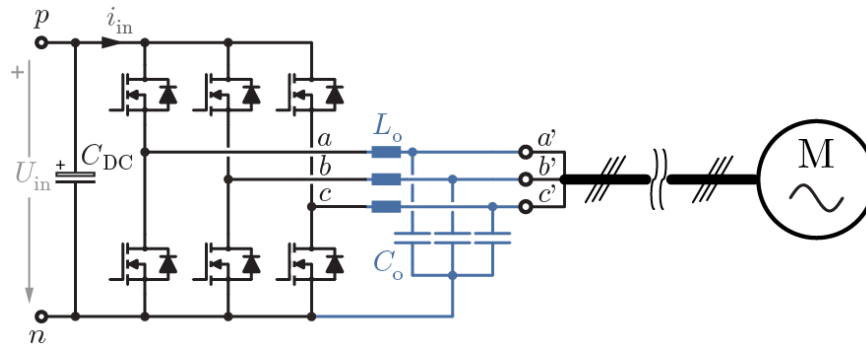
## ► Active $dv/dt$ -Filtering

- **Active Control of the  $dv/dt$ -Filter Transient Behavior** → 2-Step Transition
- **Influence of Motor Current** → Adaption of Sw. Scheme
- **DC- Connection Optional**

Source: PhD Thesis, J.P. Ström  
Lappeenranta Univ., 2009 / VACON





- **Ideally No Damping Resistors**
- **Increase of Sw. Losses** → **Low Sw. Freq.** OR **High Sw. Speed Semiconductors**



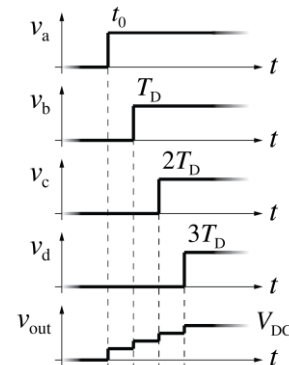
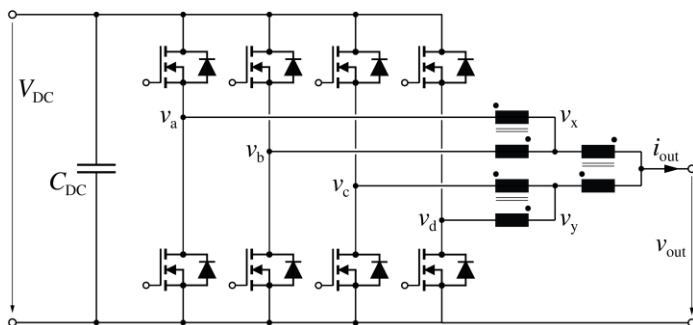
## ► Staggered/Resonant Switching

- Staggered Sw. Parallel Bridge Legs → Non-Resonant Multi-Step Transition



Source: J. Ertl et al. PCIM Europe 2017

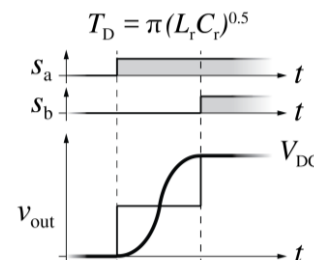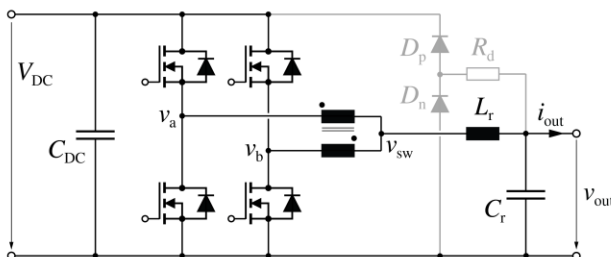- 2-Step Switching / Resonant Transition (cf. Active dv/dt Filter)




Source: J. Ertl et al. PCIM Europe 2018

- Adv. for High Power / Output Curr. Syst. Employing Parallel Bridge Legs & Local Comm. Cap.


## ► Active CM Voltage Filters
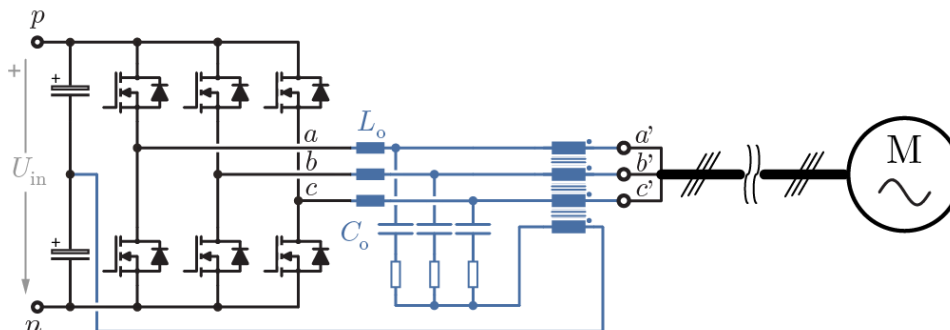
### ■ Series Compensation of CM Voltage & DM $dv/dt$ -Filtering



Source: X. Chen et al., 2007
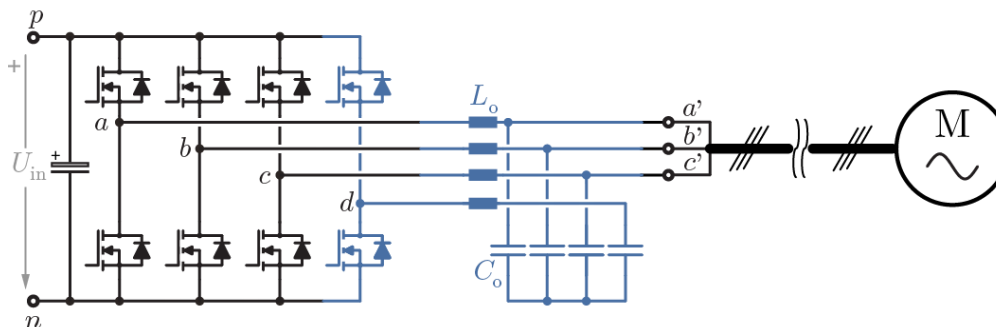
### ■ Aux. Bridge Leg → Zero CM Voltage for Active Inv. Sw. States & DM $dv/dt$ -Filtering



Source: T.A. Lipo et al., 1999

### ● Residual CM Voltage Due to Transf. & Sw. Imperfections / Complexity & Missing Zero State


# *Inverter Output Filters*

— *Sinewave Filters* —

## ► “SineFormer” Output Filter

- $f_c \ll f_s$  DM and CM (!) Output Filter Stage → Sin. Output Voltage / No Sw. Frequ. CM Voltage
- No Shielded Motor Cables Required
- Reduction of Mains-Side EMI


Source: TDK

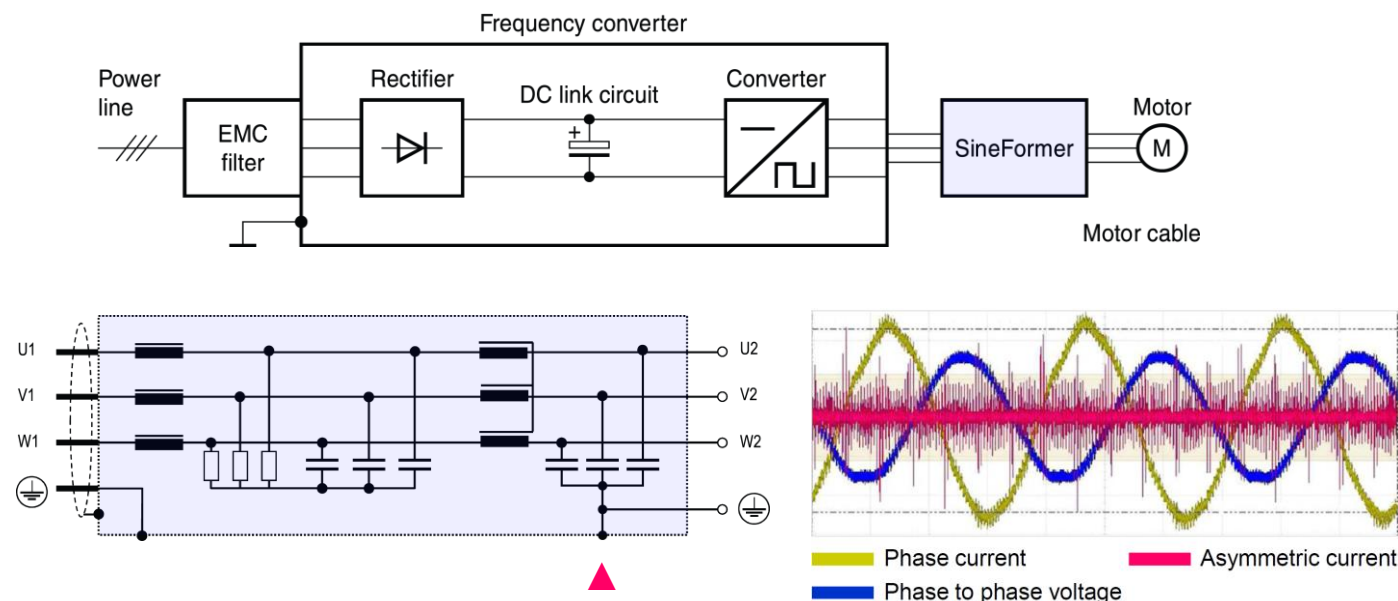

- Large Weight & Volume →  $\approx 2 \text{ kVA/dm}^3$  ( $f_s = 4 \dots 8 \text{ kHz}$ ,  $f_0 = 0 \dots 100 \text{ Hz}$ )
- Filter Cap. Starpoint Connected to PE Not DC- (Allows Retrofitting)
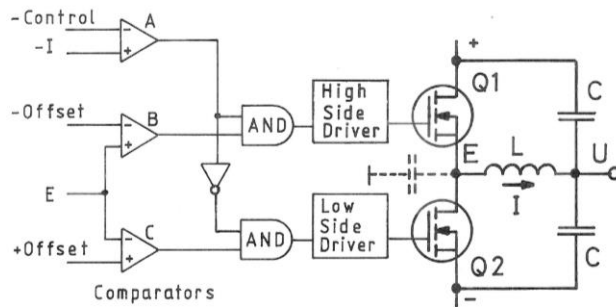
## ► Full Sinewave Filtering @ ZVS/TCM Operation

- **ZVS of Inverter Bridge Legs** (No Use of Integral Diode of Si MOSFETs)
- **High Sw. Frequency & TCM** → **Low Filter Inductor Volume**




Source: Joensson

**PCIM'88**

(POWER CONVERSION)


**CONFERENCE**

DECEMBER 8-10, 1988  
TOKYO, JAPAN

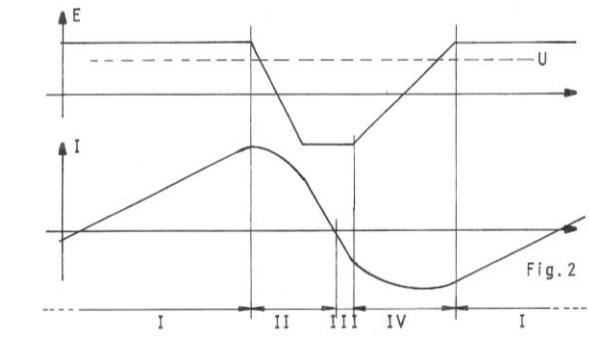

NFO Sinus® is available in size 0.37 kW up to 22 kW



Source: **NFO Sinus**®

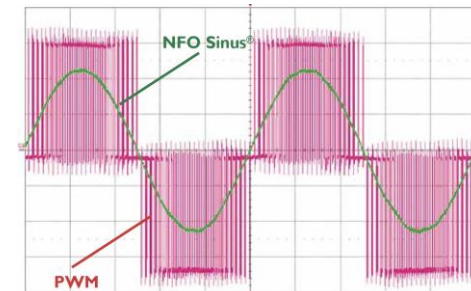

- **Widely Varying Switching Frequency** → **Voltage Headroom and/or Multiple Bridge-Legs**
- **Rel. High Current Stress on the Power Transistors**
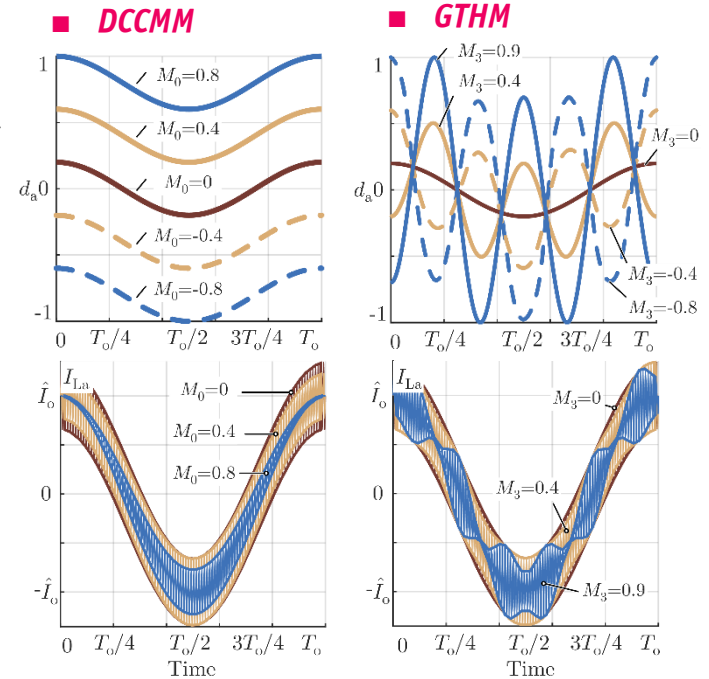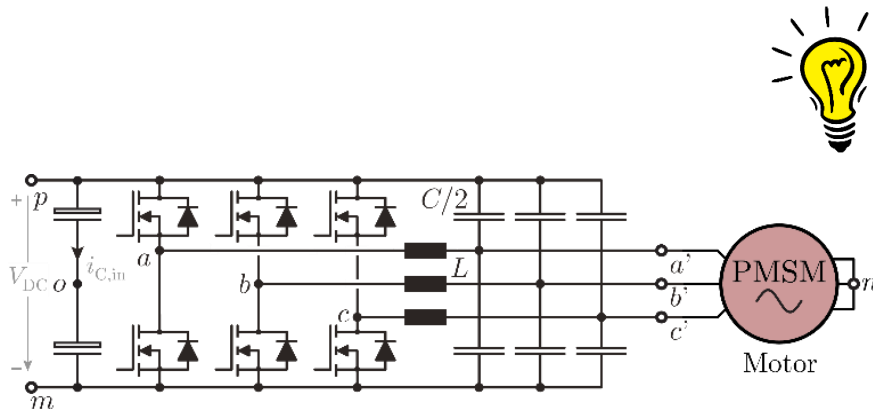
## ► Full Sinewave Filtering @ CCM Operation (1)



- **DC- Ref. LC-Filter** → Max. Ind. Current Ripple @  $d=0.5$
- **DCCMM** — Max. DC-Offset  $M_0$  Shifting Phase Voltages Towards  $d=0$  OR  $d=1$
- **GTHM** — Max. 3<sup>rd</sup> Harm.  $M_3$  for Red. of Sw. Freq. Harmonic Power



- **GTHM** — Results in Add. Cap. Reactive Power → Limited for Higher Frequencies
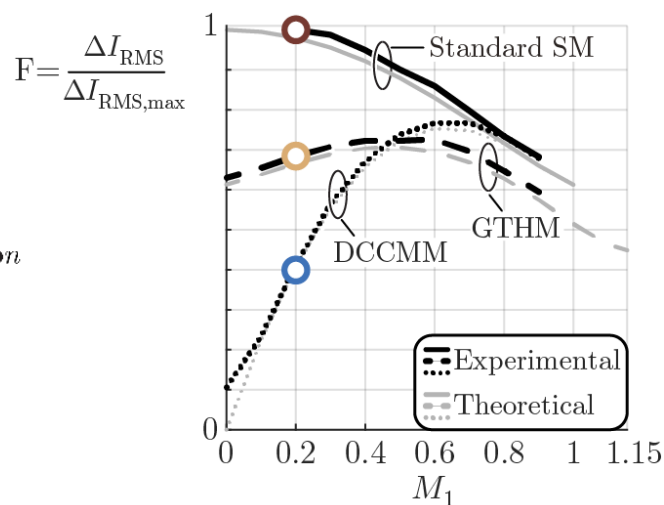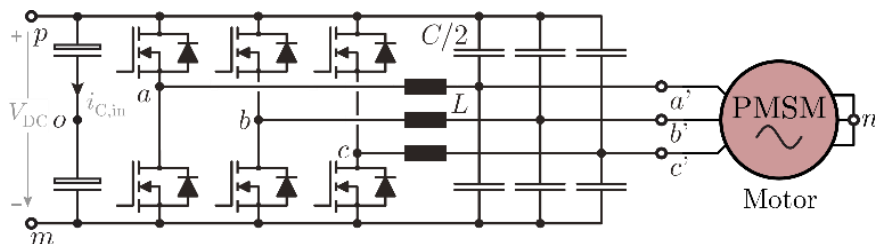
## ► Full Sinewave Filtering @ CCM Operation (2)

- **Massive Red. of Current Ripple @ Lower Modulation Index**
- **DCCMM** — Adv. for  $M = 0 \dots 0.5$
- **GTHM** — Adv. for  $M = 0.5 \dots 1.0$



- **GTHM** — Results in Add. Cap. Reactive Power → Limited for Higher Frequencies

## ***Buck+Boost Inverter***

***Z-Source Inverter etc.  
VSI & DC/DC Front-End  
Double-Bridge VSI***


***Phase-Modular Buck+Boost Inverter  
CSI & DC/DC Front-End***





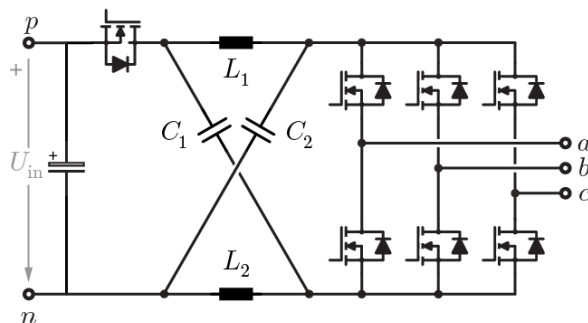
## ► “Outside-the-Box” Topologies

- **Z-Source Inverter** → Shoot-Through States Utilized for Boost Function
- **Higher Component Stress Eff. Limits Boost Operation to  $\approx 120\% U_{in}$**



Source: F.Z. Peng / 2003  
J. Rabkowski / 2007

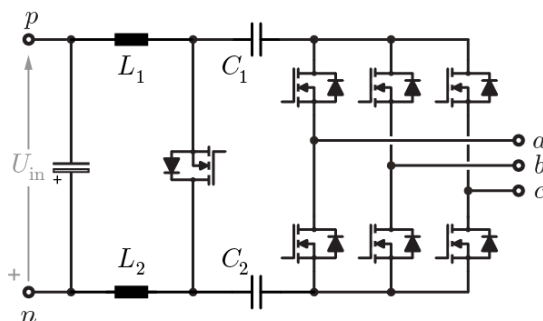- **3- $\Phi$  Back-End DC/AC Cuk-Converter**




Source: T.A. Lipo  
et al. / 2002 &  
K.D.T Ngo / 1984

- **Integration Typ. Results in Higher Comp. Stresses & Complexity / Lower Performance**
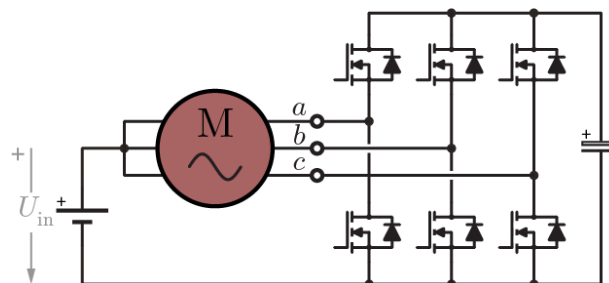
## ► Boost Converter DC-Link Voltage Adaption



- **Inverter-Integr. DC/DC Boost Conv. → Higher DC-Link Voltage / Lower Motor Current**
- **Access to Motor Star Point & Specific Motor Design Required**
- **No Add. Components**



Source: J. Pforr et al. / 2009

### ■ **Explicit Front-End DC/DC Boost Stage**

Source: www.rick-gerber.com

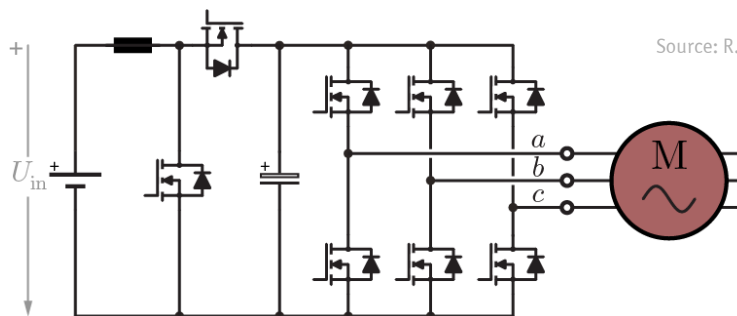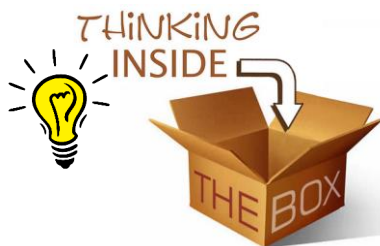


Source: R.W. Erickson et al. / 1986

→ **Analyze Coupling of the Control of Both Converter Stages → "Synergetic Control!"**
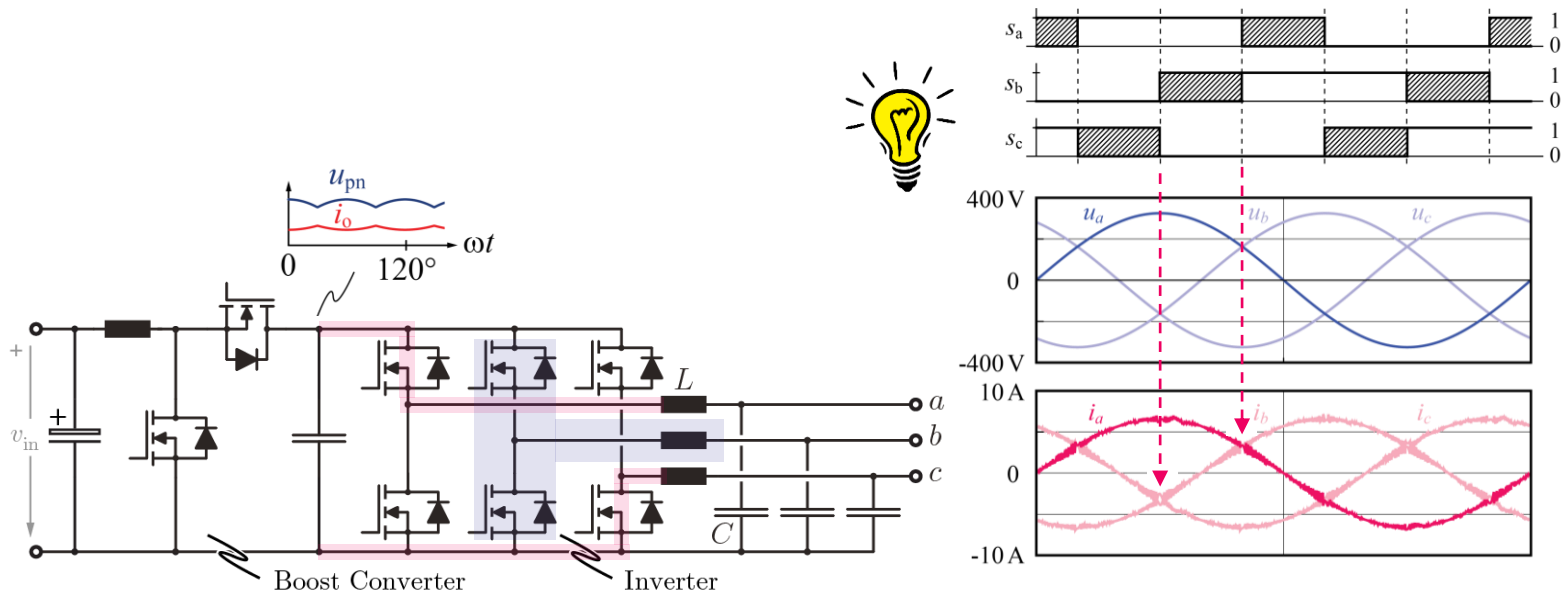
## ► Front-End DC/DC Boost Converter



- **“Synergetic Control” @ High Output Voltage**
- **2 (!) Inverter Phases Clamped** → Low Switching Losses / High Efficiency
- **Conv. PWM Inverter / Clamped Boost-Stage Operation @ Low Output Voltage**



- **Preferable for Low Dynamics Drive Systems**
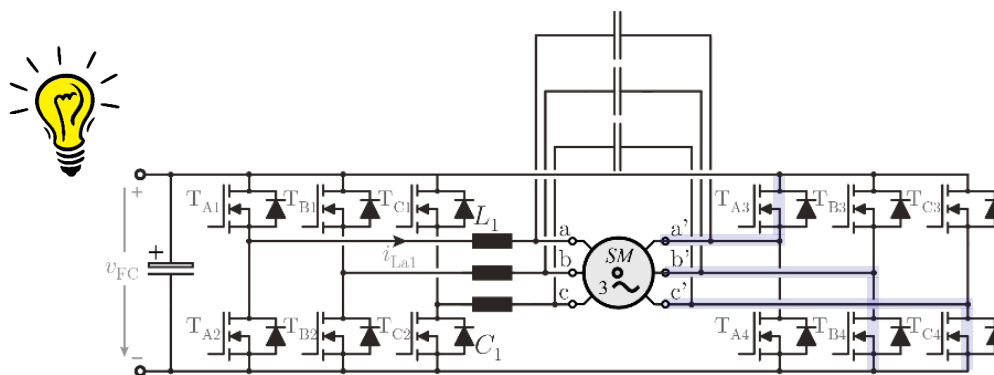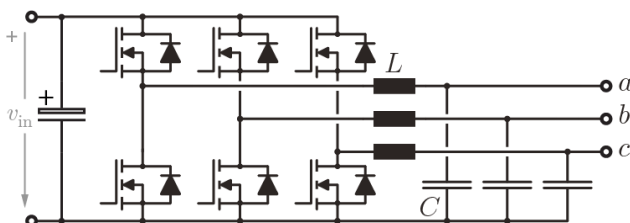
## ► Double-Bridge Inverter (1)

- *Alternative to Front-End DC/DC Converter* → *Eff. Doubles DC-Link Voltage*
- *2<sup>nd</sup> Bridge Switching with Output Freq.* → *"Unfolder" Operation*
- *Avoids Volume and Losses of Boost Stage* → *Eff. Single-Stage Conversion*
- *Only Three Inductive Components*




- *Requires Open Winding Motor & Higher Number of Gate Drives*


## ► Double-Bridge Inverter (2)
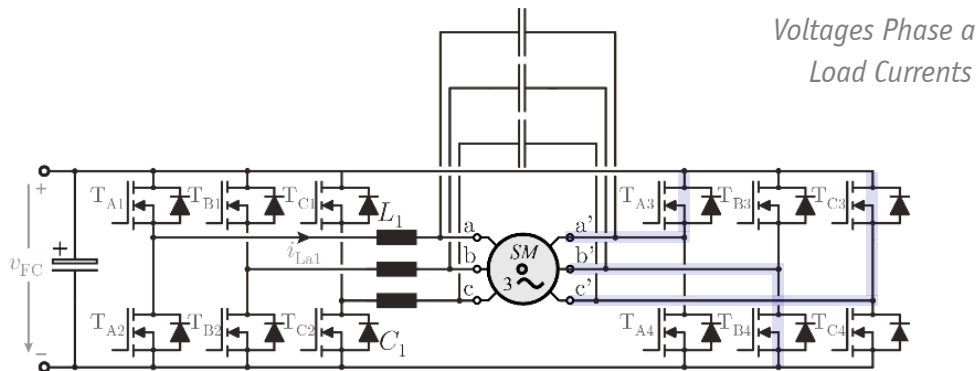
### ■ Hardware Demonstrator

$U_{FC} = 40V$   
 $P = 1.0kW$   
 $f_S = 350kHz$  (200V EPC GaN, 2 per Switch)  
 $f_0 = 5kHz$



Voltages Phase a  
Load Currents

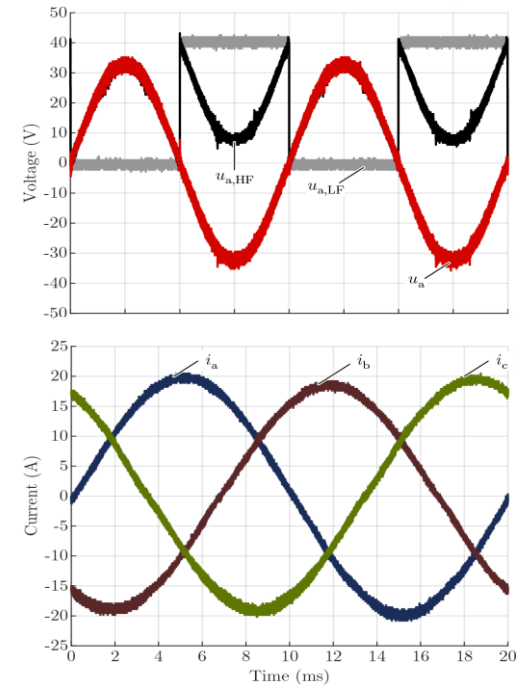



- Requires Open Winding Motor & Higher Number of Gate Drives

## ► Double-Bridge Inverter (3)

### ■ Hardware Demonstrator

$U_{FC} = 40V$   
 $P = 1.0kW$   
 $f_s = 350kHz$  (200V EPC GaN, 2 per Switch)  
 $f_0 = 5kHz$

240 W/in<sup>3</sup>

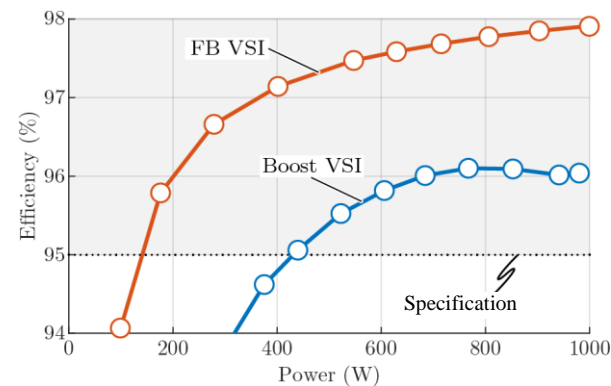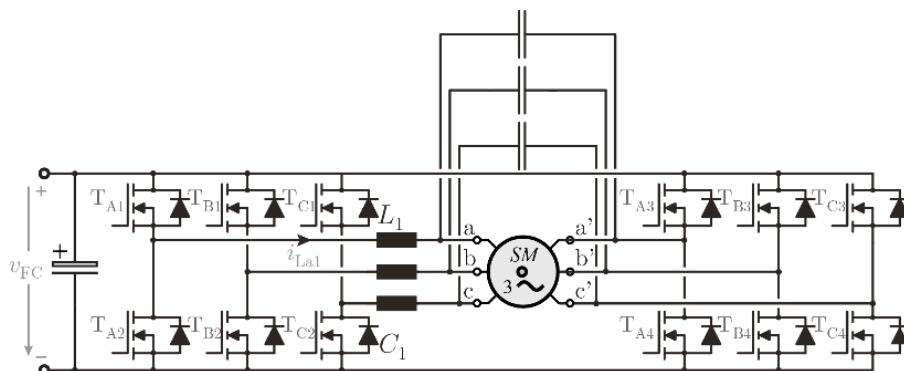

- Requires Open Winding Motor & Higher Number of Gate Drives

## *Phase-Modular Topologies*

*Boost+Buck Modules*  
*Buck+Boost Modules*

## ► General Remarks

- Usually **DC Link Voltage Midpoint** Considered as **AC Output Ref. Point**
- **Open Machine Starpoint** → Introduce **CM Voltage Shift** → **Neg. DC Rail as Reference**

Source: Cuk (1982) **NEW POLYPHASE AMPLIFIER**

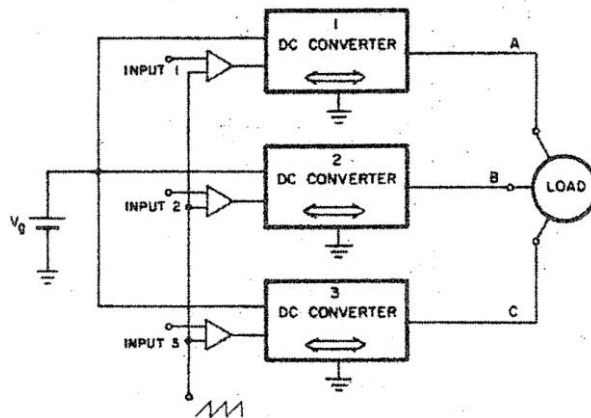


Fig. 7. New three-phase switching amplifier. Three bidirectional dc-dc converters, with their own modulators, driven by a set of three-phase sine waves, constitute three phase voltages around the differential load.

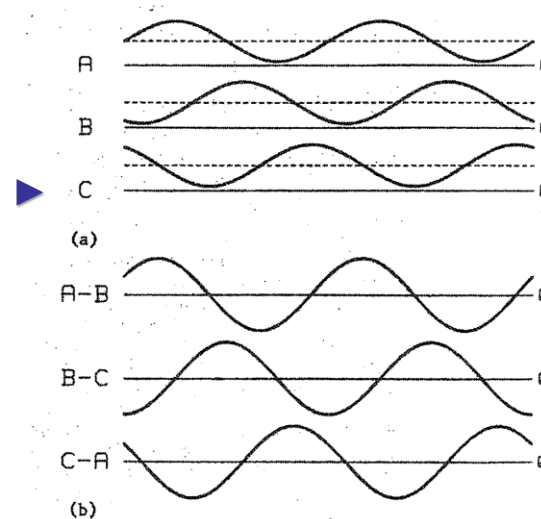



Fig. 8. (a) Line-to-ground and (b) line-to-line voltages generated by the new three phase power amplifier. The dc component of the line-to-ground voltages automatically disappears in line-to-line voltages which are pure ac.

→ Realization of **3- $\Phi$  Inverter Using 3 DC/DC Converter (Phase) Modules** — S. Cuk/1982


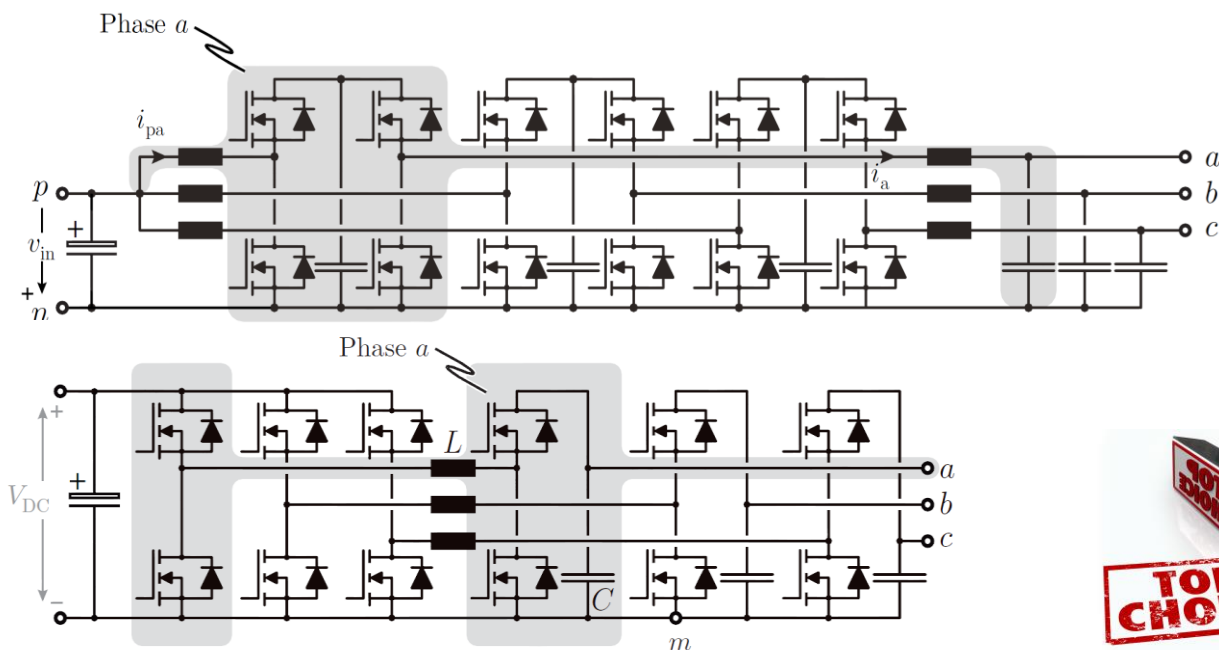
## ► Phase-Modular Boost+Buck / Buck+Boost Inverter

- **Wide Voltage Conv. Range** → Battery or Fuel-Cell Supply & Adaption to Motor Voltage
- **Continuous Output Voltage** → Explicit / Integr. LC Output Filter





→ Preference for **Low Number of Ind. Components** → Buck+Boost Concept — “Y-Inverter”


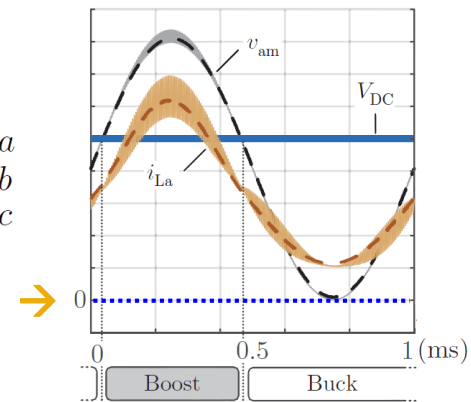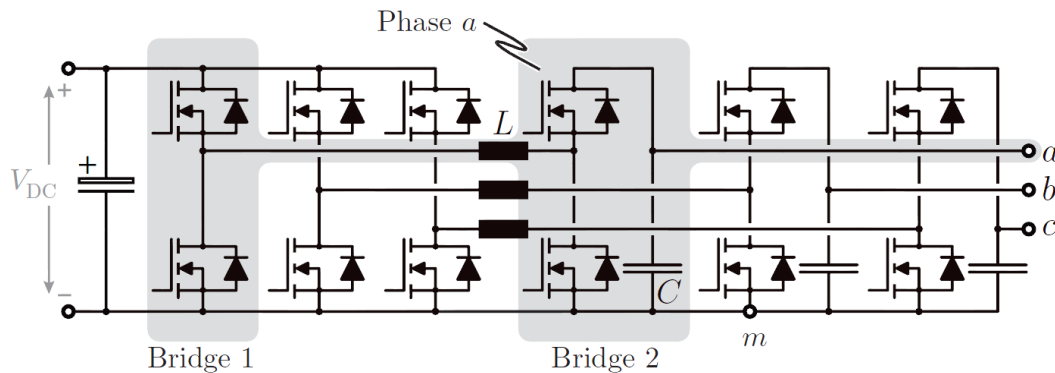
# Y-Inverter Lighthouse Project





- Three-Phase Continuous Output / Low EMI !
  - Buck+Boost Operation / Wide Input &/or Output Range
  - Standard Bridge Legs / Building Blocks
  - ZVS Operation / Extreme Power Density
- No Shielded Cables / No Insul. Stress
  - Industrial Drive
  - 1.2kV SiC MOSFETs



■ Project Scope → Hardware Demonstrator / Exp. Analysis / Comparative Evaluation

# Y-Inverter (1)

## Operating Behavior

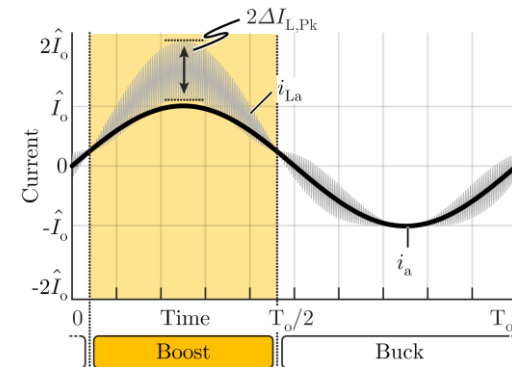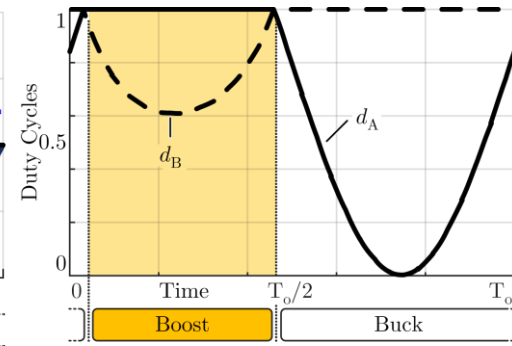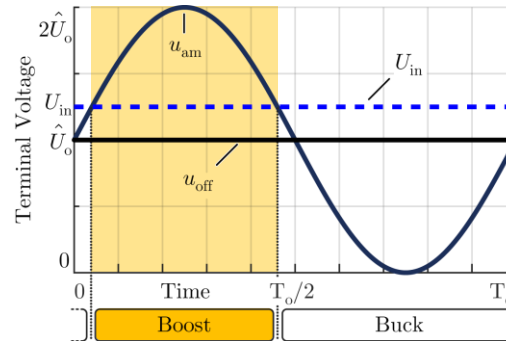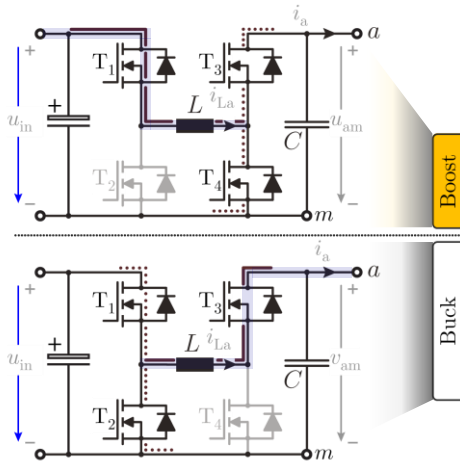


- $u_{am} < U_{in} \rightarrow$  Buck Operation
- $u_{am} > U_{in} \rightarrow$  Boost Operation
- Output Voltage Generation Referenced to DC Minus


## ► Y-Inverter (2)
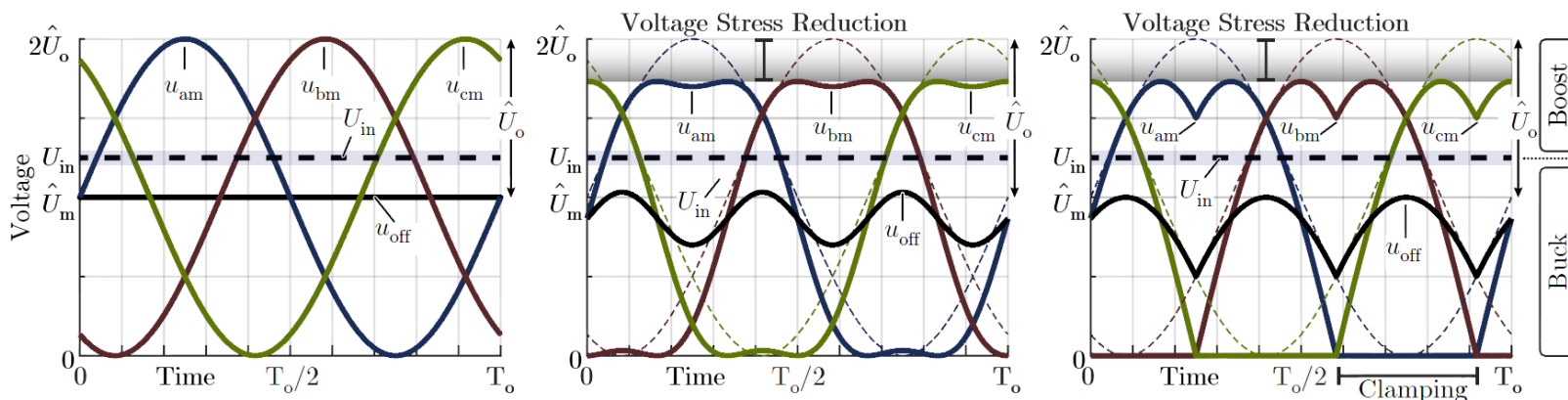
### • Modulation Schemes

- Sinusoidal Modulation → Variable Output Voltage DC Offset for Low Mod. Index
- 3<sup>rd</sup> Harmonic Injection OR Phase Clamping as Alternative Concepts




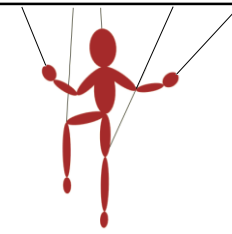- Adv. of Reduced Voltage Against DC- & Reduction of Sw. Losses



# ► Y-Inverter (3)

## • Control Structure



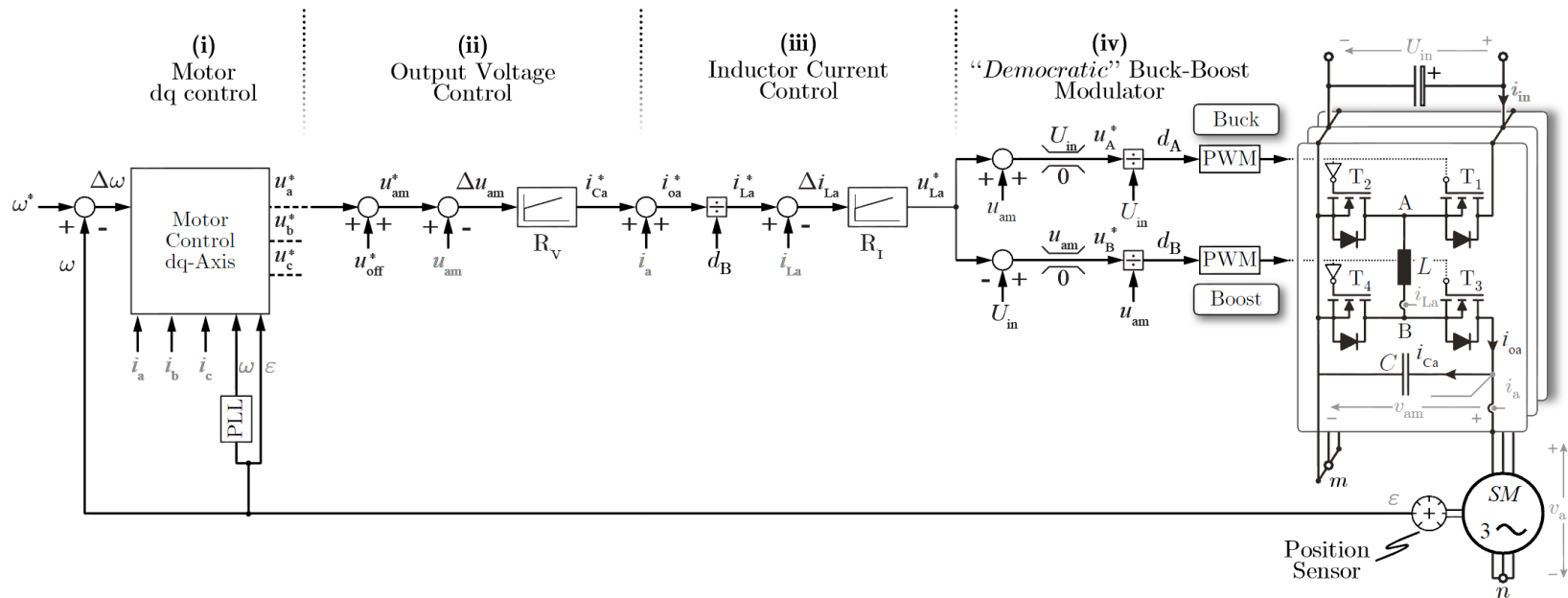


■ **"Democratic Control"** → Seamless Transition Between Buck & Boost Operation

## ► Y-Inverter Prototype (a)
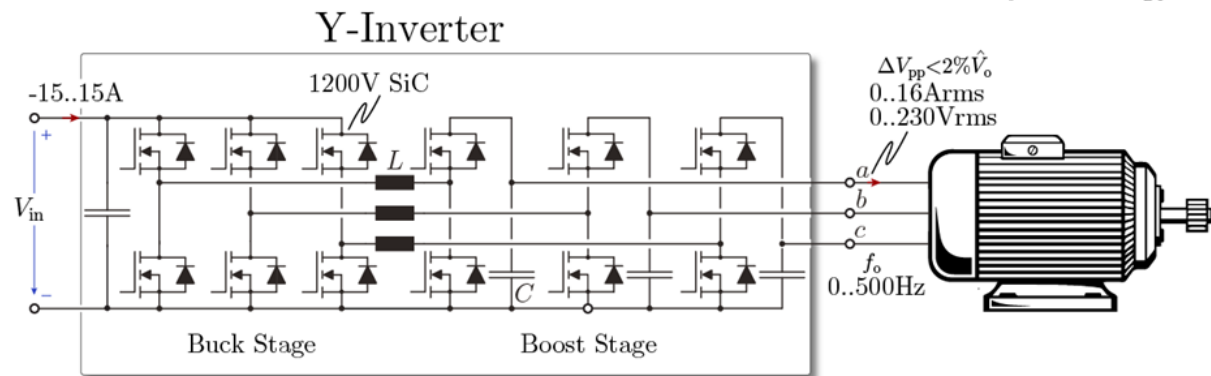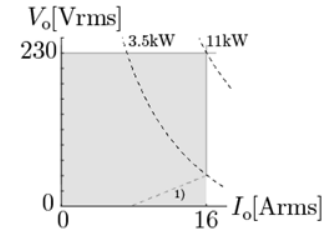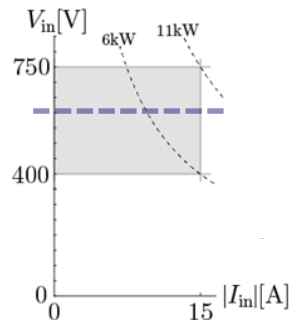
### • Demonstrator Specifications


- Wide Input Voltage Range → 400...750V<sub>DC</sub>
- Max. Input Current → ± 15A



- Max. Output Power → 6...11 kW
- Output Frequency Range → 0...500Hz
- Output Voltage Ripple → 3.2V Peak-to-Peak (incl. Add. Output Filter)
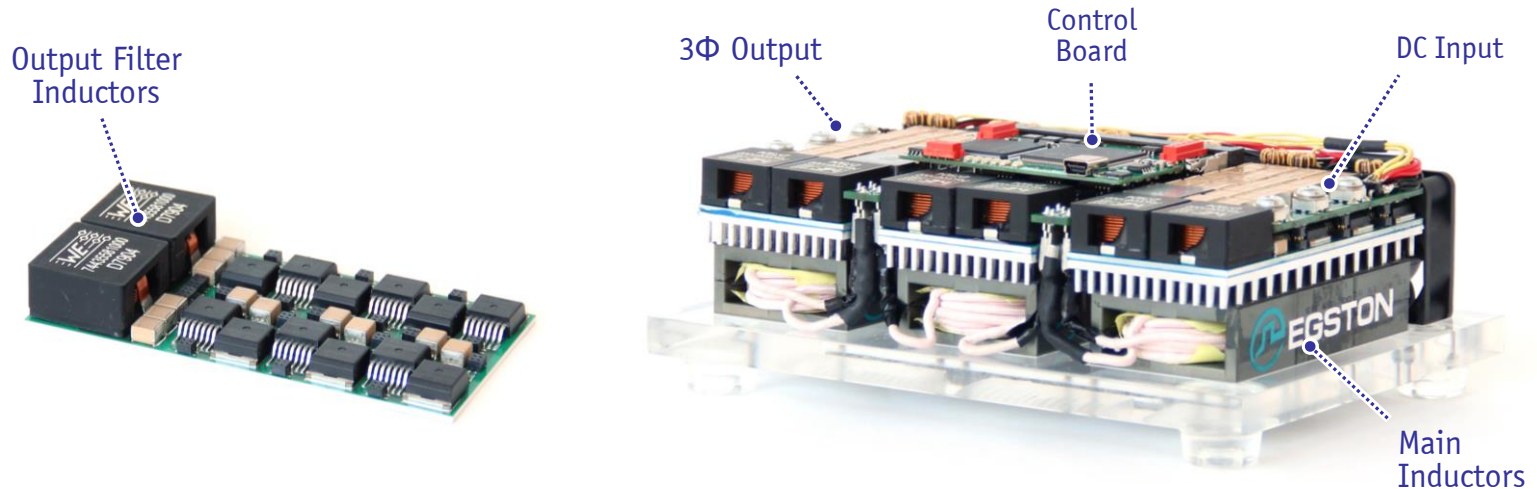
## ► *Y-Inverter Prototype (b)*

- DC Voltage Range **400...750V<sub>DC</sub>**
- Max. Input Current **± 15A**
- Output Voltage **0...230V<sub>rms</sub>** (Phase)
- Output Frequency **0...500Hz**
- Sw. Frequency **100kHz**
- **3x SiC (75mΩ)/1200V** per Switch
- **IMS Carrying Buck/Boost-Stage Semicond. & Comm. Caps & 2<sup>nd</sup> Filter Ind.**



- **Dimensions** → **160 x 110 x 42 mm<sup>3</sup>** (15kW/dm<sup>3</sup>, 245W/in<sup>3</sup>)


## ► Y-Inverter Prototype (c)

### • Measurement Results


$U_{DC} = 400V$   
 $U_{AC} = 400V_{rms}$  (Motor Line-to-Line Voltage)  
 $f_0 = 50Hz$   
 $f_s = 100kHz / DPWM$

$P = 6.5kW$

100V/div  
10A/div

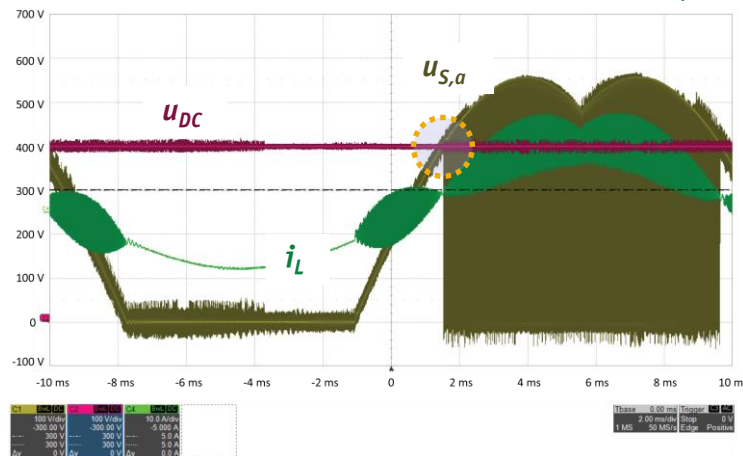

200V/div  
1V/div

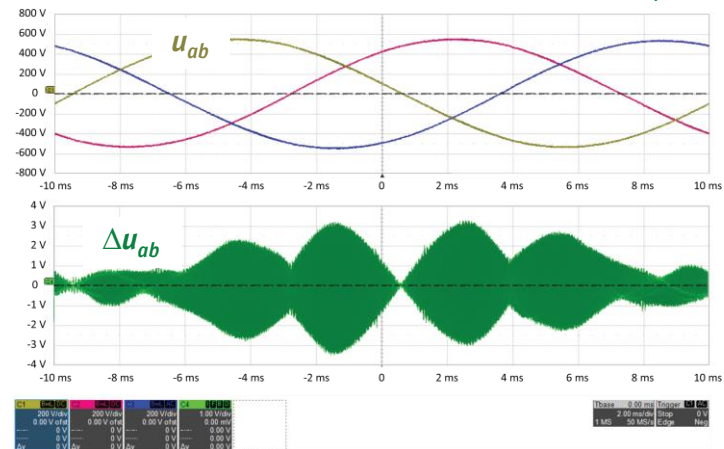



→ Line-to-Line Output Voltage Ripple < 3.2V


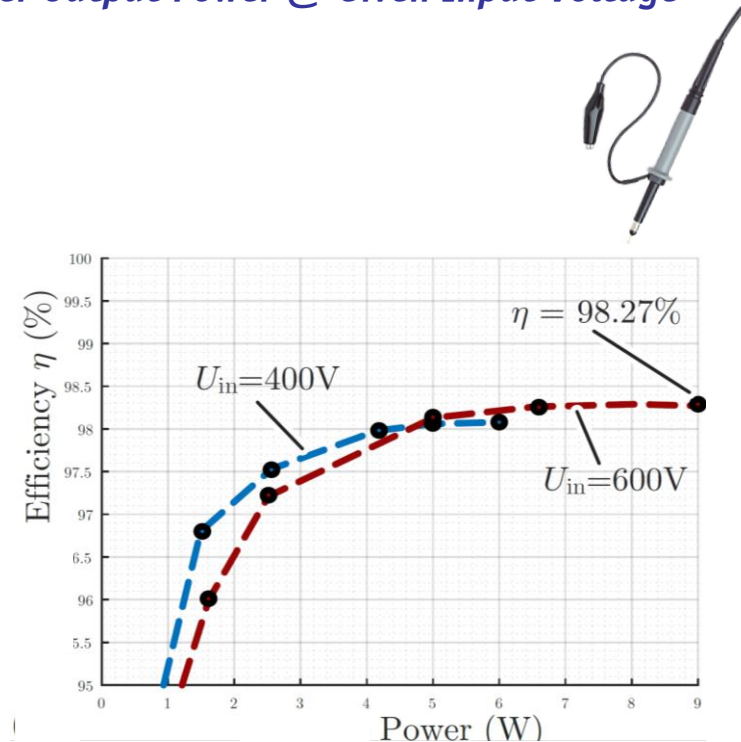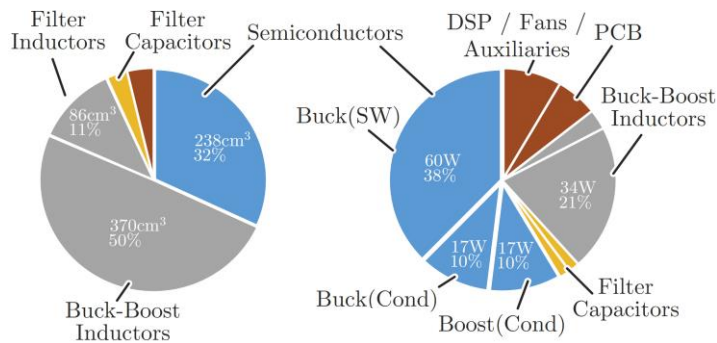
## ► Y-Inverter Prototype (d)

- Demonstrator Performance - Efficiency over Output Power @ Given Input Voltage


$$\begin{aligned}
 U_{DC} &= 400\text{V} / 600\text{V} \\
 U_{AC} &= 230\text{V}_{\text{rms}} \text{ (Motor Phase Voltage, rms)} \\
 f_s &= 100\text{kHz}
 \end{aligned}$$



→ Multi-Level Bridge Leg Structure for Ind. Comp. Volume Reduction
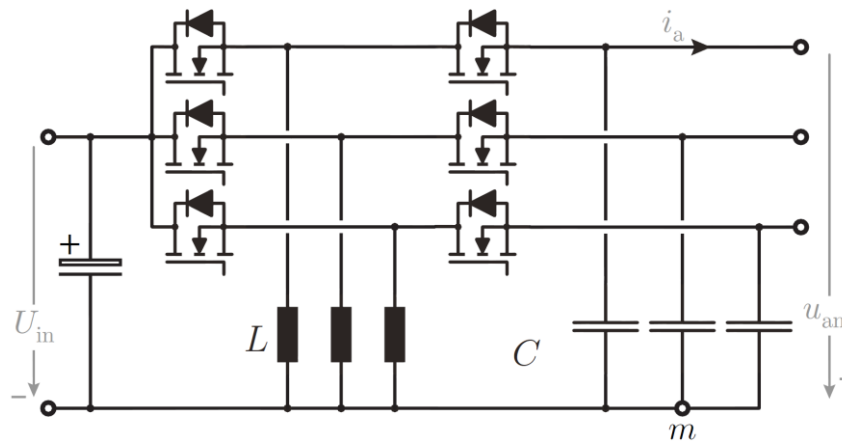
## ► *Alternative Topology*

- *Phase Modules Based on 2-Switch Buck+Boost Topology*



- **Lower Number of Switches / Higher Component Stresses** → *Low Power Applications*


## *DC/DC Buck Stage & Current Source Inverter*

*Monolithic Bidir. GaN Switches  
Synergetic Control*


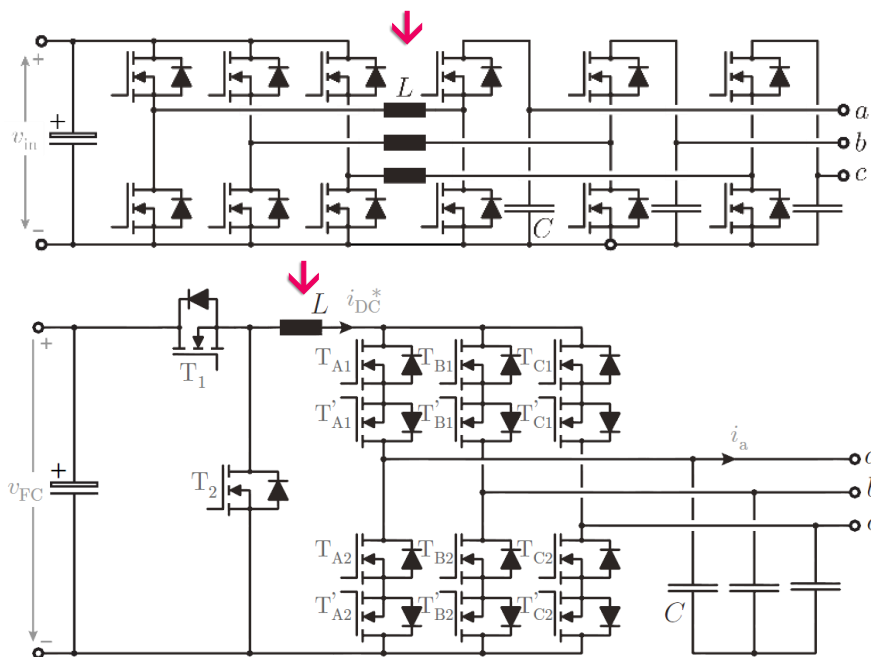
## ► Current Source Inverter (CSI) Topologies


- Phase Modular Concept → **Y-Inverter** (Buck-Stage / Current Link / Boost-Stage)
- 3- $\Phi$  Integrated Concept → **Buck-Stage & Current DC Link Inverter**



→ **Low Number of Ind. Components** & **Utilization of Bidir. GaN Semicond. Technology**
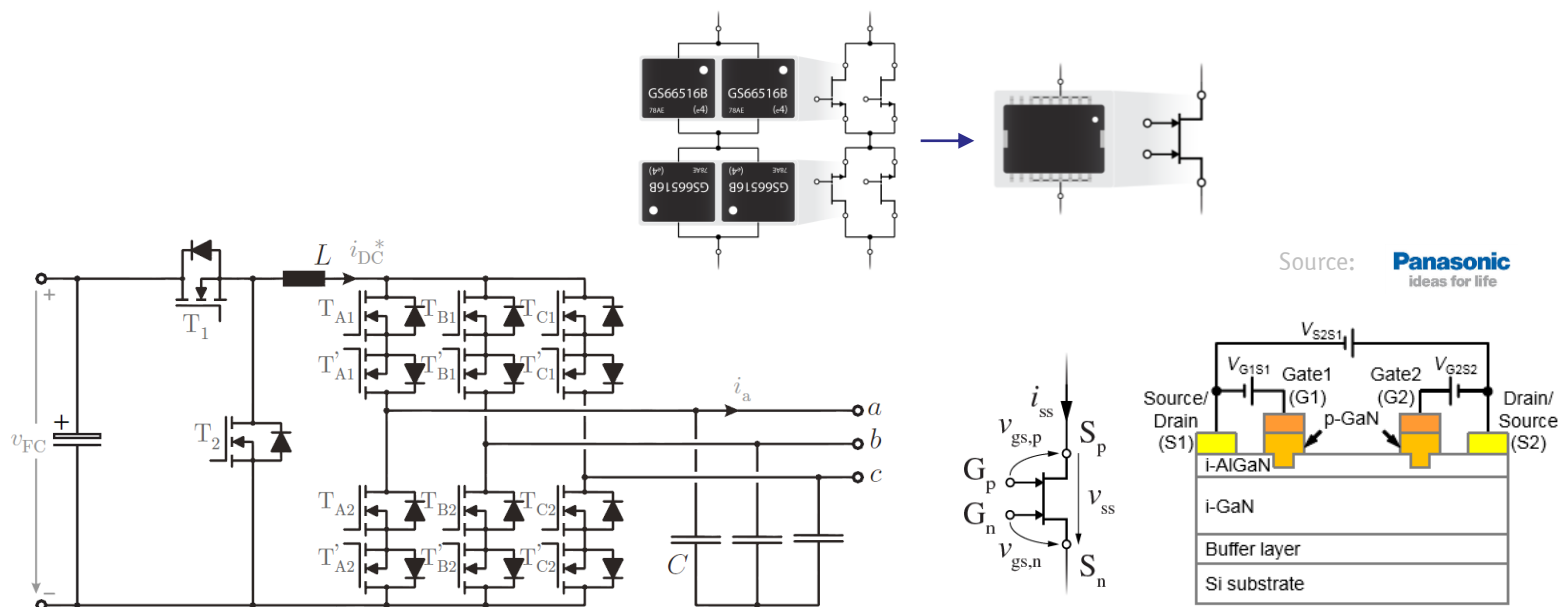
## ► 3- $\Phi$ –Integrated Buck-Boost CSI (1)



- **Basic Topology Proposed in 1984 / Ph.D. Thesis of K.D.T Ngo**
- **Bidir./Bipolar Switches  $\rightarrow$  Positive DC-Side Voltage for Both Directions of Power Flow**



- $\rightarrow$  **Monol. GaN Switches  $\rightarrow$  Factor 4 Improvement in Chip Area Comp. to Discrete Realiz.**
- $\rightarrow$  **Also Beneficial for Matrix Converter Topologies**
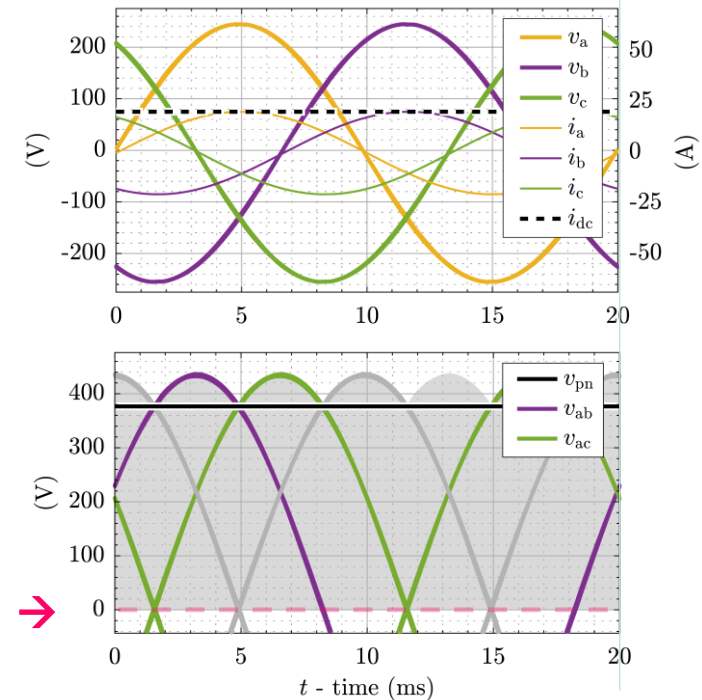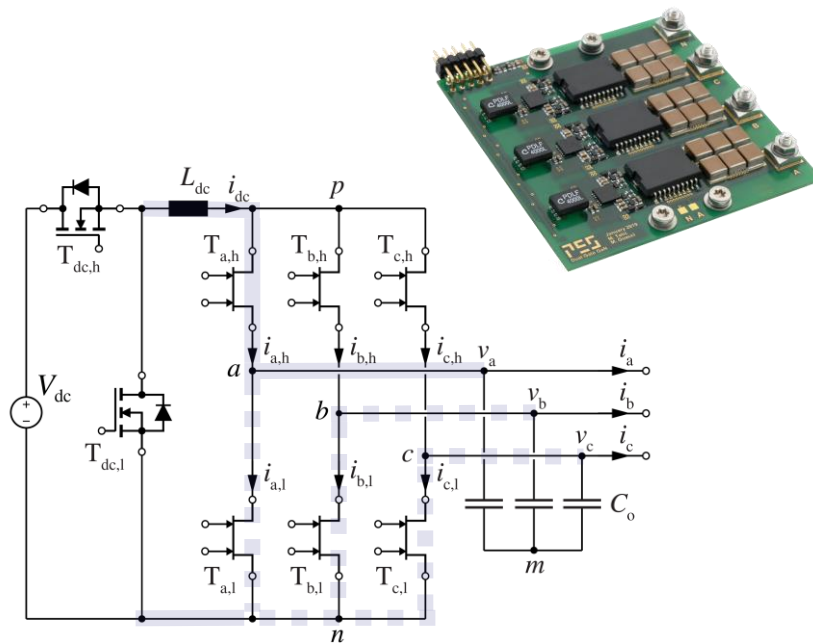
## ► 3- $\Phi$ –Integrated Buck-Boost CSI (2)



- **Monolithic Bidir. Bipolar GaN Switches Featuring 2 Gates / Full Controllability**
- **Buck-Stage for Const. DC Current / PWM CSI for Output Voltage Control**



→ **“Synergetic Control” of Buck & Inverter Stage for Red. of Sw. Losses**
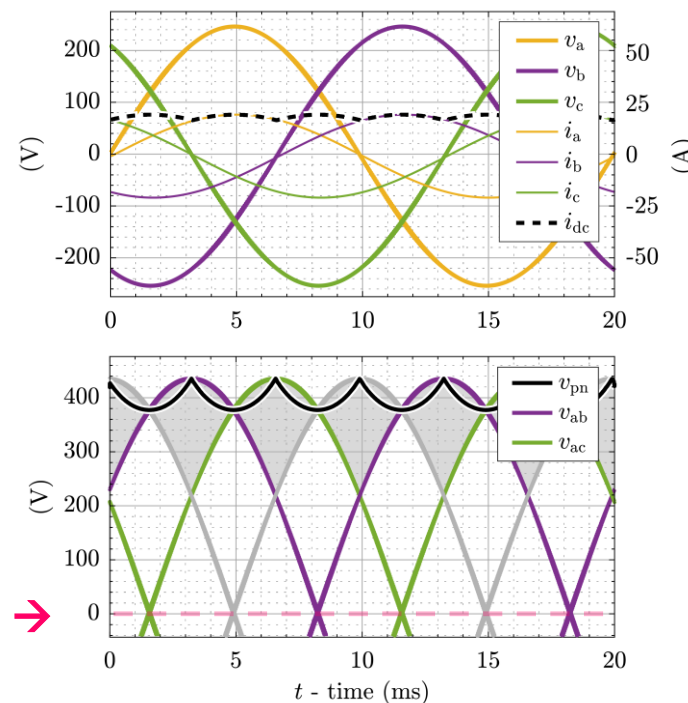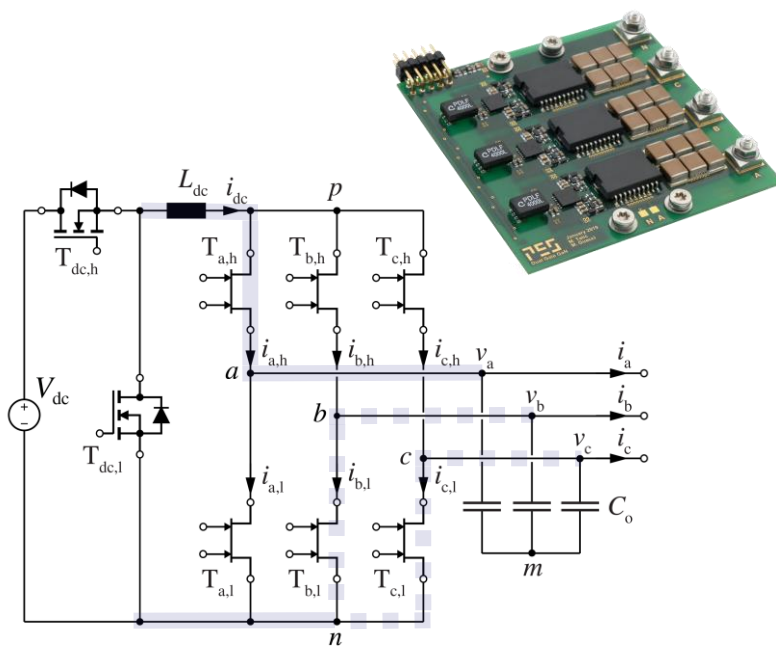
## 3- $\Phi$ -Integrated Buck-Boost CSI (3)


- **Monolithic Bidir. Bipolar GaN Switches Featuring 2 Gates / Full Controllability**
- **"Synergetic" Variable DC Current Control of Buck Stage & Inverter Stage Clamping**



→ **Experimental Analysis in Progress (Upcoming Publication @ PEDG 2019)**

## Further Concepts

### *Integrated Modular Motor Drive*



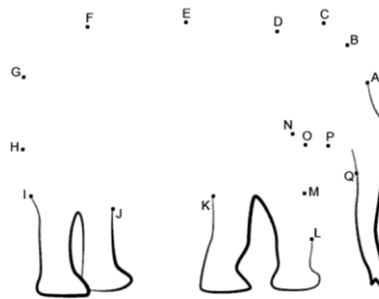



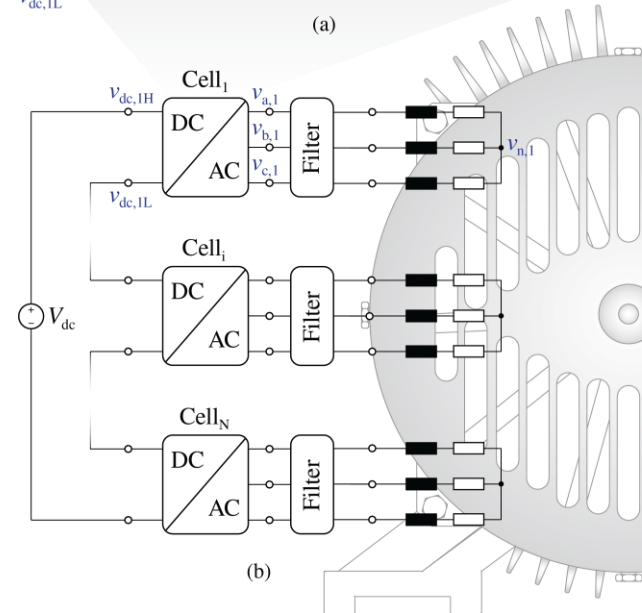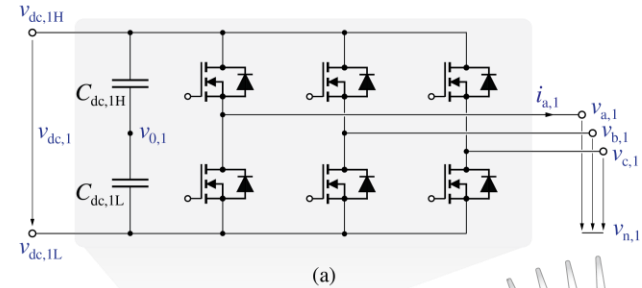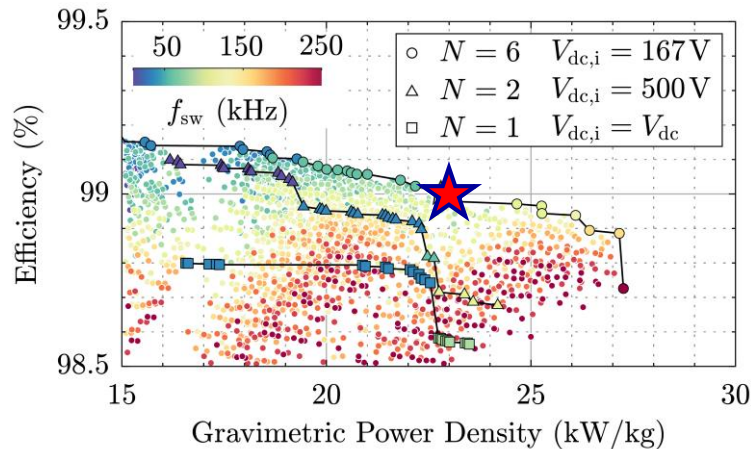
## ► Integrated Modular Motor Drive

- **Machine/Inverter Fault-Tolerant VSD**
- **Motor Integr. Low-Voltage Inverter Modules**
- **Very-High Power Density / Efficiency**
- **Supply of 3- $\Phi$  Winding Sets / Low C Buffer Cap.**

- **Rated Power**      $45\text{kW} / f_{out} = 2\text{kHz}$
- **DC-Link Voltage**    $1\text{ kV}$



→ Evaluate Machine Concept (PMSM vs. SRM etc.) / Wdg Topologies / Filter Requ. / etc.

— *Conclusions* —

## ► Conclusions

### ■ *Future Need for „SWISS Knife“-Type Systems*

- *Wide Input / Output Voltage Range*
- *Continuous / Sinusoidal Output Voltage*
- *Electromagnetically „Quiet“ - No Shielded Cables*
- *On-Line Monitoring / Industry 4.0*
- *“Plug & Play“ / Non-Expert Installation*
- *SMART Motors*

### ■ *Enabling Technologies*

- *SiC / GaN*
- *Adv. (Multi-Level) Topologies incl. PFC Rectifier*
- *“Synergetic“ Control*
- *Monolithic Bidirectional GaN*
- *Intelligent Power Modules*
- *Integration of Switch / Gate Drive / Sensing / Monitoring*
- *Adv. Modeling / Simulation / Optimization*

### ■ *System Level → Integr. of Storage, Distrib. DC Bus, Hybrid Hydr./Pneum./El. Drives etc.*



Source:  
UK Outdoor  
Store

**Thank You !**

