


Design and Experimental Analysis of a 10 kV SiC MOSFET Based 50 kHz Soft- Switching Single-Phase 3.8 kV AC / 400 V DC Solid-State Transformer



D. Rothmund, T. Guillod, D. Bortis, and J.W. Kolar

Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch

Sept. 24, 2018

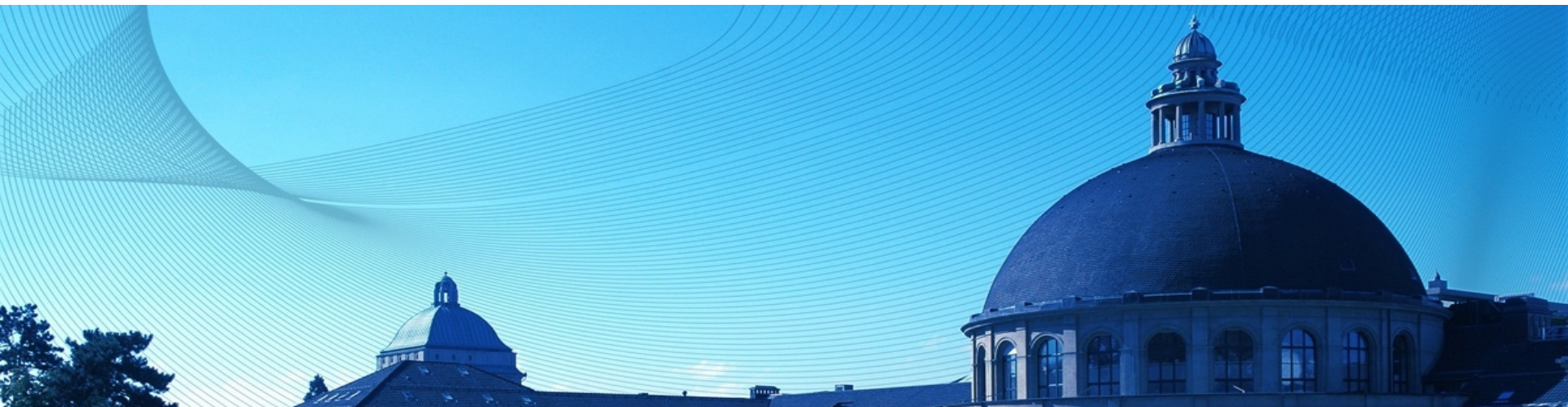

Outline

- ▶ *Future Datacenters*
- ▶ *10kV SiC MOSFET Soft-Sw. Losses*
- ▶ *Highly-Compact Isolated Gate Drive*
- ▶ *3.8kV/7kV ZVS AC/DC Converter*
- ▶ *7kV/400V ZVS DC/DC Converter*
- ▶ *Conclusions*

Future Datacenters


— *Digital Transformation* —
SST-Based MV Supply

Digital Transformation


■ Internet of Things (IoT) / Cognitive Computing

- Ubiquitous Computing / BIG DATA
- Fully Automated Manufacturing / Industry 4.0
- Autonomous Cars
- Etc.

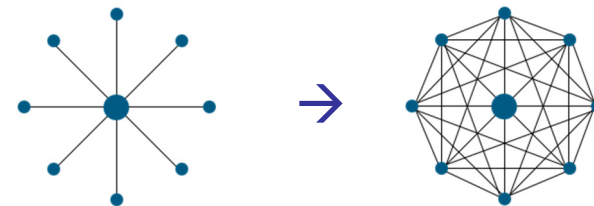
– Moving from Hub-Based to Community Concept Increases Potential Network Value Exponentially ($\sim n(n-1)$ or $\sim n \log(n)$)



Source: Intel Corp.

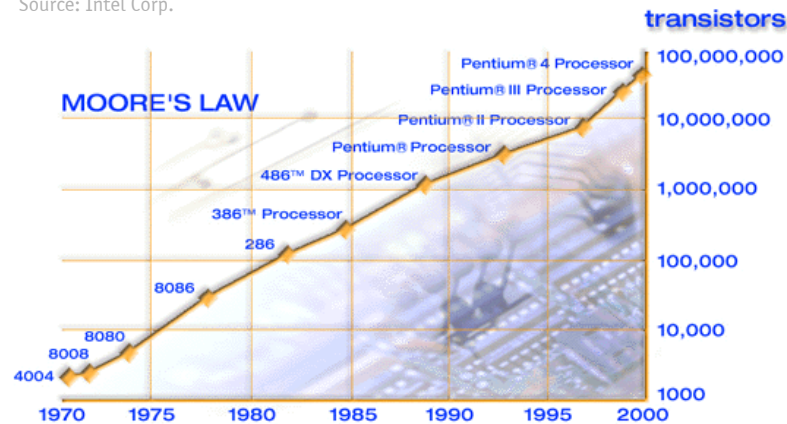

▶ Moore's Law

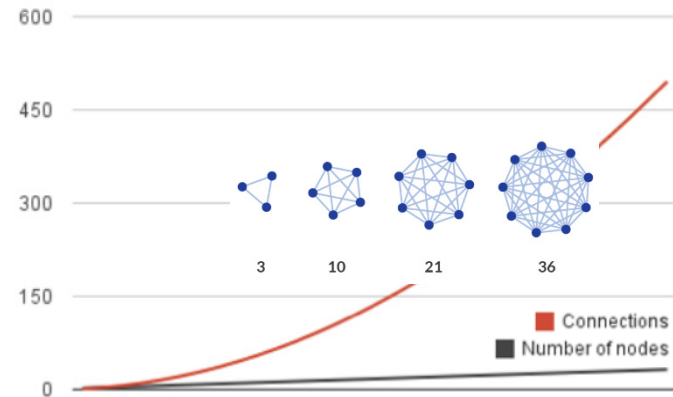


▶ Metcalfe's Law


SST-Based Datacenter 400V DC Distribution System

- Reduces Losses & Footprint
- Improves Reliability & Power Quality

— Conventional

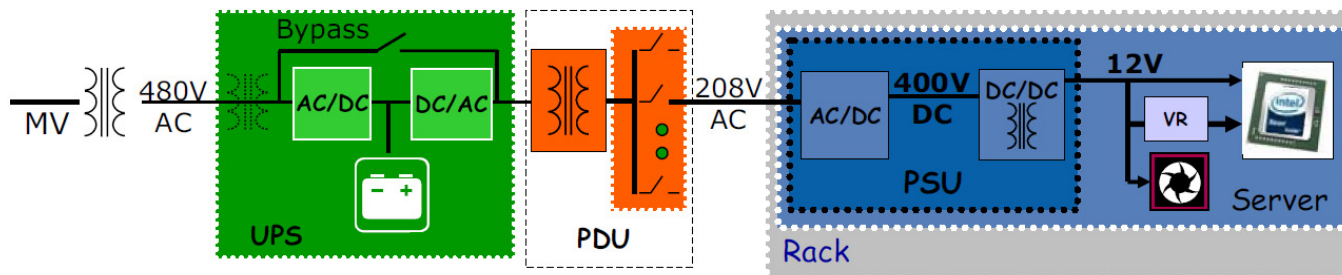

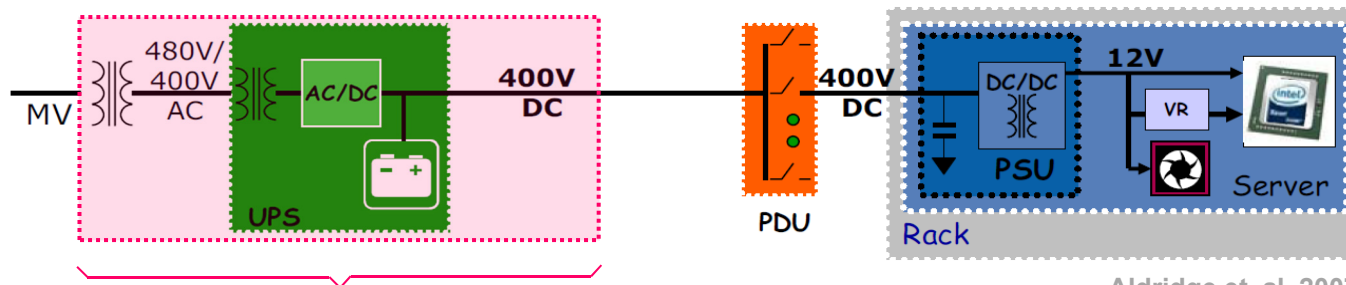— Facility-Level 400 V_{DC} Distribution → Gain in Efficiency / Complexity




Aldridge et. al. 2007

- Direct 1- Φ 3.8kV AC → 400V DC Conversion / Unidirectional SST



25kW SwiSS-Transformer

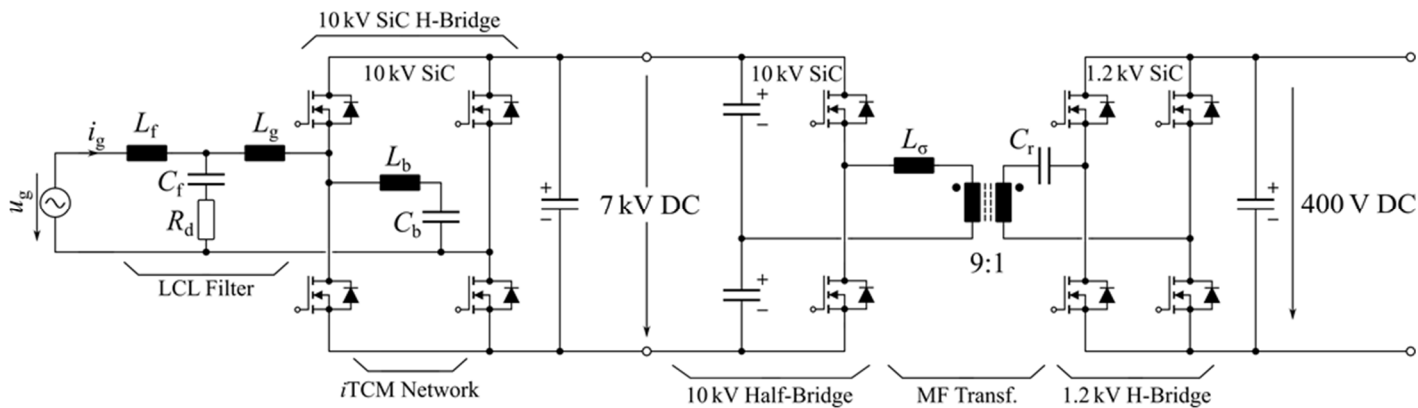- Bidirectional $1\text{-}\Phi$ $3.8\text{ kV}_{\text{rms}}$ AC \rightarrow 400 V DC Power Conversion
- Based on 10 kV SiC MOSFETs
- Full Soft-Switching



► 35...75kHz *iTCM* Input Stage

► 48kHz DC-Transformer Output Stage




10kV SiC MOSFET Soft-Switching Losses

— *Transient Calorimetric Measurement* —
Measurement Results

Trans. Calorimetric Measurement

■ Functional Principle

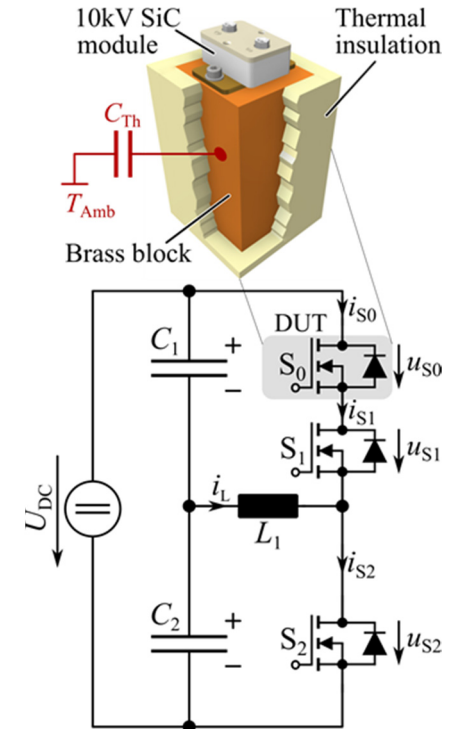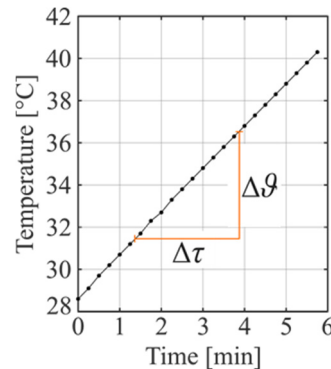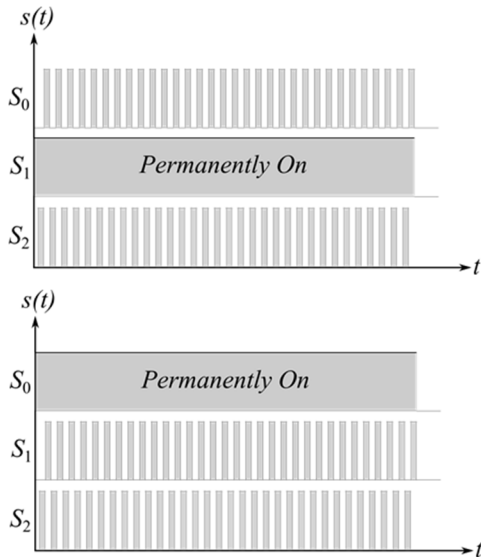- DUT on Therm. Isolated Brass Block
- Temp. Gradient Indicates Total Power Loss
- Add. Switch S_0 for Separation of Cond. & Sw. Losses
- Measurement with S_0 Switching & Cont. Turn-On





► Measurement of Cond. Losses Mandatory as $R_{DS,on}$ Depends on Drain Current

Trans. Calorimetric Measurement

■ Functional Principle

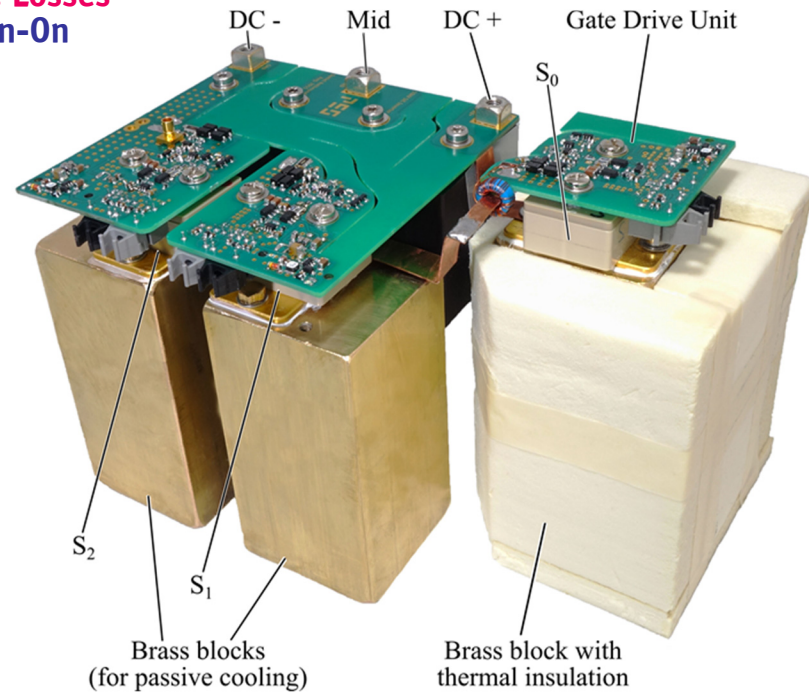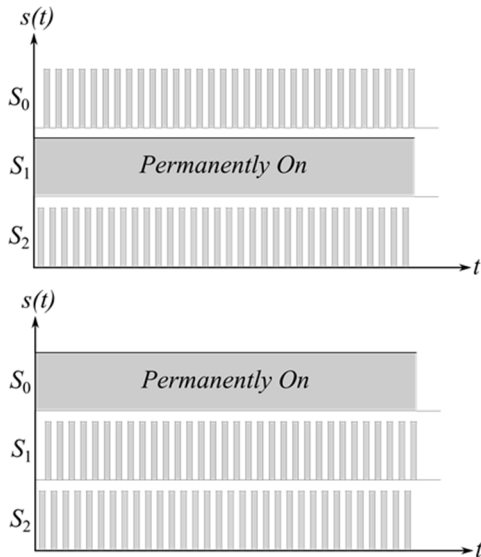- DUT on Therm. Isolated Brass Block
- Temp. Gradient Indicates Total Power Loss
- Add. Switch S_0 for Separation of Cond. & Sw. Losses
- Measurement with S_0 Switching & Cont. Turn-On






► Measurement of Cond. Losses Mandatory as $R_{DS,on}$ Depends on Drain Current

10kV SiC MOSFET Sw. Losses

■ Hard-Switching vs. Soft-Switching

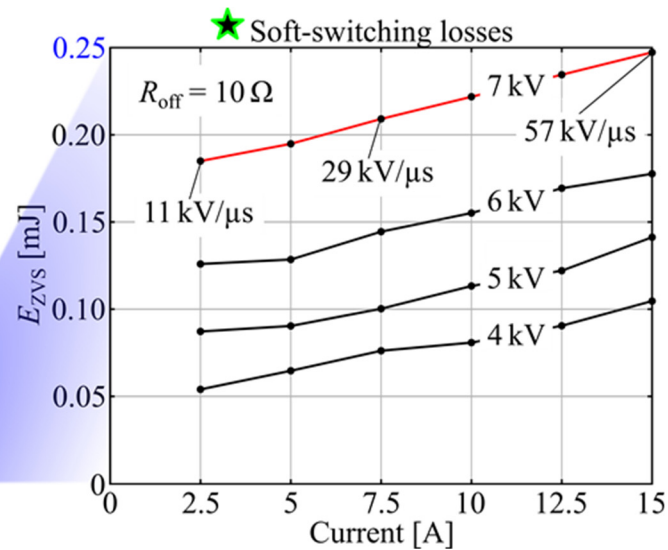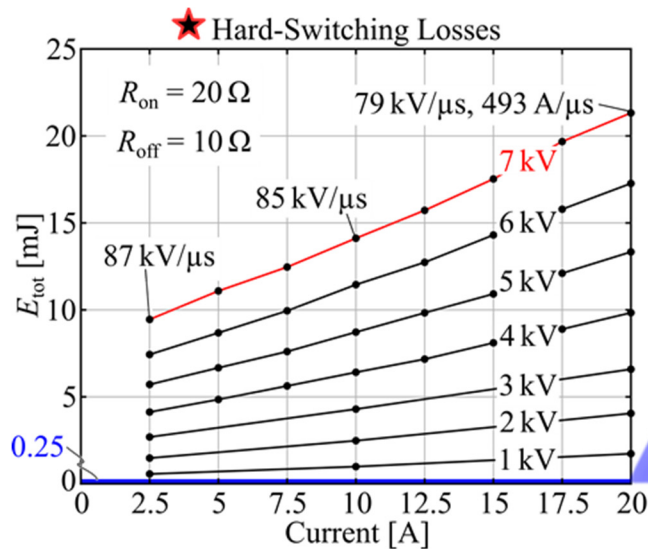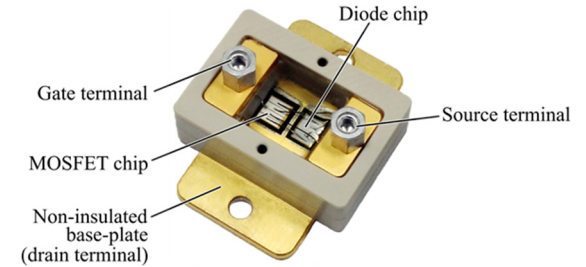- Significant Hard Sw. Losses
- **30-Times Lower Soft-Sw. Losses / lower du/dt**
- Soft-Sw. Losses Still in Range of Cond. Loss @ 50kHz



► Losses Strongly Dependent on DC-Link Voltage / Less Dependent on Current





Highly-Compact Isolated Gate Drive

*Isolated Power Supply
Ultra-Fast Overcurrent Protection*

Future All-in-One SiC Module

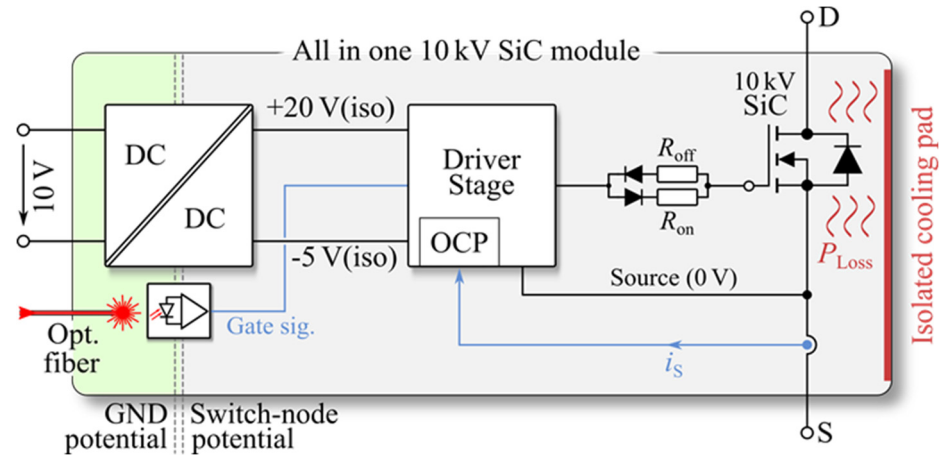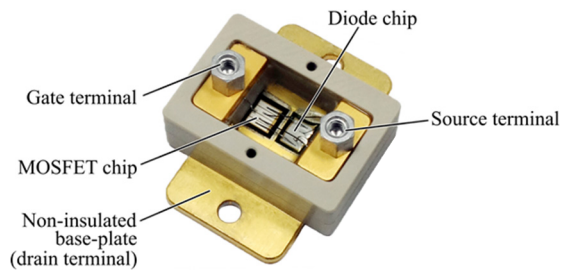- Integrated Approach
 - Integrated Isol. Signal Transmission
 - **Integrated Isol. Power Supply**
 - Integrated Driver Stage
 - Integrated Overcurrent Protection
 - Isolated Cooling Pad






► Large Dimensions of State-of-the-Art Isolation Transformers

Highly-Compact Isolated Power Supply

- Two Core Halves Separated by Isol. Material

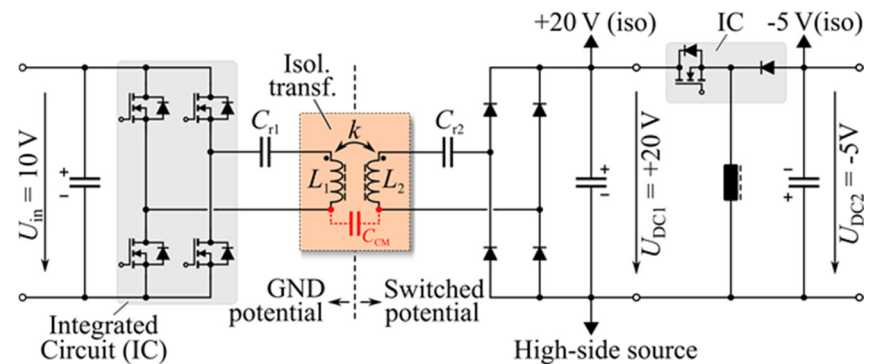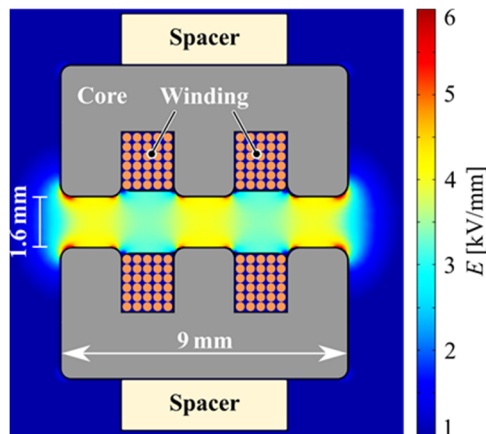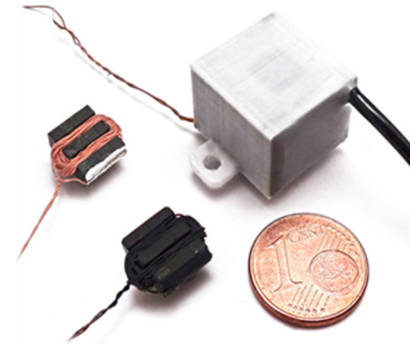- Each Core on Potential of Associated Wdg
- Potted in Silicone
- 2.6pF Coupling Cap.
- Series-Resonant DC/DC Converter





► Isolation Testing: 20kVDC for 1 Hour -- 7kV / 50...200kHz for > 50 Hours

Highly-Compact Isolated Power Supply

- Two Core Halves Separated by Isol. Material

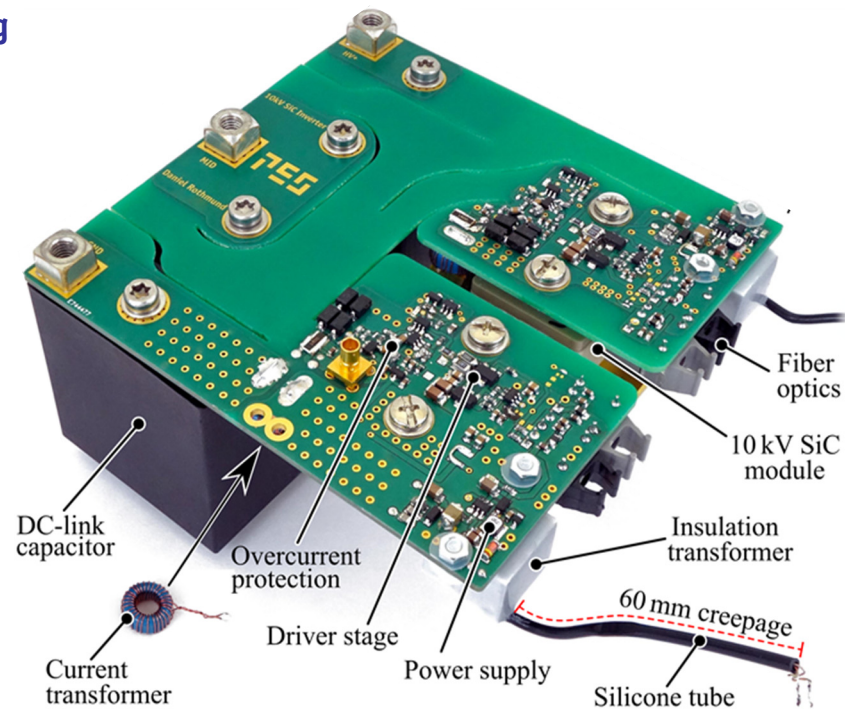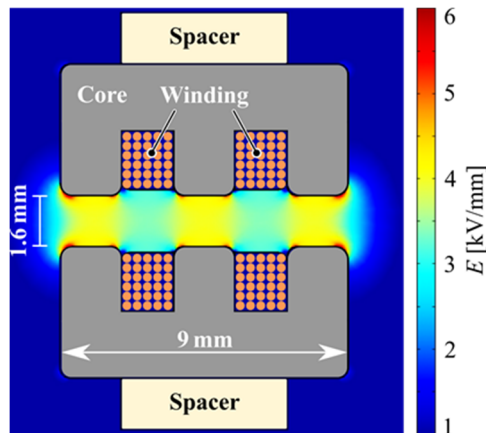
- Each Core on Potential of Associated Wdg
- Potted in Silicone
- **2.6pF Coupling Cap.**
- Series-Resonant DC/DC Converter



► **Isolation Testing:** 20kVDC for 1 Hour -- 7kV / 50...200kHz for > 50 Hours

Ultra-Fast Overcurrent Protection


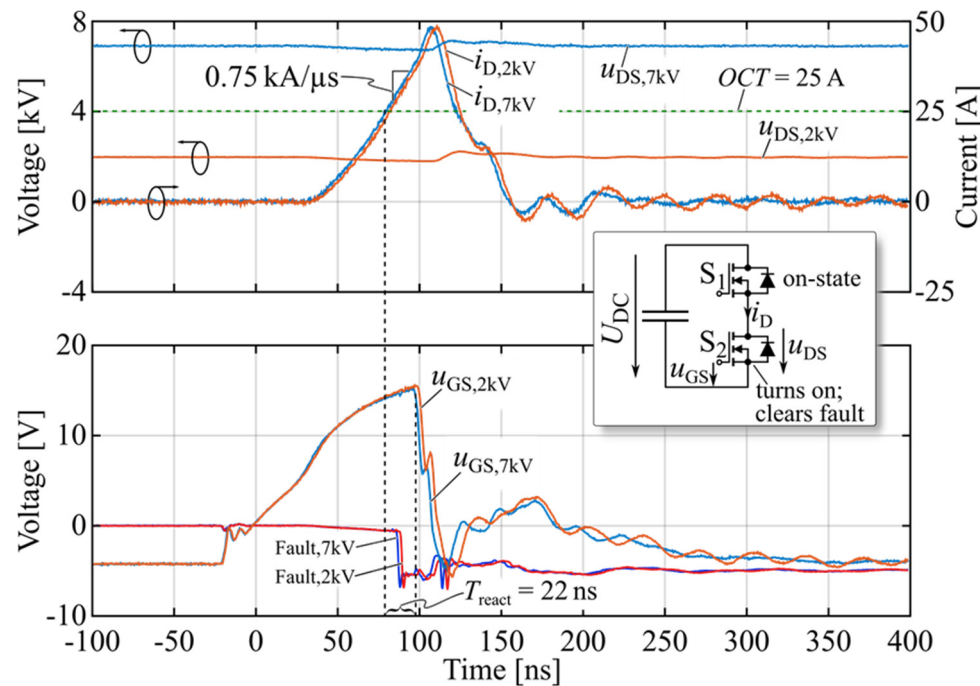
- Testing for Hard Sw. Fault & Flashover @ 7kVDC
- Current Transformer for Overcurrent Detection
- **22ns Delay** from 30A Curr. Limit Crossing to Gate Voltage Reaction



► Hard Sw. → 50A Max. Curr. / 200ns for Turn-On of Low-Side Switch @ High-Side ON

Ultra-Fast Overcurrent Protection

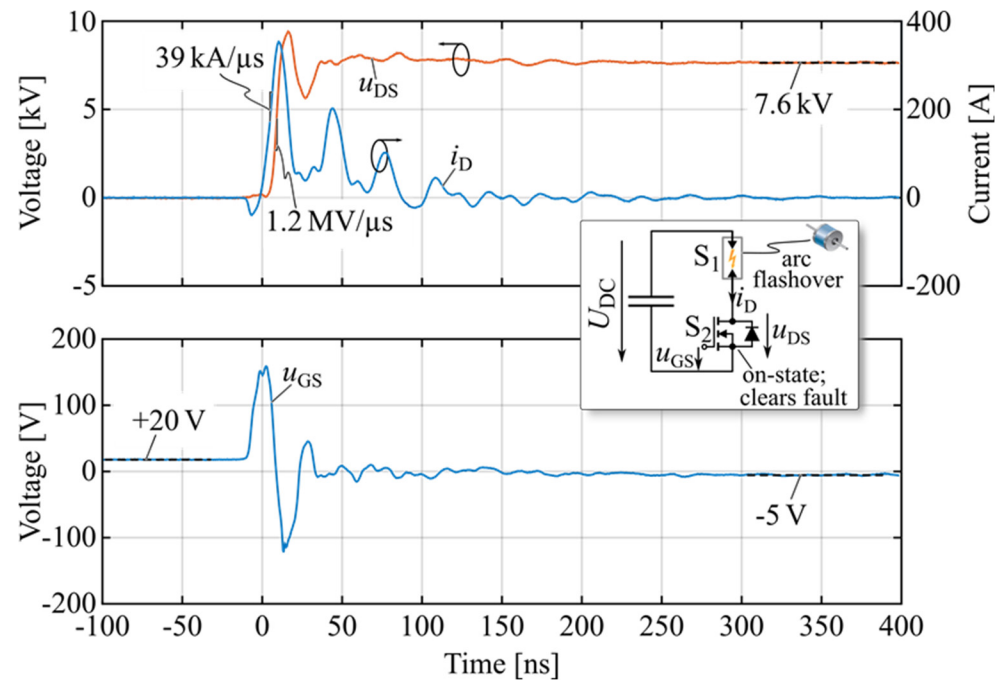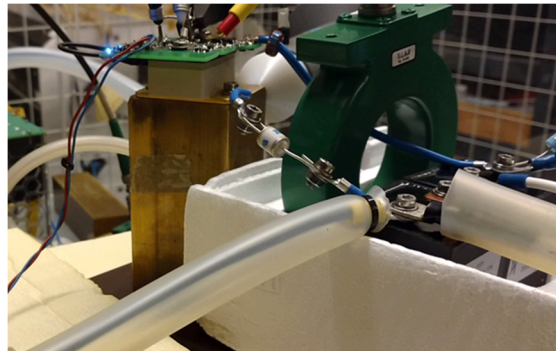- Testing for Hard Sw. Fault & Flashover @ 7kVDC
- Current Transformer for Overcurrent Detection
- **22ns Delay** from 30A Curr. Limit Crossing to Gate Voltage Reaction



► Flashover (Gas Discharge Tube) $\rightarrow du/dt = 1.2 \text{ MV}/\mu\text{s}$ - Switching 7.2kV in 6.0 ns (!)



3.8kV → 7kV ZVS AC/DC Converter

iTCM Operation
EMI Filter / Cable Resonances
Efficiency Measurement

iTCM – integrated Triang. Current Mode

■ Full-Bridge iTCM Operation Enables ZVS

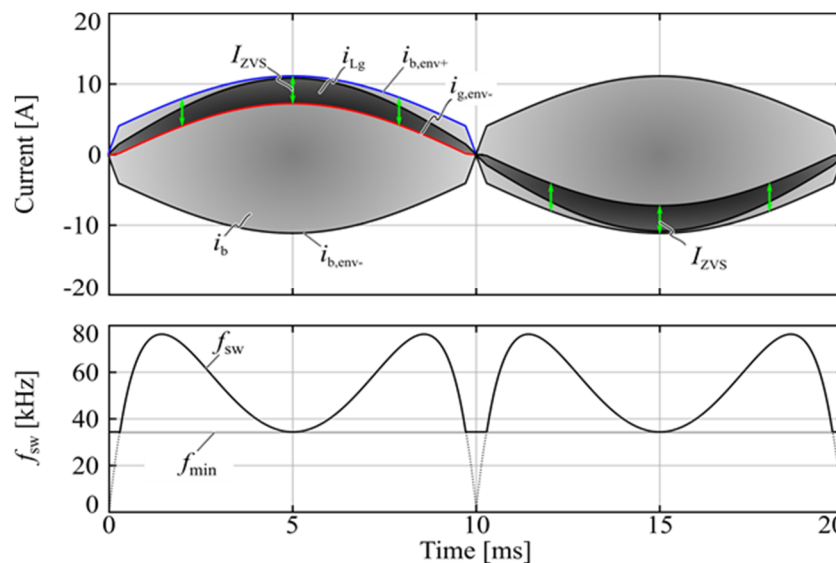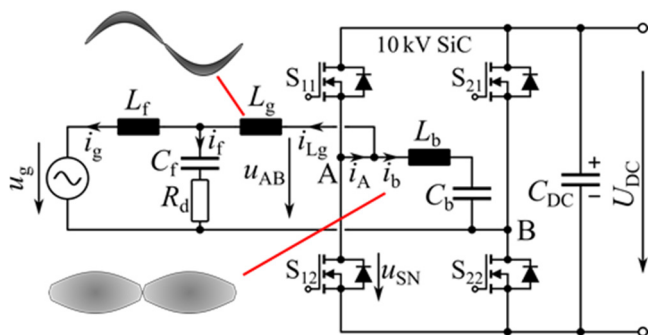- ZVS Requires Change of Sw. Current Direction in Each Sw. Period
- Open-Loop Variation of Sw. Frequency for Const. ZVS Current (35...75kHz)
- Separate Optim. of ZVS and Input Inductor Possible
- No Large Ripple Input Current





► Smooth Zero-Crossing of the Grid Current

iTCM – integrated Triang. Current Mode

- *Full-Bridge iTCM Operation Enables ZVS*

- ZVS Requires Change of Sw. Current Direction in Each Sw. Period
- **Open-Loop Variation of Sw. Frequency for Const. ZVS Current (35...75kHz)**
- Separate Optim. of ZVS and Input Inductor Possible
- No Large Ripple Input Current

★ 3.3 kW/dm³

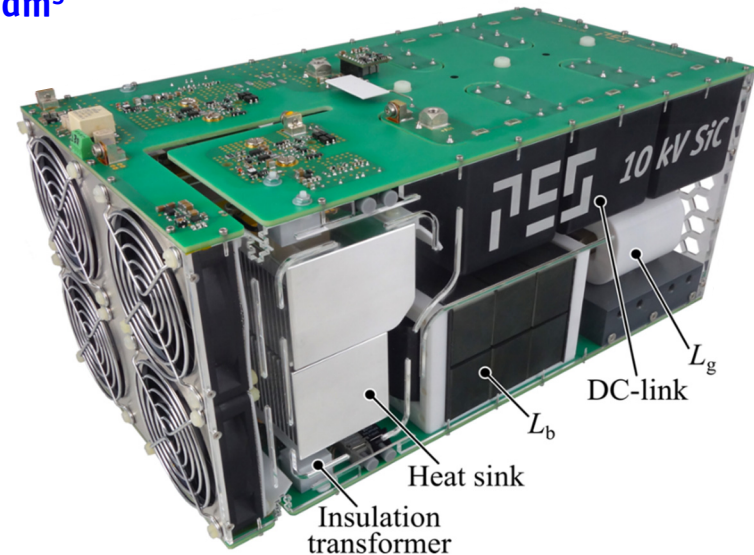
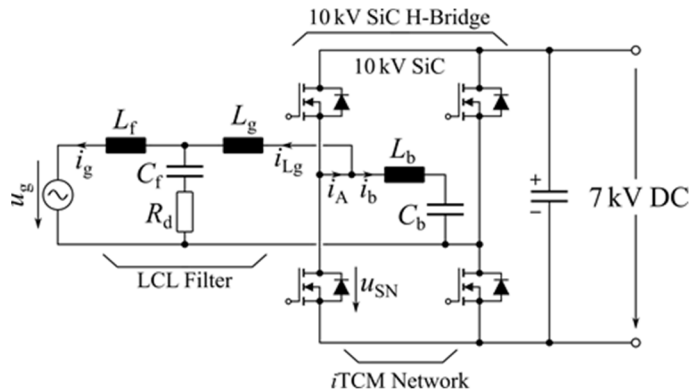


- ▶ **Smooth Zero-Crossing of the Grid Current**

iTCM – integrated Triang. Current Mode

■ Full-Bridge iTCM Operation Enables ZVS

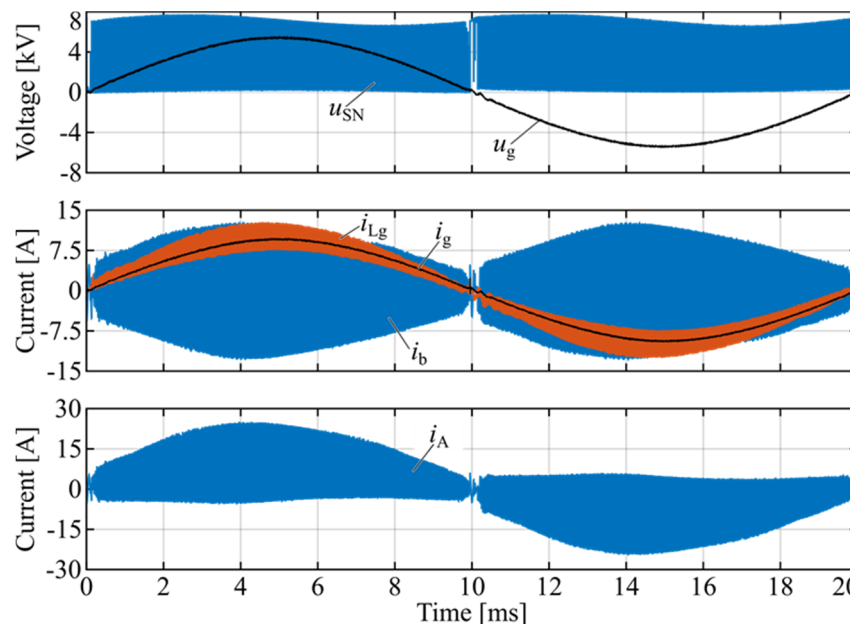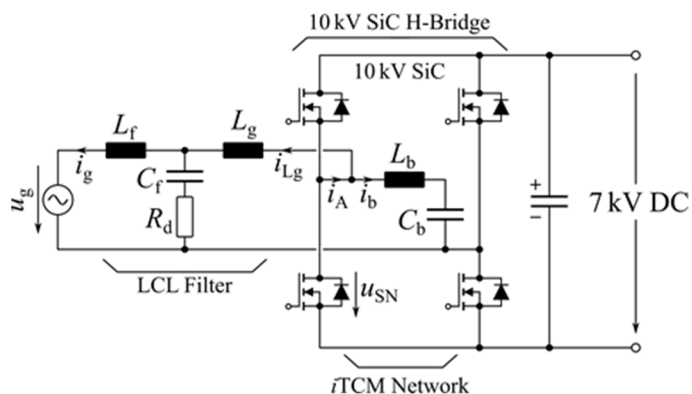
- ZVS Requires Change of Sw. Current Direction in Each Sw. Period
- Open-Loop Variation of Sw. Frequency for Const. ZVS Current (35...75kHz)
- Separate Optim. of ZVS and Input Inductor Possible
- No Large Ripple Input Current



► Full-Load Measurement (25kW @ 3.8kVrms AC, 7kV DC) - ZVS Over Full AC Cycle (!)

EMI Input Filter

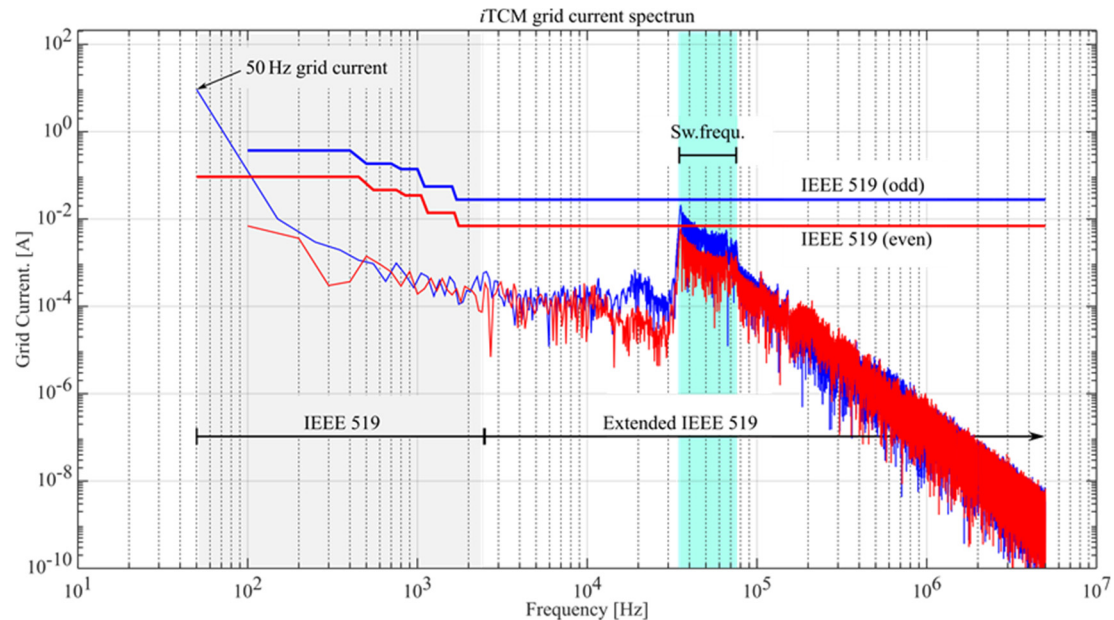- *LCL-Filter & Damping of Supply Cable Resonances*
- IEEE 519 and BDEW Harmonic Standards
- **No Standards Above 9kHz → Extension of IEEE 519 to Higher Frequ.**
- Design for Mains Current THD < 1%
- Low Losses of Damping Branch





► **iTCM Grid Current Spectrum**

EMI Input Filter

LCL-Filter & Damping of Supply Cable Resonances

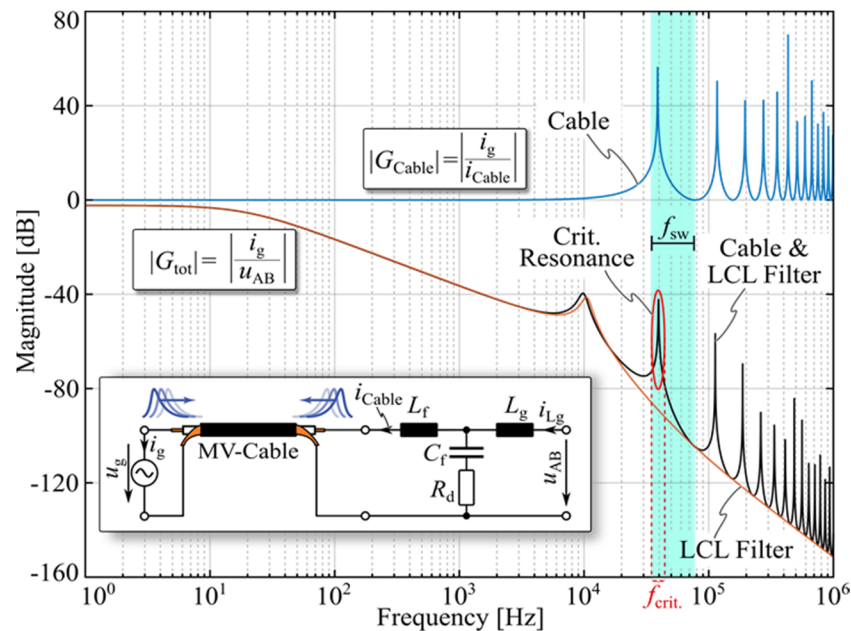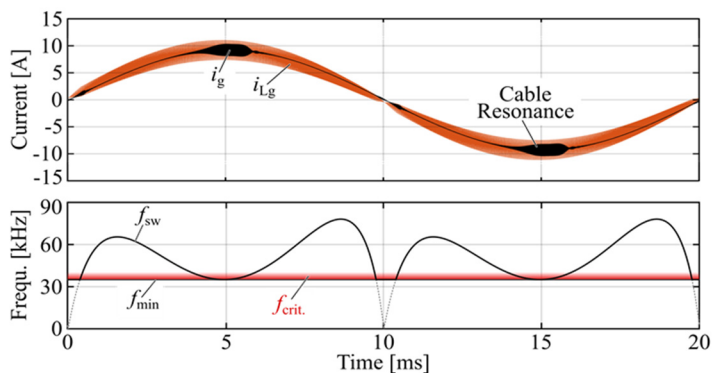- IEEE 519 and BDEW Harmonic Standards
- No Standards Above 9kHz → Extension of IEEE 519 to Higher Frequ.
- Design for Mains Current THD < 1%
- Low Losses of Damping Branch





► Undamped Operation

EMI Input Filter

LCL-Filter & Damping of Supply Cable Resonances

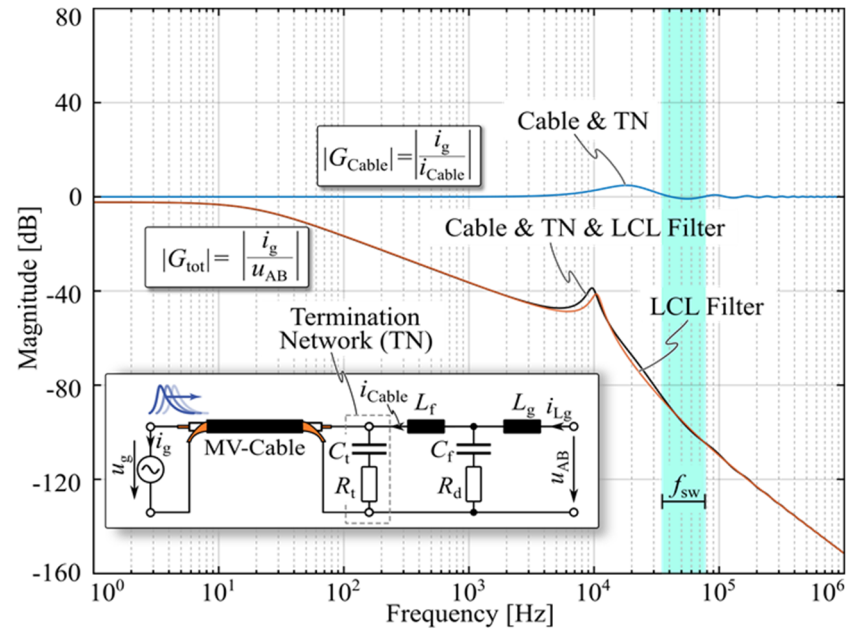
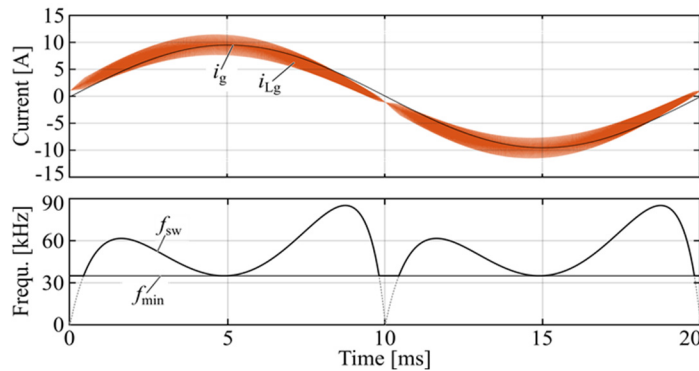
- IEEE 519 and BDEW Harmonic Standards
- No Standards Above 9kHz → Extension of IEEE 519 to Higher Frequ.
- Design for Mains Current THD < 1%
- Low Losses of Damping Branch



► Operation with Damping Branch → Clean Grid Current

Efficiency & Loss Distribution

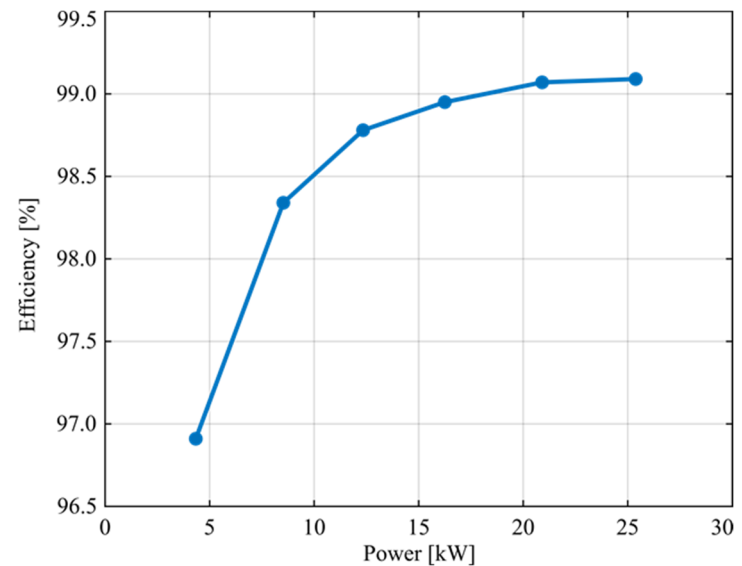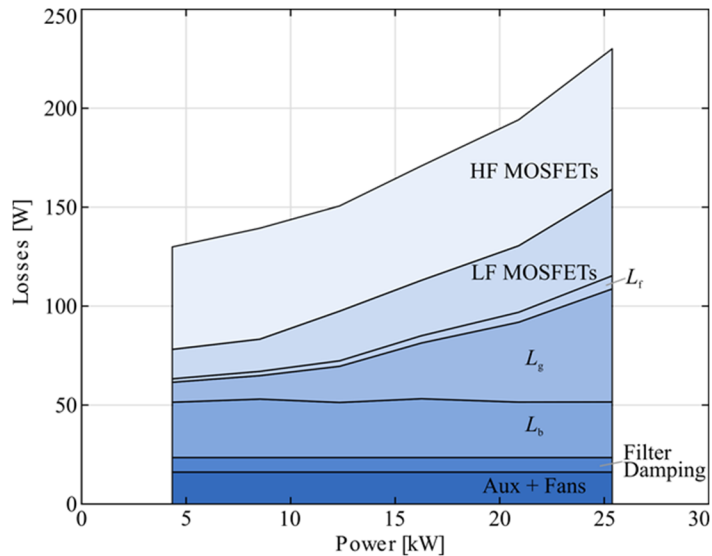- 99.1% Efficiency @ 25kW
- Low Sw. Losses Despite 35...75kHz Sw. Frequency
- Efficiency >98.75% Above 50% Rated Power



► Loss Distribution

► Efficiency



7kV → 400V ZVS Isolated DC/DC Converter

MV-Side 10kV SiC Half-Bridge
LV-Side 1.2kV SiC Full-Bridge
MF-Transformer
Waveforms & Efficiency

10kV SiC-Based DC/DC Converter

■ MV-Side Half-Bridge


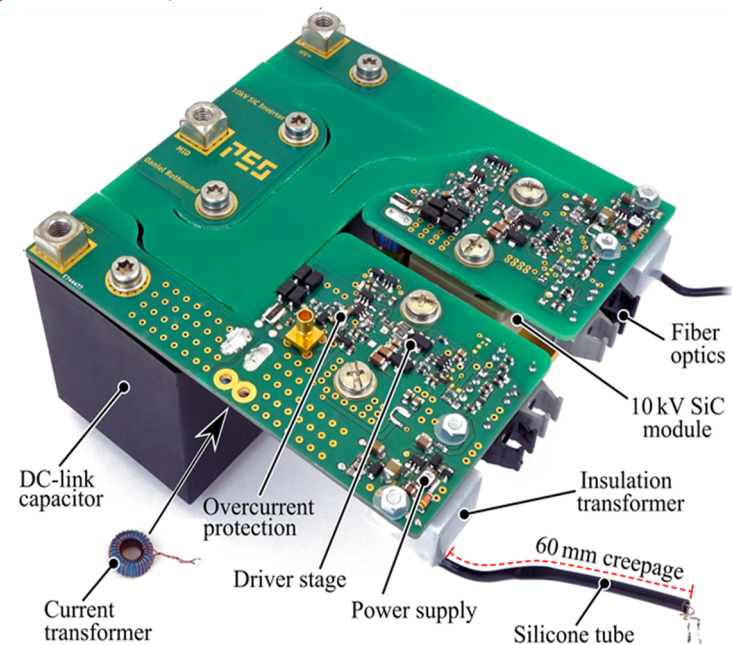
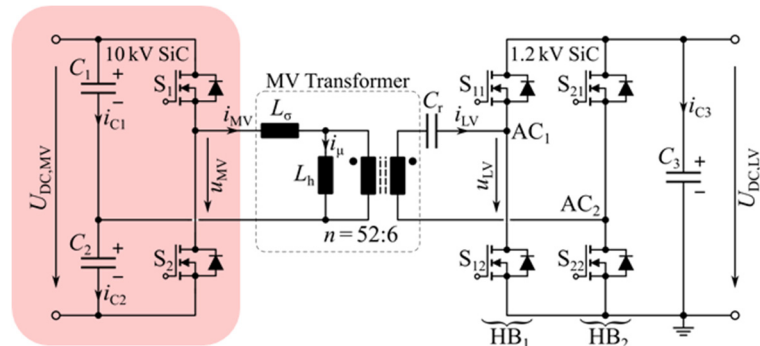
- 48kHz Sw. Frequency, ZVS
- Cooling of Power Semicond. by Floating Heatsinks (Not Shown)
- Creepage Distances Ensured by PCB Slots



► Half-Bridge for Cutting Voltage in Half / Lower Switch Count

10kV SiC-Based DC/DC Converter

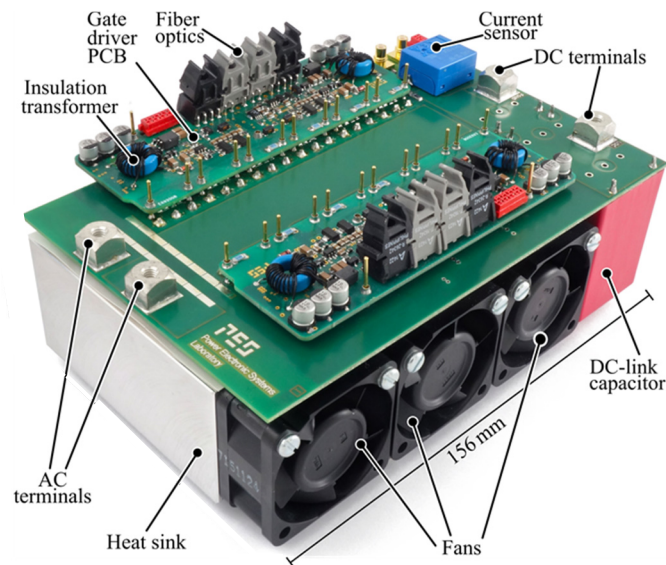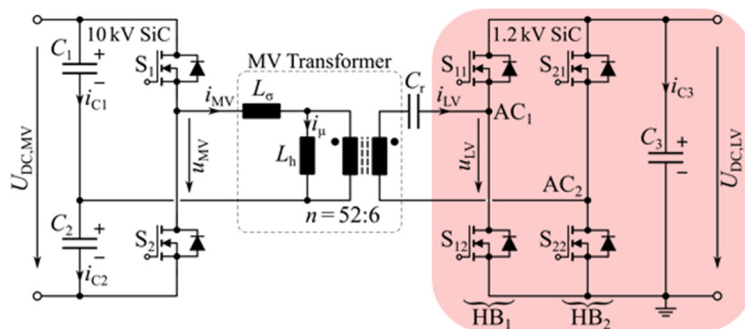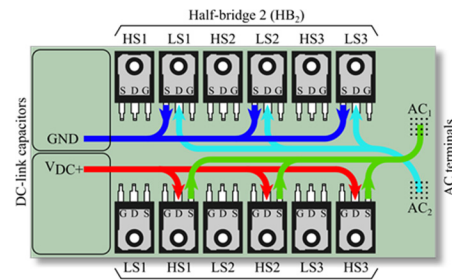- **LV-Side Full-Bridge**
- 48kHz Sw. Frequency, ZVS
- **3x1.2kV 25mΩ MOSFETs in Parallel**
- **Layout Ensures Symm. Curr. Distribution**





► **1.2kV Technology Used Due to Low On-Resistance**

10kV SiC-Based DC/DC Converter

MF-Transformer

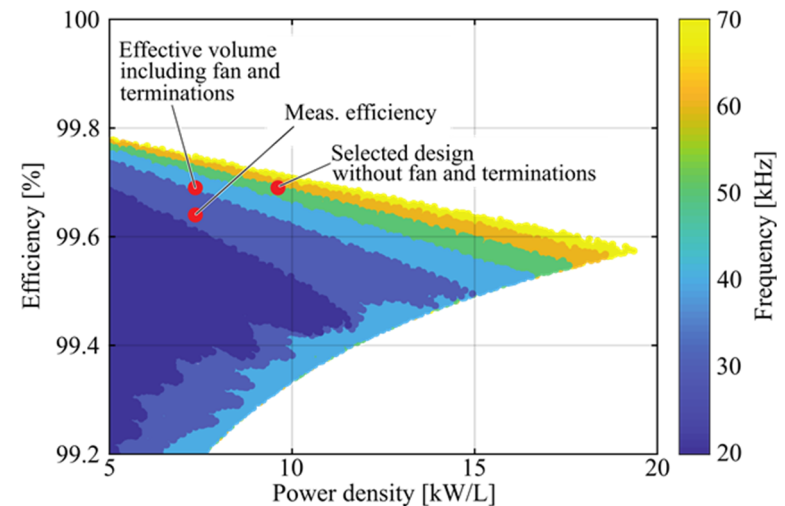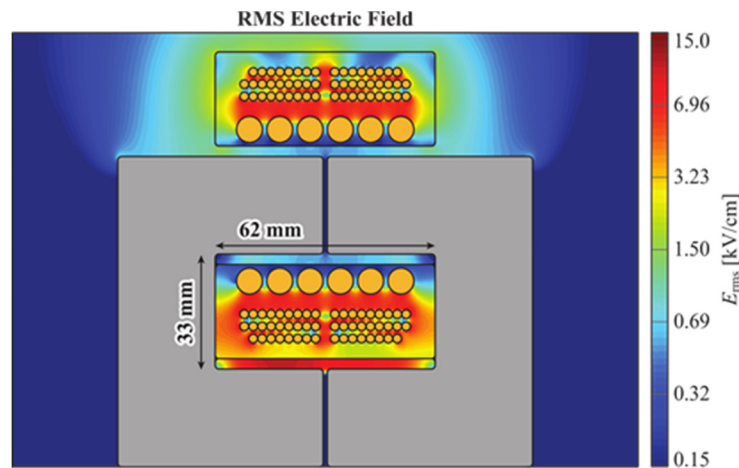- 25kW/31kVA @ 48kHz
- 15kV DM/CM Isolation
- Pareto-Optimization (# of Layers, # of Turns, E/U-Core, etc.)
- Ferrite U-Core, 71um/100um MV/LV Wdg
- 2-Chamber MV Wdg, 3 Layers





► Challenges: High El. Fields / Heat Transfer Through Insulation Material

10kV SiC-Based DC/DC Converter

■ MF-Transformer Construction

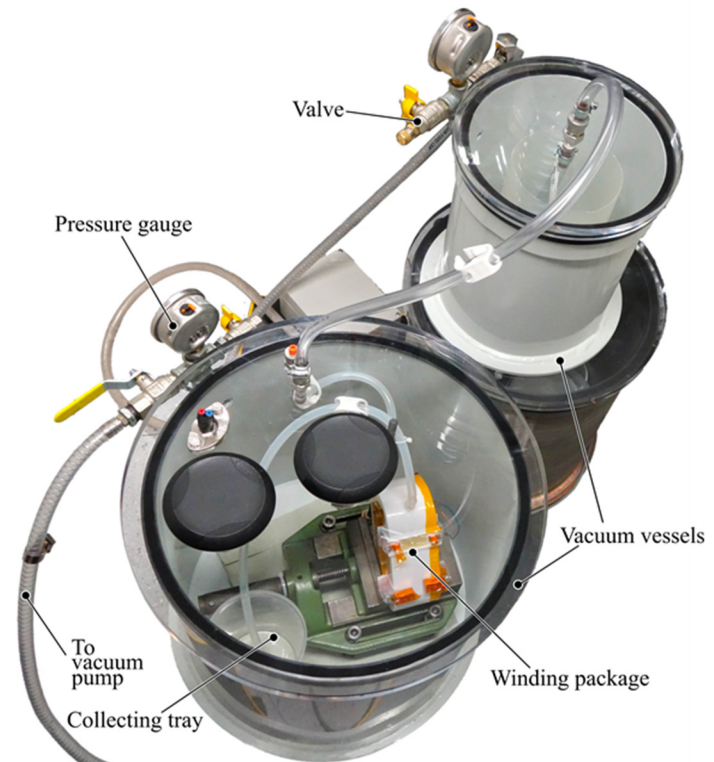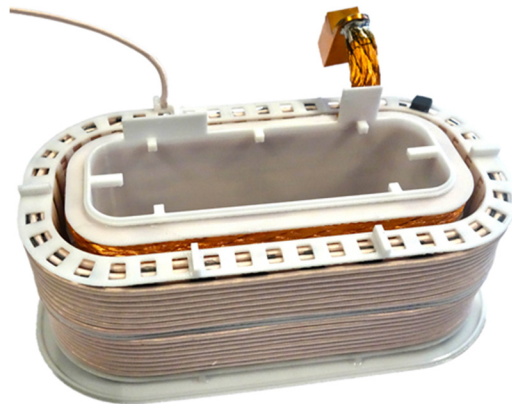- LV-Wdg Inside MV-Wdg
- Precise Positioning of Wdgs Mandatory
- Ensures MV/LV-Wdg Isolation





► Challenges: Processing Silicone Under Vacuum Avoiding Voids / Curing / etc.

10kV SiC-Based DC/DC Converter

MF-Transformer Measurement

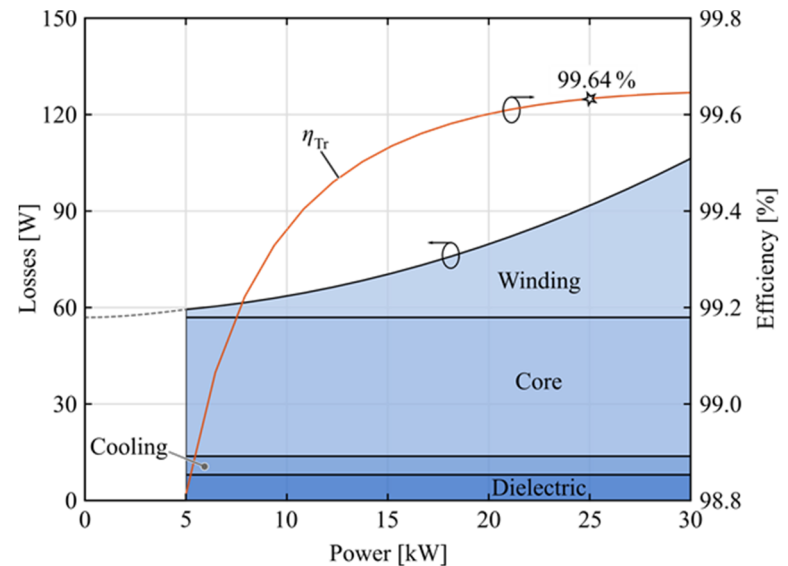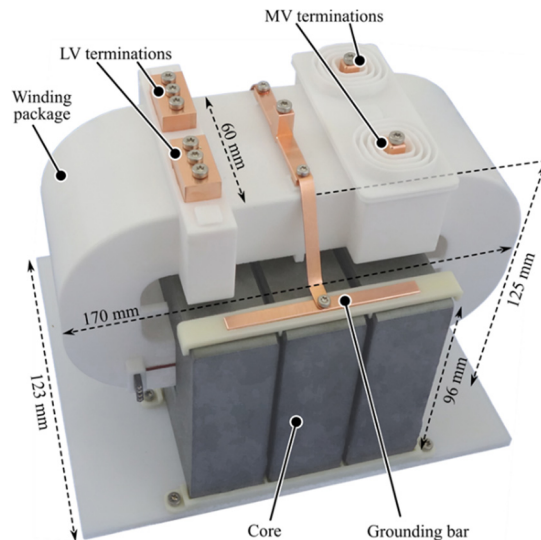- Fully Tested @ 25kW / 7 kV
- Calorimetric Loss Measurement
- **99.64% Efficiency**




► Transformer Prototype / Loss Distribution / Efficiency

10kV SiC-Based DC/DC Converter



Experimental Results

- 400V → 7kV Operation @ 25kW / 48 kHz
- ZVS of All MOSFETs Independent of Load

★ 3.8 kW/dm³

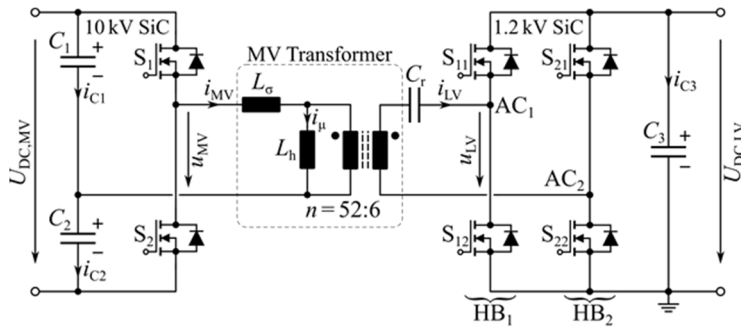


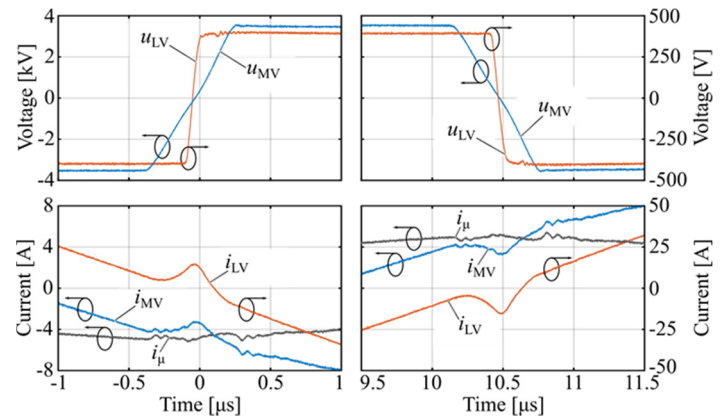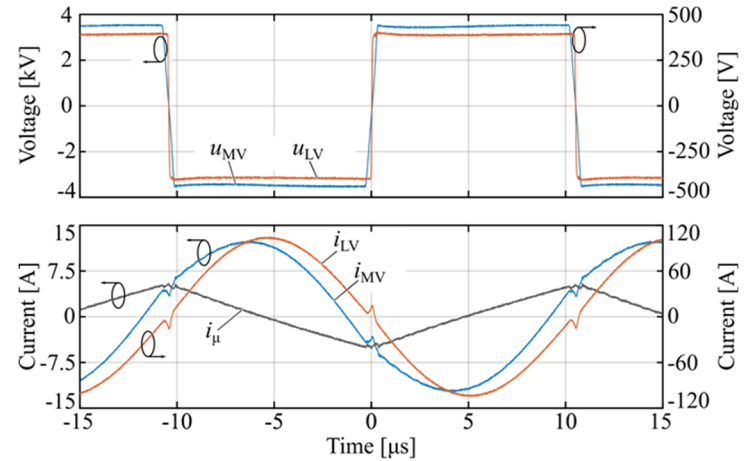► Very Robust Concerning Changes in Sw. Freq. or Component Values




Efficiency & Loss Distribution

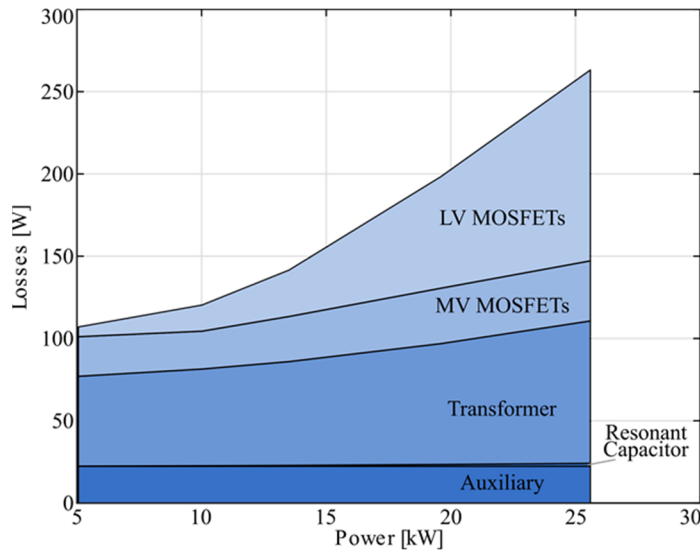- 99% Efficiency for $P > 13\text{kW}$
- LV-MOSFETs Causing Substantial Losses @ Higher Power
- Efficiency Improvement for Larger SiC Area



► Loss Distribution


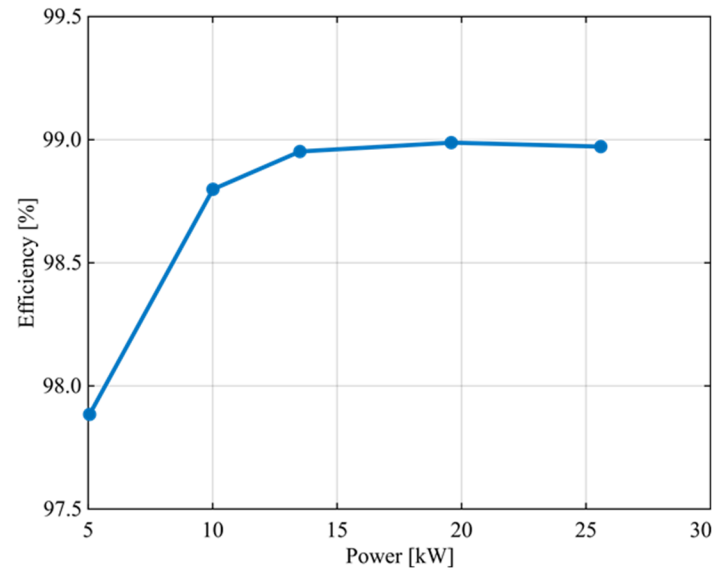


► Efficiency

— Conclusions —

Remark 1- Φ 2.4 kV_{rms} AC \rightarrow 54V DC

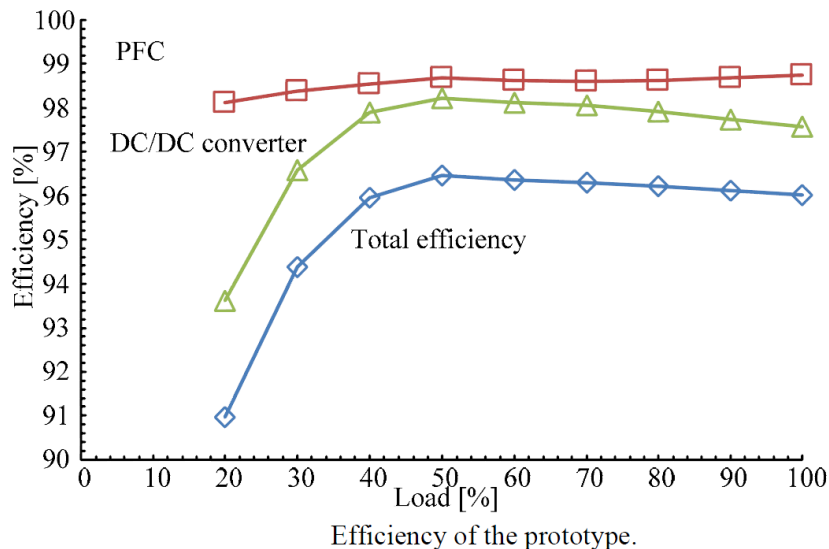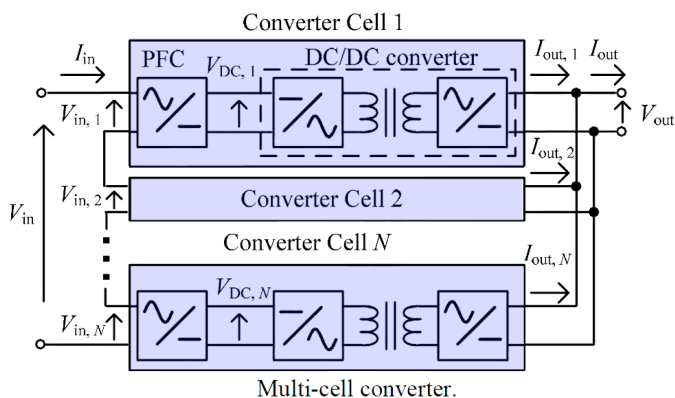
- **Published @ IEEE APEC 2017**
- **N=5 Series-Connected Cells @ MV-Side / Cost Optimum**
- **Module Input Stage \rightarrow Boost PFC Half Contr. Thyr. Rect. / 1.2kV IGBTs & SiC Diodes**
- **Module Output Stage \rightarrow 3-Level DC/DC Conv. - 600V SJ & 100V MOSFETs**



- ▶ **Power Density of 0.4kW/dm³ (6.6W/in³)**
- ▶ **96% Overall Efficiency @ 25kW**

Conclusions -- Overall Performance

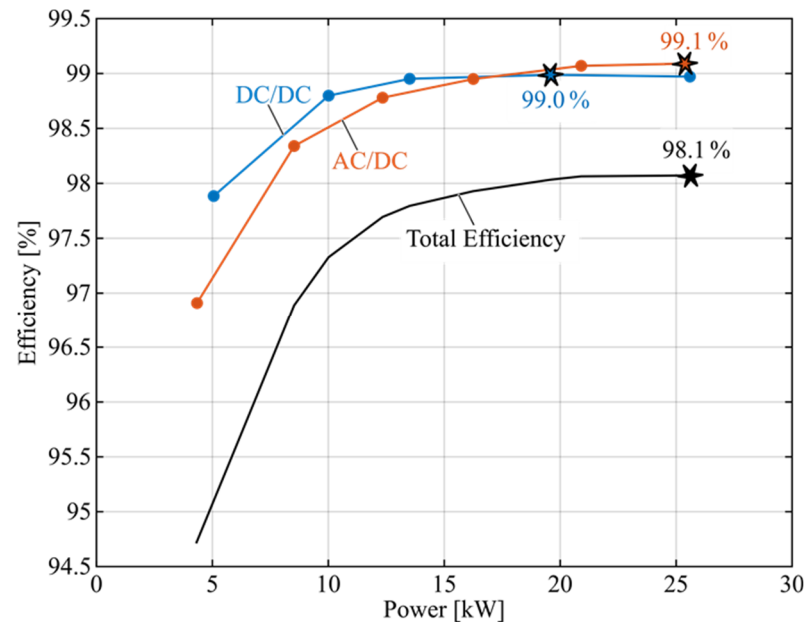- Full Soft-Switching
- 98.1% Overall Efficiency @ 25kW
- 1.8 kW/dm³ (30W/in³)



- ▶ Red. of Losses & Volume by Factor of > 2 Comp. To Alternative Approaches (!)
- ▶ Significantly Simpler System Structure Compared to Multi-Module SST Approach



■ End

Questions ?

