

The Essence of Solid-State Transformers

J. W. Kolar & J. E. Huber



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Outline

- ▶ Transformer Basics
- ▶ Power Transmission Basics
- ▶ Solid-State Transformer (SST) Motivation
- ▶ SST Concept
- ▶ Key SST Realization Challenges
 - #1 Power Semiconductors
 - #2 Topologies
 - #3 Medium Frequency Transformer
 - #4 Protection
 - #5 Availability
- ▶ Industry Demonstrator Systems
- ▶ Potential Future Applications
- ▶ Conclusions

D. Bortis
Th. Guillod
F. Krismer
G. Ortiz

Acknowledgement: D. Rothmund

Transformer Basics

History
Scaling Laws
— *Efficiency / Power Density Trade-off* —



► Classical Transformer (XFMR) – History (1)

- * 1830 - Henry/Faraday
- * 1878 - Ganz Company (Hungary)
- * 1880 - Ferranti
- * 1882 - Gaulard & Gibbs
- * 1884 - Blathy/Zipernowski/Deri

- Property of Induction
- Toroidal Transformer (AC Incandescent Syst.)
- Early Transformer
- Linear Shape XFMR (1884, 2kV, 40km)
- Toroidal XFMR (inverse type)

Europe

USA

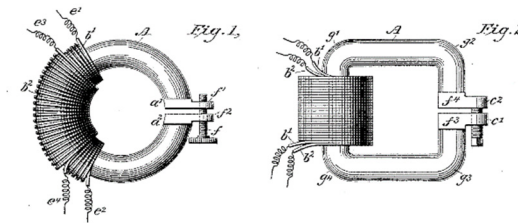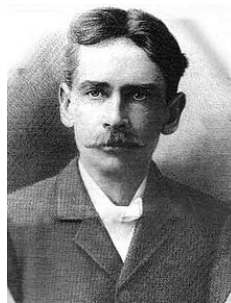

Patented Sept. 21, 1886.

No. 349,611.

W. STANLEY, Jr.
INDUCTION COIL.



- * 1885 - Stanley & (Westinghouse)

- Easy Manufact. XFMR (1st Full AC Distr. Syst.)

▶ Classical Transformer – History (2)



UNITED STATES PATENT OFFICE.

MICHAEL VON DOLIVO-DOBROWOLSKY, OF BERLIN, GERMANY, ASSIGNOR TO
THE ALLGEMEINE ELEKTRICITÄTS-GESELLSCHAFT, OF SAME PLACE.

ELECTRICAL INDUCTION APPARATUS OR TRANSFORMER.


SPECIFICATION forming part of Letters Patent No. 422,746, dated March 4, 1890.

Application filed January 8, 1890. Serial No. 336,290. (No model.)

- * 1889
- * 1891

- Dobrowolski → 3-Phase Transformer
- 1st Complete AC System (Gen.+XFMR+Transm.+El. Motor+Lamps, 40Hz, 25kV, 175km)

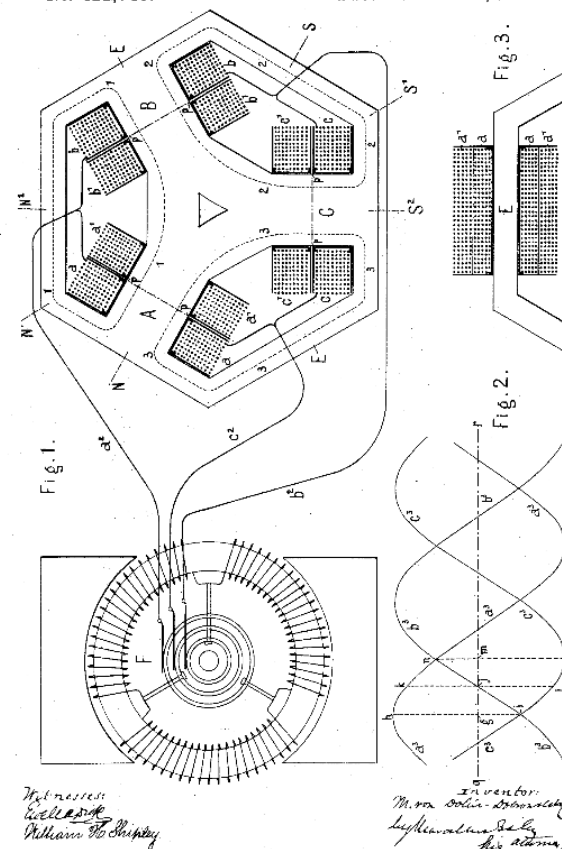(No Model.)
M. VON DOLIVO-DOBROWOLSKY.
ELECTRICAL INDUCTION APPARATUS OR TRANSFORMER.
No. 422,746. Patented Mar. 4, 1890.



Witnesses:
E. J. ...
William H. Shipley

Inventor:
M. von Dolivo-Dobrowolsky
by ...
his attorney.

► Classical Transformer – Basics (1)

- Magnetic Core Material * Silicon Steel / Nanocrystalline / Amorphous / Ferrite
- Winding Material * Copper or Aluminium
- Insulation/Cooling * Mineral Oil or Dry-Type

- Operating Frequency * 50/60Hz (El. Grid, Traction) or $16\frac{2}{3}$ Hz (Traction)
- Operating Voltage * 10kV or 20 kV (6...35kV)
- * 15kV or 25kV (Traction)
- * 400V



- Voltage Transf. Ratio * Fixed
- Current Transf. Ratio * Fixed
- Active Power Transf. * Fixed ($P_1 \approx P_2$)
- React. Power Transf. * Fixed ($Q_1 \approx Q_2$)
- Frequency Ratio * Fixed ($f_1 = f_2$)

- Magnetic Core Cross Section

$$A_{Core} = \frac{1}{\sqrt{2\pi}} \frac{U_1}{\hat{B}_{max} f N_1} \frac{1}{N_1}$$

- Winding Window
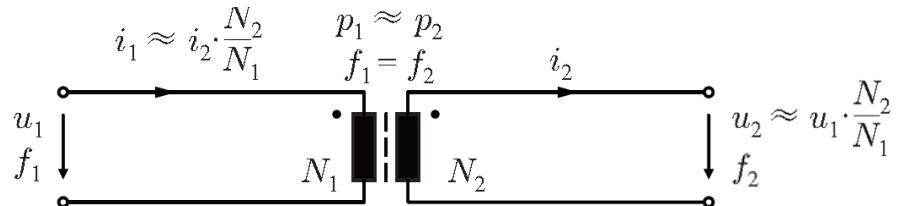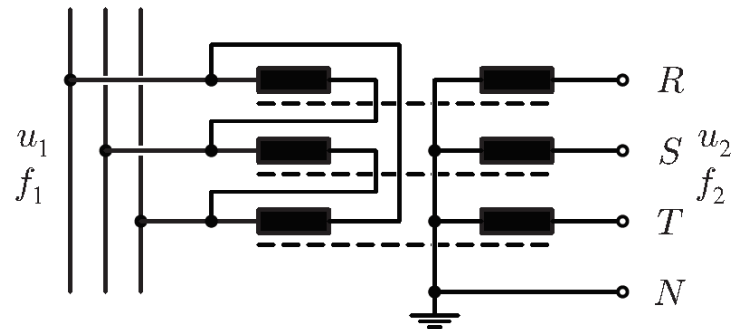
$$A_{Wdg} = \frac{2I_1}{k_W J_{rms}} N_1$$



► Classical Transformer – Basics (2)

Source: www.faceofmalawi.com



■ Advantages

- Relatively Inexpensive
- **Highly Robust / Reliable**
- Highly Efficient
- Short Circuit Current Limitation

► Classical Transformer – Basics (3)

■ Advantages

- Relatively Inexpensive
- Highly Robust / Reliable
- Highly Efficient (98.5%...99.5% Dep. on Power Rating)
- Short Circuit Current Limitation

■ Weaknesses

- Voltage Drop Under Load
- Losses at No Load
- Not Directly Controllable
- Dependency of Weight / Volume on Frequency
- Sensitivity to DC Offset Load Imbalances
- Sensitivity to Harmonics


• Construction Volume

P_t Rated Power
 k_W Window Utilization Factor
 B_{max} .. Flux Density Amplitude
 J_{rms} ... Winding Current Density
 f Frequency

$$A_{Core} A_{Wdg} = \frac{\sqrt{2}}{\pi} \frac{P_t}{k_W J_{rms} \hat{B}_{max} f} \sim L^4$$

↑ ↑ ↑

- Low Frequency → Large Weight / Volume

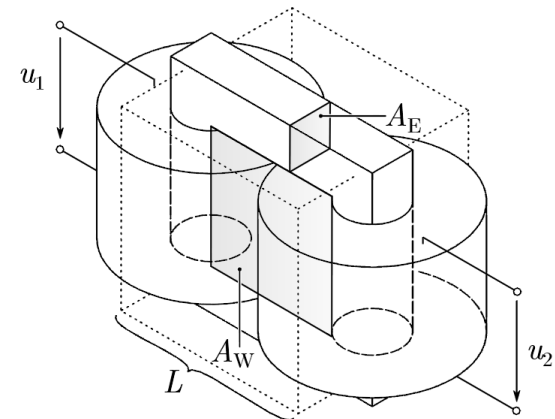

► Classical Transformer – Basics (4)

■ Advantages

- Relatively Inexpensive
- Highly Robust / Reliable
- Highly Efficient (98.5%...99.5% Dep. on Power Rating)
- Short Circuit Current Limitation

■ Weaknesses

- Voltage Drop Under Load
- Losses at No Load
- Not Directly Controllable
- Dependency of Weight / Volume on Frequency
- Sensitivity to DC Offset Load Imbalances
- Sensitivity to Harmonics

• Construction Volume


P_t Rated Power
 k_W Window Utilization Factor
 B_{\max} .. Flux Density Amplitude
 J_{rms} ... Winding Current Density
 f Frequency

$$A_{\text{Core}} A_{\text{Wdg}} = \frac{\sqrt{2}}{\pi} \frac{P_t}{k_W J_{\text{rms}} \hat{B}_{\max} f}$$

↑ ↑ ↑

- Low Frequency → Large Weight / Volume

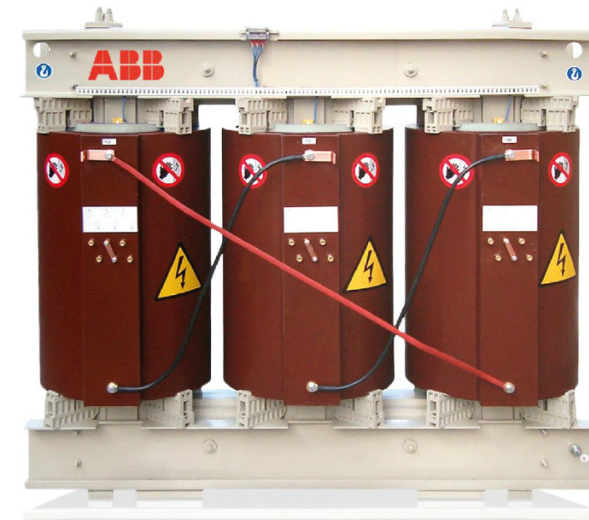Vacuum Cast Coil Dry-Type
Distribution Transformer



1 MVA – 12kV/400V @ 2600kg
0.2%/1% Losses @ No/Rated Load

► Classical Transformer – Basics (5)



■ Construction Volume

$$A_{Core} A_{Wdg} = \frac{\sqrt{2}}{\pi} \frac{P_t}{k_W J_{rms} \hat{B}_{max} f}$$




- P_t Rated Power
- k_W Window Utilization Factor
- \hat{B}_{max} .. Flux Density Amplitude
- J_{rms} ... Winding Current Density
- f Frequency

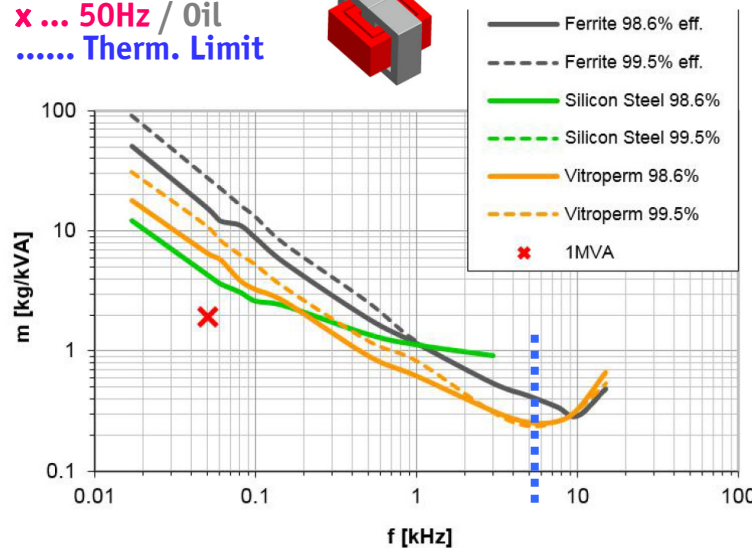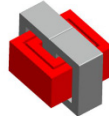180kVA
 Weight-Optimized
 Air-Cooled / Insulation
 Forced Convection
 x ... 50Hz / Oil
 Therm. Limit



Source: ABB/Drofenik


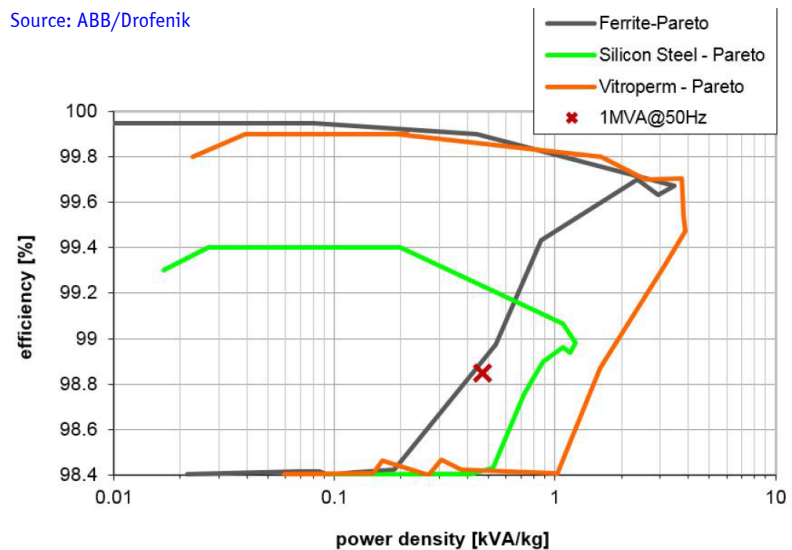


■ Higher Frequency → Lower Weight / Volume



■ Higher Volume → Higher Efficiency

► AC vs. DC Power Transmission (1)

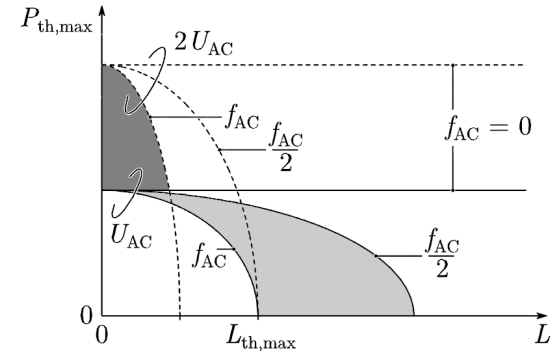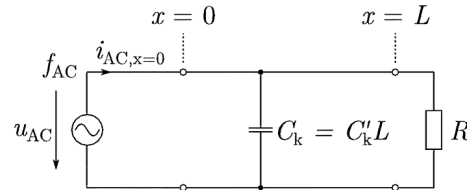■ AC Cable – Thermal Limit Due to Cap. Current @ $L = 0$



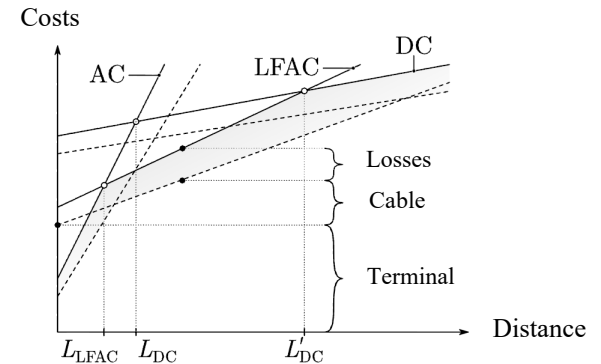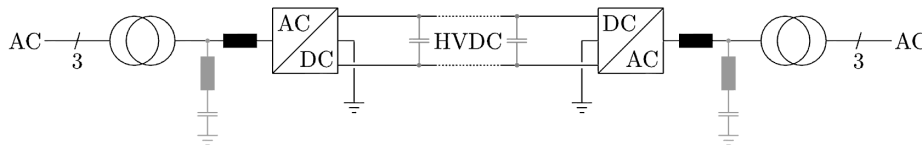■ HVDC Transmission – Advantageous for Long Distances



■ Low-Frequency AC (LFAC) as Possible (Purely Passive) Solution for Medium Transmission Distances



► AC vs. DC Power Transmission (2)

- Quadratic Dependency of Losses on Voltage Level → Reduction of Conductor Cross Section
- DC Voltage Ensures Max. Utiliz. of Isol. Voltage → Highest RMS Value / Lowest Current

$$P_{V,AC} = 3 \cdot \left(\frac{\frac{1}{3}P}{U_{AC}} \right)^2 \cdot R_L$$

$$P_{V,DC} = 2 \cdot \left(\frac{P}{2U_{DC}} \right)^2 \cdot R_L$$

$$\frac{P_{V,DC}}{P_{V,AC}} = \frac{3}{2} \cdot \left(\frac{U_{AC}}{U_{DC}} \right)^2 \Big|_{U_{DC}=\sqrt{2}U_{AC}} = 0.75$$

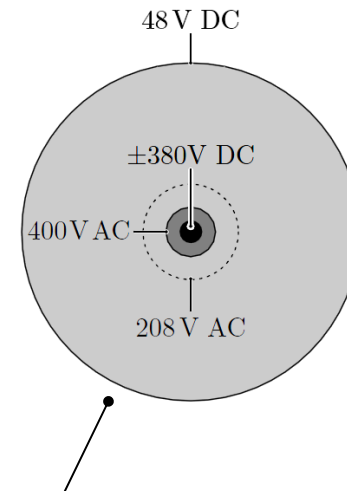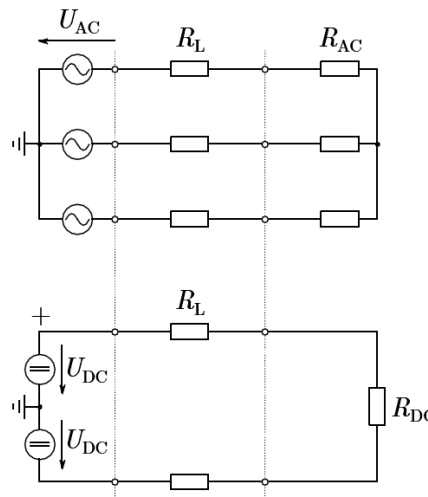

Conductor Cross Sections
for Same Losses

- Fault Current Clearing as Main Challenge of DC Distr. Systems (Missing Regular Current Zero Crossing)

SST Motivation


*Next Generation
Traction Vehicles*



► Classical Locomotives

- Catenary Voltage **15kV or 25kV**
- Frequency **$16\frac{2}{3}$ Hz or 50Hz**
- Power Level **1...10MW typ.**

Source: www.abb.com

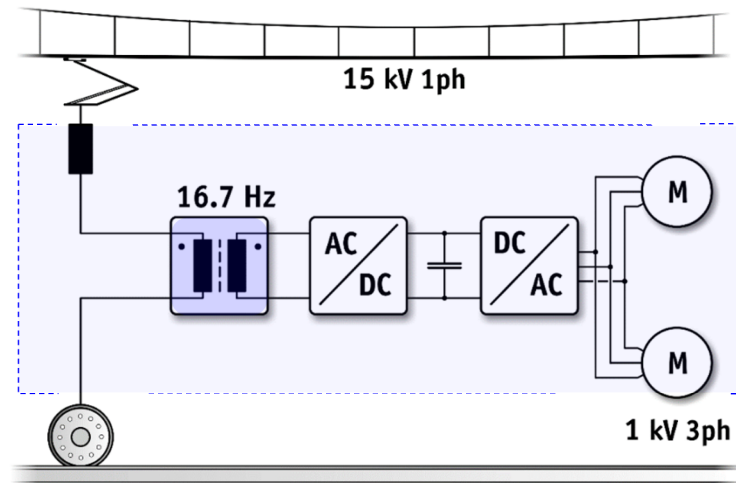

■ Transformer:


Efficiency
Current Density
Power Density

90...95% (due to Restr. Vol., 99% typ. for Distr. Transf.)
6 A/mm² (2A/mm² typ. Distribution Transformer)
2...4 kg/kVA


▶ Next Generation Locomotives

- Trends
 - * Distributed Propulsion System → Volume Reduction (Decreases Efficiency)
 - * Energy Efficient Rail Vehicles → Loss Reduction (Requires Higher Volume)
 - * Red. of Mech. Stress on Track → Mass Reduction

Source: ABB

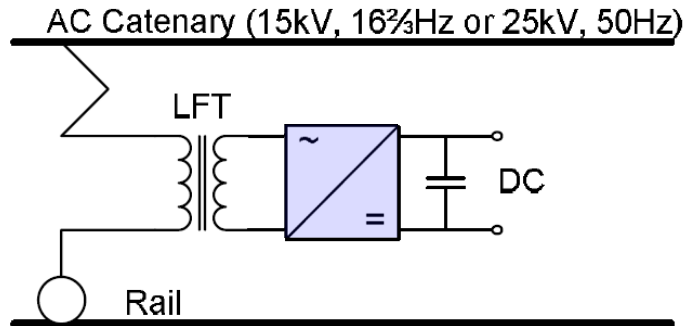

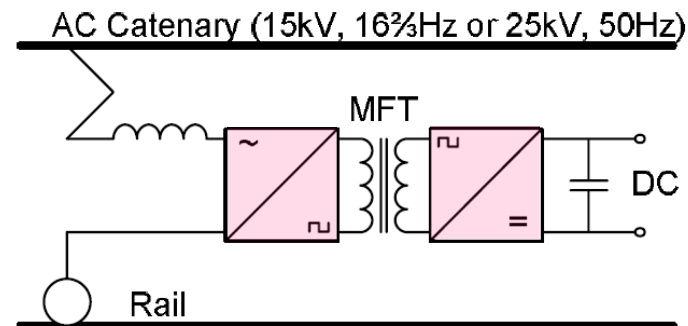Conventional AC-DC conversion with a line frequency transformer (LFT).





AC-DC conversion with medium frequency transformer (MFT).

- Replace LF Transformer by **Medium-Frequency Power Electronics Transformer** → **SST**
- **Medium Frequency Provides Degree of Freedom** → **Allows Loss Reduction & Volume Reduction**

► Next Generation Locomotives

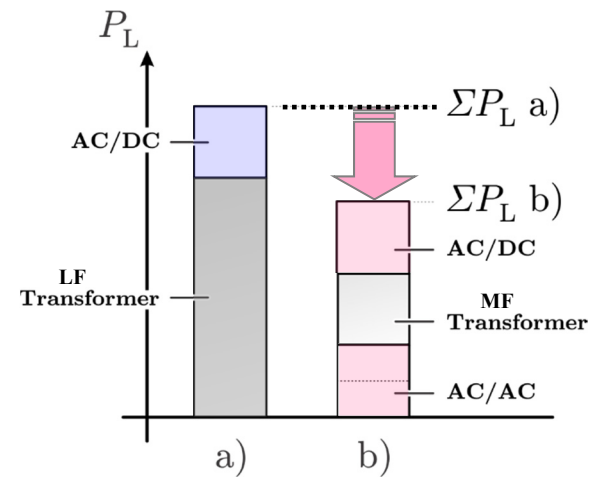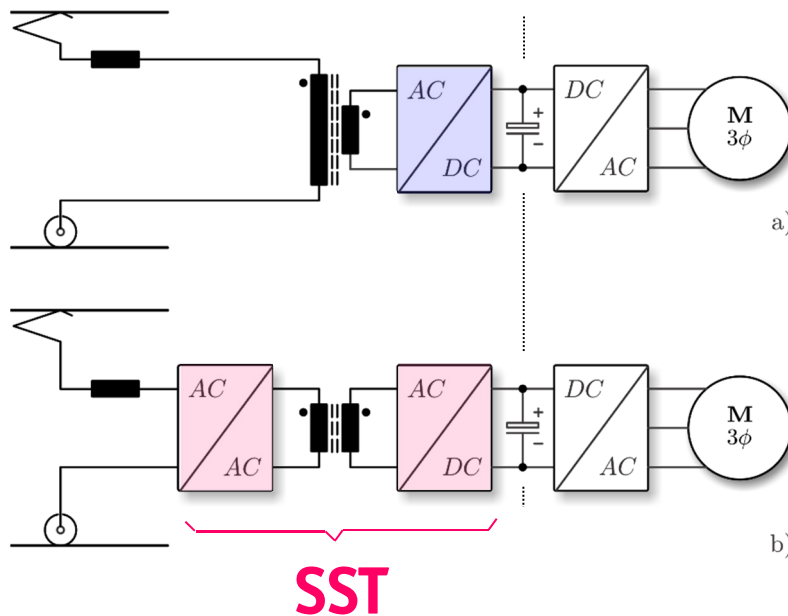- Loss Distribution of Conventional & Next Generation Locomotives



- Medium Freq. Provides Degree of Freedom → Allows Loss Reduction AND Volume Reduction


***Future Smart
EE Distribution***



Source: TU Munich

► Advanced (High Power Quality) Grid Concept

- Heinemann / ABB (2001)

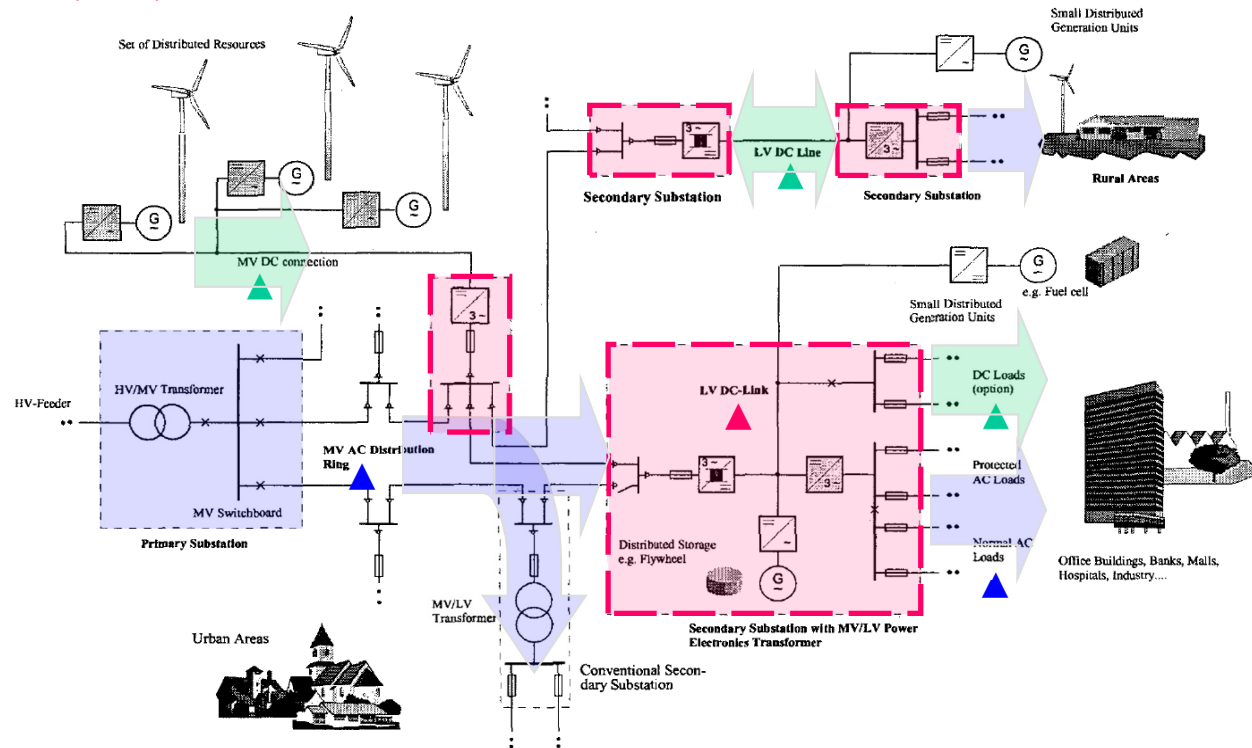

- MV AC Distribution with DC Subsystems (LV and MV) and Large Number of Distributed Resources
- MF AC/AC Conv. with DC Link Coupled to Energy Storage provide High Power Qual. for Spec. Customers

► Future Ren. Electric Energy Delivery & Management (FREEDM) Syst.


- Huang et al. (2008)

- SST as Enabling Technology for the “Energy Internet”

- Full Control of the Power Flow
- Integr. of DER (Distr. Energy Res.)
- Integr. of DES (Distr. E-Storage) + Intellig. Loads
- Protects Power Syst. From Load Disturbances
- Protects Load from Power Syst. Disturbances
- Enables Distrib. Intellig. through COMM
- Ensure Stability & Opt. Operation
- etc.
- etc.



IFM = Intellig. Fault Management


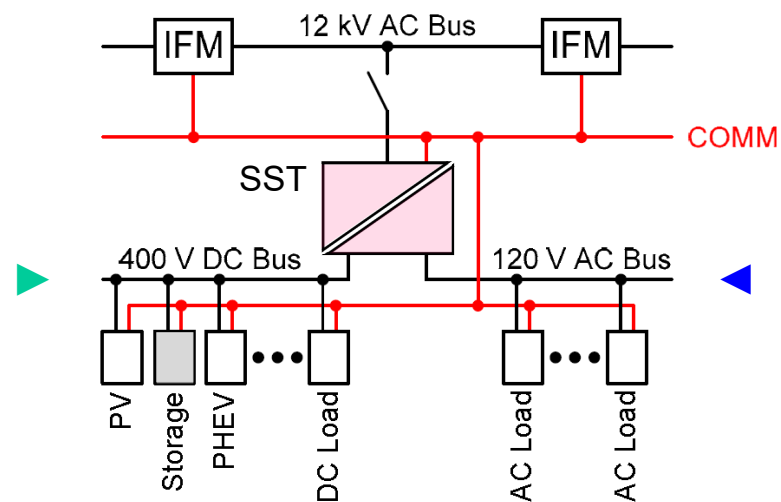


- Bidirectional Flow of Power & Information / High Bandw. Comm. → Distrib. / Local Autonomous Cntrl

► Terminology (1)

McMurray
Brooks
EPRI
ABB
Borojevic
Wang
etc.

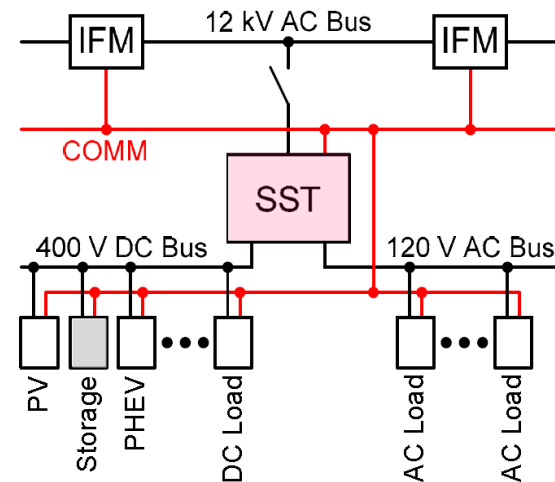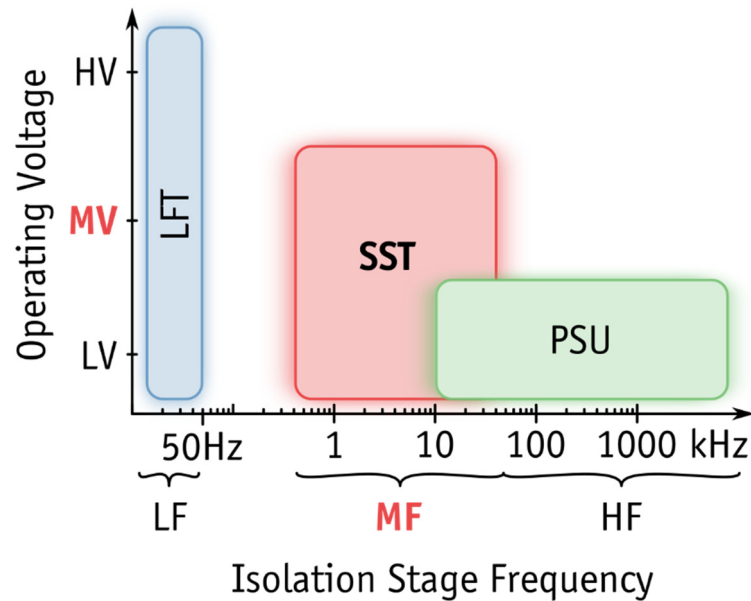Electronic Transformer (1968)
Solid-State Transformer (SST, 1980)
Intelligent Universal Transformer (IUT™)
Power Electronics Transformer (PET)
Energy Control Center (ECC)
Energy Router



► Terminology (2)

United States Patent [19]

Brooks et al.

[11] 4,347,474

[45] Aug. 31, 1982

[54] SOLID STATE REGULATED POWER TRANSFORMER WITH WAVEFORM CONDITIONING CAPABILITY

← “... Solid State Regulated Power Transformer ...”

[75] Inventors: James L. Brooks, Oxnard; Roger I. Staab, Camarillo, both of Calif.; James C. Bowers; Harry A. Nienhaus, both of Tampa, Fla.

[73] Assignee: The United States of America as represented by the Secretary of the Navy, Washington, D.C.

[21] Appl. No.: 188,419

[22] Filed: Sep. 18, 1980


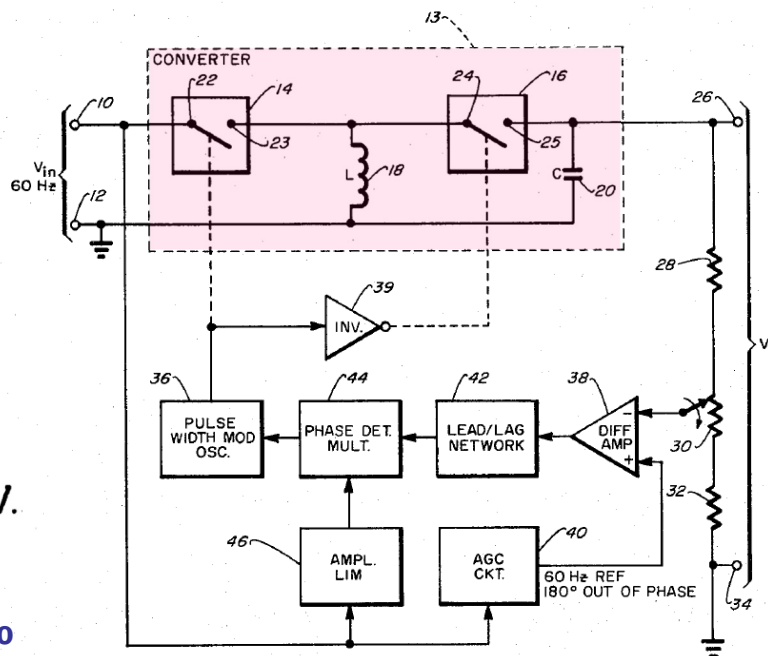


Fig. 1.

- No Isolation (!)
- “Transformer” with Dyn. Adjustable Turns Ratio


► Passive Transformer → SST

■ Efficiency Challenge

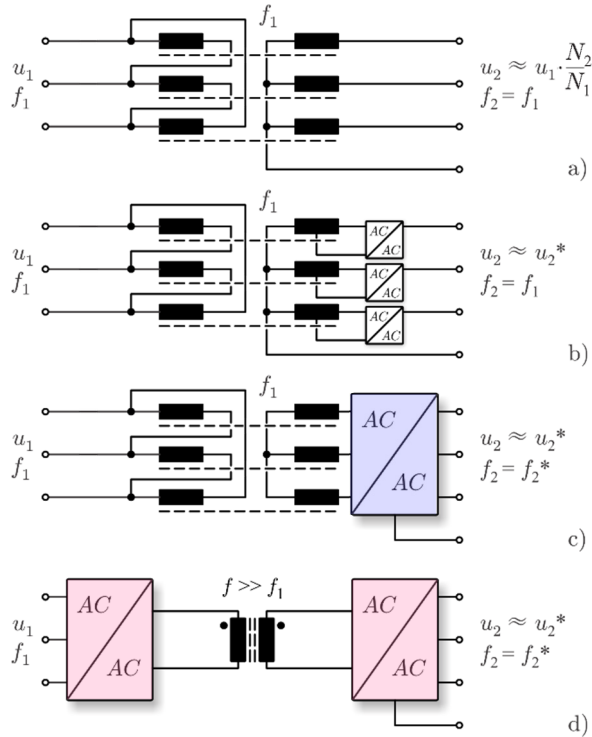

LF Isolation
Purely Passive (a)
Series Voltage Comp. (b)
Series AC Chopper (c)

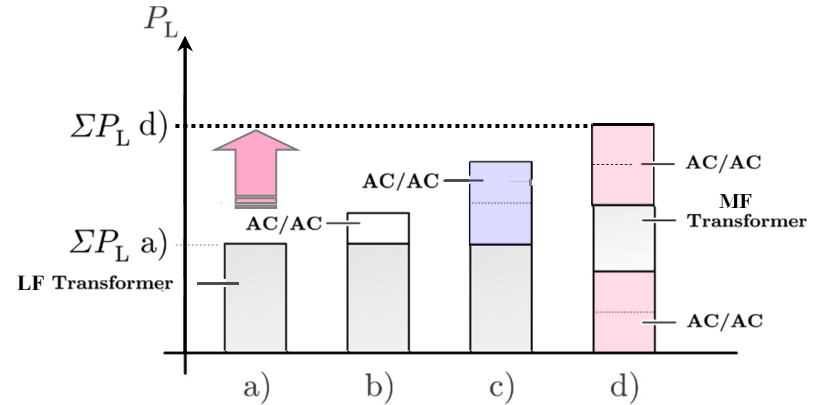MF Isolation
Active Input & Output Stage (d)



- Medium Freq. → Higher Transf. Efficiency Partly Compensates Converter Stage Losses
- Medium Freq. → Low Volume, High Control Dynamics

**SST Concept
Implementation**





Challenge #1/5

— *Availability / Selection of
Power Semiconductors* —



Available Si Power Semiconductors

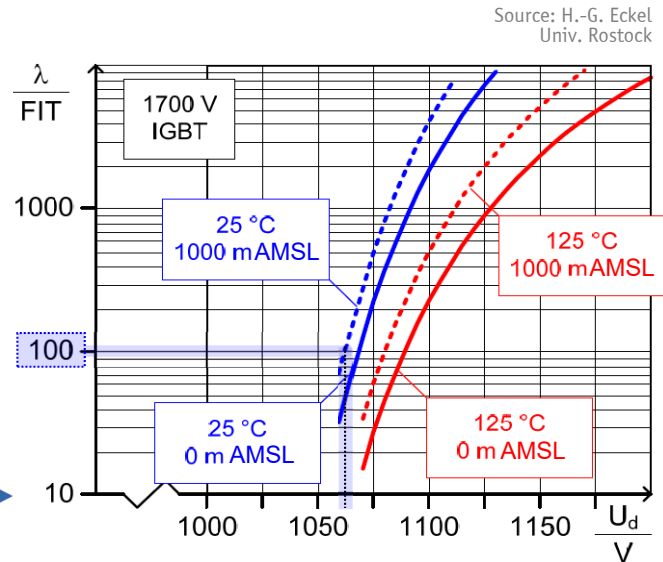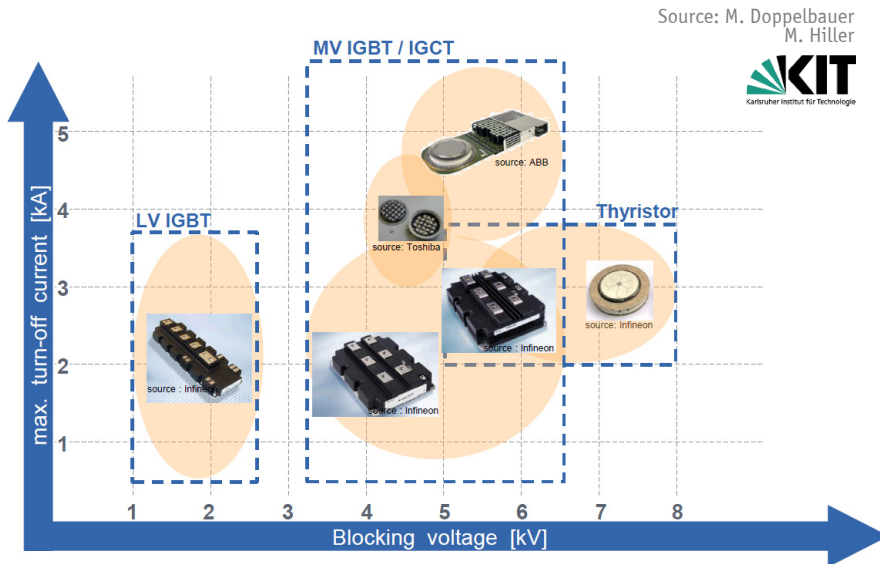- 1200V/1700V Si-IGBTs Most Frequently Used in Industry Applications
- Derating Requirement due to Cosmic Radiation
1700V Si-IGBTs → ≈1000V max. DC Voltage





- Interfacing to Medium Voltage → Multi-Level Converter Topologies

SiC Power Semiconductors

- Samples

- * 10kV & 15kV / 10A MOSFETs
- * 10kV & 15kV / 8A JBS Diodes
- * 15kV / 20A IGBTs

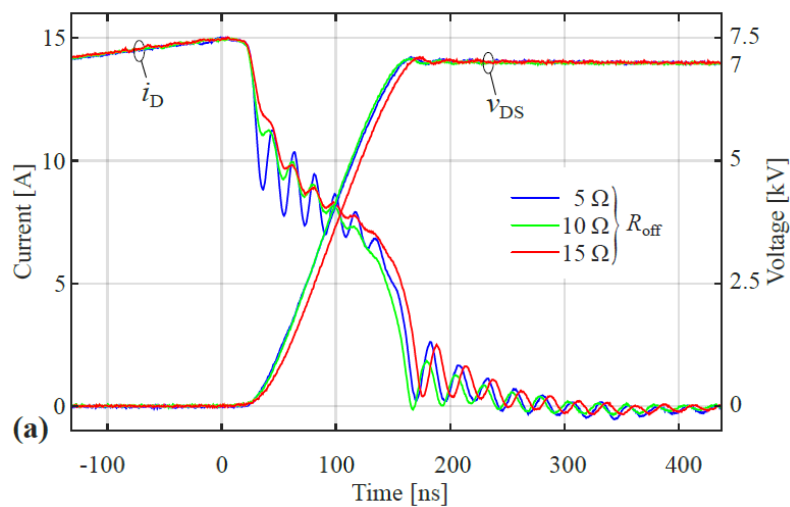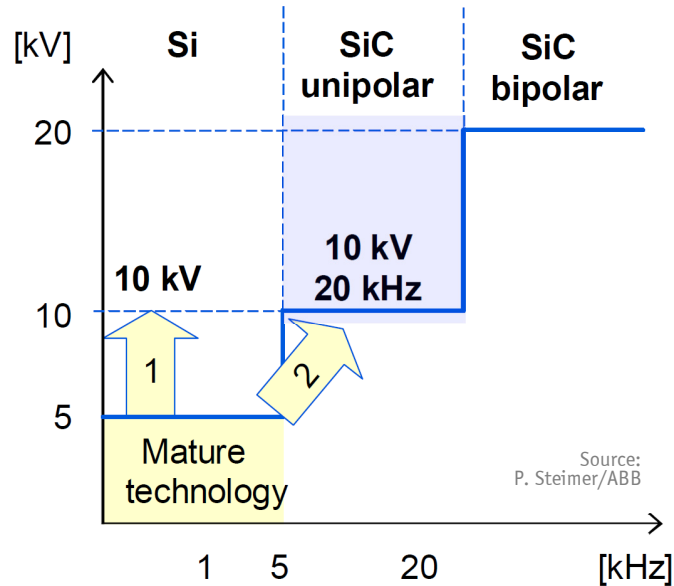- Soft-Switching (ZVS) Performance
10kV MOSFET @ 15A
(250uJ)





Interfacing to Medium Voltage → Two-Level OR Multi-Level Converter Topologies

► SiC Power Semiconductors

- Samples *Wolfspeed*
- * 10kV & 15kV / 10A MOSFETs
- * 10kV & 15kV / 8A JBS Diodes
- * 15kV / 20A IGBTs

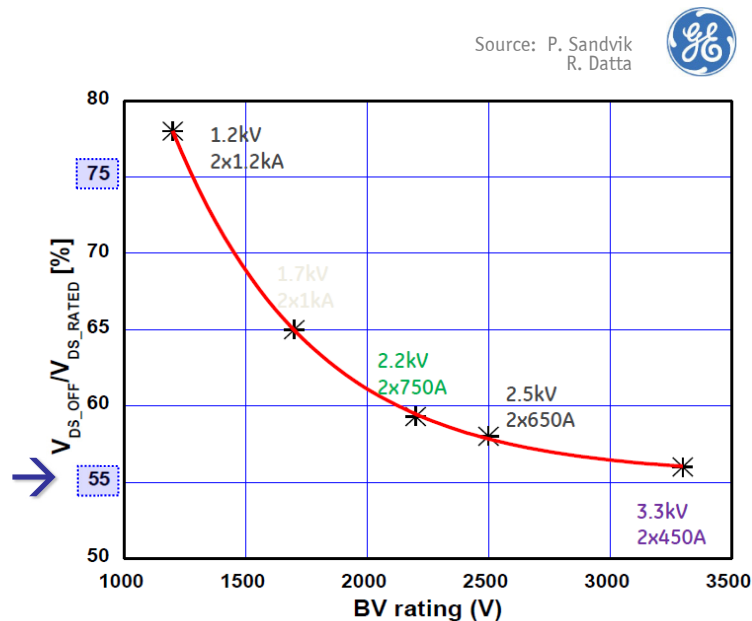
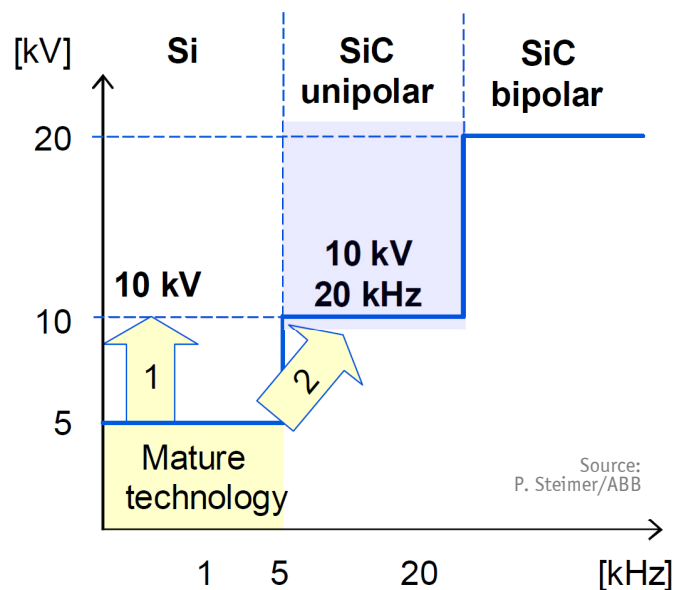
- Derating Requirement due to Cosmic Radiation for 100 FIT @ 25°C & 0 m AMSL
 $A_{act} = 7.2 \text{ cm}^2$



■ Interfacing to Medium Voltage → Two-Level OR Multi-Level Converter Topologies

► Commercially Available SiC Power Semiconductors

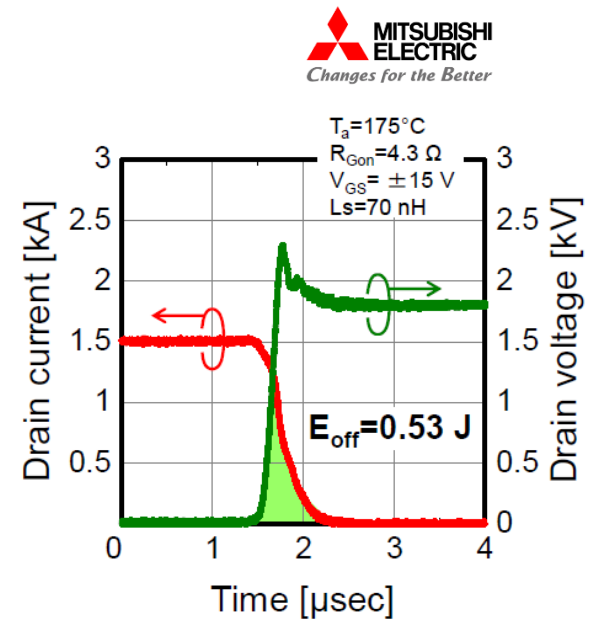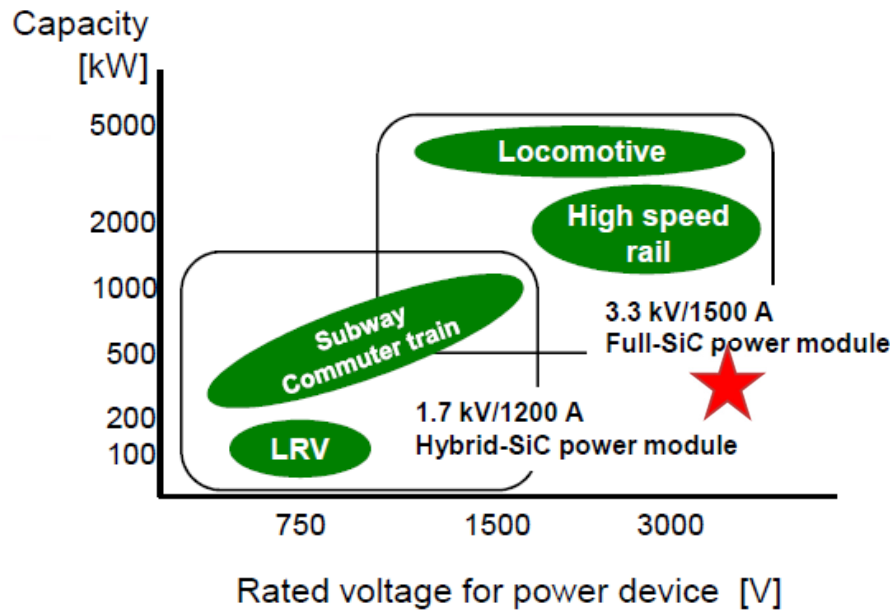- High Current 3.3kV / 1.7kV / 1.2 kV Power Modules
- Mitsubishi (CREE, ROHM, GE, etc.)



- 6.5kV Samples Available


Challenge #2/5

Creation of MV \rightarrow LV
SST Topologies




► Interfacing to Medium Voltage

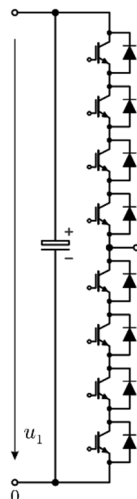- Partitioning of Blocking Voltage
- Series Connection or Multi-Cell and Multi-Level Approaches
- High Number N Cells \rightarrow Quadratically Reduces Curr. Harmonics



* Two-Level Topology

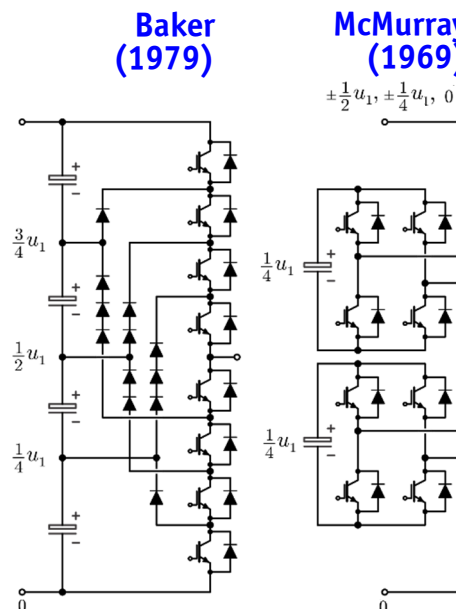


Baker (1979)

McMurray (1969)

$$\pm \frac{1}{2}u_1, \pm \frac{1}{4}u_1, 0$$



Marquardt (2001)

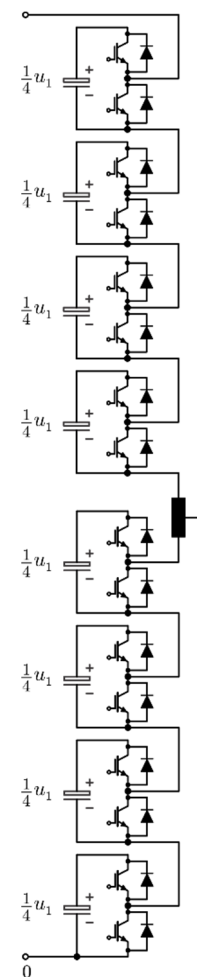



Alesina/Venturini (1981)




* Multi-Level/
Multi-Cell
Topologies

► Scaling of Series Interleaving of Converter Cells

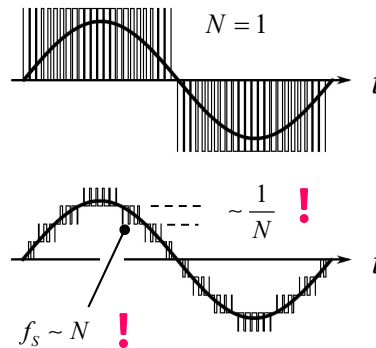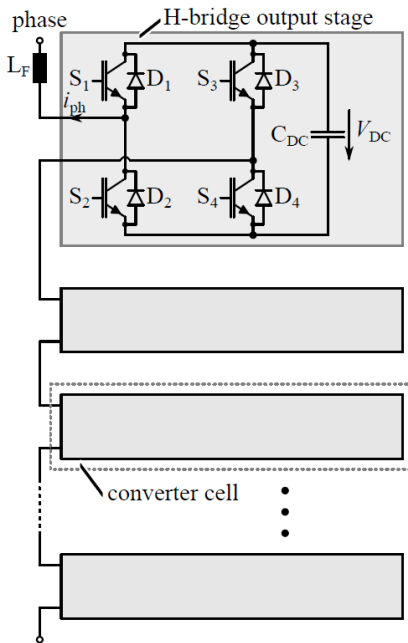- Interleaved Series Connection Dramatically Reduces Switching Losses (or Harmonics)



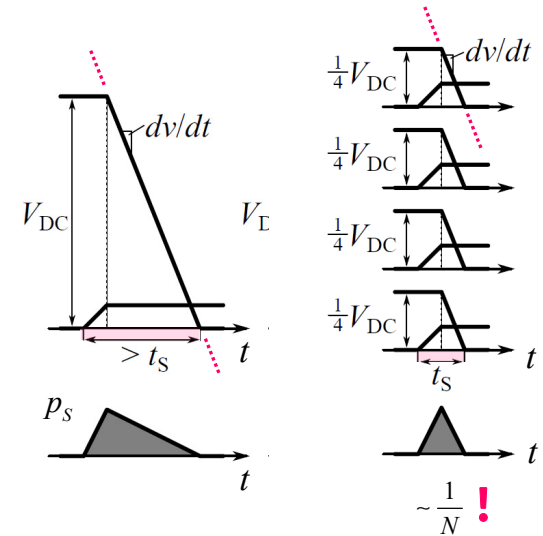– Scaling of Switching Losses for Equal $\Delta i/I$ and dv/dt



$$P_{S,N} \approx P_{S,N=1} \cdot \left(\frac{1}{2N^2} \dots \frac{1}{N^3} \right)$$

- Converter Cells Could Operate at VERY Low Switching Frequency
- Minimization of Passives (Filter Components)



United States Patent

[11] 3,581,212


[54] **FAST RESPONSE STEPPED-WAVE SWITCHING
POWER CONVERTER CIRCUIT**
18 Claims, 13 Drawing Figs.

- [72] Inventor **William McMurray**
Schenectady, N.Y.
- [21] Appl. No. **846,354**
- [22] Filed **July 31 1969** ← **1969!**
- [45] Patented **May 25, 1971**
- [73] Assignee **General Electric Company**

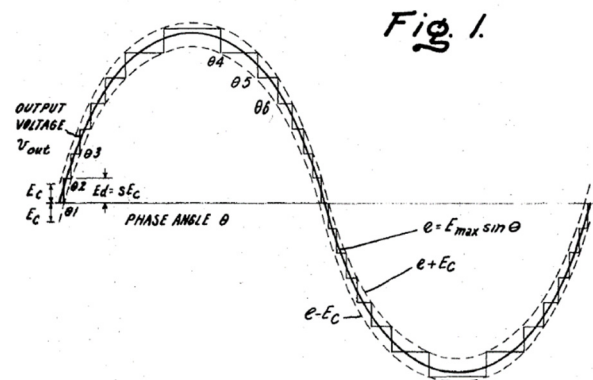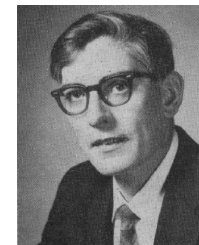Inventor:
William McMurray;
by Ronald R. Campbell
His Attorney.



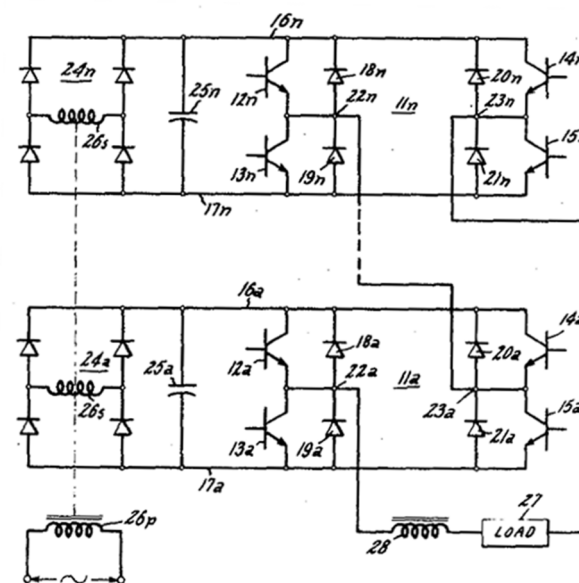
- Cascaded H-Bridge Multi-Cell Converter (1-Φ AC/AC SST)



► Partitioning of AC/AC Power Conversion

■ Introduction of Intermediate DC-Links

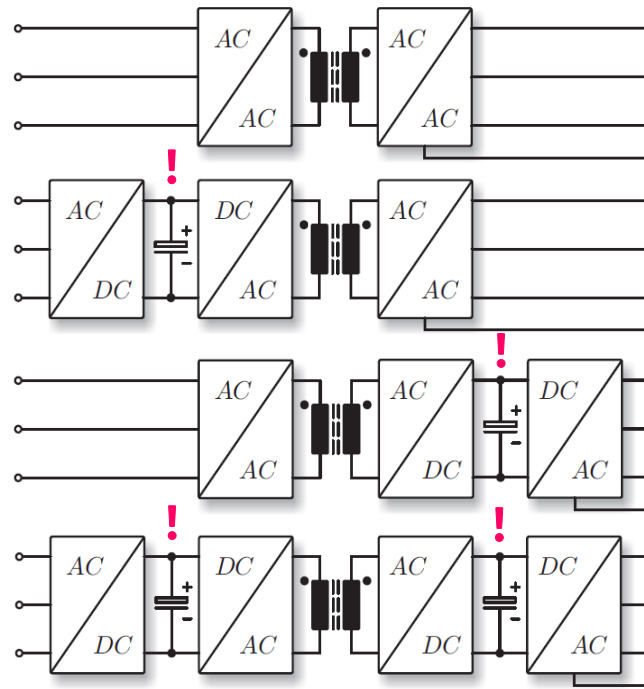
- Connection to DC Distribution Lines
- Basic Converter Building Blocks
- Integration of Energy Storage





- Direct AC/AC Conversion – Isolated Back End – Isolated Front End - DC/DC Conv. Isolation

▶ Electronic Transformer - History

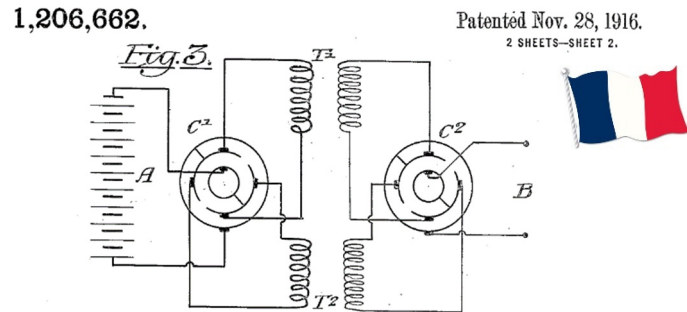
- System Using Mech. Switches *Patented Already in 1913 (!)*
- Mechanical Sw. → Tubes → Mercury Arc Valves → Solid State Switches



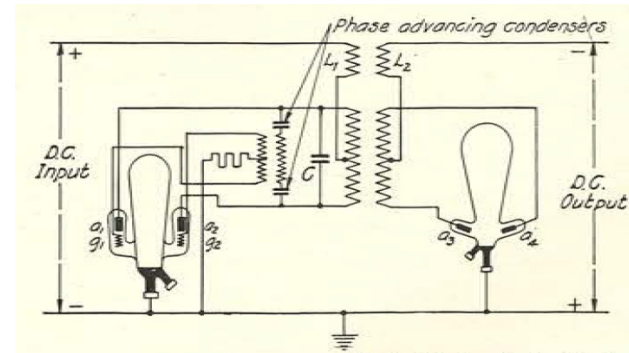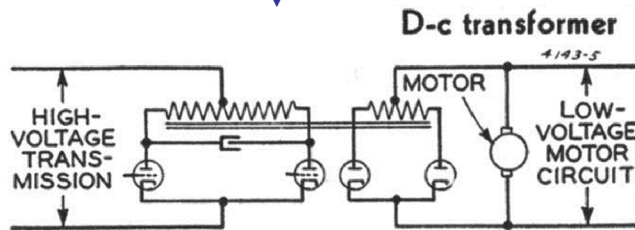1913 — P.M.J. Boucherot
 1944 — E.F.W. Alexanderson et al.



1928 — D.C. Prince
 1968 — W. McMurray

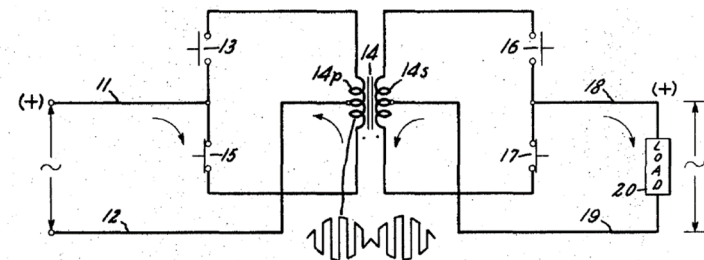


- "Transformer of Cont. Current" / "DC Transformer" / "Electronic Transformer"

United States Patent Office

3,517,300
Patented June 23, 1970

1

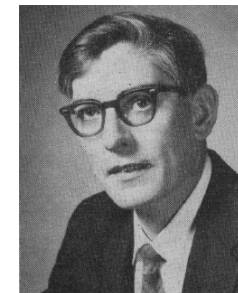3,517,300
POWER CONVERTER CIRCUITS HAVING A HIGH FREQUENCY LINK
William McMurray, Schenectady, N.Y., assignor to General Electric Company, a corporation of New York
Filed Apr. 16, 1968, Ser. No. 721,817
Int. Cl. H02m 5/16, 5/30
U.S. Cl. 321-60 14 Claims



Inventor:
William McMurray;
by Donald F. Campbell
His Attorney.


1968!

Filed April 16, 1968

ABSTRACT OF THE DISCLOSURE

Several single phase solid state power converter circuits have a high frequency transformer link whose windings are connected respectively to the load and to a D-C or low frequency A-C source through inverter configuration switching circuits employing inverse-parallel pairs of controlled turn-off switches (such as transistors or gate turn-off SCR's) as the switching devices. Filter means are connected across the input and output terminals. By synchronously rendering conductive one switching device in each of the primary and secondary side circuits, and alternately rendering conductive another device in each switching circuit, the input potential is converted to a high frequency wave, transformed, and reconstructed at the output terminals. Wide range output voltage control is obtained by phase shifting the turn-on of the switching devices on one side with respect to those on the other side by 0° to 180°, and is used to effect current limiting, current interruption, current regulation, and voltage regulation.


Fig. 1a

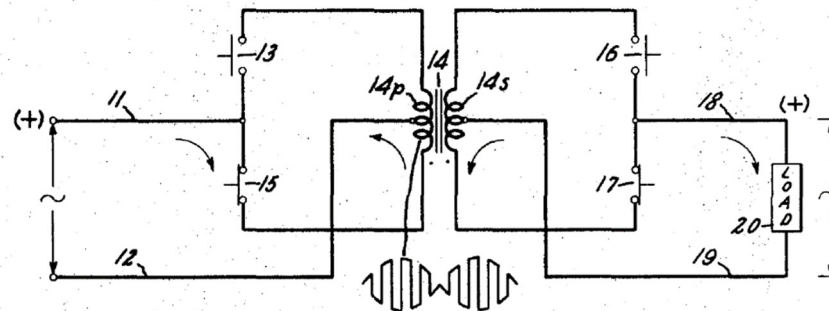


- Electronic Transformer ($f_1 = f_2$)
- AC or DC Voltage Regulation & Current Regulation/Limitation/Interruption

► Electronic Transformer

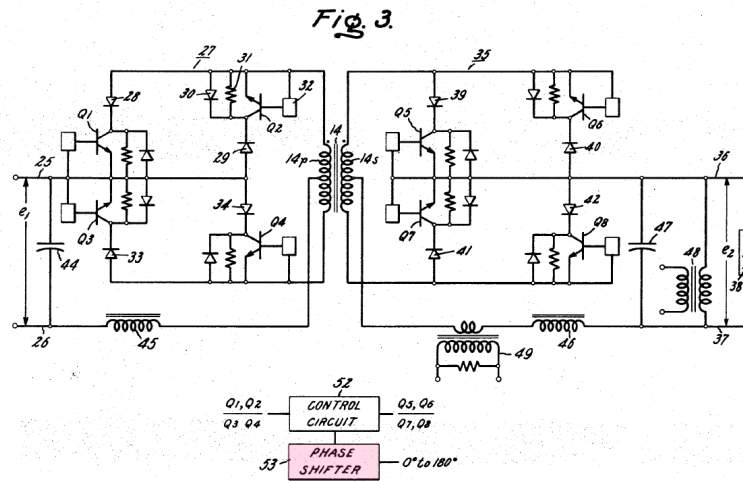- Inverse-Paralleled Pairs of Turn-off Switches
- 50% Duty Cycle of Input and Output Stage



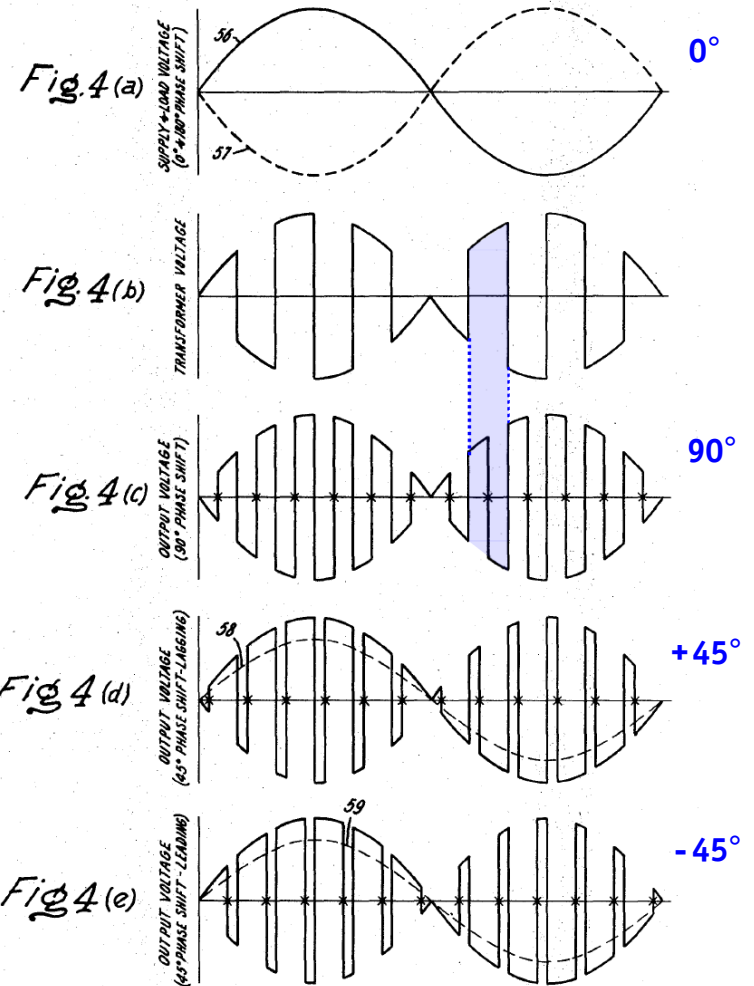- $f_1 = f_2 \rightarrow$ Not Controllable (!)
- Voltage Adjustment by Phase Shift Control (!)



United States Patent [19]

[11] Patent Number: 5,027,264



DeDoncker et al.

[45] Date of Patent: Jun. 25, 1991 ← 1991

 [54] **POWER CONVERSION APPARATUS FOR DC/DC CONVERSION USING DUAL ACTIVE BRIDGES** ← "... Dual Active Bridges ..."

 [75] Inventors: **Rik W. DeDoncker**, Niskayuna, N.Y.;
Mustansir H. Kheraluwala;
Deepakraj M. Divan, both of
 Madison, Wis.

[22] Filed: Sep. 29, 1989

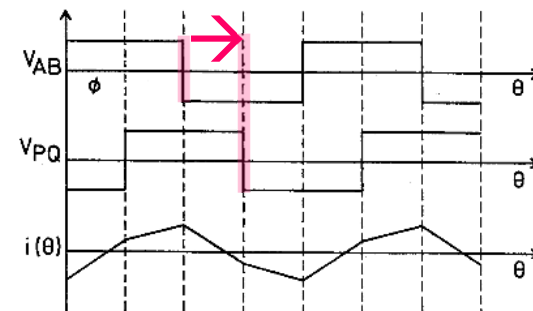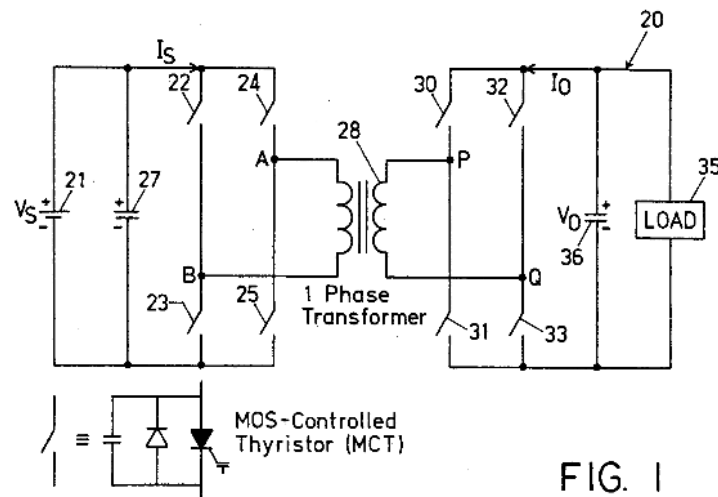

- Soft Switching in a Certain Load Range
- Power Flow Control by Phase Shift between Primary & Secondary Voltage

IEEE TRANSACTIONS ON INDUSTRIAL ELECTRONICS AND CONTROL INSTRUMENTATION VOL. IECI-17, NO. 3, MAY 1970

← 1970 !


A Method of Resonant Current Pulse Modulation for Power Converters



FRANCISC C. SCHWARZ, SENIOR MEMBER, IEEE


■ Load-Insensitive DCM Series Resonant *Thyristor* Converter

- Resonant Tank

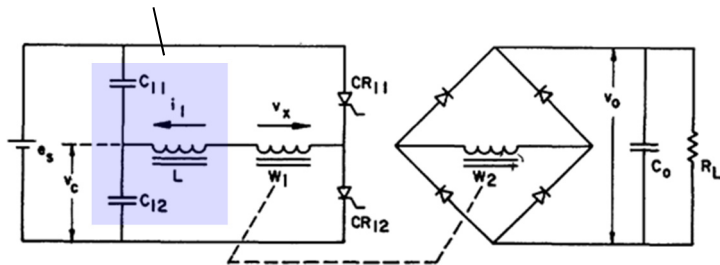




- Transformer Voltage
- Transformer Current

Fig. 4. Alternative simplified schematic of a controllable and load-insensitive series capacitor dc converter with transfer of inductive energy to the load.

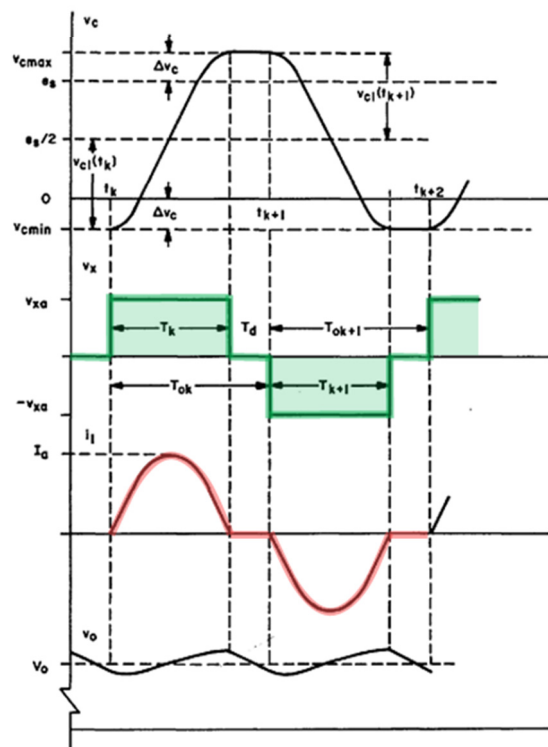

► Half-Cycle DCM Series Resonant Converter (HC-DCM-SRC)

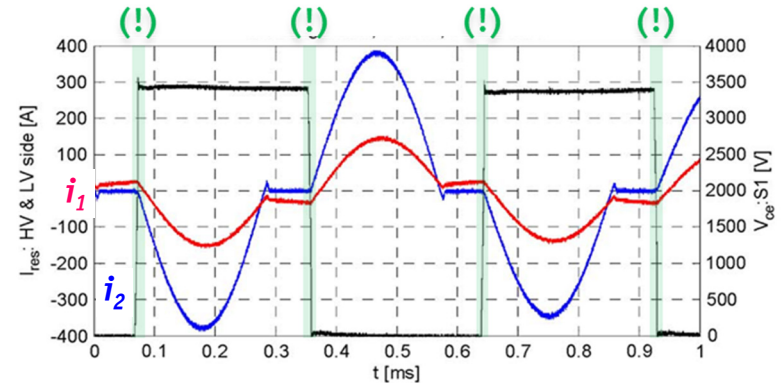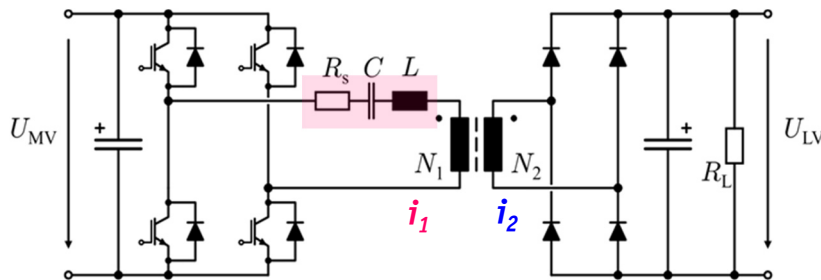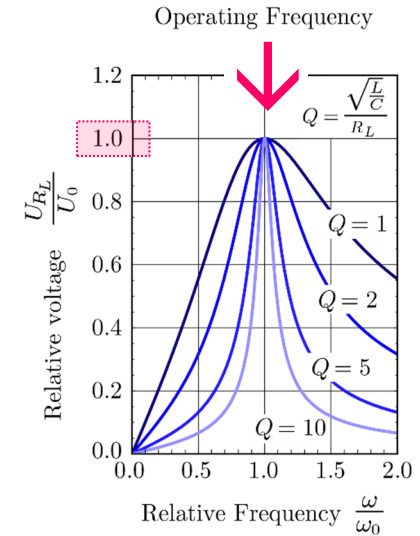- $f_s \approx$ Resonant Frequency \rightarrow "Unity Gain" ($U_2/U_1=N_2/N_1$)
- Fixed Voltage Transfer Ratio Independent of Transferred Power (!)
- Power Flow / Power Direction Self-Adjusting
- No Controllability / No Need for Control
- ZCS of All Devices




Remark – Concept also Used for Low-Power

- BCM Bus Converter Family
- Sine Amplitude Converter (SAC)
- Fixed Voltage Conversion Ratio DC/DC Converter




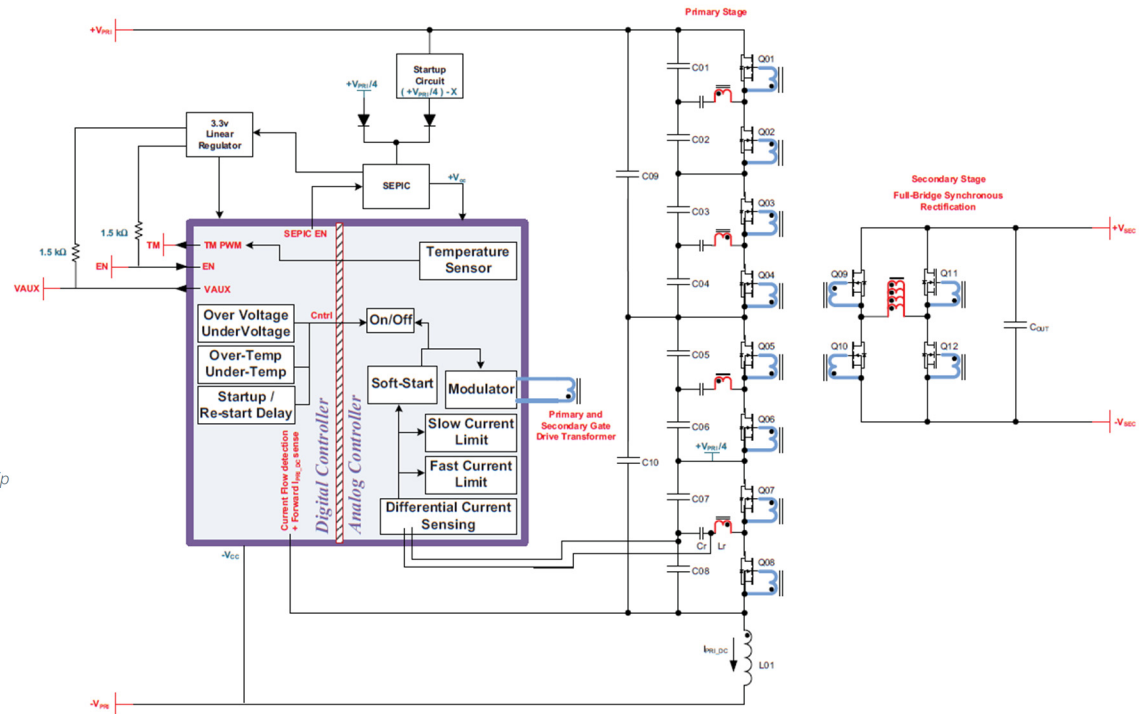- Very High Power Density
- Very High Efficiency




► Classification of SST Topologies


■ Number of Levels Series/Parallel Cells

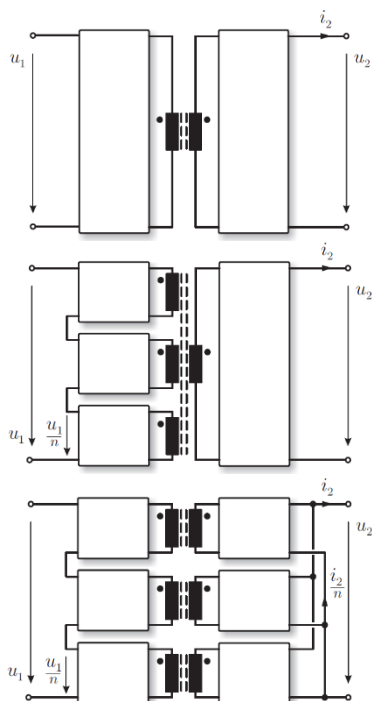

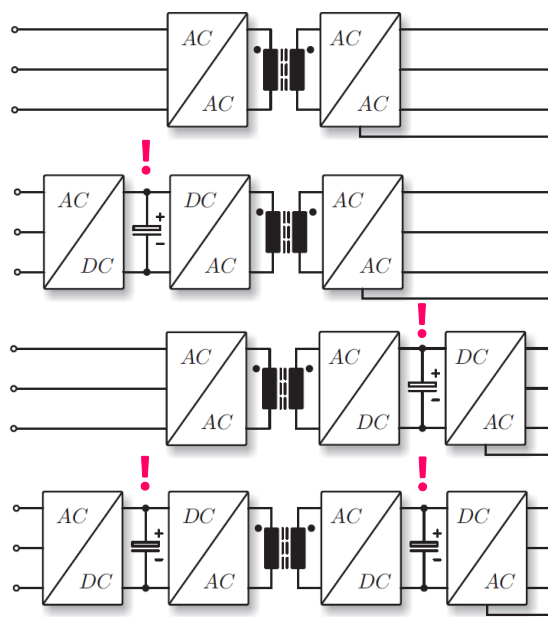■ Degree of Power Conversion Partitioning




■ Degree of Phase Modularity

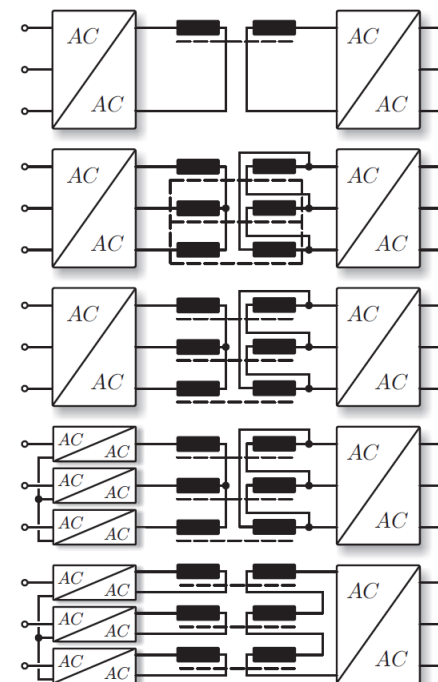

► 3-Dimensional Topology Selection Space

► Classification of SST Topologies

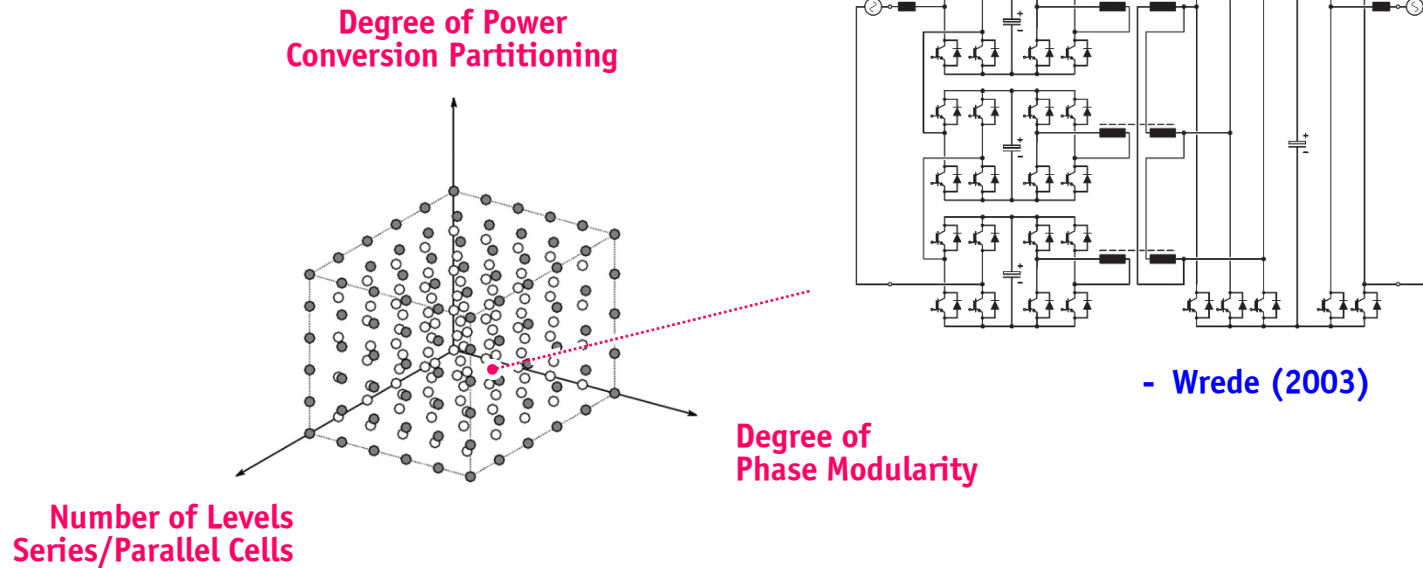

■ Very (!) Large Number of Possible Topologies

- Partitioning of Power Conversion
- Splitting of 3ph. System into Individual Phases
- Splitting of Medium Operating Voltage into Lower Partial Voltages
- Matrix & DC-Link Topologies
- Phase Modularity
- Multi-Level/Cell Approaches

Combining the Basic Concepts I




———— *Single-Phase AC-DC Conversion /* ————
Traction Applications



Cascaded H-Bridges w. Isolated Back End



- Multi-Cell Concept (AC/DC Front End & Soft-Switching Resonant DC//DC Converter)
- Input Series / Output Parallel Connection – Self Symmetrizing (!)
- Highly Modular / Scalable
- Allows for Redundancy
- High Power Demonstrators: **ABB** **BOMBARDIER** **ALSTOM** etc.

Source: Zhao / Dujic (ABB / 2011)

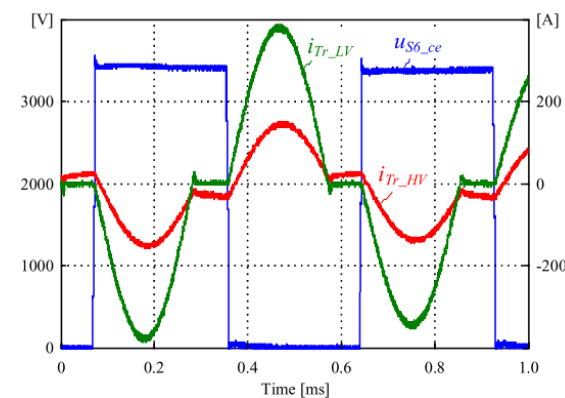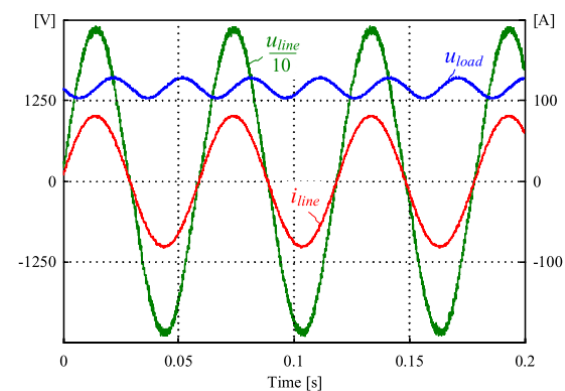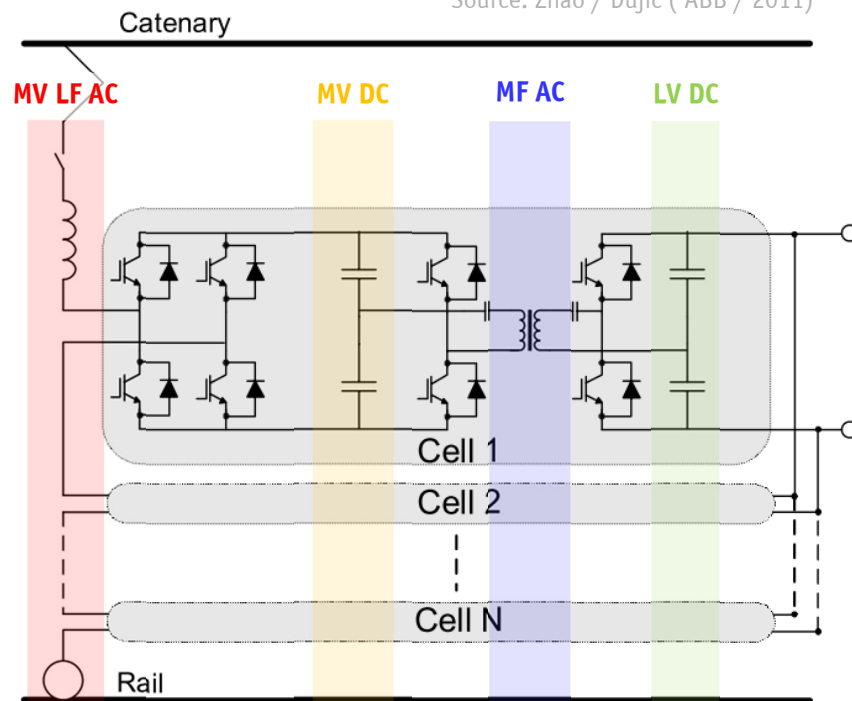



► Current Shaping & Isolation → Isolation & Current Shaping

■ Isolated DC/DC Back End

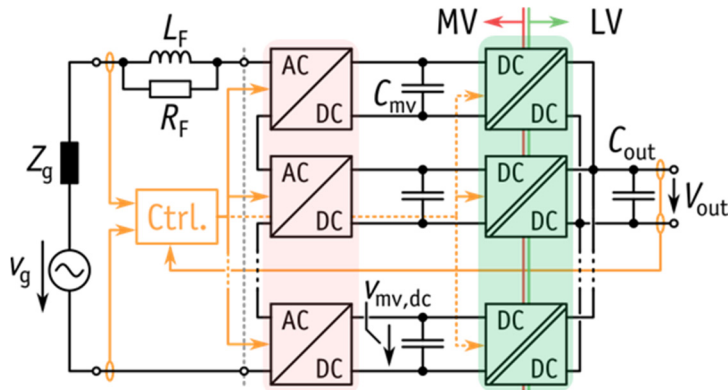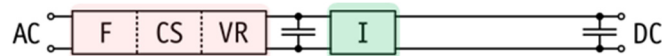

- Typical Multi-Cell SST Topology
- Two-Stage Multi-Cell Concept
- Direct Input Current Control
- Indirect Output Voltage Control
- High Complexity at MV Side


■ Isolated AC/AC | AC | Front End

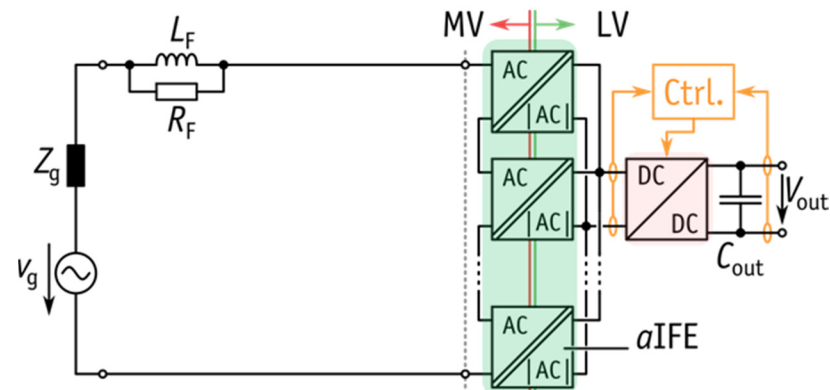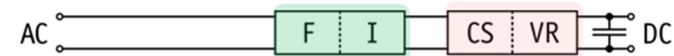

- Swiss SST (S3T)
- Two-Stage Multi-Cell Concept
- Indirect Input Current Control
- Direct Output Voltage Control
- Low Complexity on MV Side


► Modular Multilevel Converter

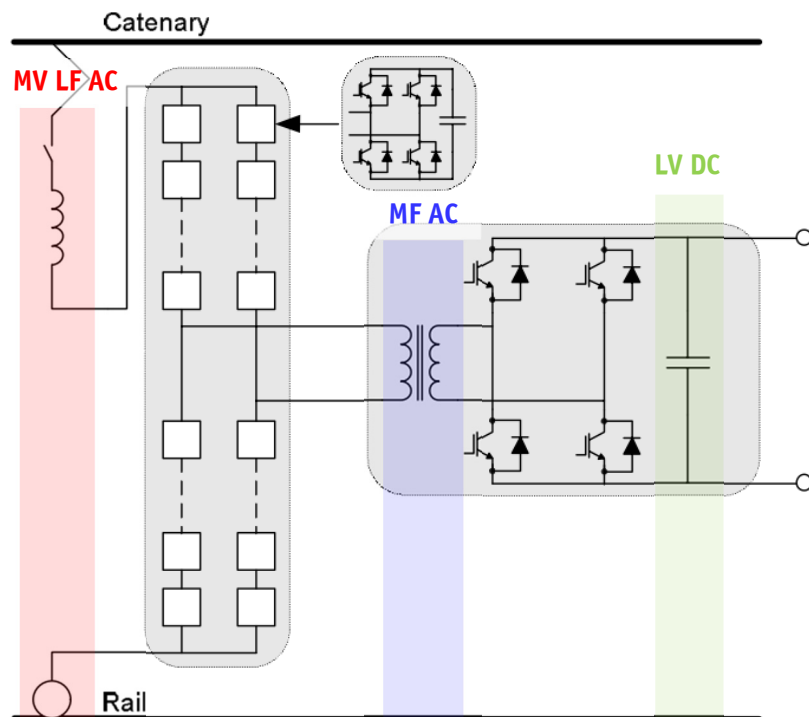- Single Transformer Isolation
- Highly Modular / Scalable
- Allows for Redundancy
- Challenging Balancing on Cell DC Voltages




SIEMENS
- Marquardt/Glinka (2003)

Source: Zhao / Dujic (ABB / 2011)

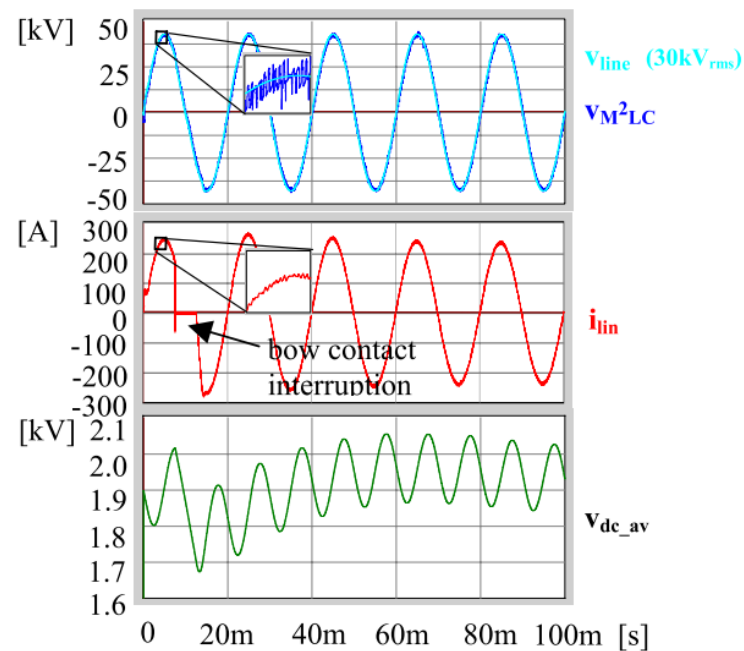

Combining the Basic Concepts II

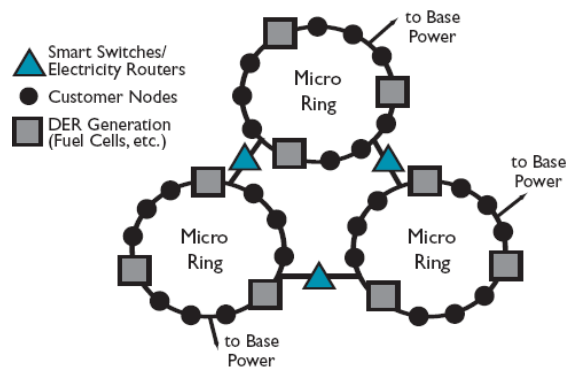Three-Phase AC-AC Conversion / Smart Grid Applications




Source: **EPRI** | ELECTRIC POWER RESEARCH INSTITUTE

MEGALink @ ETH Zurich

$$S_N = 630\text{kVA}$$

$$U_{LV} = 400\text{ V}$$

$$U_{MV} = 10\text{kV}$$

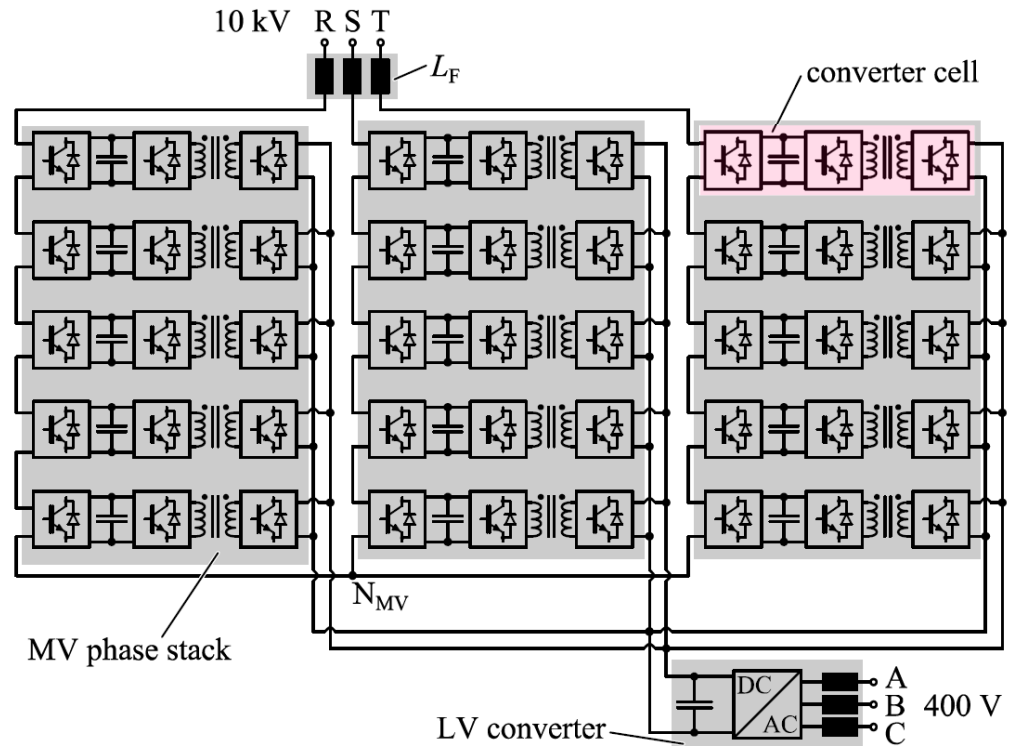


- 2-Level Inverter on LV Side
- HC-DCM-SRC DC//DC Conversion
- Cascaded H-Bridge MV Structure – ISOP Topology



▶ Optimum Number of Converter Cells

- **Trade-Off** High Number of Levels → High Conduction Losses/ Low Cell Sw. Frequ./Losses (also because of Device Char.)

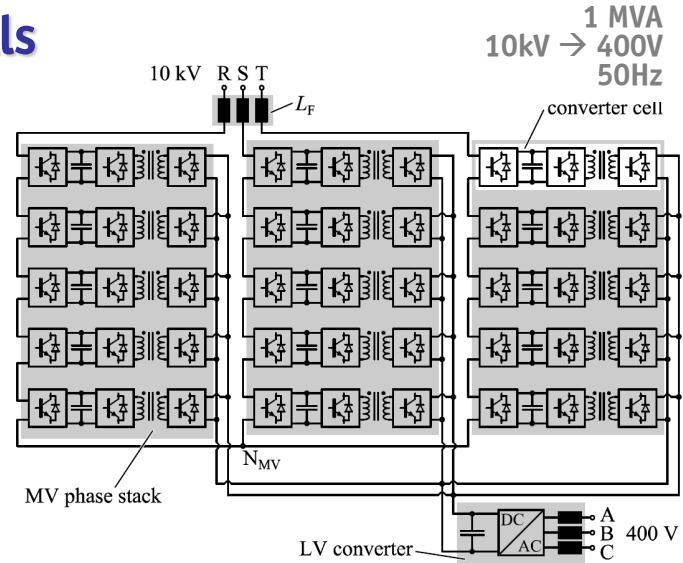- Opt. Device Voltage Rating for Given MV Level
- η -Pareto Opt. (Compliance to IEEE 519 @ Eff. Sw. Frequ., only Cascaded H-Bridges, i.e. DC/DC Converter Stages Not Considered)



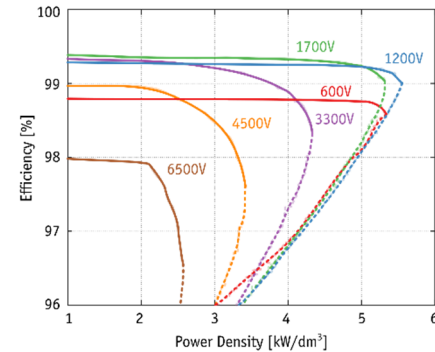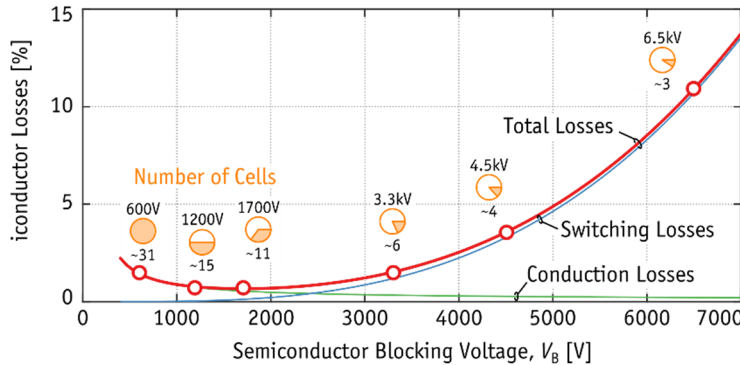
$$L_F = 10\% \Delta i_{pp} / \hat{I}_N = 1\%$$



- 1700V Power Semiconductors Best Suited for 10kV Mains → 10kV or Higher SiC Not Required (!)

► Single-Cell Structure (SiC)

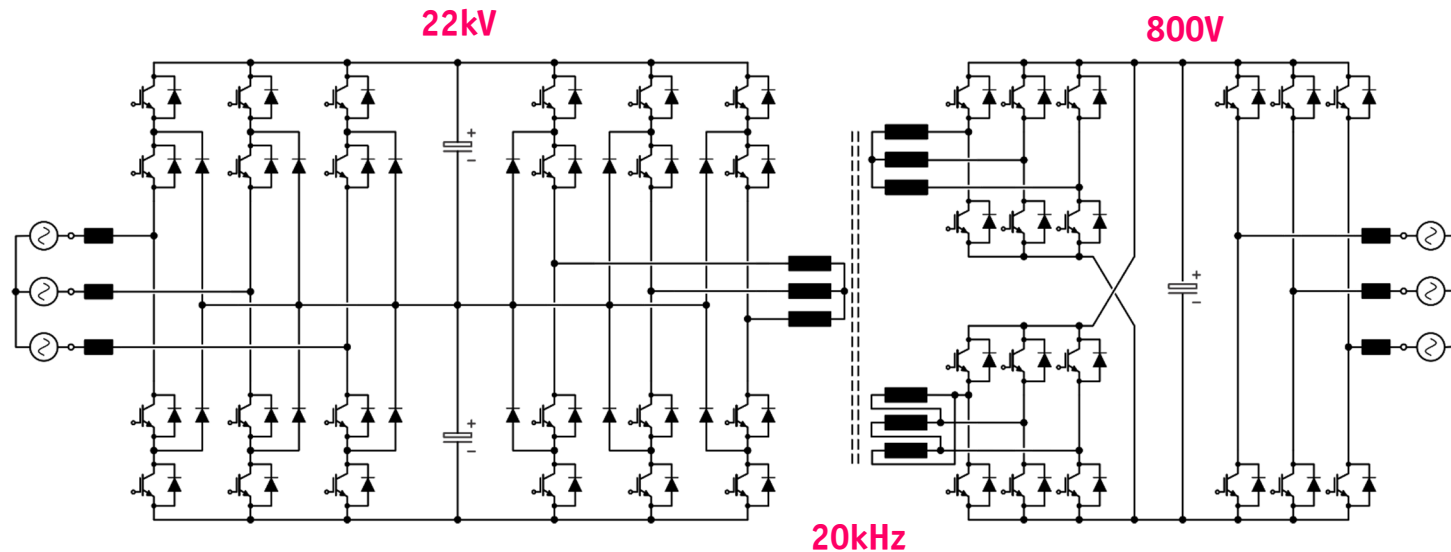- 13.8kV → 480V
- Scaled Prototype
- 15kV SiC-IGBTs, 1200V SiC MOSFETs



- Redundancy Only for Series-Connection of Power Semiconductors (!)

Challenge #3/5

—————

Medium-Frequency Transformer Design



—————

- *Heat Management*
- *Isolation*



► MF Transformer Design – Cold Plates/ Water Cooling

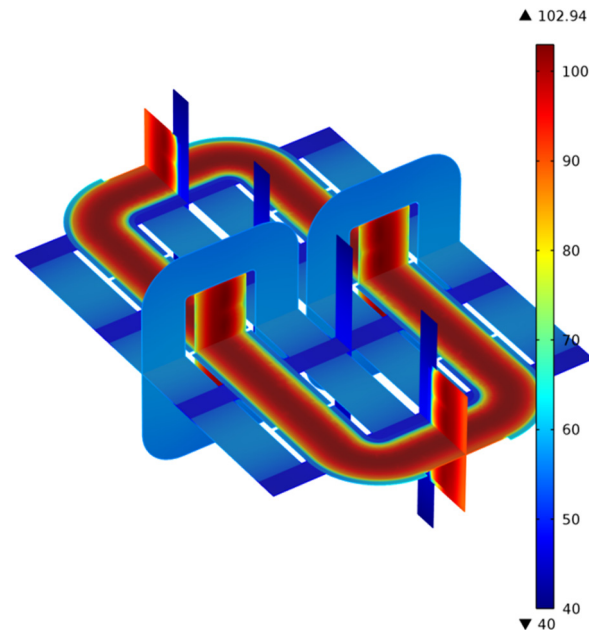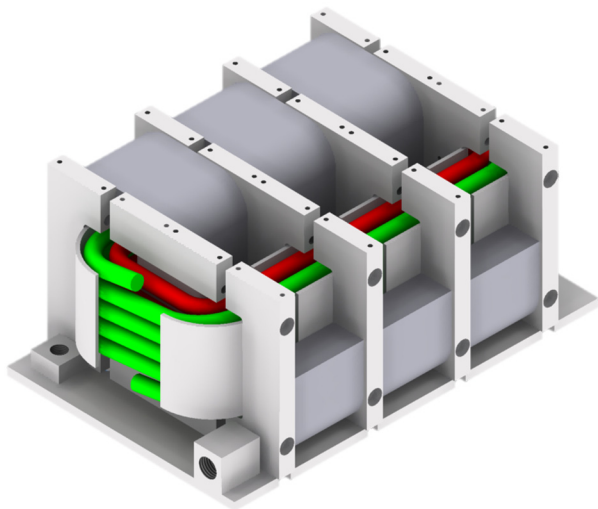- Nano-Crystalline 160kW/20kHz Transformer (ETH, Ortiz 2013)







- Combination of Heat Conducting Plates and Top/Bottom Water-Cooled Cold Plates
- FEM Simulation Comprising Anisotropic Effects of Litz Wire and Tape-Wound Core

► Water-Cooled 20kHz Transformer

- **Power Rating** **166 kW**
- **Efficiency** **99.5%**
- **Power Density** **32 kW/dm³**

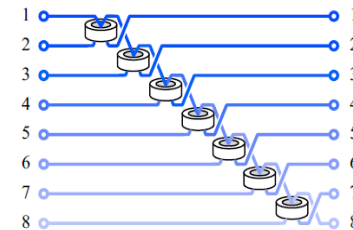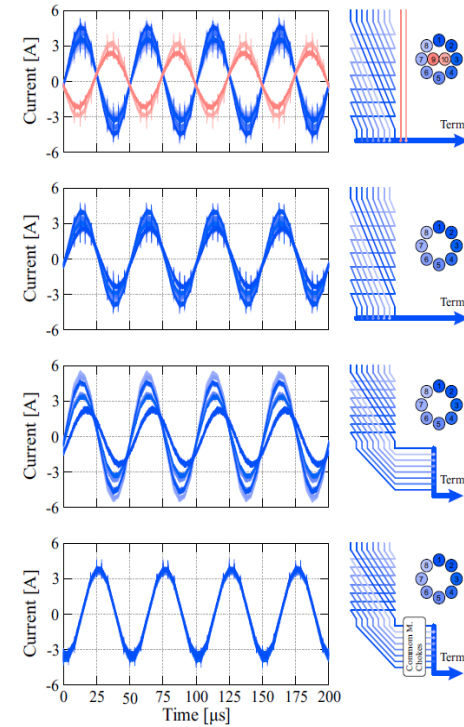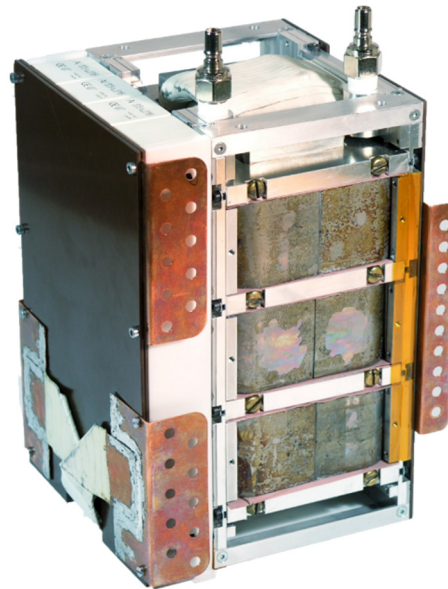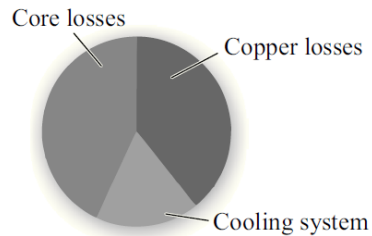
- **Nanocrystalline Cores with 0.1mm Airgaps between Parallel Cores for Equal Flux Partitioning**
- **Litz Wire (10 Bundles) with CM Chokes for Equal Current Partitioning**



► Further MF Transformer Examples

- Coaxial Windings – Shell Type
- Tunable Leakage Inductance
- Simple Terminations

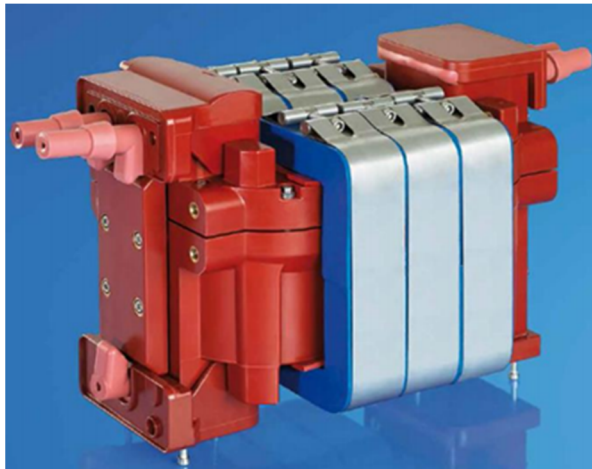
- 450kW @ 8 kHz / 50kg
- 99.7% Efficiency
- Dry Type / Liquid Isolation for 34.5kV



STS (2014)
www.sts-trafo.com

- 350kW @ 8 kHz
- Water Cooling / Hollow Conductors
- Isolation for 33kV

Steiner (2007)

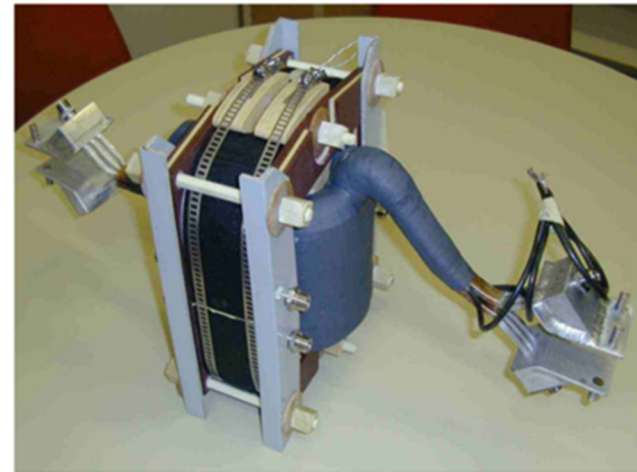

- 1 MVA @ 50Hz → 2600kg / 99% Efficiency @ Rated Load (!)

Challenge #4/5

Mains ← *SST* → *Load*
Protection





► Conv. MV → LV XFRM – Overvoltage Requirements

- Extreme Overvoltage Stresses on the MV Side for Conv. Distr. Grids
- SST More Appropriate for Local Industrial MV Grids

- ① Internal Fault
 - ② Lightning Surge
 - ③ Switching Transient
 - ④ MV Short Circuit
 - ⑤ LV Short Circuit
 - ⑥ Non-Ideal Load

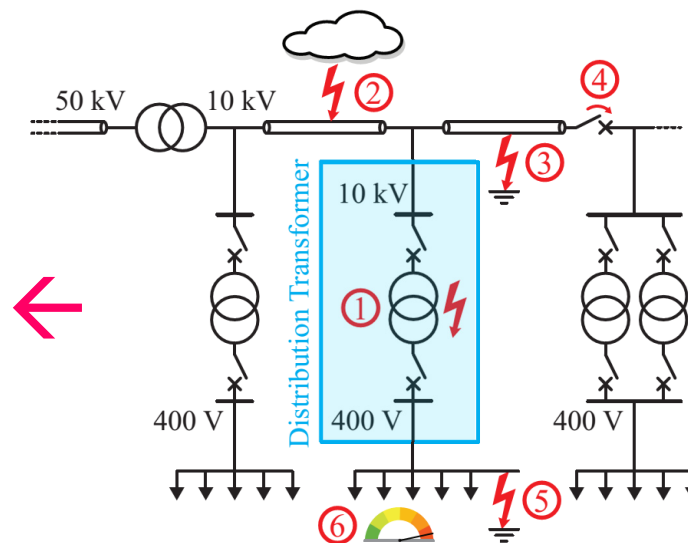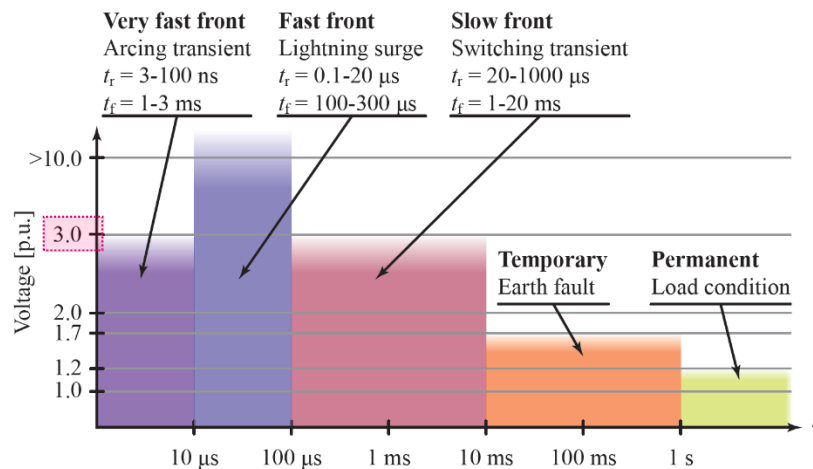
● Conv. MV Grid Time-Voltage Characteristic



► Overvoltage Protection of SST


■ Missing Analysis of SST Faults (Line-to-Line, Line-to-Gnd, S.C., etc.) & Protection Schemes

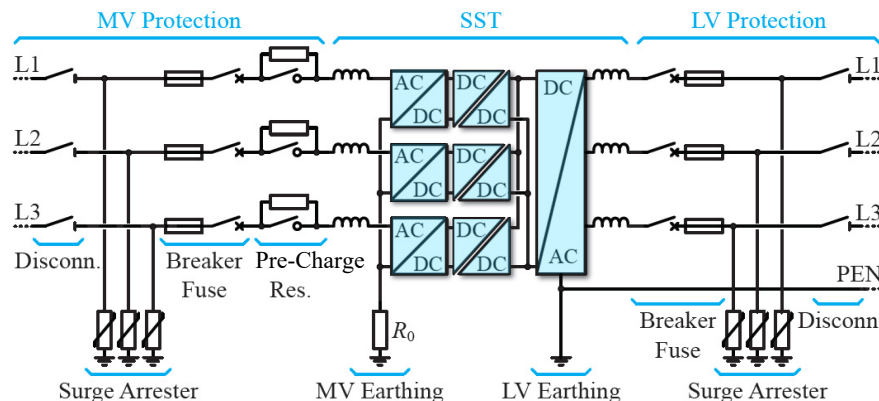● Proposed SST Protection Scheme with Minimum # of Protection Devices



● Overvoltage Protection (Lightning Strike)

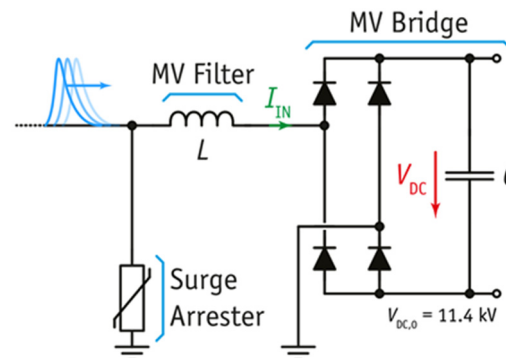- * High Arrester Clamping Voltage
- * Filter Inductor > 8% for Current Limiting
- * Requires Min. DC Link Capacitance
- * Sufficient Blocking Capability
- * Grounding – Lower Stress if Unearthed




■ Protection Scheme Needs to Consider: Selectivity / Sensitivity / Speed / Safety / Reliability

► Conv. MV→LV XFRM – Overcurrent Requirements



400V Fuse / 630kVA XFRM

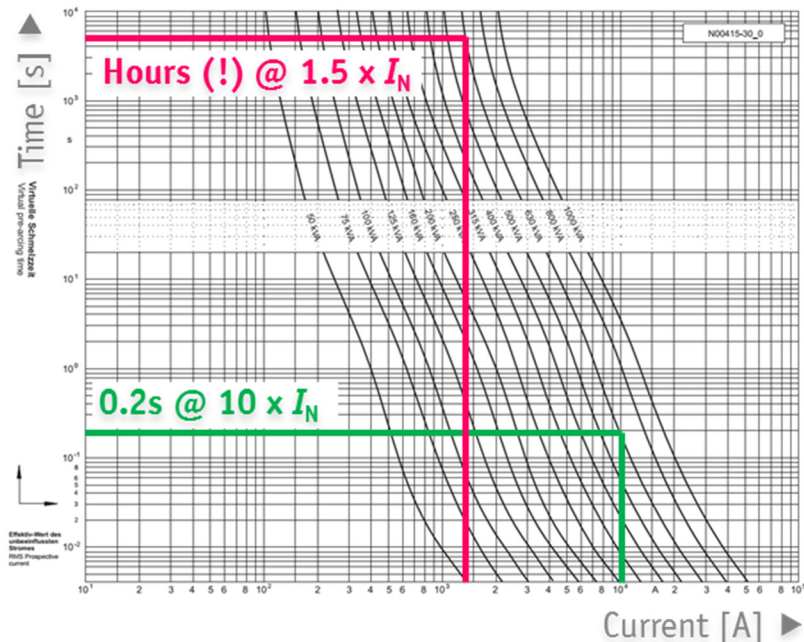


- Very High Currents Required to Trip Fuses OR Protection Relays
- Low-Freq. XFRM must Provide Short-Circuit Currents of up to 10 Times Nominal Current for 200 ms

- Lower Grid Voltage Levels → Higher Relative Short Circuit Currents
- SST is NOT (!) a 1:1 Replacement for a Conventional Low-Frequency XFRM


Challenge #5/5

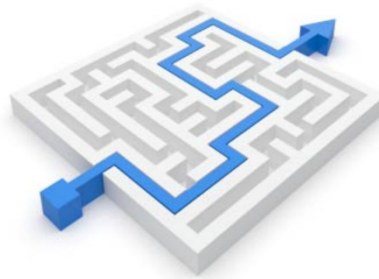*Ensuring Reliability of Highly Complex
Multi-Cell Converter Topologies*




► Reliability Model (1) – Failure Rate

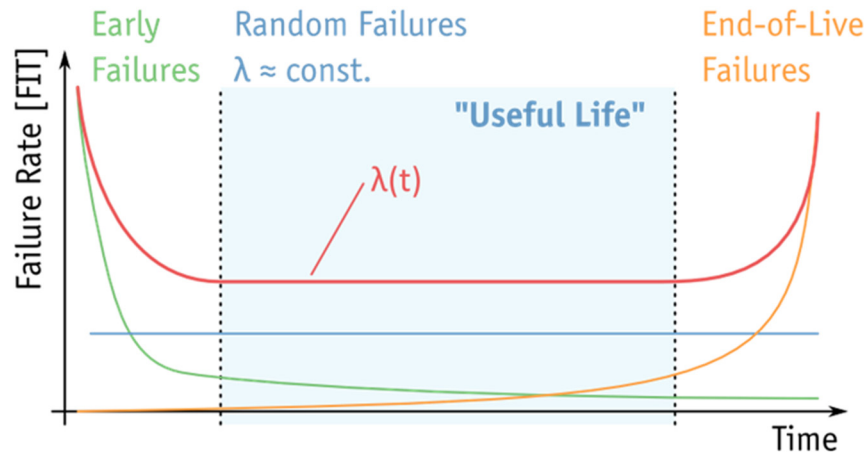- Failure Rate $\lambda(t)$ is a Function of Time – „Bathtub Curve“
- Useful Life Dominated by Random Failures $\rightarrow \lambda(t) = \text{const.}$
- $[\lambda] = 1 \text{ FIT}$ (1 Failure in 10^9 h)
- Typ. Value for IGBTs: 100 FIT



Source: H.-G. Eckel
Univ. Rostock

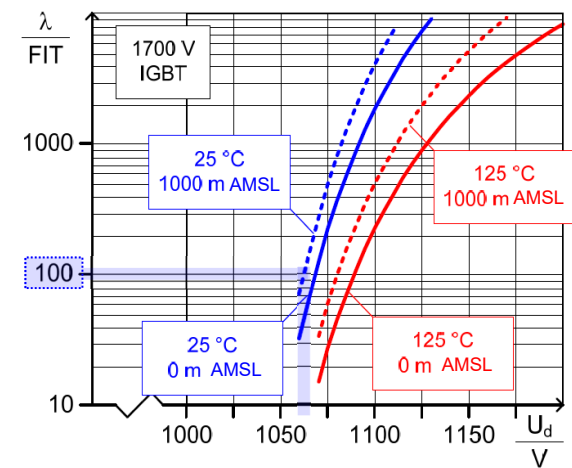


- Sources for Empirical Component Failure Rate Data : MIL-HDBK-217F, IEC Standard 62380, etc.

► Reliability Model (2) – Reliability Function

- **Reliability Function:** Probability of System being Operational after t :

$$R(t) = e^{-\int_0^t \lambda(x) dx} = e^{-\lambda t}$$


$\lambda(t) = \text{const.}$

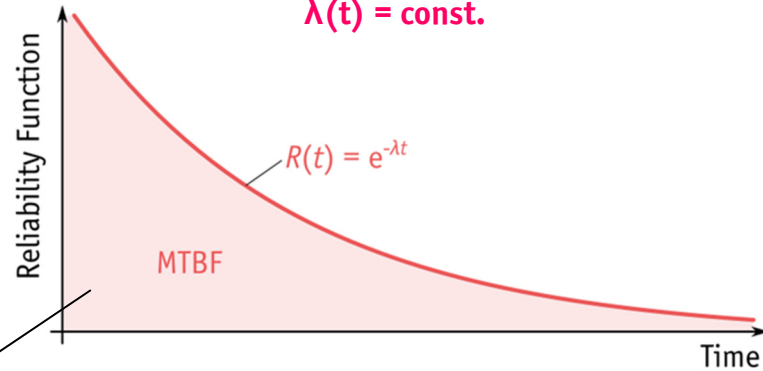

- **Mean Time Between Failures**


$$\text{MTBF} = \int_0^{\infty} R(t) dt = \int_0^{\infty} e^{-\lambda t} dt = \frac{1}{\lambda}$$

- **Series Structure**

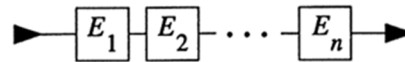

$$\lambda_S = \sum_{i=1}^n \lambda_i$$


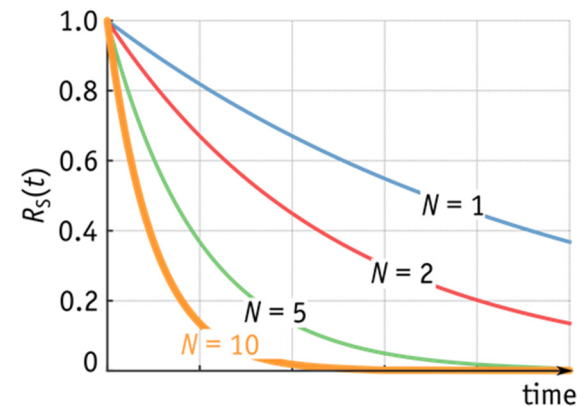
Independent Cells with Equal Failure Rate





Redundancy in Multi-Cell Converter Systems

- k -out-of- n Redundancy**
Redundancy of Cells in Phase Stack

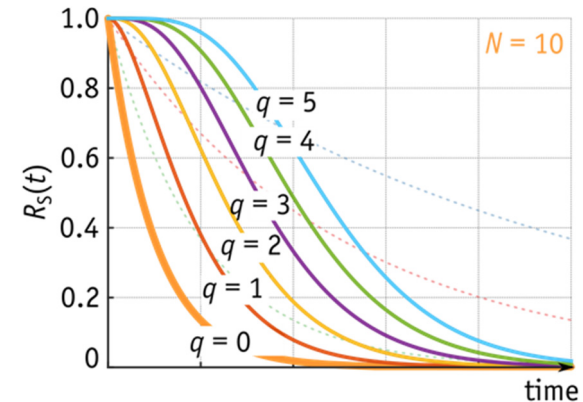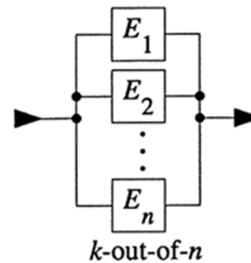System is Operational as Long as at Least k -out-of- n Subsystems are Working



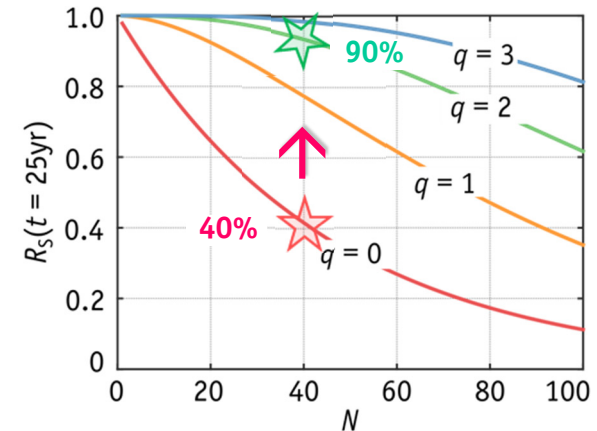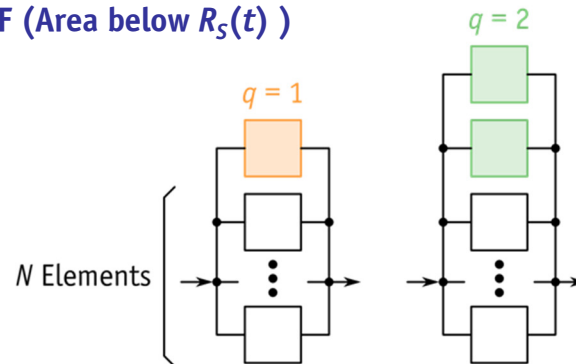- Effect of q Redundant Cells on $R_S(t)$ and/or MTBF (Area below $R_S(t)$)




- Redundancy Significantly Improves System Level Reliability (!)

Redundancy in Single-Cell Converter Systems

Source: M. Doppelbauer
M. Hiller


Example: Three-Level MV Motor Drive


Redundant Series Device

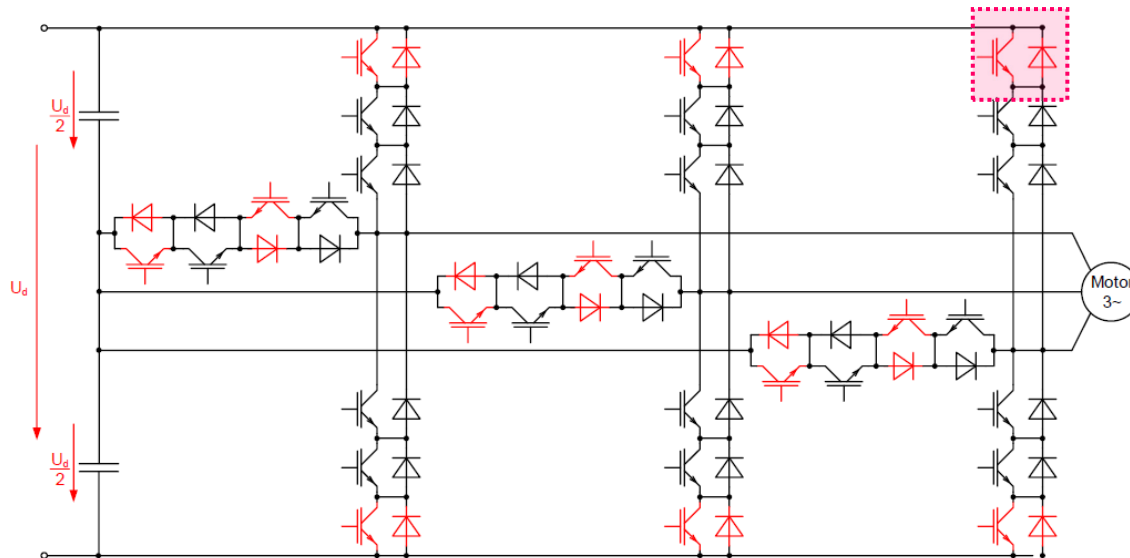

Press-Pack NPC Phase Module



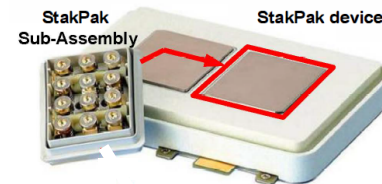- Fail-to-Short Behavior Required (!)
- Only Feasible with Press-Pack Modules




SST Demonstrator Systems

Future Locomotives
Smart Grid Applications

▶ 1ph. AC/DC Power Electronic Transformer - PET

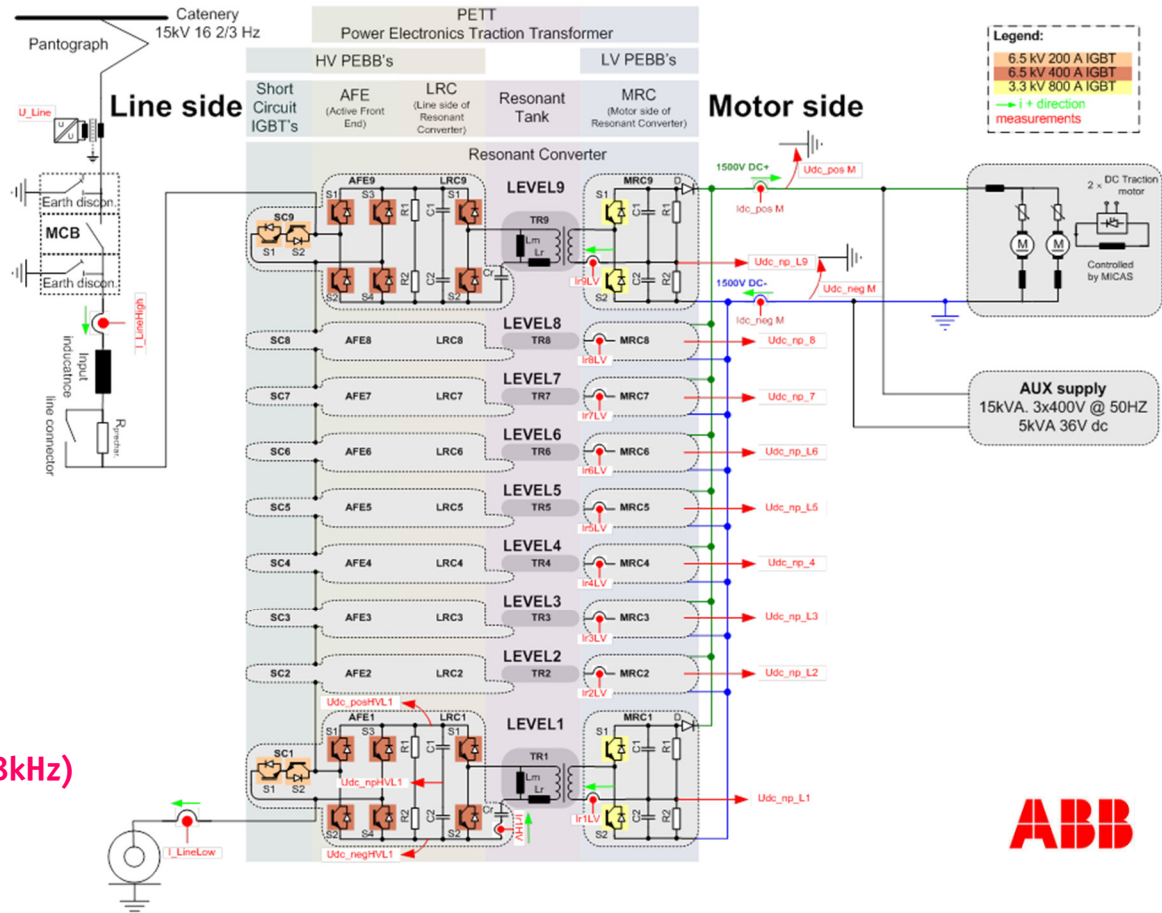- Dujic et al. (2011)
- Heinemann (2002)
- Steiner/Stemmler (1997)
- Schibli/Rufer (1996)



$P = 1.2\text{MVA}, 1.8\text{MVA pk}$
9 Cells (Modular)

54 x (6.5kV, 400A IGBTs)
18 x (6.5kV, 200A IGBTs)
18 x (3.3kV, 800A IGBTs)



9 x MF Transf. (150kVA, 1.8kHz)
1 x Input Choke

▶ 1.2 MVA 1ph. AC/DC Power Electronic Transformer

- Cascaded H-Bridges – 9 Cells
- Resonant LLC DC/DC Converter Stages



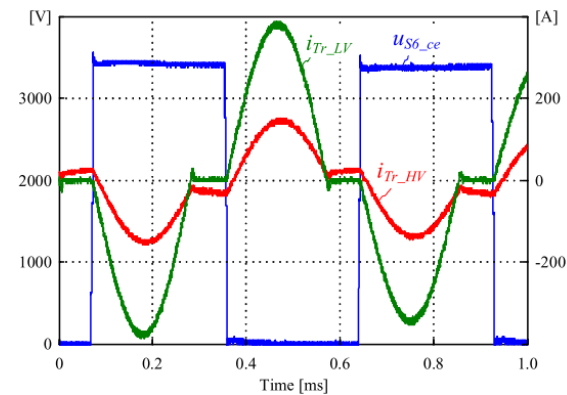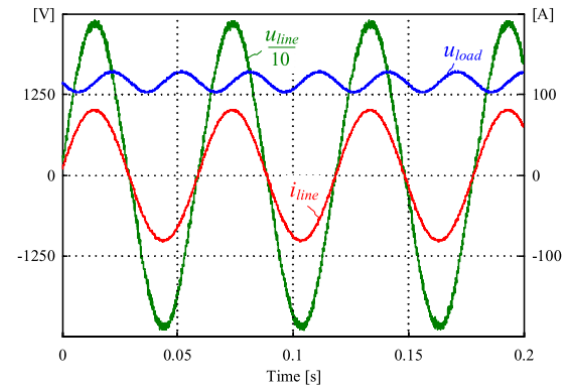- Same Overall Volume as Conv. System
- Future Development Targets Cutting Volume in Half




▶ 1.2 MVA 1ph. AC/DC Power Electronic Transformer

- Cascaded H-Bridges – 9 Cells
- Resonant LLC DC/DC Converter Stages



- Same Overall Volume as Conv. System
- Future Development Targets Cutting Volume in Half



Efficiency

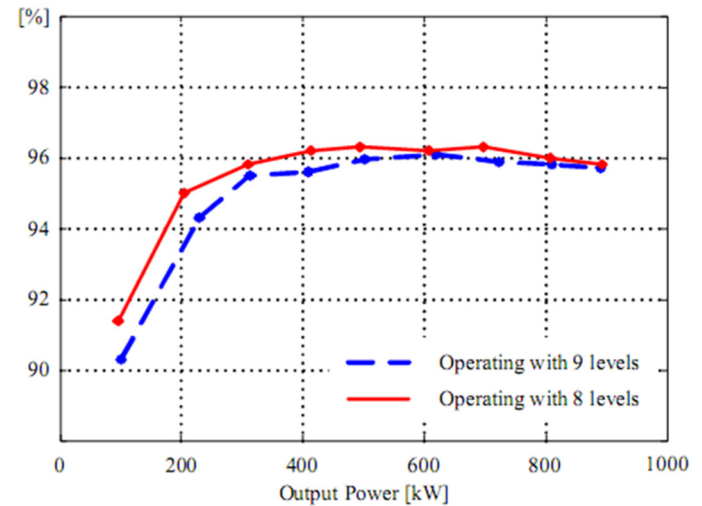

► SiC-Enabled Solid-State Power Substation



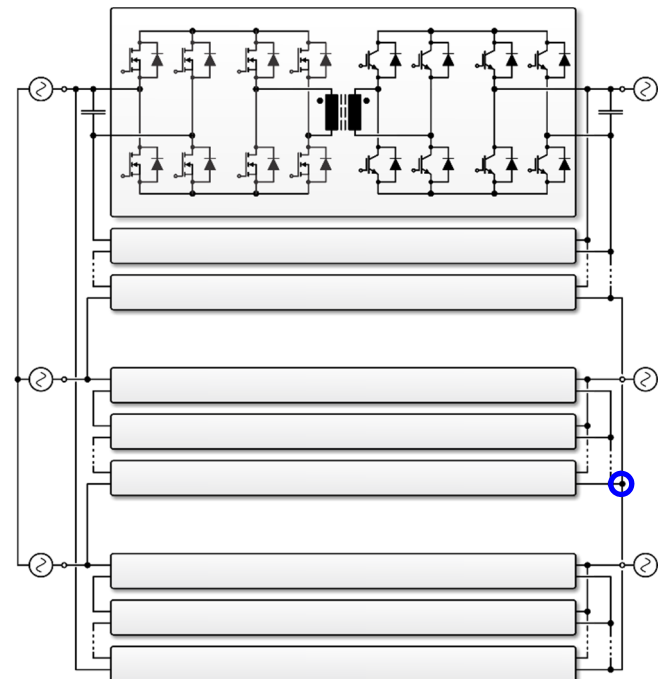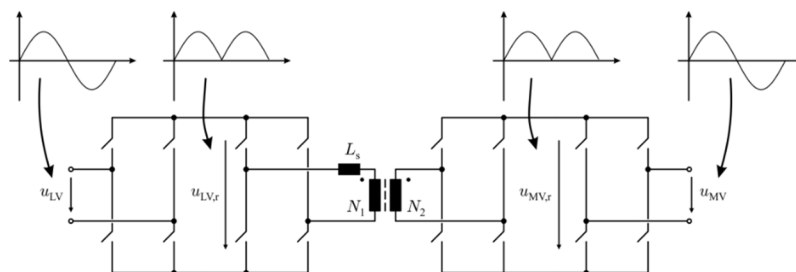- Das et al. (2011)
- Lipo (2010)
- Weiss (1985 for Traction Appl.)
- Fully Phase Modular System
- Indirect Matrix Converter Modules ($f_1 = f_2$)
- MV Δ -Connection (13.8kV_{L-L}, 4 Modules in Series)
- LV Y-Connection (265V, Modules in Parallel)




- SiC Enabled 20kHz/1MVA “Solid State Power Substation”
- 97% Efficiency @ Full Load / 1/3rd Weight / 50% Volume Reduction (Comp. to 60Hz)

► SiC-Enabled Solid-State Power Substation

- Das et al. (2011)

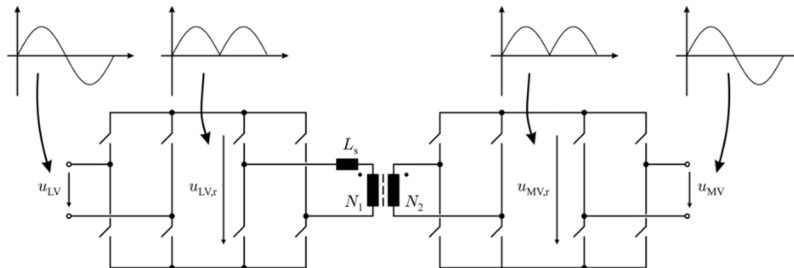- Fully Phase Modular System
- Indirect Matrix Converter Modules ($f_1 = f_2$)
- MV Δ -Connection (13.8kV_{L-L} , 4 Modules in Series)
- LV Y-Connection (265V , Modules in Parallel)





- SiC Enabled 20kHz/1MVA "Solid State Power Substation"
- 97% Efficiency @ Full Load / 1/3rd Weight / 50% Volume Reduction (Comp. to 60Hz)

► SST vs. LF Transformer + AC/AC or AC/DC Converter

- Specifications
 - 1MVA
 - 10kV Input
 - 400V Output
 - 1700V IGBTs (1kHz/8kHz/4kHz)

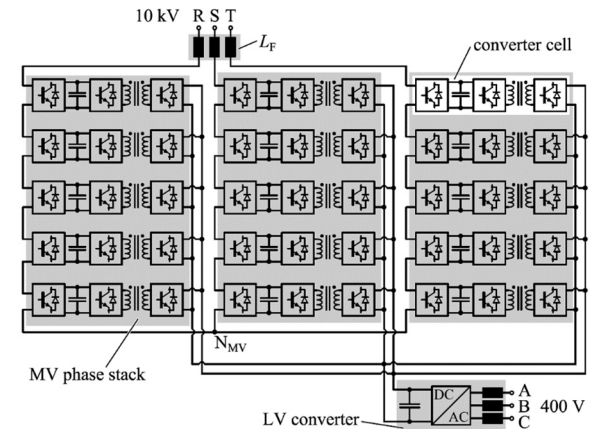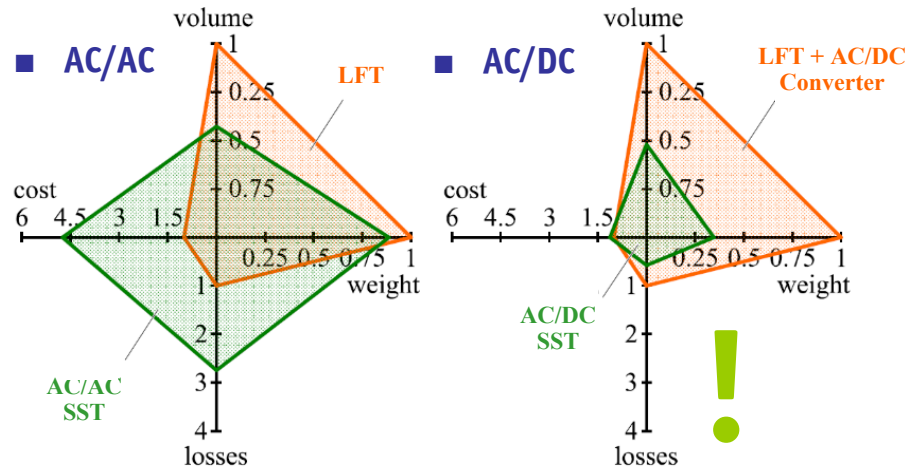- LF Transformer
 - 98.7 %
 - 16.2 kUSD
 - 2600kg (5700lb)



- Clear Efficiency/Volume/Weight Advantage of SST for DC Output (98.2%)
- Weakness of AC/AC SST vs. Simple LF Transformer (98.7%) - 5 x Costs, 2.5 x Losses

Potential Future SST Application Areas

Datcenters
High Power/Fast EV Charging
Off-Shore Wind
Oil and Gas Industry
Power-to-Gas
Distributed Propulsion Aircraft
More Electric Ships



► Green / Zero Datacenters

- Ranging from Medium Voltage to Power-Supplies-on-Chip
- Short Power Supply Innovation Cycles
- Modularity / Scalability
- Higher Availability
- Higher Efficiency
- Higher Power Density
- Lower Costs

Server-Farms
up to 450 MW
99.9999% / <30s/a
\$1.0 Mio./Shutdown

Since 2006
Running Costs >
Initial Costs


Source: REUTERS/Sigtryggur Ari

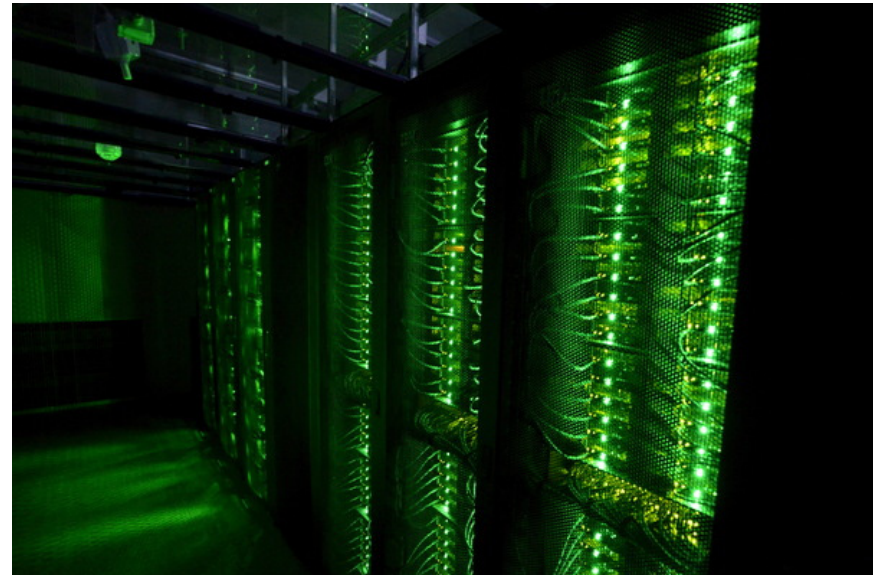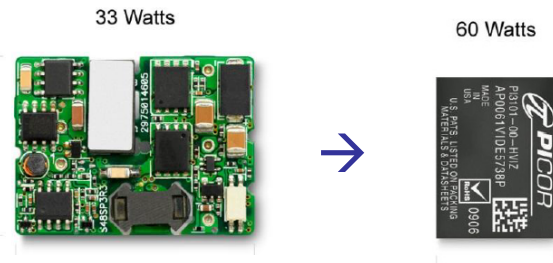


► SST-Based 400V DC-Distribution System

- Reduces Losses & Footprint
- Improves Reliability & Power Quality

— Conventional

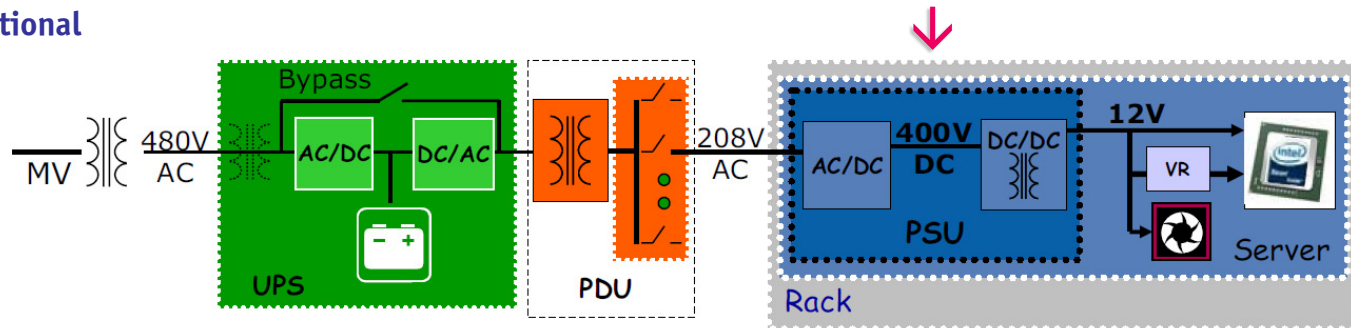

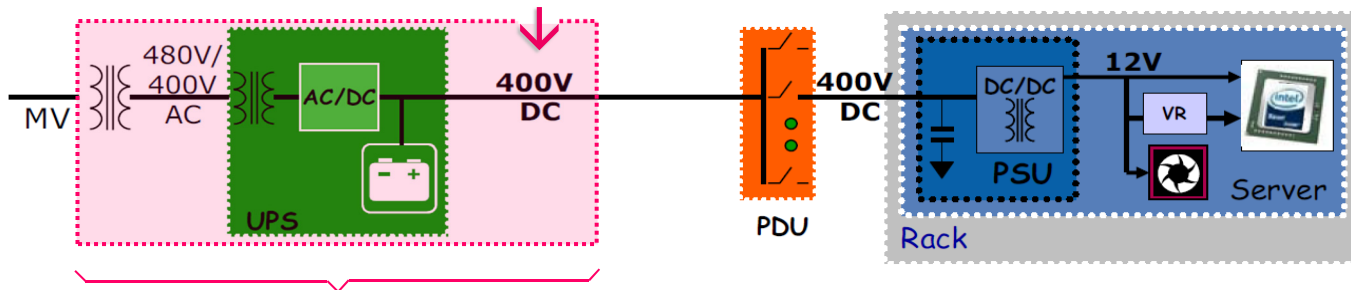— Facility-Level 400 V_{DC} Distribution → Gain in Efficiency / Complexity




- Direct 3- Φ 6.6kV AC → 400V DC Conversion / Unidirectional SST

25kW SwiSS-Transformer

- Bidirectional $1-\Phi$ 3.8 kV_{rms} AC \rightarrow 400V DC Power Conversion
- Based on 10kV SiC MOSFETs
- Full Soft-Switching

★ 3.3 kW/dm³

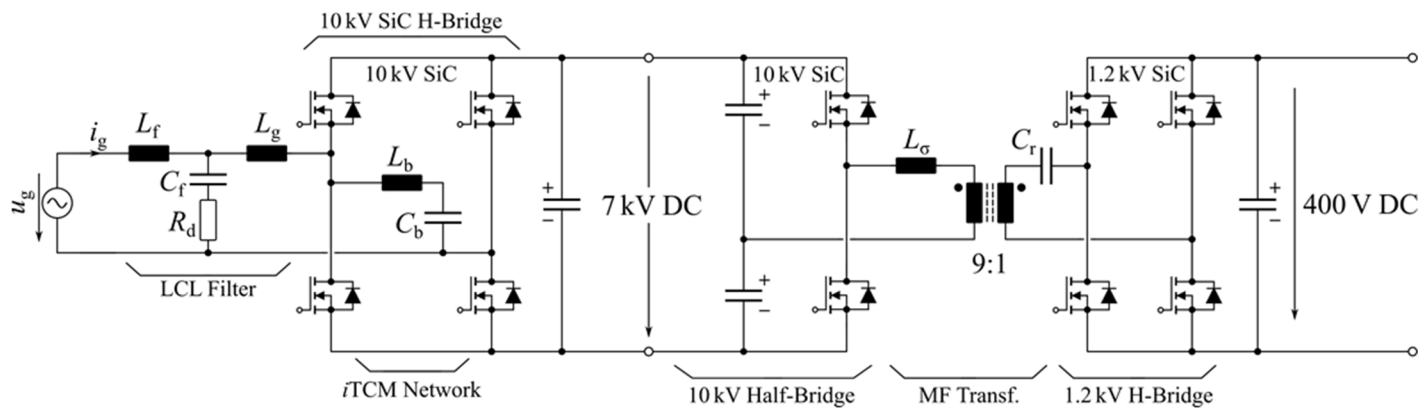

★ 3.8 kW/dm³



► 35...75kHz iTCM Input Stage

► 48kHz DC-Transformer Output Stage

▶ 3.8kV → 7kV ZVS AC/DC Converter

■ Full-Bridge *i*TCM – integrated Triang. Current Mode Operation Enables ZVS

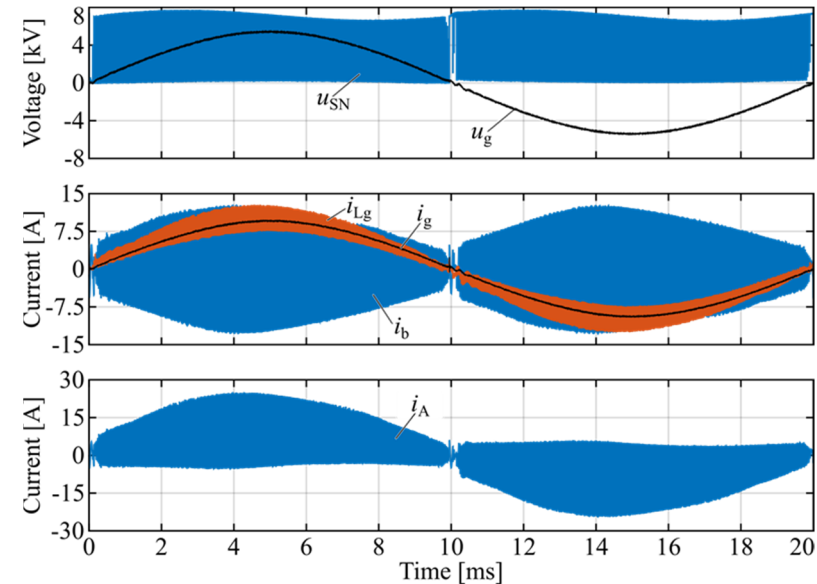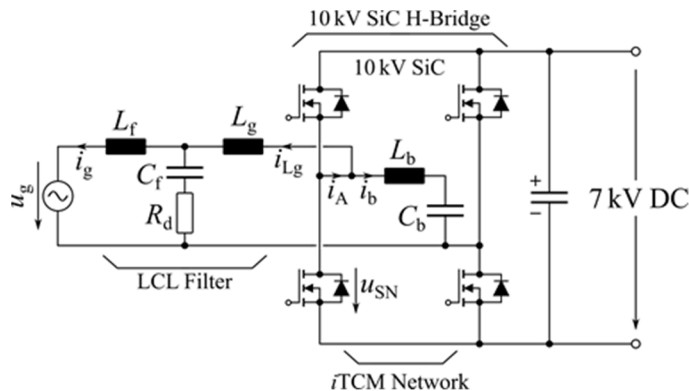- ZVS Requires Change of Sw. Current Direction in Each Sw. Period
- Open-Loop Variation of Sw. Frequency for ZVS (35...75kHz)
- Separate Optim. of ZVS and Input Inductor Possible
- No Large Ripple Input Current





▶ Full-Load Measurement (25kW @ 3.8kVrms AC, 7kV DC) - ZVS Over Full AC Cycle (!)

▶ 3.8kV → 7kV ZVS AC/DC Converter

■ Full-Bridge *i*TCM – integrated Triang. Current Mode Operation Enables ZVS

- ZVS Requires Change of Sw. Current Direction in Each Sw. Period
- Open-Loop Variation of Sw. Frequency for Const. ZVS Current (35...75kHz)
- Separate Optim. of ZVS and Input Inductor Possible
- No Large Ripple Input Current

★ 3.3 kW/dm³

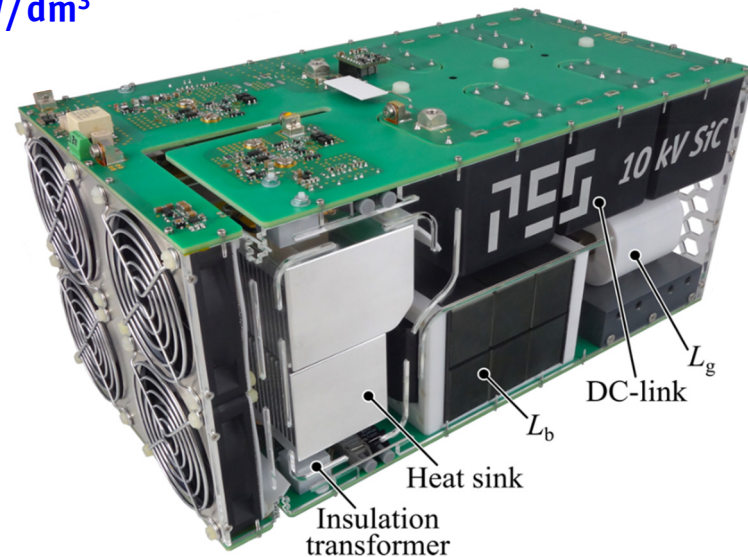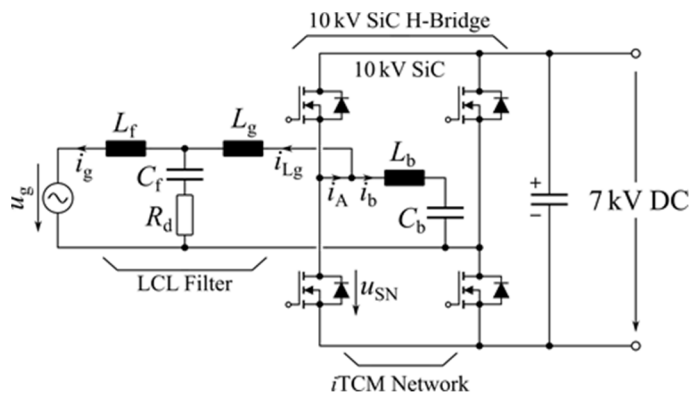



▶ Full-Load Measurement (25kW @ 3.8kVrms AC, 7kV DC) - ZVS Over Full AC Cycle (!)

► 7kV → 400V DC/DC Converter

■ MV-Side Half-Bridge

- 48kHz Sw. Frequency, ZVS
- Cooling of Power Semicond. by Floating Heatsinks (Not Shown)
- Creepage Distances Ensured by PCB Slots

★ 3.8 kW/dm³

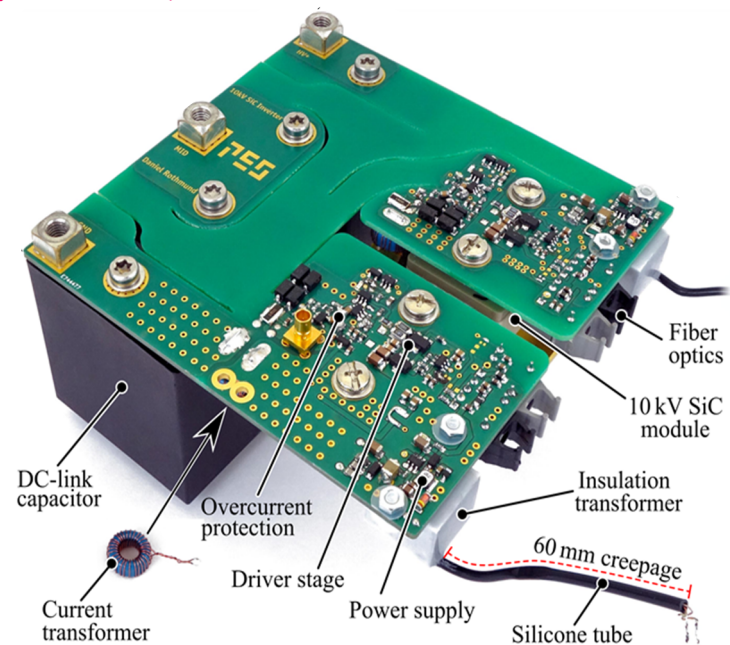
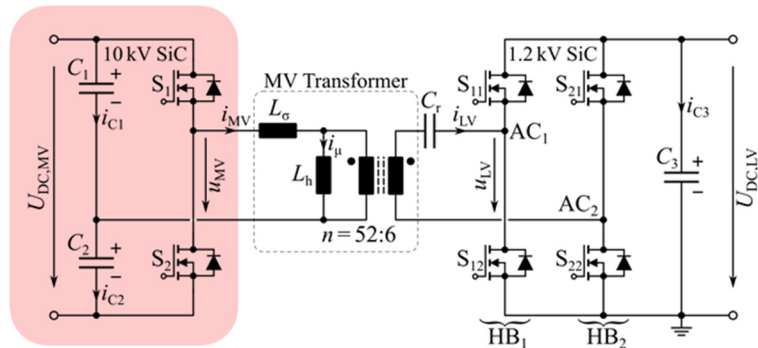


► Half-Bridge for Cutting Voltage in Half / Lower Switch Count

► 7kV → 400V DC/DC Converter

■ MF-Transformer Measurement

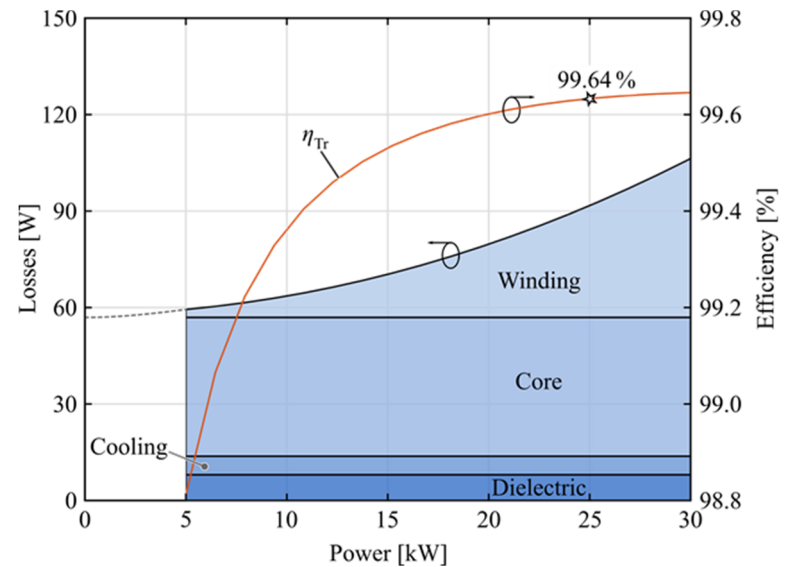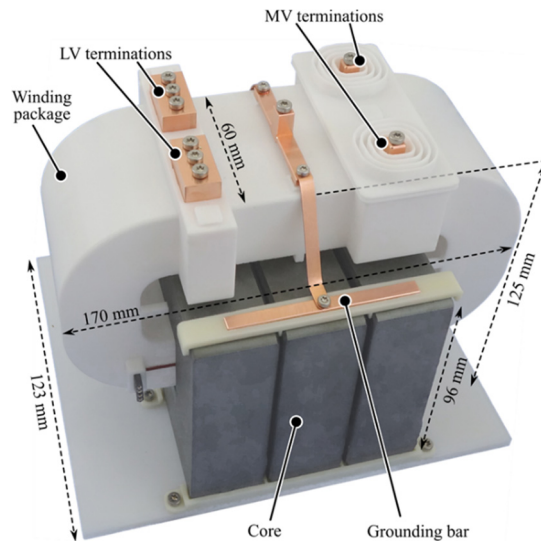
- Fully Tested @ 25kW / 7 kV
- Calorimetric Loss Measurement
- **99.64% Efficiency**



► Transformer Prototype / Loss Distribution / Efficiency

► Overall Performance

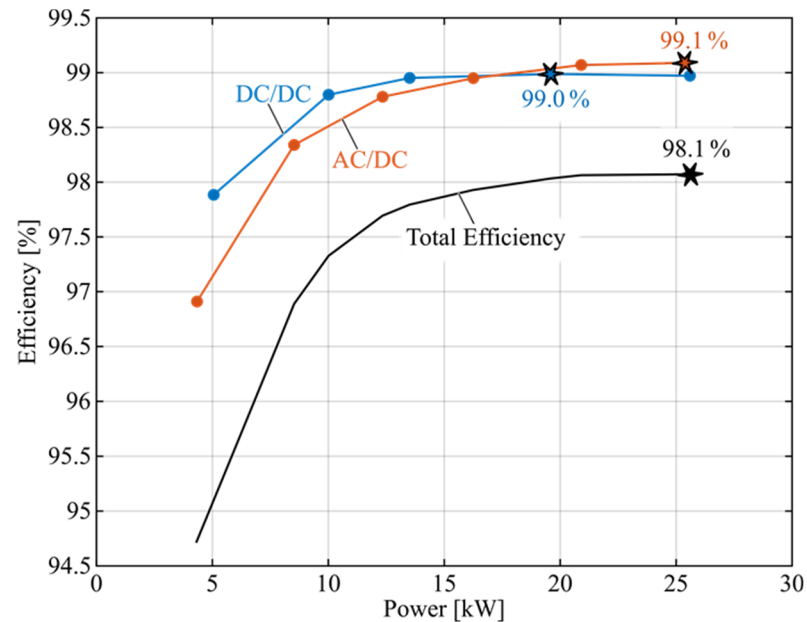- Full Soft-Switching
- 98.1% Overall Efficiency @ 25kW
- 1.8 kW/dm³ (30W/in³)




- Red. of Losses & Volume by Factor of >2 Comp. to Alternative Approaches (!)
- Significantly Simpler Compared to Multi-Module SST Approach

► Ultra-Fast / High-Power EV Charging

- **Medium Voltage** Connected Modular Charging Systems (e.g. Porsche *FlexBox* incl. Cooling)
- **Very Wide Output Voltage Range** (200...800V)




Source: Porsche Mission-E Project

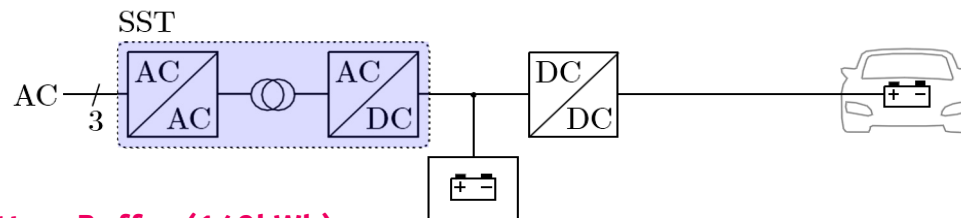

- **Local Battery Buffer (140kWh)**
- **320kW → 400km Range in 20min**

► On-Shore/Off-Shore Windfarms

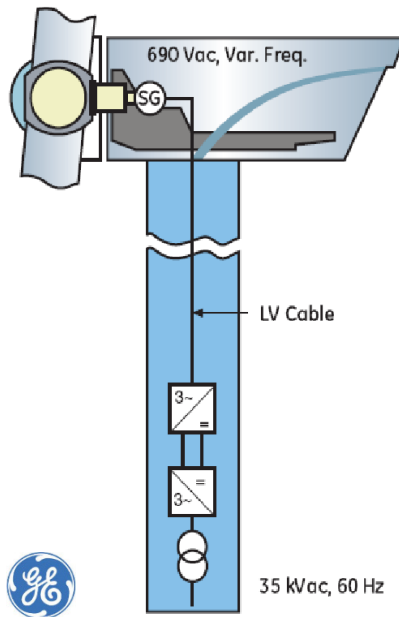- **Current 690V Electrical System** → Significant Cabling Weight/Costs & Space Requirement
- **Future Local Medium-Frequency Conv. to Medium-Voltage AC or DC**




► On-Shore Wind Power System



► On-Shore/Off-Shore Windfarms

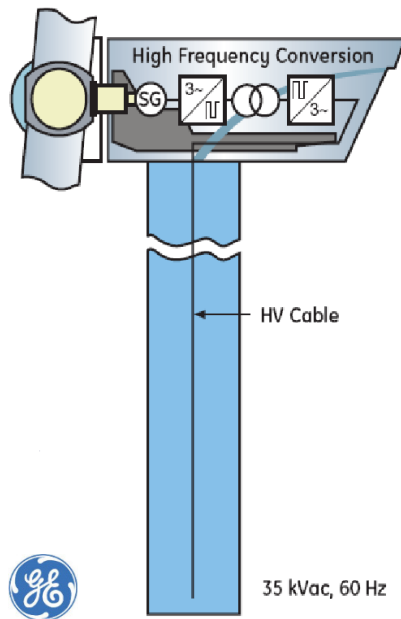- **Current 690V Electrical System** → Significant Cabling Weight/Costs & Space Requirement
- **Future Local Medium-Frequency Conv. to Medium-Voltage AC or DC**




► **Future Off-Shore System**

Source: M. Prahm / Flickr





DC Collection Grids

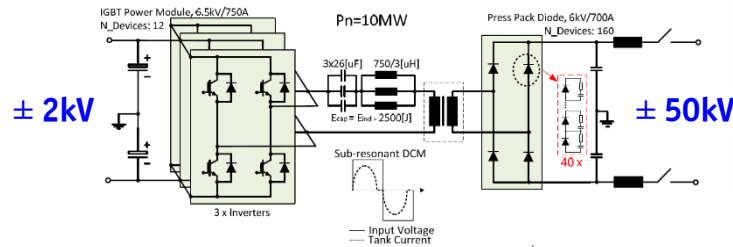- ± 50kV DC Offshore Collection Grid
- ± 50kV / ± 320kV DC/DC Offshore Substation
- ± 320kV HVDC Transmission to Shore



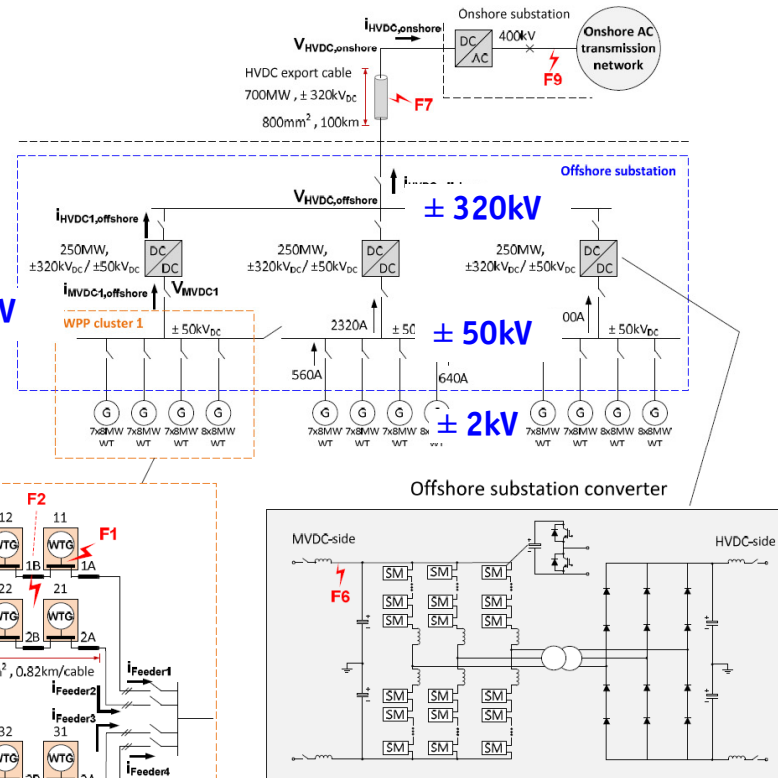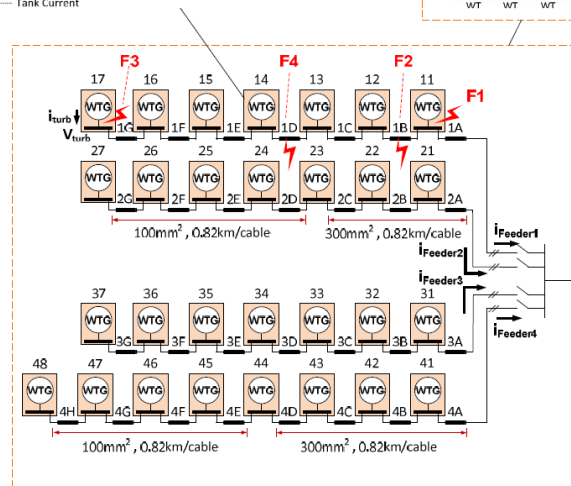- Unidirectional Series Resonant MF DC→MVDC Conversion in Each Wind Turbine




- MMLC-Based MF Isolation

Source: Kjaer/2016

► Power-to-Gas

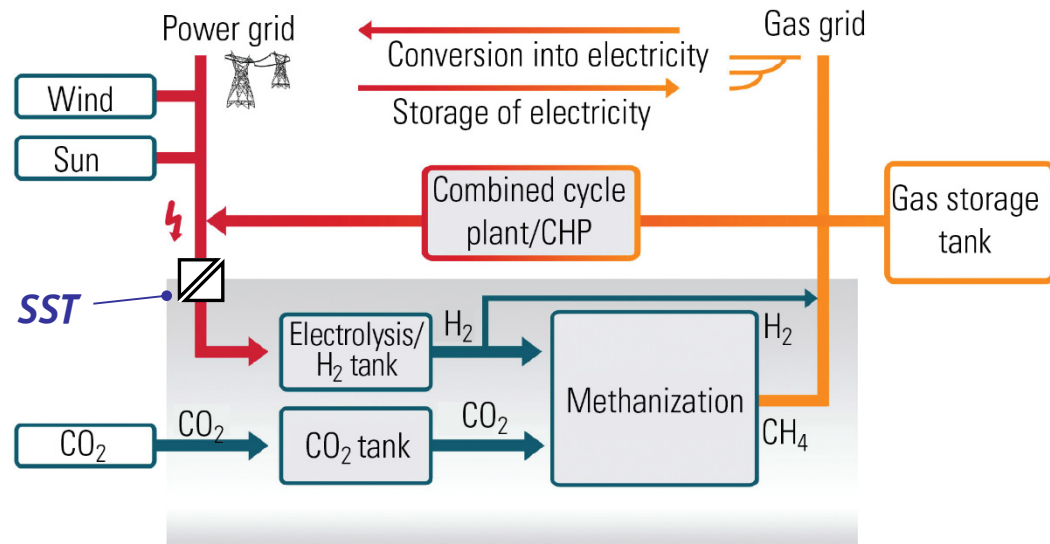
- **Electrolysis for Conversion of Excess Wind/Solar Electric Energy into**
 - Hydrogen
 - Fuel-Cell Powered Cars
 - Heating
- High-Power @ Low DC Voltage (e.g. 220V)
- Very Well Suited for MV-Connected SST-Based Power Supply



– Hydrogenics 100 kW H₂-Generator ($\eta=57\%$)

Source: www.r-e-a.net

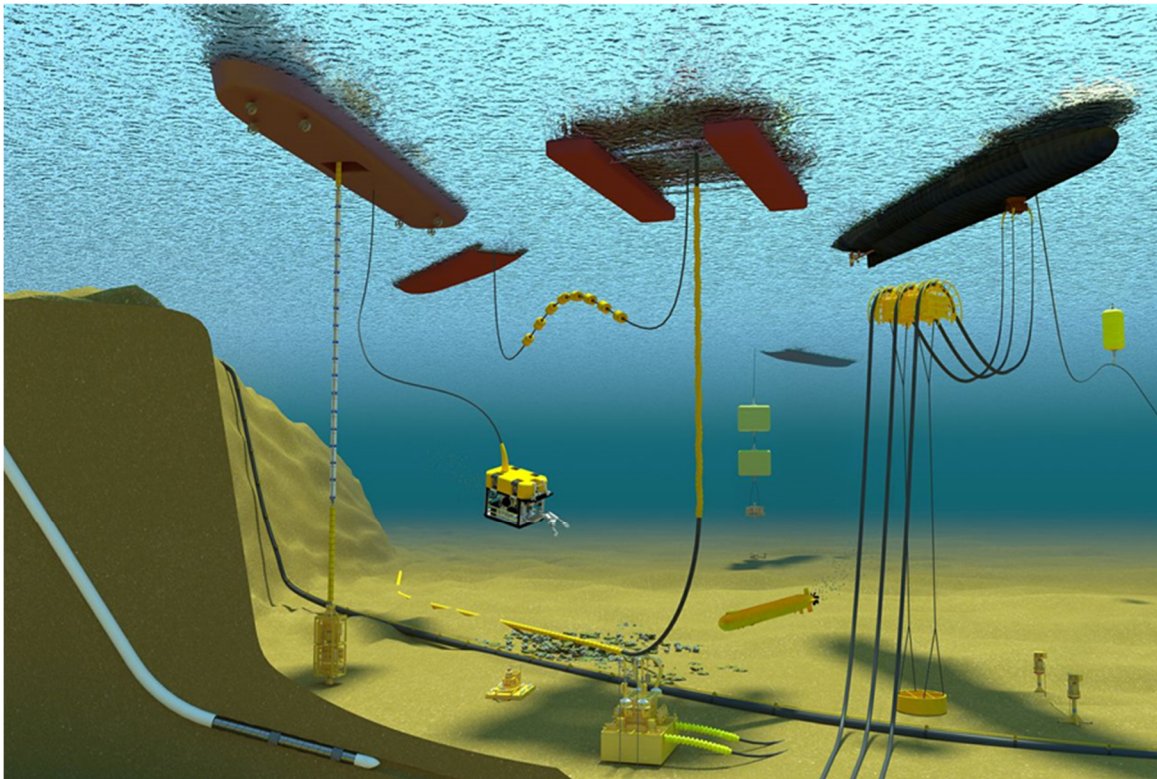► *Subsea Applications – Oil & Gas Processing*





- **ABB's Future Subsea Power Grid** → "Develop All Elements for a Subsea Factory"

Future Subsea Distribution Network

- Transmission Over DC, No Platforms/Floaters
- Longer Distances Possible
- Subsea O&G Processing

- Weight Optimized Power Electronics

Source: Devold (ABB 2012)

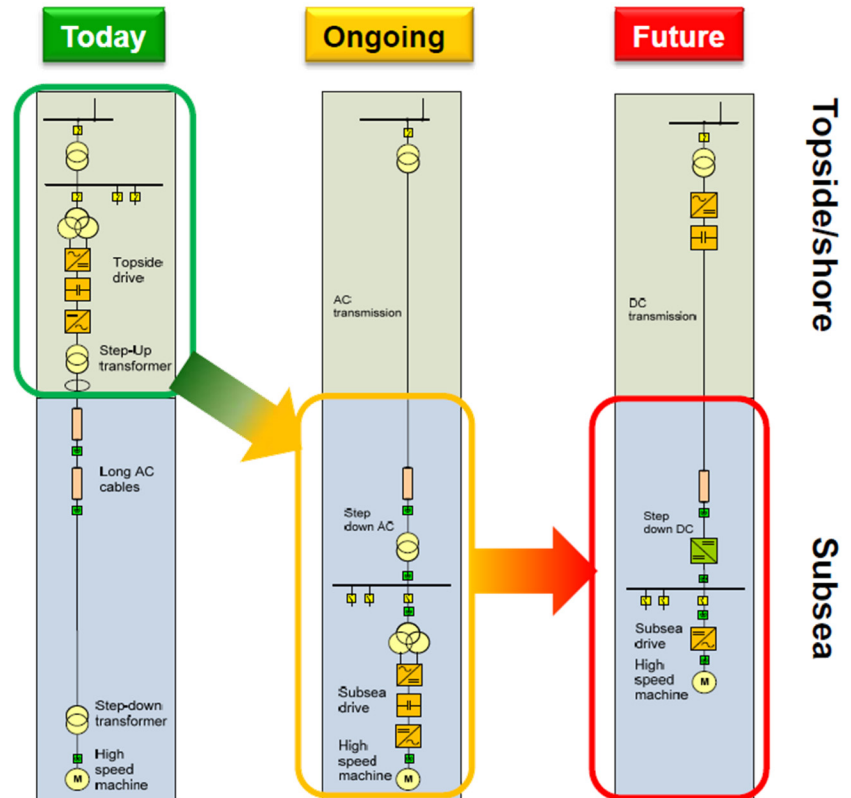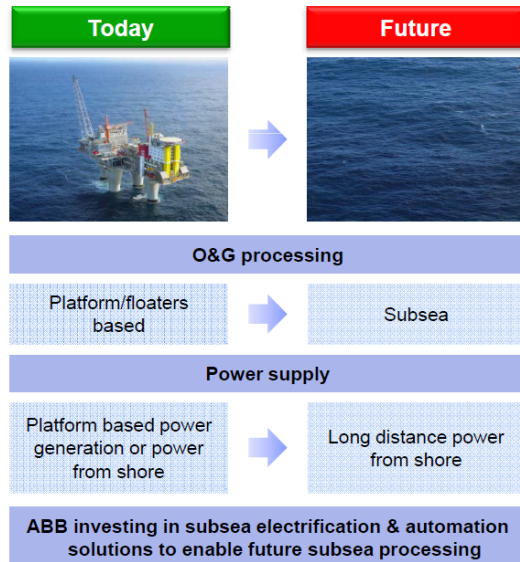

► *Future Hybrid & Distributed Propulsion Aircraft*

■ **Cut Emissions Until 2050**

- **CO₂ by 75%,**
- **NO_x by 90%,**
- **Noise Level by 65%**

Source:

EADS


Future Hybrid
Distributed Propulsion Aircraft



- **Eff. Optim. Gas Turbine**
- **Distrib. Fans (E-Thrust)**
- **1000Wh/kg Batteries**

- **Supercond. Motors**
- **MV Power Distribution**


► Future Distributed Propulsion Aircraft

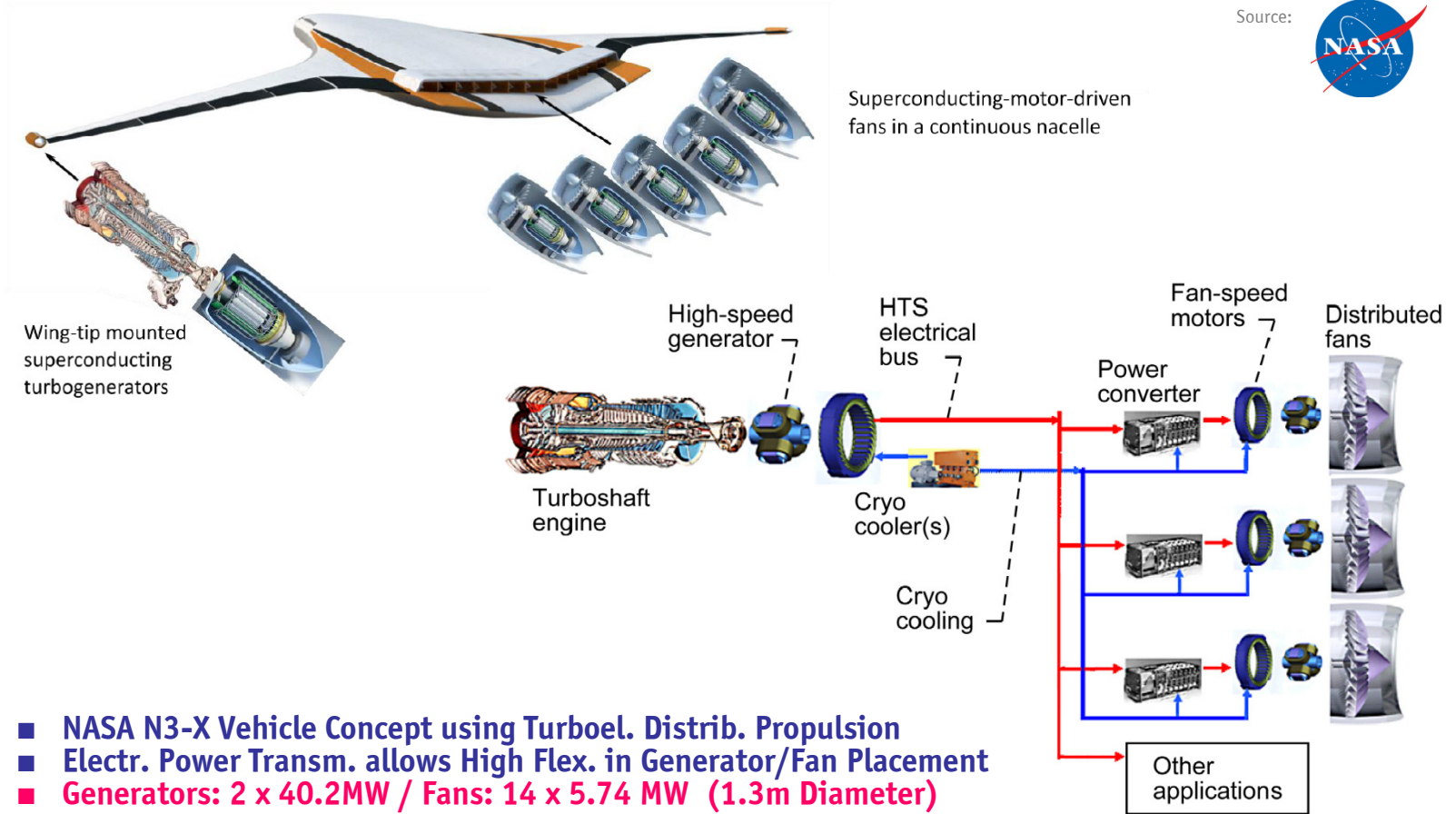

► *Future Naval Applications*

- **MV Cellular DC Power** Distribution on Future Combat Ships etc.



Source:
General Dynamics

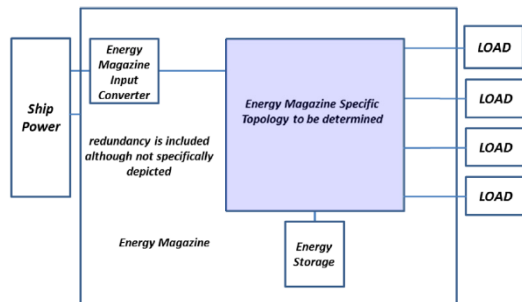

- **“Energy Magazine” as Extension of Electric Power System / Individual Load Power Conditioning**
- **Bidirectional Power Flow for Advanced Weapon Load Demand**
- **Extreme Energy and Power Density Requirements**

► Future Naval Applications

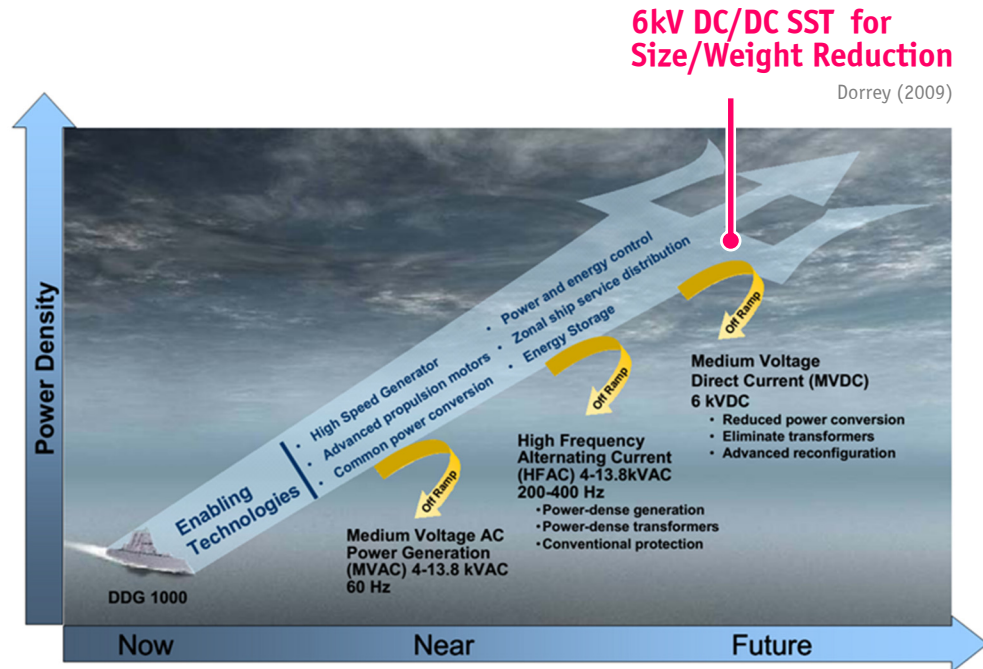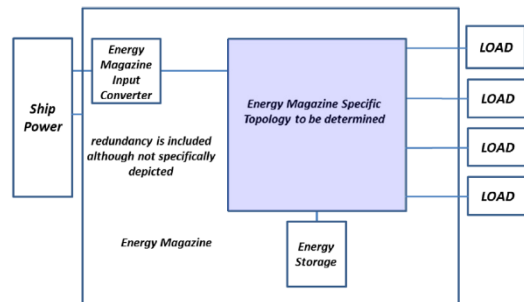- **MV Cellular DC Power Distribution** on Future Combat Ships etc.



- **“Energy Magazine” as Extension of Electric Power System / Individual Load Power Conditioning**
- **Bidirectional Power Flow for Advanced Weapon Load Demand**
- **Extreme Energy and Power Density Requirements**

Conclusions

*SST Limitations / Concepts
Research Areas*

► SST Ends the “War of Currents”

THE CURRENT WAR
THE TALE OF AN EARLY TECH RIVALRY

DC

DIRECT CURRENT

The flow of electricity is in one direction only. The system operates at the same voltage level throughout and is not as efficient for high-voltage, long distance transmission.

Direct current runs through:

- Battery-Powered Devices
- Fuel and Solar Cells
- Light Emitting Diodes

"TESLA'S IDEAS ARE SPLENDID, BUT THEY ARE UTTERLY IMPRACTICAL."
- THOMAS EDISON

THOMAS EDISON VS. **NIKOLA TESLA**

You would have never found two geniuses so spiteful of each other beyond turn-of-the-century inventors Nikola Tesla and Thomas Edison. They worked together—and hated each other. Let's compare their life, achievements, and embittered battles.

AC

ALTERNATING CURRENT

Electric charge periodically reverses direction and is transmitted to customers by a transformer that could handle much higher voltages.

Alternating current runs through:

- Car Motors
- Radio Signals
- Appliances

"IF EDISON HAD A NEEDLE TO FIND IN A HAYSTACK, HE WOULD PROCEED AT ONCE UNTIL HE FOUND THE OBJECT OF HIS SEARCH. I WAS A SORRY WITNESS OF SUCH DOINGS, KNOWING THAT A LITTLE THEORY AND CALCULATION WOULD HAVE SAVED HIM 90 PERCENT OF HIS LABOR."
- NIKOLA TESLA

1847 BORN 1858

Milan, Ohio BIRTHPLACE Smiljan, Croatia

Wizard of Menlo Park NICKNAME Wizard of the West

Home-schooled and self-taught EDUCATION Studied math, physics, and mechanics at The Polytechnic Institute at Graz

Mass communication and business FORTE Electromagnetism and electromechanical engineering

Trial and error METHOD Getting inspired and seeing the invention in his mind in detail before fully constructing it

DC (Direct Current) WAR OF CURRENTS: ELECTRICAL TRANSMISSION IDEA AC (Alternating Current)

Incandescent light bulb; phonograph; cement making technology; motion picture camera; DC motors and electric power NOTABLE INVENTIONS Tesla coil - resonant transformer circuit; radio transmitter; fluorescent light; AC motors and electric power generation system

1,093 NUMBER OF US PATENTS 112

0 NUMBER OF NOBEL PRIZES WON 0

1 NUMBER OF ELEPHANTS ELECTROCUTED 0

1931—Passed away peacefully in his New Jersey home, surrounded by friends and family. DEATH 1943—Died lonely and in debt in Room 3527 at the New Yorker Hotel

FALLING OUT

Edison promised Tesla a generous reward if he could smooth out his direct current system. The young engineer took on the assignment and ended up saving Edison more than \$100,000 (millions of dollars by today's standards). When Tesla asked for his rightful compensation, Edison declined to pay him. Tesla resigned shortly after and the elder inventor spent the rest of his life campaigning to discredit his counterpart.

Genius is one percent inspiration and ninety nine percent perspiration.
- Thomas Edison

LATE BLOOMER

Thomas Edison, the youngest in his family, didn't learn to talk until he was almost 4 years old.

WAR OF CURRENTS OFFICIALLY SETTLED

In 2007, Con Edison ended 125 years of direct current electricity service that began when Thomas Edison opened his power station in 1882. It changed to only provide alternating current.

EDISON FRIES AN ELEPHANT

In order to prove the dangers of Tesla's alternating current, Thomas Edison staged a highly publicized electrocution of the three-ton elephant known as "Topsy." She died instantly after being shocked with a 6,600-volt AC charge.

NOBEL PRIZE CONTROVERSY

In 1915, both Edison and Tesla were to receive Nobel Prizes for their strides in physics, but ultimately, neither won. It is rumored to have been caused by their animosity towards each other and refusal to share the coveted award.


SOURCES: CHENEY, MARGARET. "TESLA: MAN OUT OF TIME." | UHN, ROBERT. "TESLA: MASTER OF LIGHTNING." | THOMASEDISON.COM | PBS.ORG | WEB.MIT.EDU | WIRED.COM

A COLLABORATION BETWEEN GOOD AND COLUMN FIVE

■ No “Revenge” of T.A. Edison but Future “Synergy” of AC and DC Systems !

► The Solid-State Transformer Hype

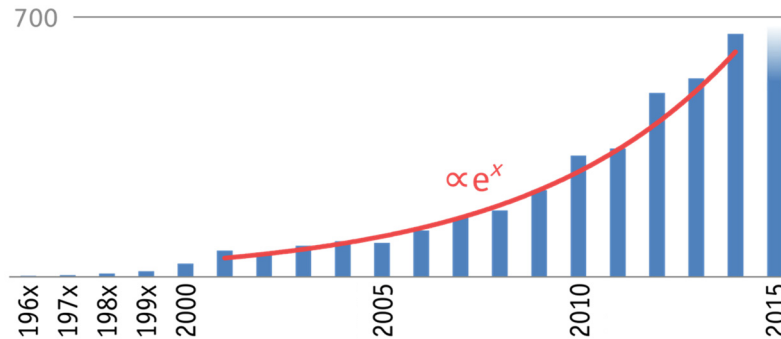- Large # of Publications !
- Research on Main Application Challenges Currently Largely Missing



- Protection (?)
- Control in Active Grids (?)
- System Level Adv. (?)

Source: And Update My Website

► SST Applications → *The Road Ahead*

- NOT (!) Weight / Space Limited
- Smart Grid, Stationary Applications



- AC/AC
- Efficiency Challenge
- More Eff. Voltage Control by
 - * Tap Changers
 - * Series Regulators (Partial Power)
- Not Compatible w. Existing Infrastr.
- Cost / Robustness / Reliability



- AC/DC
- Efficiency Challenge more Balanced
- "Local" Applic. (Datacenters, DC Distr.)
- Cost / Robustness / Reliability



- DC/DC
- No Other Option (!)
- MV DC Collection Grids (Wind, PV)
- Sw. Frequ. as DOF of Design


- Weight / Space Limited
- Traction Applic. etc.



- DC/DC
- AC/DC
- AC/AC
- Sw. Frequ. as DOF of Design
- Low Weight/Volume @ High Eff.
- Local Applic. (Load/Source Integr.)




► SST Development Cycles - Outlook

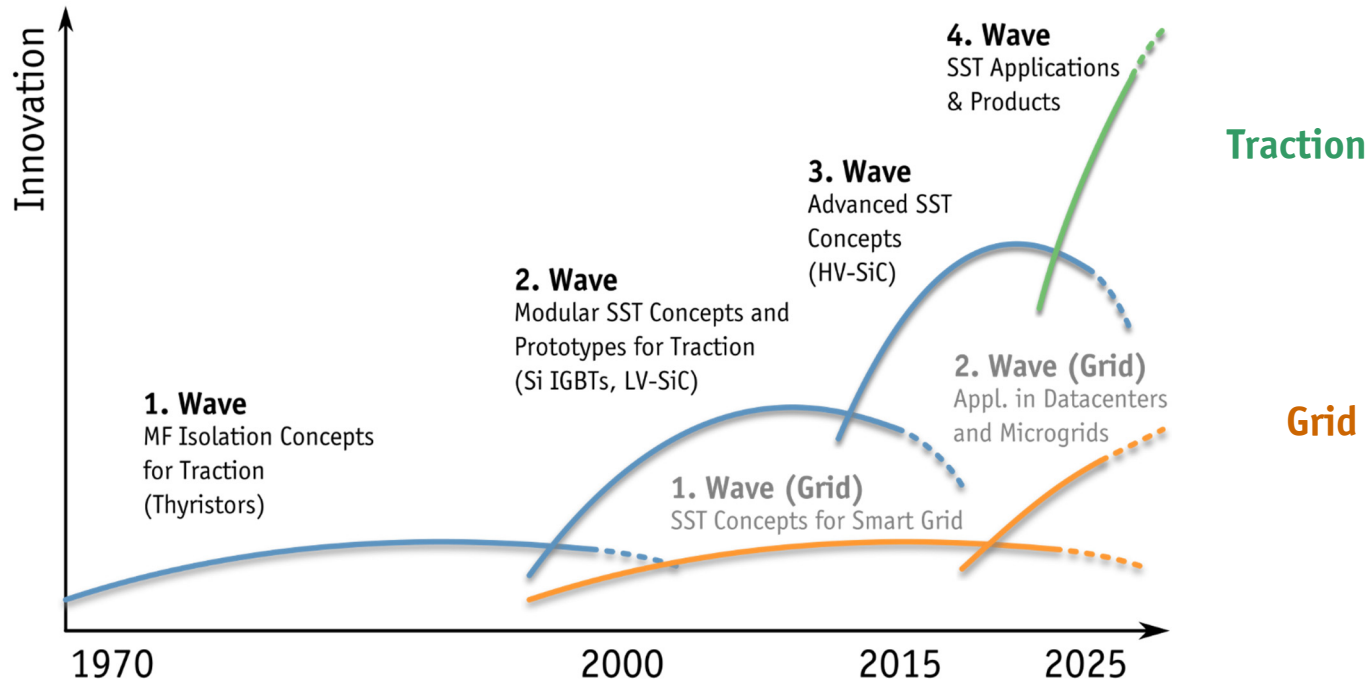

- Development Reaching Over Decades – Matched to “Product” Life Cycle

Remark "Hybrid" Transformers

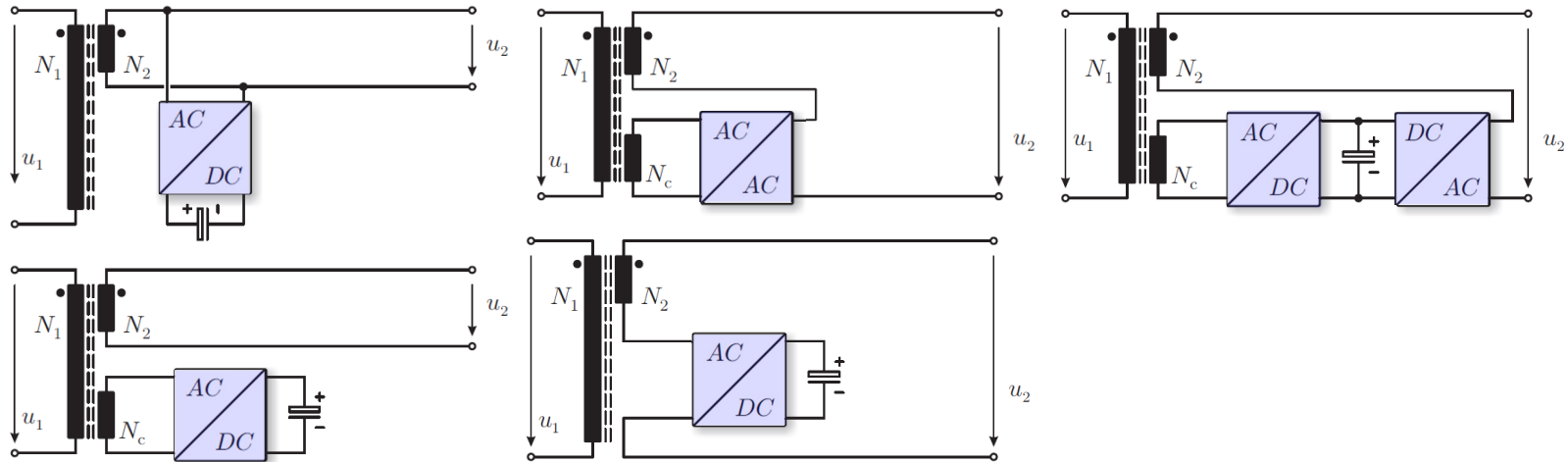- Combination of Mains-Frequ. Transformer & SST
- Fractional Power Processing → High Efficiency
- Low Blocking Voltage Requirement
- Simplified Protection



► **Shunt Connection**

- Reactive Curr. Inj.
- Harm. Curr. Inj.


► **Series Connection**

- Reactive Voltage Inj.
- Phase Shiftg / Volt. Cntrl

► **Combined Connection**

- Reactive / Harm. Curr. Inj.
- Volt. Cntrl / Phase Shiftg

► Current SST Research Status

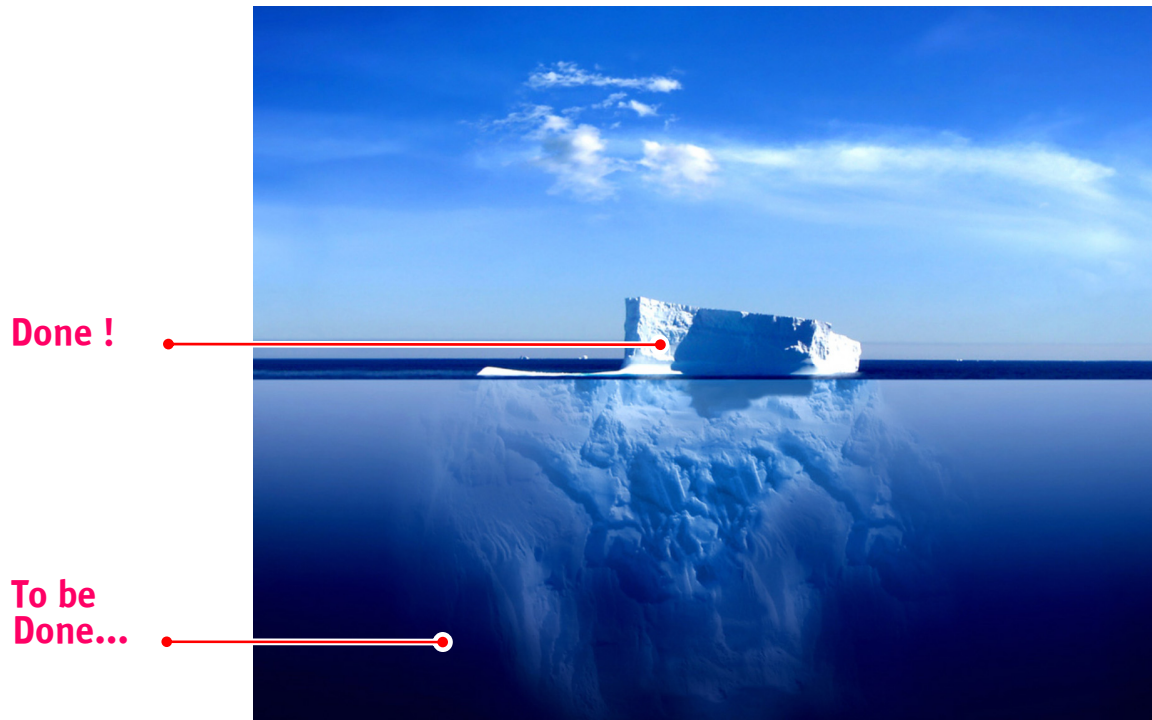

- Huge *Multi-Disciplinary Challenges / Opportunities (!)* are Still Ahead

Thank You!

Questions



www.pes.ee.ethz.ch/publications.html