

The **Google** Little Box Challenge

Ultra-Compact GaN- or SiC-Based Single-Phase DC/AC Power Conversion


Johann W. Kolar



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



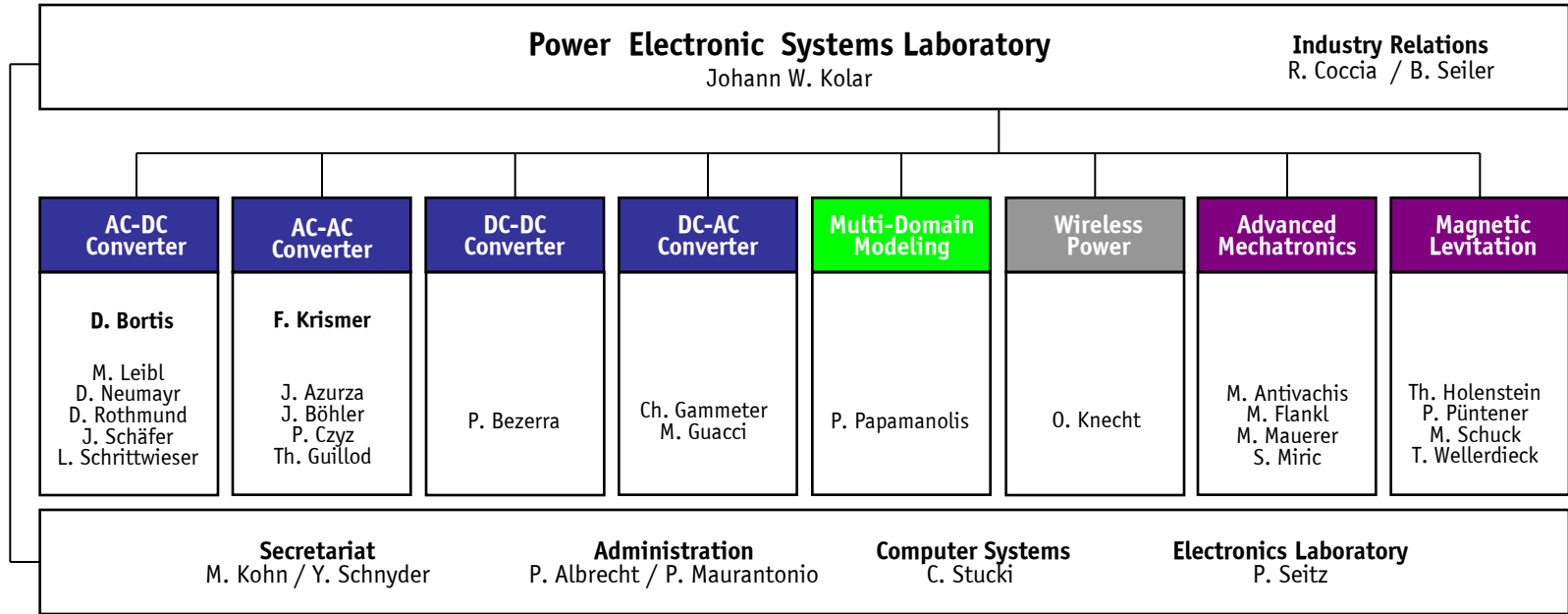► ETH Zurich - Power Electronic Systems Laboratory



22 Ph.D. Students
2 Post Docs



Leading Univ.
in Europe

Outline

- ▶ The **Google** Little Box Challenge
- ▶ *Little Box 1.0*
- ▶ *Concepts & Performances of Other Finalists*
- ▶ *Little Box 2.0*
- ▶ **Conclusions**

D. Bortis
D. Neumayr
O. Knecht
F. Krismer
M. Guacci
L. Camurca
M. Kasper
E. Hatipoglu

Acknowledgement


Google Little Box Challenge

Requirements
The Grand Prize
Finalists & Finals

LITTLE BOX CHALLENGE



 - Design / Build the 2kW 1-Φ Solar Inverter with the Highest Power Density in the World
- Power Density > 3kW/dm³ (> 50W/in³, multiply kW/dm³ by Factor 16)
- Efficiency > 95%
- Case Temp. < 60°C
- EMI FCC Part 15 B



■ Push the Forefront of New Technologies in R&D of High Power Density Inverters

The Grand Prize

- Highest Power Density ($> 50\text{W}/\text{in}^3$)
- Highest Level of Innovation




\$1,000,000

- Timeline
 - Challenge Announced in Summer 2014
 - **2000+ Teams Registered** Worldwide
 - 100+ Teams Submitted a Technical Description until July 22, 2015
 - **18 Finalists (3 No-Shows)**

LITTLE BOX CHALLENGE Finalists

* and FH IZM / Fraza d.o.o.

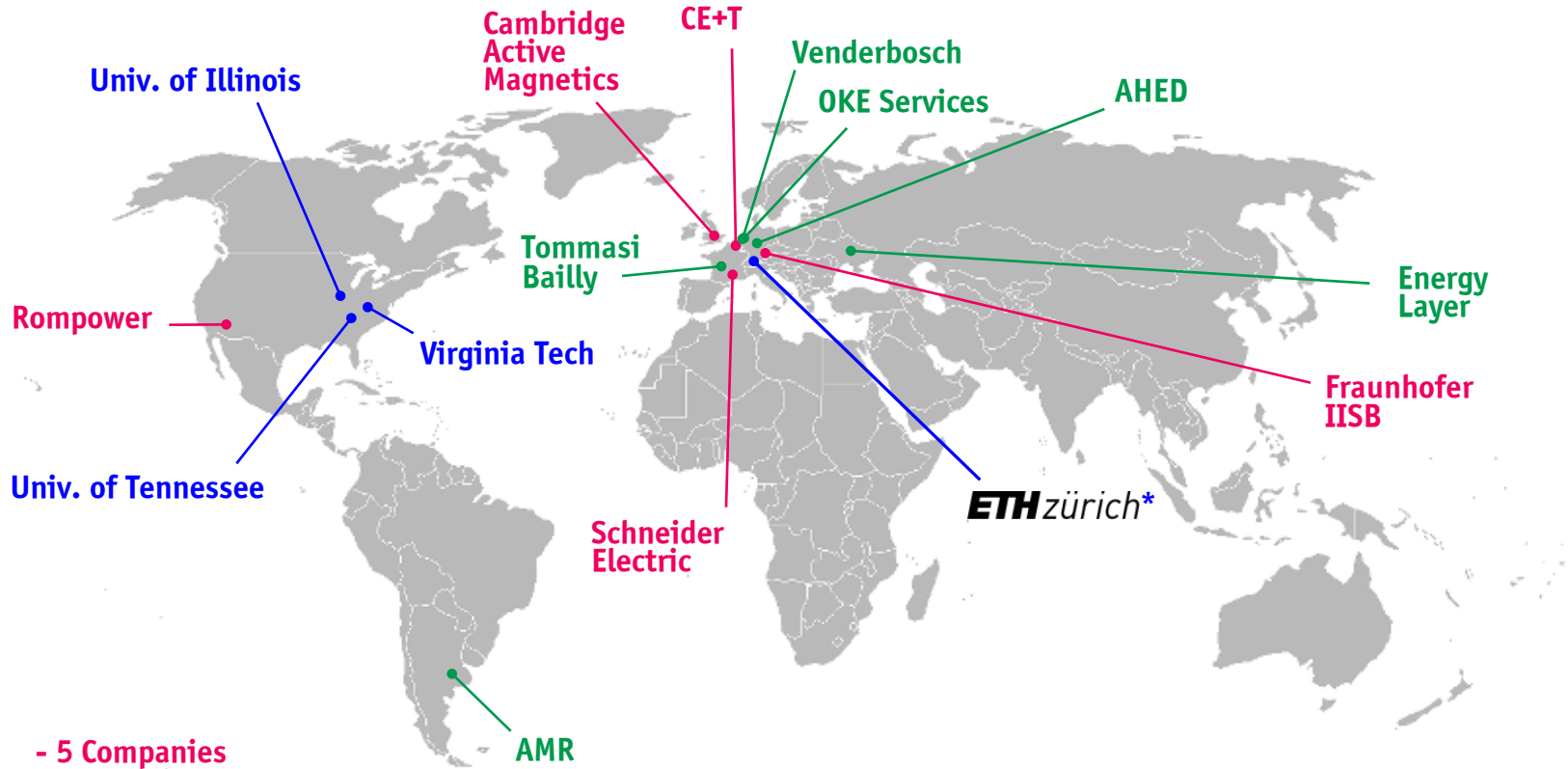



- 5 Companies
- 6 Consultants
- 4 Universities

15 Teams/Participants in the Final @ NREL



LITTLE BOX CHALLENGE

Final Presentations

  

- Finalists Invited to NREL / USA
- Presentations on Oct. 21, 2015
- Subsequent Testing by NREL



Little Box 1.0

Converter Topology
Modulation & Control
Technologies /Components
Mechanical Concept
Exp. Analysis

Acknowledgement




*Derivation of
Converter Concept*




————— *1- Φ Output Power
Pulsation Buffer* —————

Power Pulsation Buffer

- Parallel Buffer @ DC Input

 




- Series Buffer @ DC Input

 

- Parallel Approach for Limiting Voltage Stress on Converter Stage Semiconductors

Passive Power Pulsation Buffer (1)

- Electrolytic Capacitor

   

$S_0 = 2.0 \text{ kVA}$
 $\cos \Phi_0 = 0.7$
 $V_{C,max} = 450 \text{ V}$
 $\Delta V_C / V_{C,max} = 3 \%$



 
 

EPCOS
 5 x 493 μF / 450 V
 $C = 2.46 \text{ mF}$

■ $C > 2.2 \text{ mF} / 166 \text{ cm}^3 \rightarrow$ Consumes 1/4 of Allowed Total Volume !



Passive Power Pulsation Buffer (2)

- Series Resonant Circuit / Used in Rectifier Input Stage of Locomotives




- * $C_r = 20 \mu\text{F}$
- * $L_r = 127 \text{ mH} @ v_{Lr} = 400 \text{ V}$

■ Unacceptably Large Inductor Volume !  → Electronic Inductor

Partial Active Power Pulsation Buffer

 - Coupling Capacitor & "Electronic Inductor" Processing Only *Partial Power*



Electronic Inductor →



- * Ertl (1999)
- * Enslin (1991)
- * Pilawa (2015)

- Low $U_{C,aux}$ → Low Converter Losses
- High Values of C_k, C_{aux} Required for Low $U_{C,aux}$
- Full-Bridge Aux. Converter Allows Lower $U_{C,aux}$




Full Active Power Pulsation Buffer



* Kyritsis (2007)

 - Large Voltage Fluctuation Foil or Ceramic Capacitor
- Buck- or Boost-Type DC/DC Interface Converter
- Buck-Type allows Utilizing 600V Technology



CeraLink
TDK



108 x 1.2 μF / 400 V
 $C_k \approx 140 \mu\text{F}$
 $V_{Ck} = 23.7 \text{cm}^3$

- Significantly Lower Overall Volume Compared to Electrolytic Capacitor




*Output Stage
Topology / Modulation*


Derivation of Output Stage Topology (1)

- Inversion of Basic 1- Φ PFC Rectifier Topology

- Boost-Type
1- Φ PFC Rectifier

 


- DC/|AC| Buck Converter & Mains Frequency "Unfolder"

 

* Erickson (2009) \rightarrow Analysis Only for $\cos \Phi = -1$

Advanced DC/|AC|-Buck Conv. & Unfolder

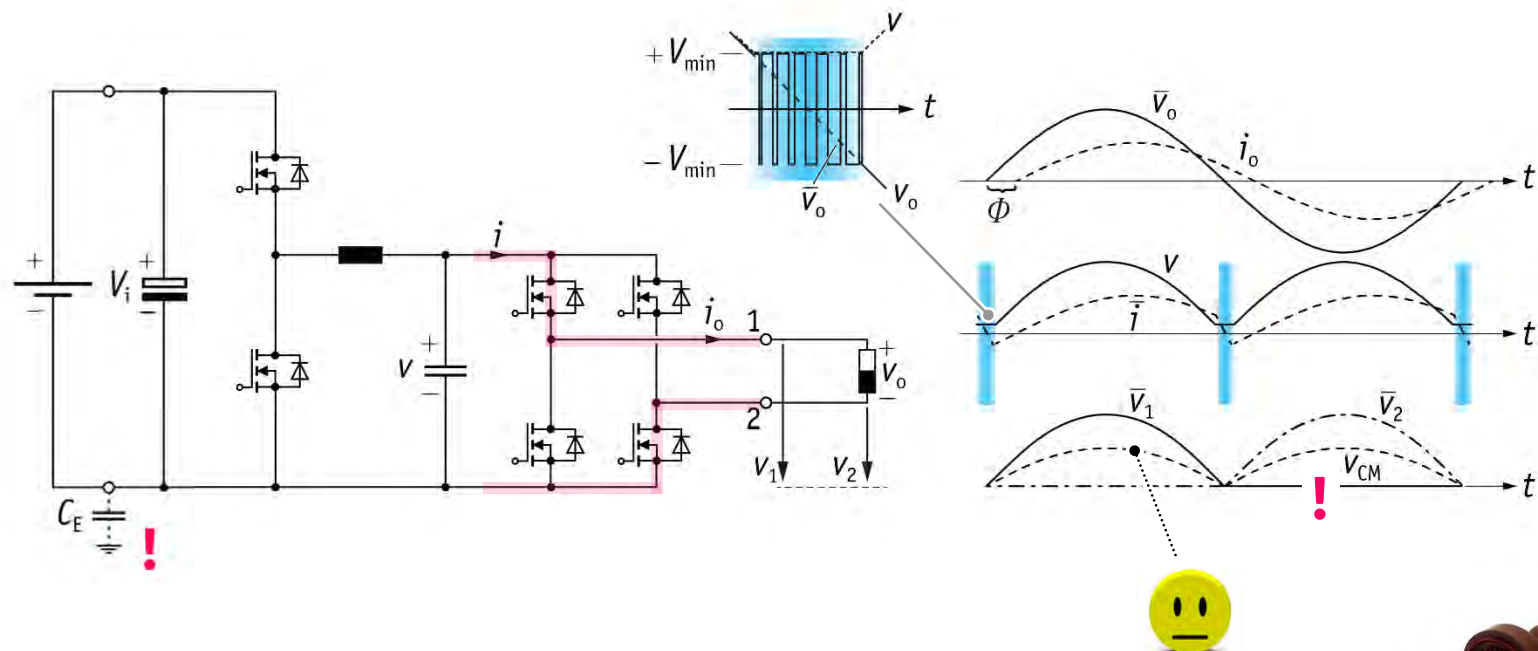- Temporary PWM Operation of Unfolder @ $U < U_{min}$ to Avoid AC Current Distortion




- CM Component of Output Voltage v_0
- Larger EMI Filtering Requirement Due to Temporary High-Freq. Switching of Unfolder



Advanced Full-Bridge DC/AC Conv. Topology

- New Control Concept - PWM Operation of Mains Freq. Unfolder Bridge Leg @ $|u| < u_{0,min}$



 


- CM Component u_{CM} of Generated Output Voltage
- Potentially Larger EMI Filtering Requirement



Symmetric PWM Full-Bridge AC/DC Conv. Topology

  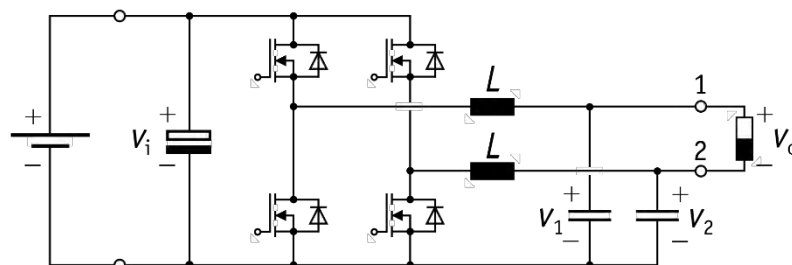- Symmetric PWM Operation of Both Bridge Legs
- No Low-Frequency CM Output Voltage Component







- DM Component of u_1 and u_2 Defines Output u_o
- CM Component of u_1 and u_2 Represents Degree of Freedom of the Modulation (!)

ZVS of Output Stage / TCM Operation



* Henze (1988)


 
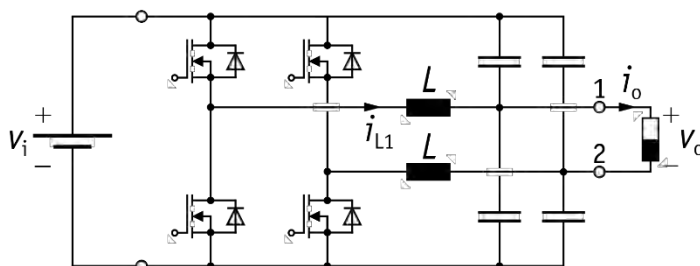
 
 
- TCM Operation for Resonant Voltage Transition @ Turn-On/Turn-Off



- Requires Only Measurement of Current Zero Crossings, $i = 0$
- Variable Switching Frequency Lowers EMI

4D-Interleaving

    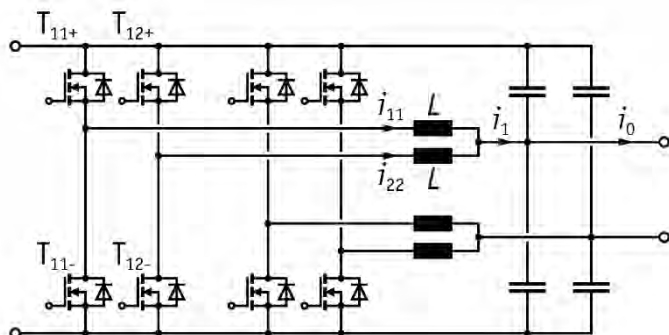- Interleaving of 2 Bridge Legs per Phase - Volume / Filtering / Efficiency Optimum
- Interleaving in Space & Time – Within Output Period
- Alternate Operation of Bridge Legs @ Low Power
- Overlapping Operation @ High Power




- Opt. Trade-Off of Conduction & Switching Losses / Opt. Distribution of Losses



Remark: iTCM Inverter Topology


- TCM : Challenging Inductor Design → Superposition of HF & LF Currents
- iTCM: Adding LC-Circuit between Bridge Legs → Separation of LF & HF Currents → $L \gg L_B$

- TCM

 

- Low Output Current Ripple
- PWM Modulation Applicable
- Dedicated LF and HF Inductor Designs Possible

- iTCM

 


- Reduced Filtering Effort
- Simple Control Strategy
- Improved Converter Efficiency

* P. Jain (2015)



Selection of Switching Frequency

 - Significant Reduction in EMI Filter Volume for Increasing Sw. Frequency




- Doubling Sw. Fequ. f_s Cuts Filter Volume in Half
- Upper Limit due to Digital Signal Processing Delays / Inductor & Sw. Losses – Heatsink Volume

EMI Filter Topology (1)

- Conventional Filter Structure

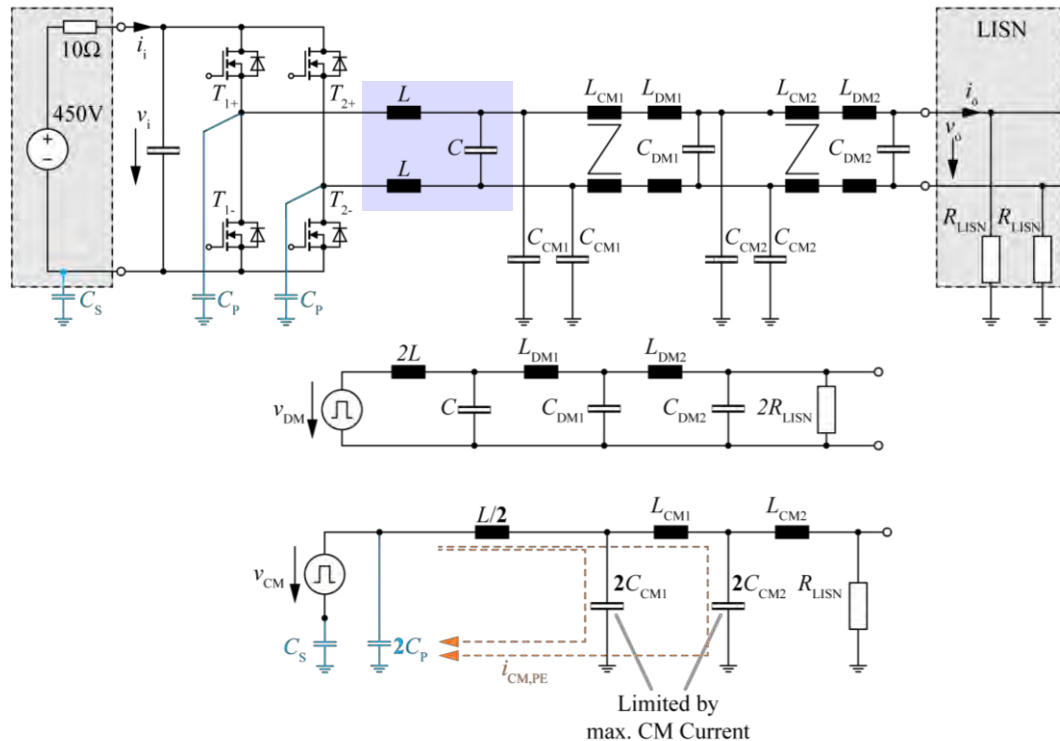
- DM Filtering Between the Phases
- CM Filtering Between Phases and PE



- CM Cap. Limited by Earth Current Limit – Typ. 3.5mA for PFC Rectifiers (GLBC: 5mA then 50mA !)
- Large CM Inductor Needed – Filter Volume Mainly Defined by CM Inductors

EMI Filter Topology (2)

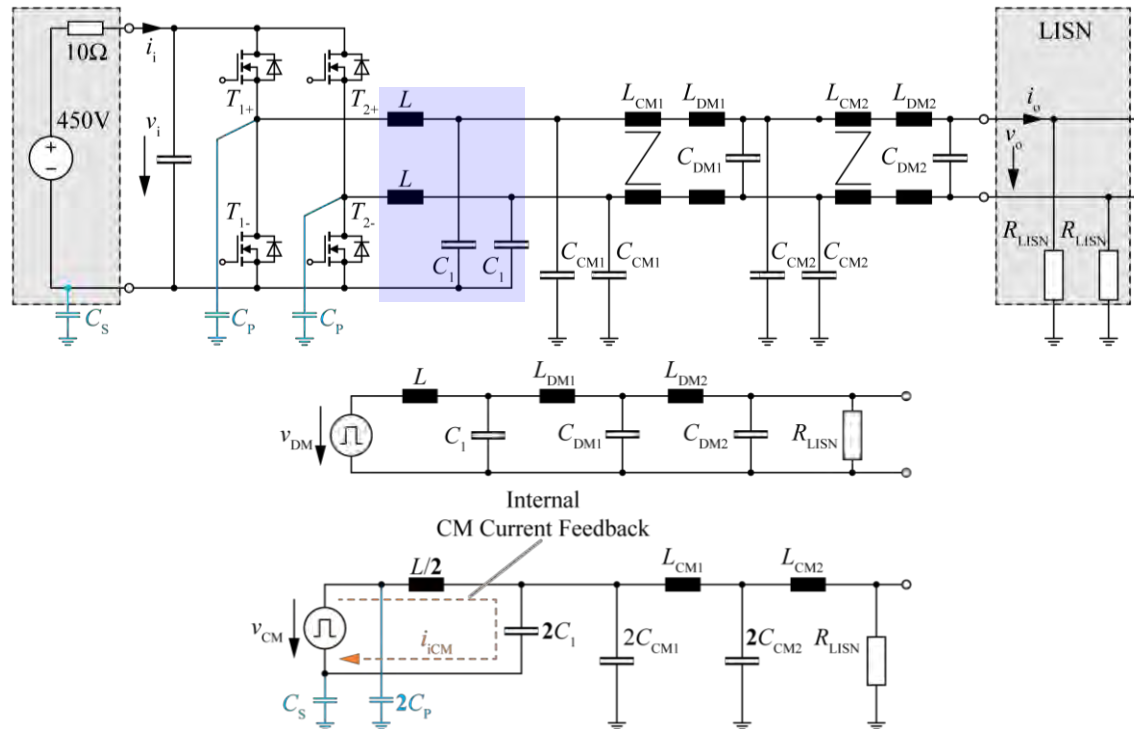- Filter Structure with Internal CM Capacitor Feedback
- Filtering to DC- (and optional to DC+)




- No Limitation of CM Capacitor C_1 Due to Earth Current Limit $\rightarrow \mu\text{F}$ Instead of nF Can be Employed
- Allows Downsizing of CM Inductor and/or Total Filter Volume

Final Converter Topology

- Interleaving of 2 Bridge Legs per Phase
- Active DC-Side Buck-Type Power Pulsation Buffer
- 2-Stage EMI AC Output Filter

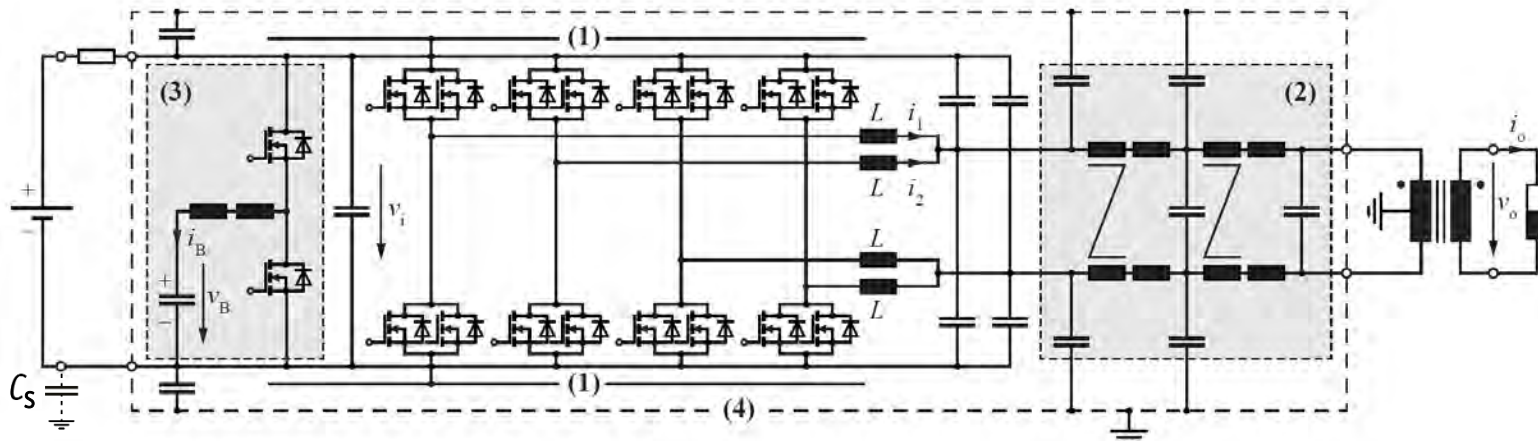- (1) Heat Sink
- (2) EMI Filter
- (3) Power Pulsation Buffer
- (4) Enclosure



- ZVS of All Bridge Legs @ Turn-On/Turn-Off in Whole Operating Range (4D-TCM-Interleaving)
- Heatsinks Connected to DC Bus / Shield to Prevent Cap. Coupling to Grounded Enclosure




Technologies

Power Semiconductors
HF Inductors
Cooling
Etc.



Evaluation of Power Semiconductors (1)

 
 
 
- Accurate Measurement of ZVS Losses Using Calorimetric Approach
- High Sw. Frequency for Large Ratio of Sw. and Conduction Losses



- Direct Measurement of the Sum of Sw. and Conduction Losses
- Subtraction of the Conduction Losses Known from Calibration
- Fast Measurement by $C_{th} \cdot \Delta T / \Delta t$ Evaluation

Evaluation of Power Semiconductors (2)

   - Comparison of Soft-Switching Performance of $\sim 60\text{m}\Omega$, 600V/650V/900V GaN, SiC, Si MOSFETs
- Measurement of Energy Loss per Switch and Switching Period




- GaN MOSFETs Feature Highest Soft-Switching Performance
- Similar Soft-Switching Performance Achieved with Si and SiC
- Almost No Voltage-Dependency of Soft-Switching Losses for Si-MOSFET


High Frequency Inductors (1)

- Multi-Airgap Inductor with Multi-Layer Foil Winding Arrangement Minim. Prox. Effect
- Very High Filling Factor / Low High Frequency Losses
- Magnetically Shielded Construction Minimizing EMI
- Intellectual Property of F. Zajc / Fraza

 - $L = 10.5\mu\text{H}$
- 2 x 8 Turns
- 24 x $80\mu\text{m}$ Airgaps
- Core Material DMR 51 / Hengdian
- 0.61mm Thick Stacked Plates
- 20 μm Copper Foil / 4 in Parallel
- 7 μm Kapton Layer Isolation
- 20m Ω Winding Resistance / $Q \approx 600$
- Terminals in No-Leakage Flux Area







■ Dimensions - 14.5 x 14.5 x 22mm³

 

High Frequency Inductors (2)

    - High Resonance Frequency → Inductive Behavior up to High Frequencies
- Extremely Low AC-Resistance → Low Conduction Losses up to High Frequencies
- High Quality Factor



- Shielding Eliminates HF Current through the Ferrite → Avoids High Core Losses
- Shielding Increases the Parasitic Capacitance


High Frequency Inductors (3)



* Knowles (1975!)



- Cutting of Ferrite Introduces Mech. Stress
- Significant Increase of the Loss Factor
- Reduction by Polishing / Etching (5 μm)

 ■ Comparison of Temp. Increase of a Bulk and a Sliced Sample @ 70mT / 800kHz



Thermal Management

  - 30°C max. Ambient Temperature
- 60°C max. Allowed Surface and Air Outlet Temperature
- Evaluation of Optimum Heatsink Temperature for Thermal Isolation of Converter




- Minimum Volume Achieved w/o Thermal Isolation with Heatsink @ max. Allowed Surface Temp.


Thermal Management

- Overall Cooling Performance Defined by Selected Fan Type and Heatsink


- Radial Blower

 




- Axial Fan

 

 - Square Cross Section of Heatsink for Using a Fan



- Flat and Wide Heatsink for Blower

  
 


- Optimal Fan and Heat Sink Configuration Defined by Total Cooling System Length
- Cooling Concept with Blower Selected → Higher CSPI for Larger Mounting Surface

Final Thermal Management Concept (1)

- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters

  
- 200um Fin Thickness
- 500um Fin Spacing
- 3mm Fin Height
- 10mm Fin Length
- $CSPI = 37 \text{ W}/(\text{dm}^3 \cdot \text{K})$
- 1.5mm Baseplate



- $CSPI_{eff} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$ Considering Heat Distribution Elements
- Two-Side Cooling \rightarrow Heatsink Temperature = 52°C @ 80W (8W by Natural Convection)

Final Thermal Management Concept (2)

 - CSPI = 37 W/(dm³.K)
- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters
- CSPI_{eff}=25 W/(dm³.K) incl. Heat Cond. Layers





- CSPI_{eff} = 25 W/(dm³.K) Considering Heat Distribution Elements
- Two-Side Cooling → Heatsink Temperature = 52°C @ 80W (8W by Natural Convection)

$i=0$ Detection

- Analyzed Methods
 - Shunt Current Measurement
 - Measurement of the $R_{ds,on}$
 - Two Antiparallel Diodes
 - Giant Magneto-Resistive Sensor
 - Hall Element
- Saturable Inductor


 
 
Various Drawbacks
 Losses, No Galvanic Isolation, Low Signal-to-Noise Ratio (SNR), Size, Bandwidth, Realization Effort



- Galvanic Isolation, High SNR, Small Size, High Bandwidth, Simple Design
- Min. Core Volume/Cross Section for Min. Core Losses

$i=0$ Detection

 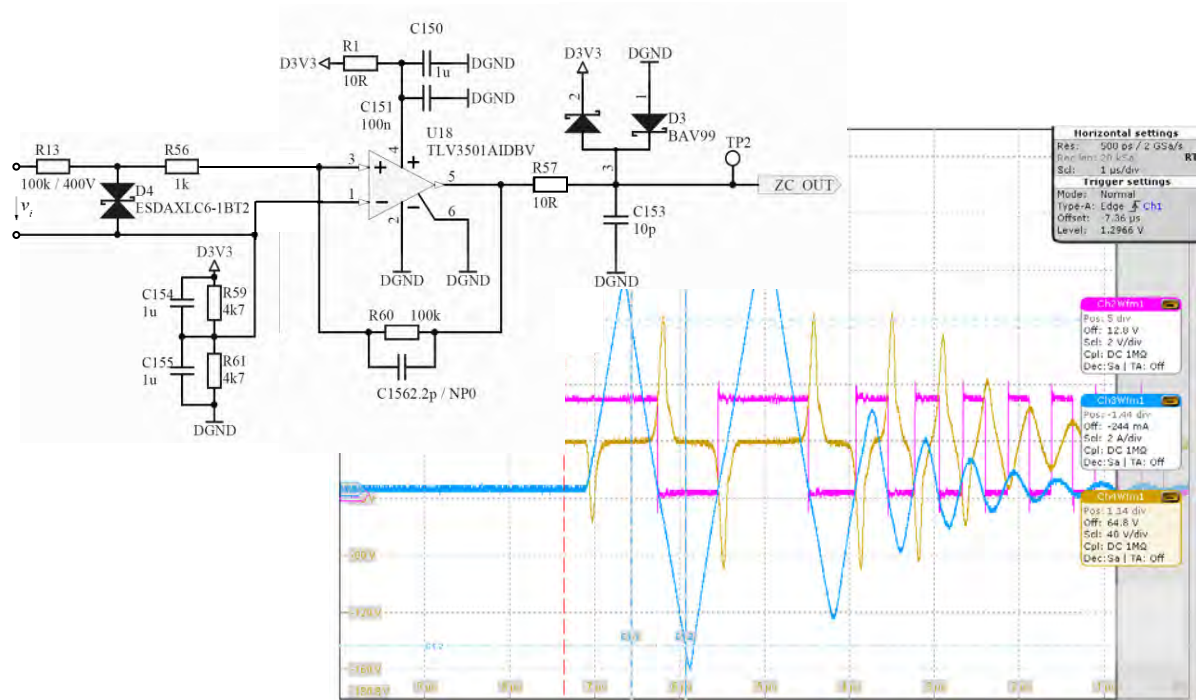 
- Saturable Inductor – Toroidal Core R4 x 2.4 x 1.6, EPCOS (4mm Diameter)
- Core Material N30, EPCOS



- Operation Tested up to 2.5MHz Switching Frequency

Active Power Pulsation Buffer

- New Cascaded Control Structure

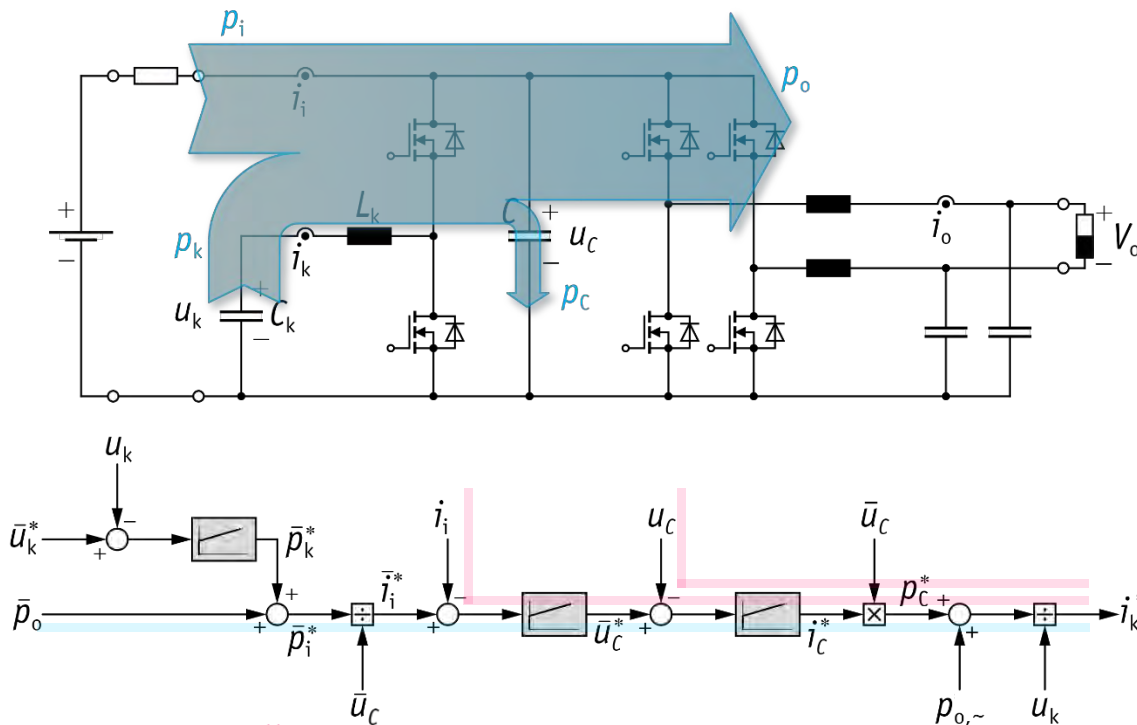



- P-Type Resonant Controller
- Feedforward of Output Power Fluctuation
- Underlying Input Current (i_i) / DC Link Voltage (u_c) Control



Final Active Power Pulsation Buffer

- High Energy Density 2nd Gen. 400VDC CeraLink Capacitors Utilized as Energy Storage
- Highly Non-Linear Behavior → Optimal DC Bias Voltage of 280VDC
- Losses of 6W @ 2kVA Output Power

  - 108 x 1.2 μ F / 400 V
- 23.7cm³ Capacitor Volume




- Effective Large Signal Capacitance of $C \approx 160\mu$ F

3D-CAD Construction →

Mechanical Construction (1)

 
- Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$



■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$

Mechanical Construction (2)

 
- Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$



■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$

Mechanical Construction (3)

 
- Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$



■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$

Mechanical Construction (4)

 
- Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$



■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$

Mechanical Construction (5)

 - Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$



■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$

Experimental Results

Hardware
Output Voltage/Input Current Quality
Efficiency



Little Box 1.0 - Prototype

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

- 8.2 kW/dm³
- 8.9cm x 8.8cm x 3.1cm
- 96,3% Efficiency @ 2kW
- $T_c=58^\circ\text{C}$ @ 2kW


- $\Delta u_{\text{DC,pp}}$ = 1.1%
- $\Delta i_{\text{DC,pp}}$ = 2.8%
- $\text{THD}+N_U$ = 2.6%
- $\text{THD}+N_I$ = 1.9%

- Compliant to All *Original Specifications* (!)

- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



★ 135 W/in³

 

Little Box 1.0 - Prototype

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

- 8.2 kW/dm³
- 8.9cm x 8.8cm x 3.1cm
- 96,3% Efficiency @ 2kW
- $T_c=58^\circ\text{C}$ @ 2kW


- $\Delta u_{DC} = 1.1\%$
- $\Delta i_{DC} = 2.8\%$
- $THD+N_U = 2.6\%$
- $THD+N_I = 1.9\%$

- Compliant to All *Original Specifications* (!)

- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



★ 135 W/in³

 


Little Box 1.0 - Measurement Results (1)


- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

- Ohmic Load / 2kW

 Output Current (10 A/div)
 Inductor Current Bridge Leg 1-1 (10 A/div)
 Inductor Current Bridge Leg 1-2 (10 A/div)



 DC Link Voltage (AC-Coupl., 2 V/div)
 Buffer Cap. Voltage (20 V/div)
 Buffer Cap. Current (10 A/div)
 Output Voltage (200 V/div)




Compliant to All Specifications

Little Box 1.0 - Measurement Results (2)

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer


★ $\eta_w=95.07\%$ Weighted Efficiency

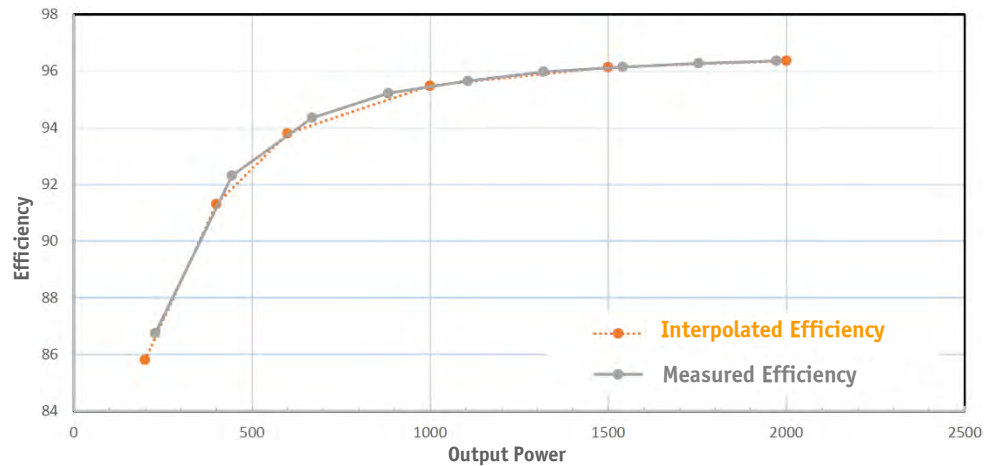

- Compliant to All Specifications

Little Box 1.0 - Measurement Results (3)

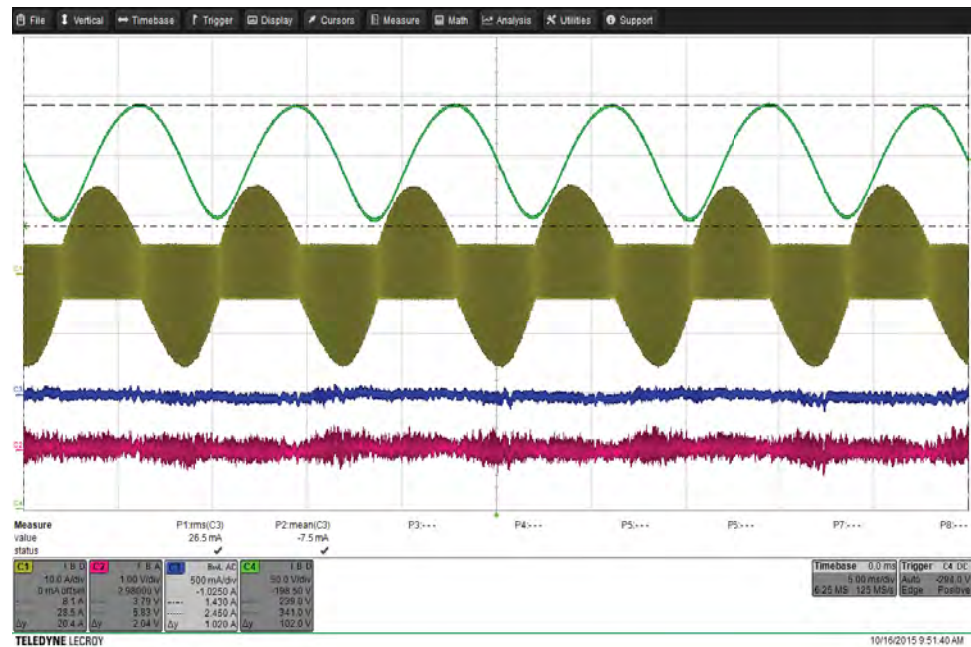- System Employing Active Ceralink 1- Φ Power Pulsation Buffer




Buffer Cap. Voltage (50V/div)
 Buffer Cap. Current (10A/div)
 Conv. Inp. Curr. (AC Coupl. 500mA/div)
 DC Link Voltage (AC Coupl. 1V/div)


- Stationary Operation @ 2kW Output Power

Little Box 1.0 - Volume and Loss Distribution

Volume Distribution (240cm³)

 

Loss Distribution (75W)

 

- Large Heatsink (incl. Heat Conduction Layers)
- Large Losses in Power Fluctuation Buffer Capacitor (!)
- TCM Causes Relatively High Conduction & Switching Losses @ Low Power
- Relatively Low Switching Frequency @ High Power – Determines EMI Filter Volume

- ***Other Finalists***

Topologies
Switching Frequencies
Power Density / Efficiency Comparison →



Detailed Descriptions:
www.LittleBoxChallenge.com



Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

Note: Numbering of Teams is Arbitrary

 
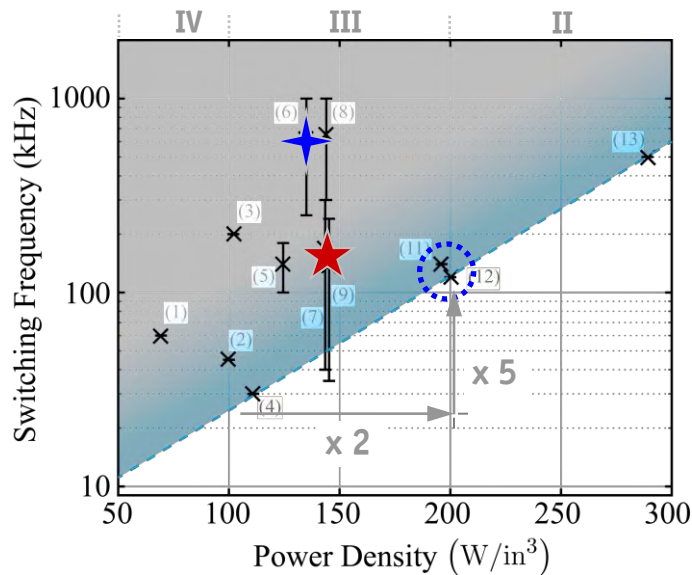


- 70...300 W/in^3
- 35 kHz...500kHz...1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps of Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)

Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

Note: Numbering of Teams is Arbitrary

  

- (1) Virginia Tech
- (2) Schneider Electric
- (3) EPRI (Univ. of Tennessee)
- (4) Venderbosch
- (5) Energy Layer


- (6) ETH Zurich
- (7) Rompower
- (8) Tommasi-Bailly
- (9) Red Electric Devils
- (10) AHED

- (11) FH IISB
- (12) Univ. of Illinois
- (13) AMR
- (14) OKE
- (15) Cambridge Magnetics

Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

Note: Numbering of Teams is Arbitrary

 


- (1) Virginia Tech
- (2) Schneider Electric
- (3) EPRI (Univ. of Tennessee)
- (4) Venderbosch
- (5) Energy Layer
- (6) ETH Zurich
- (7) Rompower
- (8) Tommasi-Bailly
- (9) Red Electric Devils
- (10) AHED
- (11) FH IISB
- (12) Univ. of Illinois
- (13) AMR

- 70...300 W/in³
- 35 kHz...500kHz...1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps of Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)



Category I: 300 – 400 W/in³ (1 Team)

 - “Over the Edge”
- Hand-Wound Overstressed & Too Small Electrolytic Capacitors (210uF/400V)
- No Voltage Margin of Power Semiconductors (450V GaN, Hard Switching)
- 50V Voltage Source for Semicond. Voltage Stress Reduction
- Low-Frequ. CM AC Output Component




- Alternate Switching of Full-Bridge Legs
- Input Cap. of Full-Bridge Used for Power Pulsation Buffering
- 256 W/in³ (400 W/in³ Claimed) / 1MHz
- Multi-Airgap Toroidal Inductors (3F46, $C_p \approx 1.5\text{pF}$)
- Bare GaN Dies Directly Attached to Pin-Fin Heatsink
- High Speed Fan (Mini Drone Motor & Propeller)



Category I: 300 – 400 W/in³ (1 Team)

 - “Over the Edge”
- Hand-Wound Overstressed Electrolytic Capacitors (210uF (?)/400V)
- No Voltage Margin of Power Semiconductors (450V GaN, Hard Switching)
- 50V Voltage Source for Semicond. Voltage Stress Reduction





- Alternate Switching of Full-Bridge Legs
- Input Cap. of Full-Bridge Used for Power Pulsation Buffering
- 256 W/in³ (400 W/in³ Claimed) / 1MHz
- Multi-Airgap Toroidal Inductors (3F46, $C_p \approx 1.5\text{pF}$)
- Bare Dies Directly Attached to Pin-Fin Heatsink
- High Speed Fan (Mini Drone Motor & Propeller)




Category II: 200 – 300 W/in³ (4 Teams) – Example #1

  - "At the Edge"
- High Complexity
- 7-Level Flying Capacitor Converter
- Series-Stacked Active Power Buffer




- 216 W/in³
- 100V GaN
- Integrated Switching Cell
- 720kHz Eff. Sw. Freq. (7 x 120kHz)

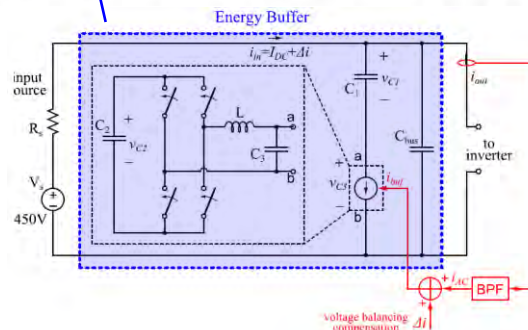

Category II: 200 – 300 W/in³ (4 Teams) – Example #2

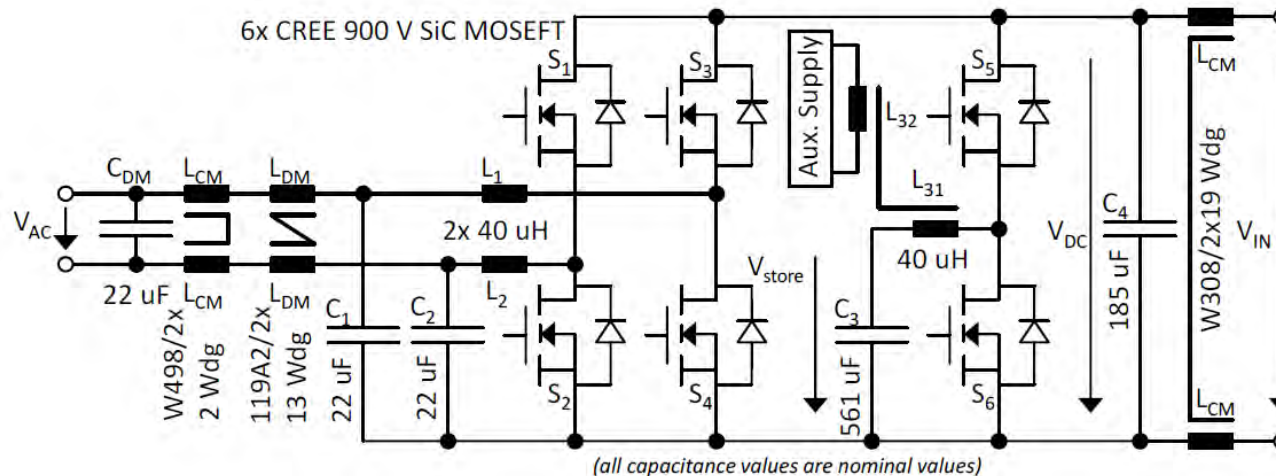- “At the Edge”
- Very Well Engineered Assembly (e.g. 3D-Printed Heatsink w. Integr. Fans, 1 PCB Board, etc.)
- No Low-Frequ. Common-Mode AC Output Component




- 201W / in³
- Multi-Airgap (8 Gaps) Inductors
- 900V SiC @ 140kHz (PWM, Soft Sw. Around i=0 & Hard Switching)
- Buck-Type Active DC-Side Power Pulsation Filter / Ceramic Capacitors (X6S)



Category III: 100 – 200 W/in³ (8 Teams) – Example

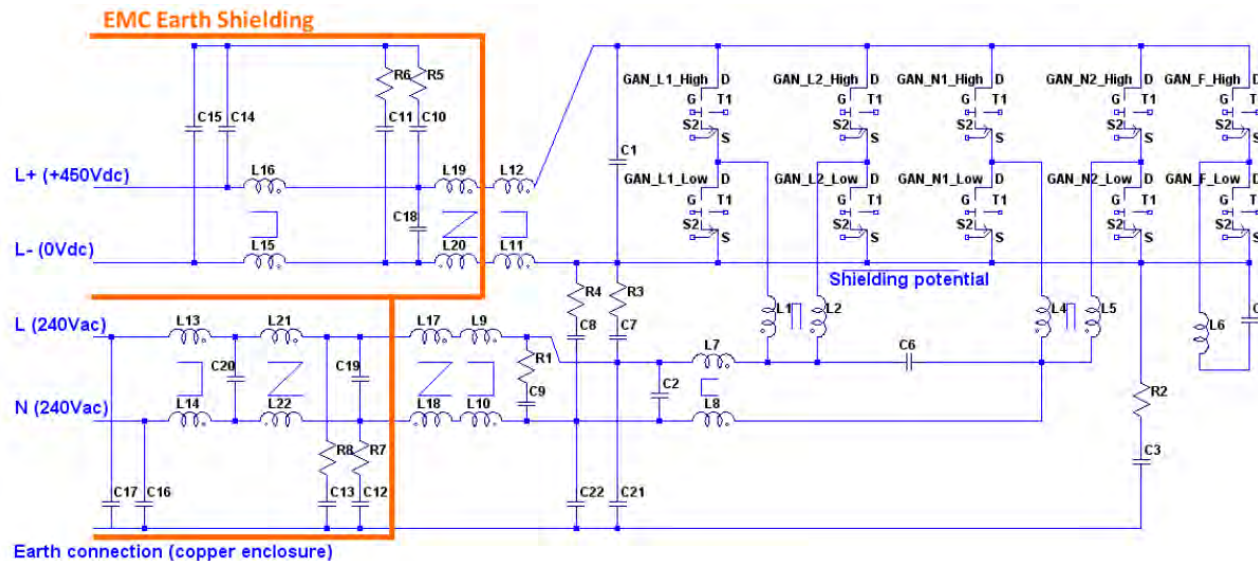- “Advanced Industrial”
- Sophisticated 3D Sandwich Assembly incl. Cu Honeycomb Heatsink
- Shielded Multi-Stage EMI Filter @ DC Input and AC Output
- No Low-Frequ. Common-Mode AC Output Component




- 143 W/in³
- GaN @ ZVS (35kHz...240kHz)
- 2 x Interleaving for Full-Bridge Legs
- Buck-Type DC-Side Active Power Pulsation Filter (<150μF)





Category III: 100 – 200 W/in³ (8 Teams) – Example

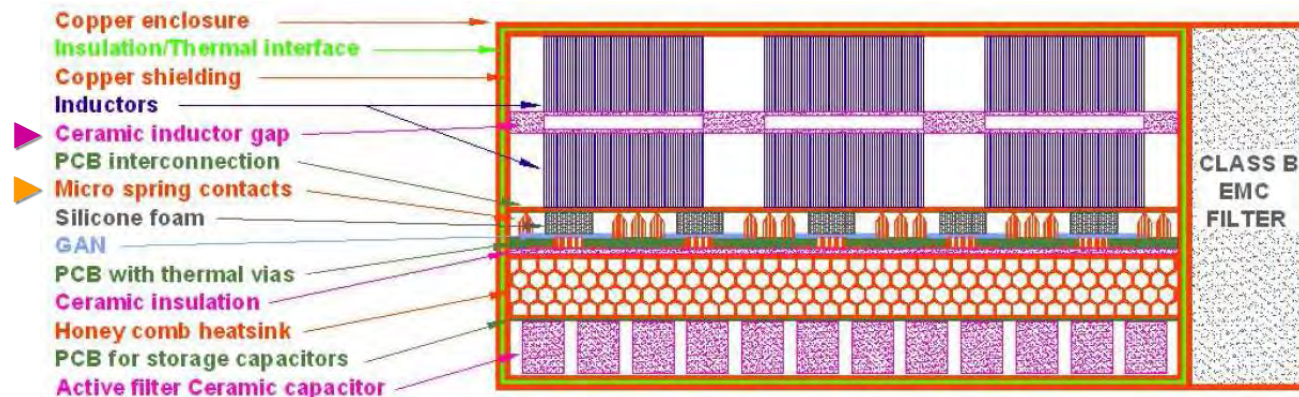- **“Advanced Industrial”**
- **Sophisticated 3D Sandwich Assembly** incl. Cu Honeycomb Heatsink
- Shielded Multi-Stage EMI Filter @ DC Input and AC Output
- No Low-Frequ. Common-Mode AC Output Component




- 143 W/in³
- GaN @ ZVS (35kHz...240kHz)
- 2 x Interleaving for Full-Bridge Legs
- Buck-Type DC-Side Active Power Pulsation Filter (<150μF)



Category IV: 50 – 100 W/in³ (1 Team)

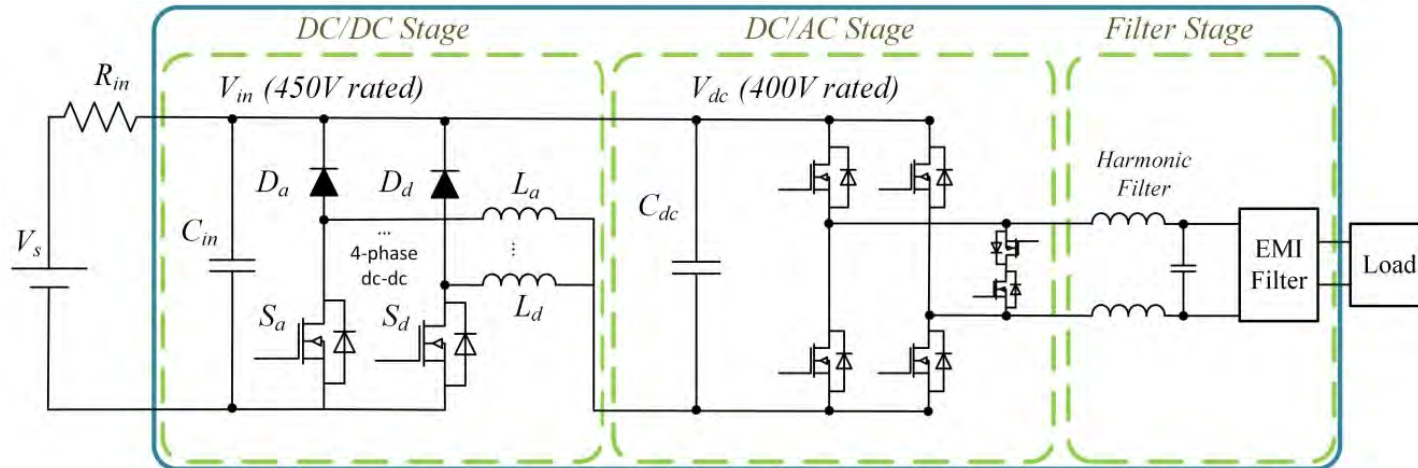- “Industrial”
- 400V_{max} Full-Bridge Input Voltage
- DC-Link Cap. Used as Power Pulsation Buffer (470uF)
- GaN Transistors / SiC Diodes (400kHz DC/DC, 60kHz DC/AC)
- Multi-Stage EMI Filter @ AC Output and L_{CM} + Feed-Trough C_{CM} @ DC Inp. (Not Shown)



- ≈ 70 W/ in³
- 98% CEC (Weighted) Efficiency
- 4.4% DC Input Current Ripple
- 54°C Surface Temp. / Cooling with 10 Mirco-Fans

- **Competition
Conclusions**
*Key Technologies
Power Density Limit* →

Google Little Box Challenge Summary

Overall

- Engineering "Jewels"
- No (Fundamentally) New Approach / Topology
- Passives & 3D-Packaging are Finally Defining the Power Density
- Careful Heat Management (Adv. Heat Sink, Heat Distrib., 2-Side Integr. Cooling, etc.)
- Careful Mechanical Design (3D-CAD, Single PCB, Avoid Connectors, etc.)
- Clear Power Density / Efficiency Trade-Off


200W/in³ (12kW/dm³) Achievable

- $f_s < 150\text{kHz}$ (Constant)
- SiC (Not GaN)
- ZVS (Partial, i.e. Around $i=0$)
- Full-Bridge Output Stage
- Active Power Pulsation Buffer (Buck-Type, X6S Cap.)
- Conv. EMI Filter Structure
- Multi-Airgap Litz Wire Inductors
- DSP Only (No FPGA)

100+ Teams
3 Members / Team, 1 Year
300 Man-Years
3300 USD / Man-Year



Little Box 2.0

 



250 W/in³

DC/ | AC | Converter + Unfolder
PWM vs. TCM incl. Interleaving
 η -Pareto Limits for Non-Ideal Switches
Final 3D-CAD
Preliminary Exp. Results





Little Box 2.0 – New Converter Topology (1)

- **Alternative Converter Topology** → Only Single HF Bridge Leg + 60Hz-Unfolder
- **DC/|AC| - Buck Converter + Full-Bridge Unfolder** OR **HF Half-Bridge & Half-Bridge Unfolder**

 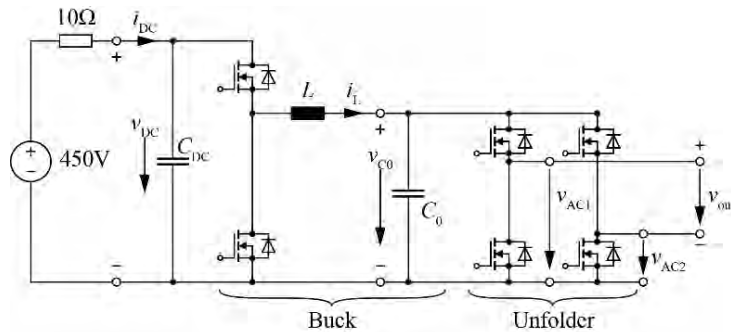

  
- v_{C0} Easy to Generate/Control
- Higher Conduction Losses Due to FB-Unfolder
- Lower CM-Noise (DC & $n \times 120\text{Hz-Comp.}$)
- $C_{CM}=700\text{nF}$ Allowed for 50mA Gnd Current



- v_{AC1} More Difficult to Generate/Control
- Lower Conduction Losses
- Higher CM-Noise (DC and $n \times 120\text{Hz-Comp.}$)
- $C_{CM}=150\text{nF}$ Allowed for 50mA Gnd Current

Little Box 2.0 – New Converter Topology (2)

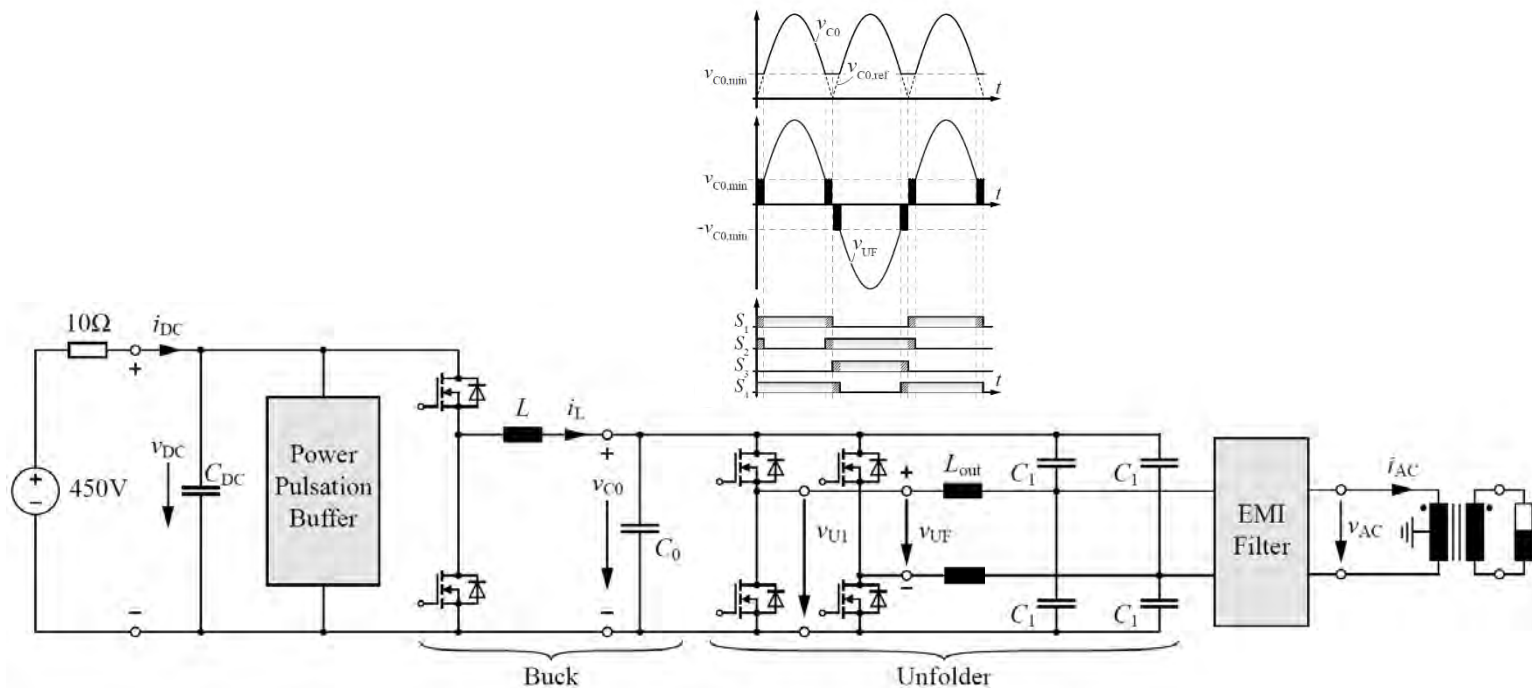
- **Alternative Converter Topology - DC/AC** - Buck Converter + Unfolder
- **60Hz-Unfolder** (Temporary PWM for Ensuring Continuous Current Control)
- **TCM or PWM of DC/AC** - Buck-Converter




- **Full Optimization** of All Converter Options for **Real Switches** / X6S Power Pulsation Buffer

Little Box 2.0 – Multi-Objective Optimization

 - DC/AC - Buck Converter (Single Bridge Leg) + Unfolder & PWM Shows Best Performance
- Full-Bridge Would Employ 2 Switching Bridge Legs - Larger Volume & Losses
- Interleaving Not Advantageous – Lower Heatsink Vol. but Larger Total Vol. of Switches and Inductors




-- 4D-Interleaving Considered for TCM

 

■ $\rho = 250\text{W/in}^3$ (15kW/dm³) @ $\eta = 98\%$ Efficiency Achievable for Full Optimization

Little Box 2.0 – Control Structure

 


- Each Stage (Buck & Unfolder) Controlled with Cascaded Current and Voltage Loop
- Without Switching of Unfolder Control Like for Conventional Boost PFC Rectifier

*3D-CAD Construction
of the Final System*




250 W/in³

 ■ Little Box 2.0 – Final Mechanical Construction (1)




- $60 \text{ mm} \times 50 \text{ mm} \times 45 \text{ mm} = 135 \text{ cm}^3 (8.2 \text{ in}^3) \rightarrow 14.8 \text{ kW/dm}^3 (243 \text{ W/in}^3)$

 Little Box 2.0 – Final Mechanical Construction (2)



■ $60 \text{ mm} \times 50 \text{ mm} \times 45 \text{ mm} = 135 \text{ cm}^3 (8.2 \text{ in}^3) \rightarrow 14.8 \text{ kW/dm}^3 (243 \text{ W/in}^3)$

 
Little Box 2.0 – Final Mechanical Construction (3)



■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)




 Little Box 2.0 – Final Mechanical Construction (4)



■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)

 Little Box 2.0 – Final Mechanical Construction (5)




■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)




Little Box 2.0 – Measured Waveforms


- DC/|AC| Buck-Stage Output Voltage & Inductor Current

 

■ Resistive Load

 


■ Inductive Load

 


■ Capacitive Load

Little Box 2.0 – Preliminary Efficiency Measurements

- Performance of First DC/ | AC | - Buck Converter + Unfolder Prototype
- PWM Operation
- Without Power Pulsation Buffer

 

 - 98% for Res. Load Achievable if Cond. Losses of PCB (Copper Cross Sect.) & Unfolder ($R_{ds,on}$) are Red.



Source: whiskeybehavior.info

Overall Summary



Performance Limits / Future Requirements

- 220...250W/in³ for Two-Level Bridge Leg + Unfolder
- 250...300W/in³ for Highly Integrated Multi-Level Approach
- Isol. Distance Requirements Difficult to Fulfill
- Fulfilling Industrial Inp. Overvoltage Requirem. would Signific. Reduce Power Density

- Low Frequency (20kHz...120kHz) SiC vs. HF (200kHz...1.2MHz) GaN
- Multi-Cell Concepts for LV Si (or GaN) vs. Two-Level SiC (or GaN)

- New Integr. Control Circuits and $i=0$ Detection for Sw. Frequency >1MHz
- Integrated Gate Drivers & Switching Cells
- High Frequency Low Loss Magnetic Materials
- High Bandwidth Low-Volume Current Sensors
- Low Loss Ceramic Capacitors Tolerating Large AC Ripple
- Passives w. Integr. Heat Management and Sensors
- 3D Packaging

- New U-I-Probes Required for Ultra-Compact Conv. R&D
- Specific Systems for Testing → Devices Equipped with Integr. Measurement Functions
- Convergence of Sim. & Measur. Tools → Next Gen. Oscilloscope
- New Multi-Obj. Multi-Domain Simulation/Optim. Tools

Thank You !

